



UTHM

Universiti Tun Hussein Onn Malaysia

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2014/2015**

COURSE NAME : ELECTRONIC TESTING AND MAINTENANCE

COURSE CODE : BWC 31203

PROGRAMME : 3 BWC

EXAMINATION DATE : JUNE 2015 / JULY 2015

DURATION : 3 HOURS

INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF FOUR (4) PAGES

- Q1** (a) Briefly differentiate between the ideal transformer and real transformer. (4 marks)
- (b) What is leakage inductance? Why is measurement of leakage inductance important? (5 marks)
- (c) Draw the schematic diagram of transformer with open circuit secondary terminal, which consist of leakage inductance (LL). How is leakage inductance measured? (11 marks)
- Q2** (a) Describe about the following precision instrument elements for test and measurement.
- (i) Impedance
 - (ii) Phase shift
 - (iii) Series and parallel equivalencies
- (12 marks)
- (b) A particular AC series circuit has a resistor of 4Ω , a reactance across an inductor of 8Ω and a reactance across a capacitor of 11Ω . Show the complex impedance of the circuit in RLC graph and express it in both rectangular and polar form. (4 marks)
- (c) Referring to the **Q2(b)**, suppose we have a current of 10 A in the circuit, find the magnitude of the voltage across
- (i) the resistor (V_R)
 - (ii) the inductor (V_L)
 - (iii) the capacitor (V_C)
 - (iv) the combination (V_{RLC})
- (4 marks)

- Q3 (a) Based on **Figure Q3(a)**, is the circuit inductive or capacitive? Determine the current by the complex version of Ohm's Law and also the RMS current.

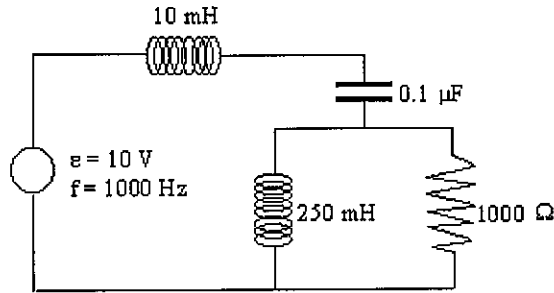


Figure Q3(a)

(10 marks)

- (b) Discuss the major sources of measurement errors and ways to minimize errors. (10 marks)

- Q4 (a) Derive the shielding effectiveness (S.E.) below of an infinite sheet of a good conductor using plane wave shielding theory

$$S.E. = 20 \log \frac{\eta_o}{4\eta_s} + 20 \log e^{t/\delta}$$

(14 marks)

- (b) A transformer generating primarily a magnetic field is located 10 cm from a shielding structure. The shielding structure is made from a 1 cm thick sheet of copper. Estimate the shielding effectiveness of this structure at 1.5 kHz. (Hint: The wave impedance with the magnetic dipole source at the position of the shield is given by $\eta_o \approx \omega\mu r$). Given $\mu = 4\pi \times 10^{-7} \text{H.m}^{-1}$, $\sigma_{copper} = 5.7 \times 10^7 \text{S/m}$.

(6 marks)

- Q5** (a) What is an Operational Amplifier (op-amp)? (2 marks)
- (b) Suggest three test-circuit topologies that commonly used for bench and production testing of DC parameters in op-amp. (3 marks)
- (c) Suggest five DC test parameters and briefly describe each of them. (15 marks)

- END OF QUESTION -