

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

FINAL EXAMINATION SEMESTER I SESSION 2015/2016

COURSE NAME : ELECTRICAL PRINCIPLES I
COURSE CODE : DAR 11003
PROGRAMME : 1 DAR
EXAMINATION DATE : DECEMBER 2015/ JANUARY 2016
DURATION : 3 HOURS
INSTRUCTION : ANSWER **FIVE(5)** QUESTIONS ONLY

THIS PAPER CONSISTS OF TWELVE (12) PAGES

CONFIDENTIAL

Q1 For the circuit of **Figure Q1**:

- (a) Find the total resistance R_T . (3 marks)
- (b) Find the source current I_S . (2 marks)
- (c) Find the currents I_2 , I_3 and I_5 . (9 marks)
- (d) Find the voltages V_2 and V_4 . (6 marks)

Q2 (a) For the circuit of **Figure Q2(a)**, determine the current through each resistor using mesh analysis.

(10 marks)

- (b) For the circuit of **Figure Q2(b)**, determine the magnitude and polarity of the voltage across each resistor using nodal analysis.

(10 marks)

Q3 (a) Using superposition, find the voltage V_2 for the network in **Figure Q3(a)**.

(10 marks)

- (b) Determine the Thévenin equivalent circuit for the networks of **Figure Q3(b)** external to the resistor R .

(10 marks)

Q4 (a) For the network in **Figure Q4(a)**:

- (i) Determine the value of resistor R for maximum power to R . (4 marks)
- (ii) Determine the maximum power to resistor R . (8 marks)

- (b) Determine the Norton equivalent circuit for the networks of **Figure Q4(b)** external to the resistor R .

(8 marks)

Q5 (a) For the series circuit of **Figure Q5(a)**:

- (i) Determine the mathematical expressions for inductor current i_L and voltage v_L following the closing of the switch.

(8 marks)

- (ii) Determine inductor current i_L and voltage v_L after one time constant.

(4 marks)

- (b) Find the necessary current to establish a flux of 3×10^{-4} Wb in the series magnetic circuit in **Figure Q5(b)**. Please refer to **Figure Q5(c)** and **Figure Q5(d)** for normal magnetization curve.

(8 marks)

Q6 (a) For the circuit of **Figure Q6(a)**:

- (i) Find the time required for capacitor voltage v_c to reach 60 V following the closing of the switch.

(8 marks)

- (ii) Calculate the capacitor current i_C at the instant capacitor voltage $v_c = 60$ V.

(6 marks)

- (b) Find the sinusoidal expression for the applied voltage e_{in} for the system of **Figure Q6(b)** if

$$V_a = 60 \sin(\omega t + 30^\circ)$$

$$V_b = 30 \sin(\omega t - 30^\circ)$$


$$V_c = 40 \sin(\omega t + 120^\circ)$$



(6 marks)



Q7 Write the analytical expression for the waveforms of **Figure Q7** with the phase angle in degrees.



(20 marks)

- END OF QUESTION -

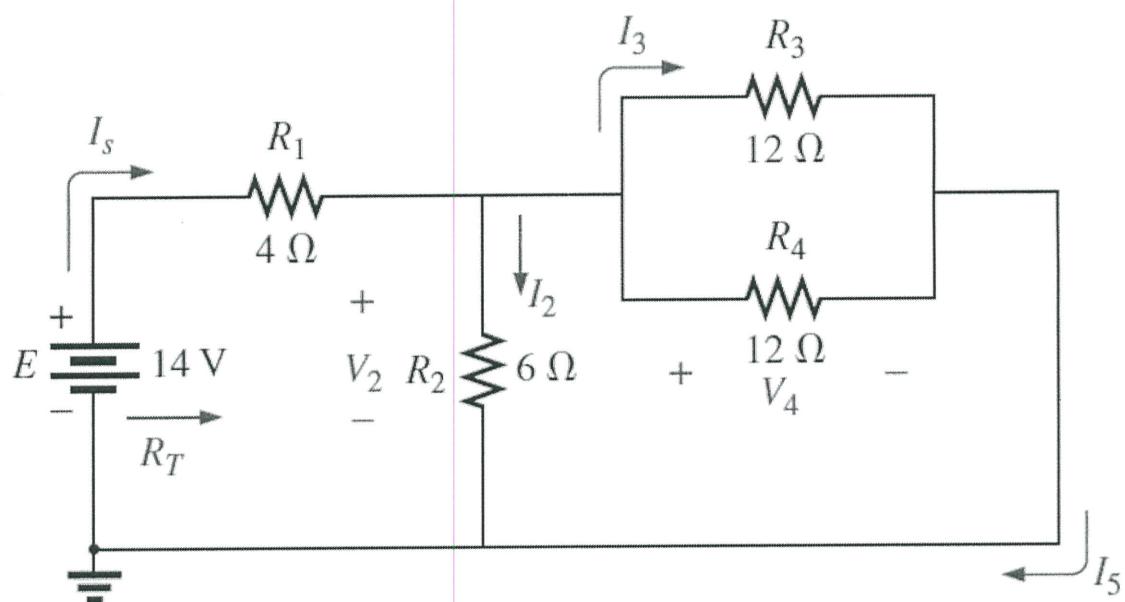FINAL EXAMINATIONSEMESTER / SESSION: SEM I/ 2015/2016
COURSE: ELECTRICAL PRINCIPLES IPROGRAMME: 1 DAR
COURSE CODE: DAR 11003**FIGURE Q1**

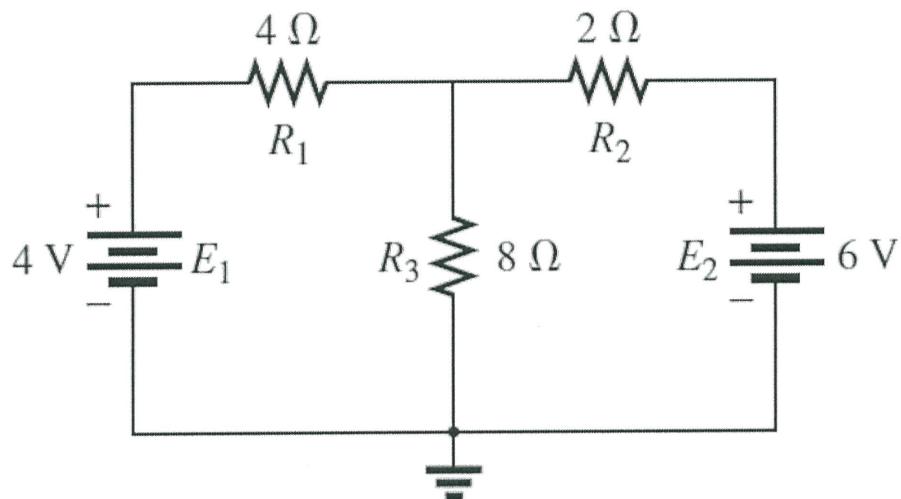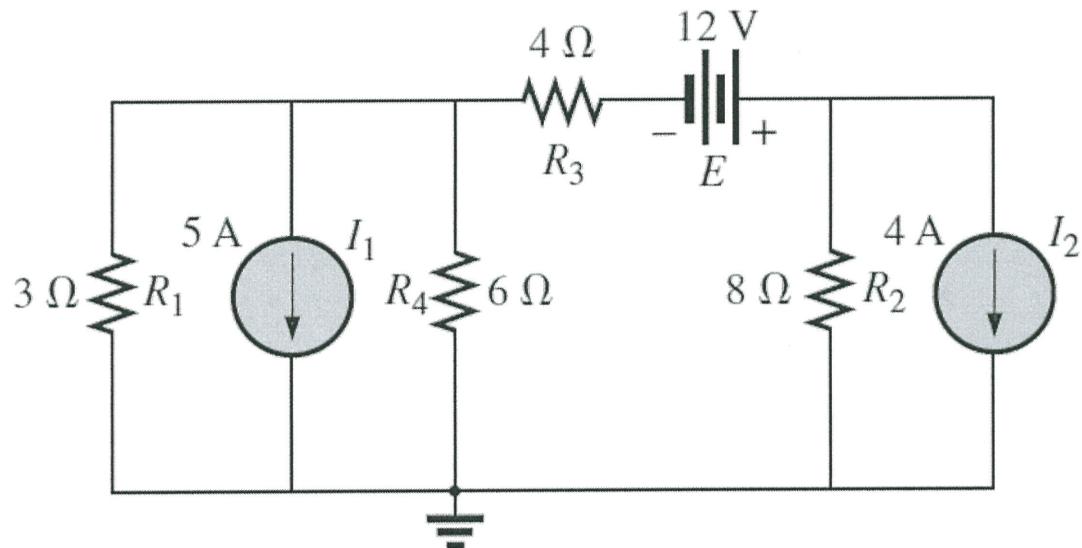FINAL EXAMINATIONSEMESTER / SESSION: SEM I/ 2015/2016
COURSE: ELECTRICAL PRINCIPLES IPROGRAMME: 1 DAR
COURSE CODE: DAR 11003**FIGURE Q2(a)****FIGURE Q2(b)**

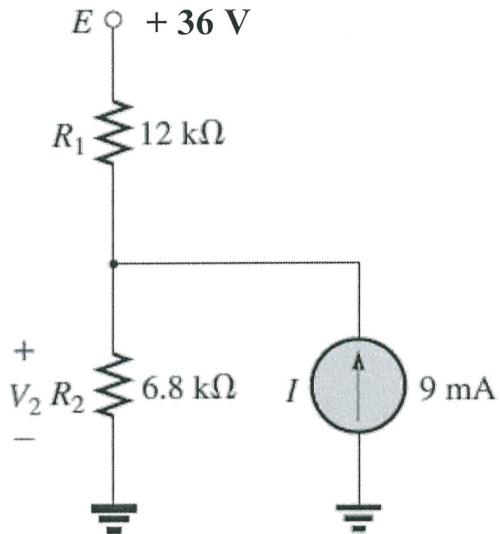
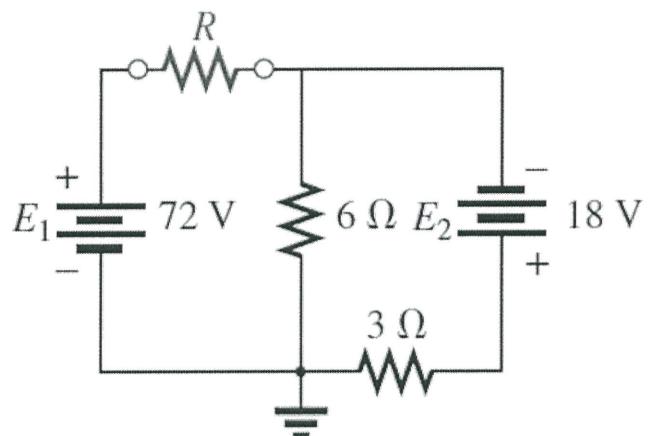
FINAL EXAMINATIONSEMESTER / SESSION: SEM I/ 2015/2016
COURSE: ELECTRICAL PRINCIPLES IPROGRAMME: 1 DAR
COURSE CODE: DAR 11003**FIGURE Q3(a)****FIGURE Q3(b)**

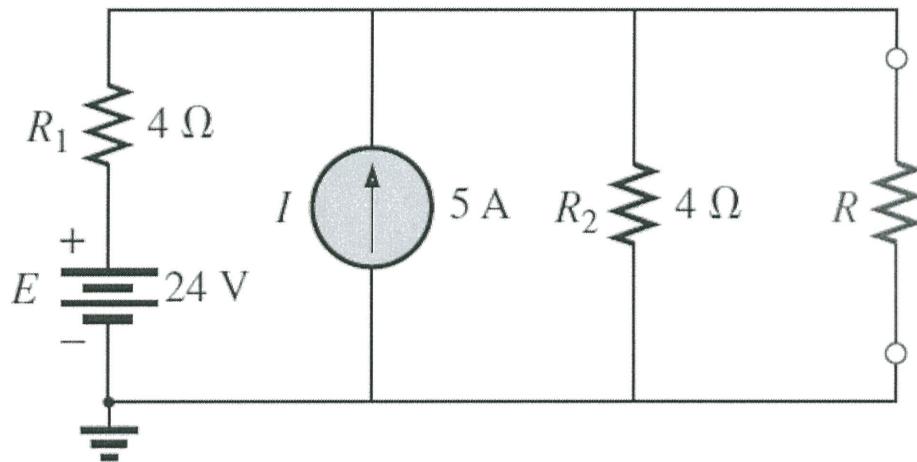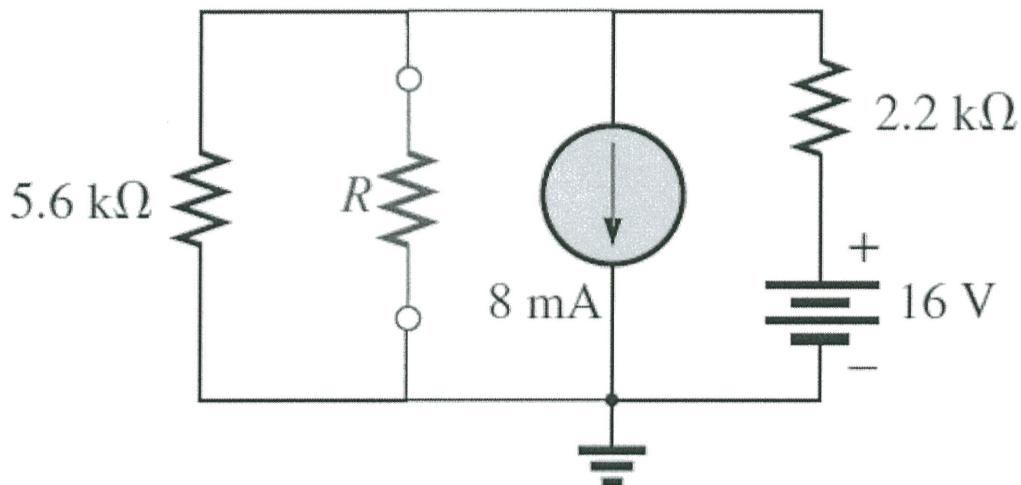FINAL EXAMINATIONSEMESTER / SESSION: SEM I/ 2015/2016
COURSE: ELECTRICAL PRINCIPLES IPROGRAMME: 1 DAR
COURSE CODE: DAR 11003**FIGURE Q4(a)****FIGURE Q4(b)**

FINAL EXAMINATION


SEMESTER / SESSION: SEM I / 2015/2016
 COURSE: ELECTRICAL PRINCIPLES I


PROGRAMME: 1 DAR
 COURSE CODE: DAR 11003

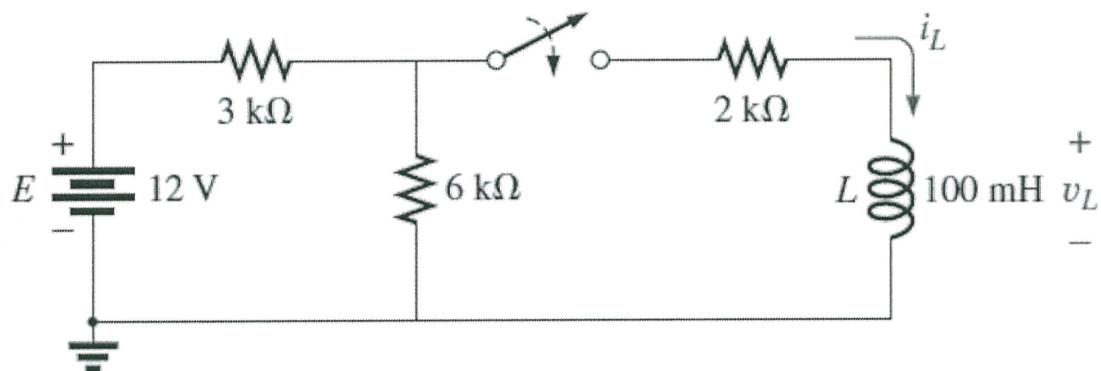
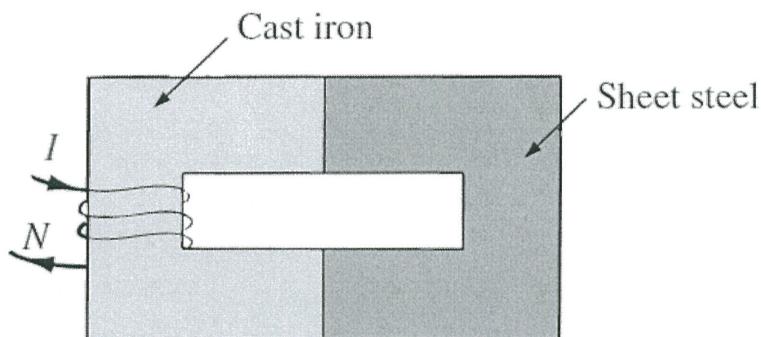
**FIGURE Q5(a)**

$$\begin{aligned}l_{\text{iron core}} &= l_{\text{steel core}} = 0.3 \text{ m} \\ \text{Area (throughout)} &= 5 \times 10^{-4} \text{ m}^2 \\ N &= 100 \text{ turns}\end{aligned}$$

FIGURE Q5(b)

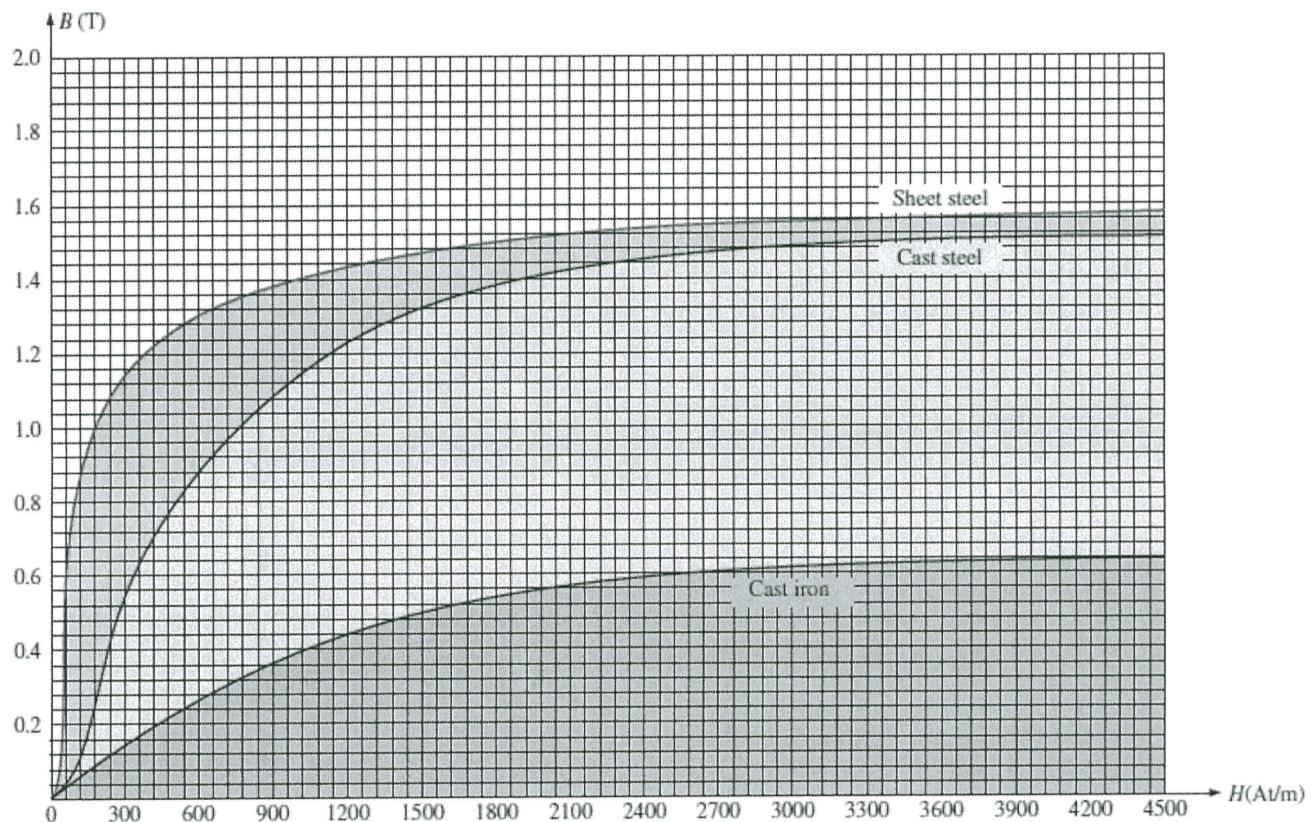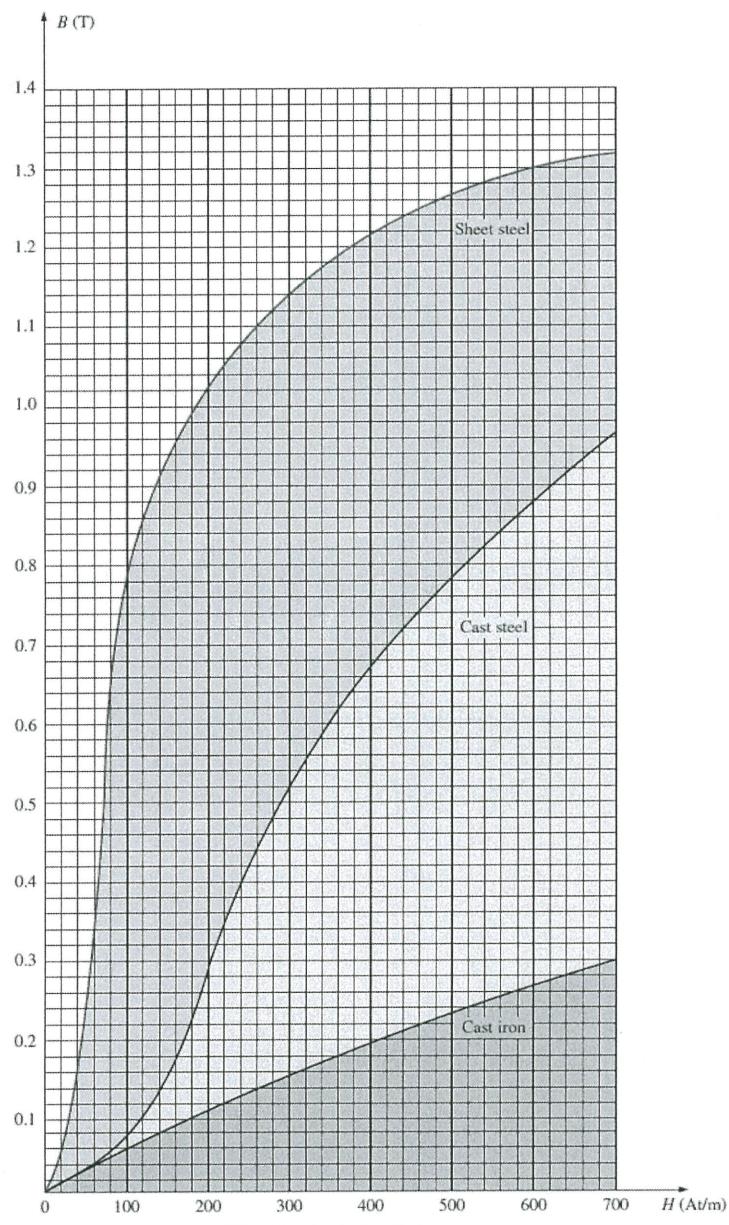FINAL EXAMINATIONSEMESTER / SESSION: SEM I/ 2015/2016
COURSE: ELECTRICAL PRINCIPLES IPROGRAMME: 1 DAR
COURSE CODE: DAR 11003**FIGURE Q5(c)***Normal magnetization curve for three ferromagnetic materials.*


FINAL EXAMINATIONSEMESTER / SESSION: SEM I/ 2015/2016
COURSE: ELECTRICAL PRINCIPLES IPROGRAMME: 1 DAR
COURSE CODE: DAR 11003**FIGURE Q5(d)***Expanded view of Figure Q5(c) for the low magnetizing force region.*

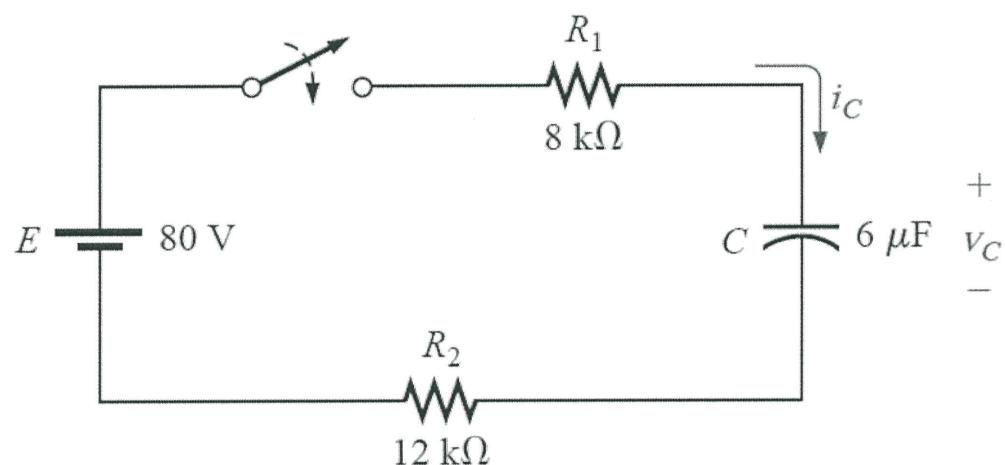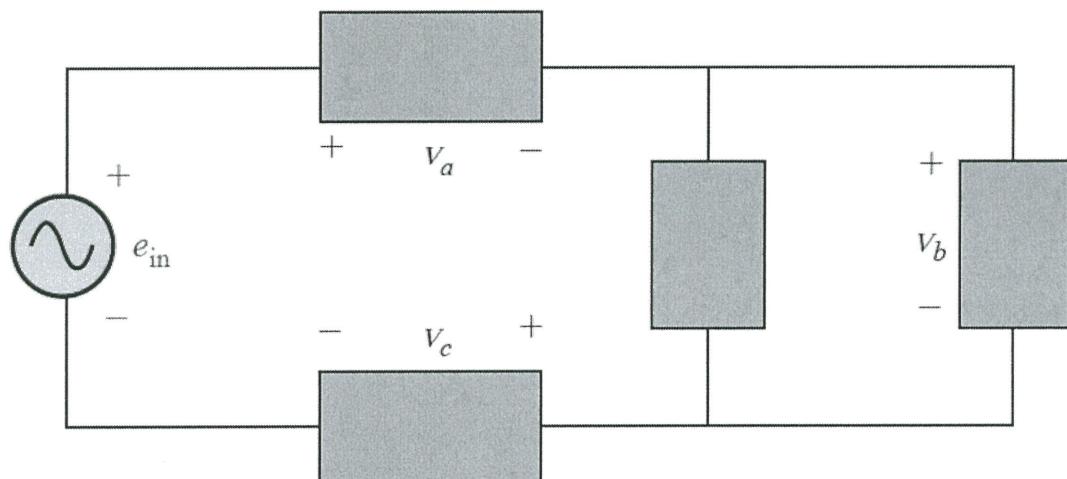FINAL EXAMINATIONSEMESTER / SESSION: SEM I/ 2015/2016
COURSE: ELECTRICAL PRINCIPLES IPROGRAMME: 1 DAR
COURSE CODE: DAR 11003**FIGURE Q6(a)****FIGURE 6(b)**


FINAL EXAMINATION

SEMESTER / SESSION: SEM I / 2015/2016
COURSE: ELECTRICAL PRINCIPLES I


PROGRAMME: 1 DAR
COURSE CODE: DAR 11003

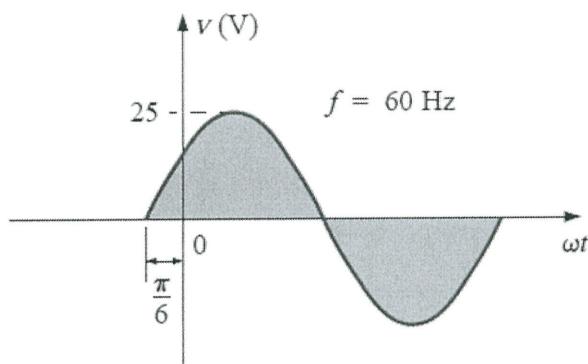


(a)

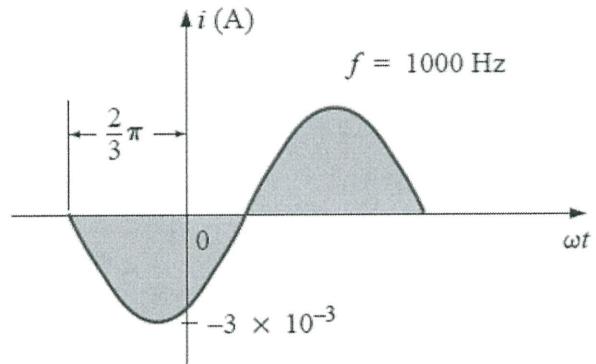

(b)

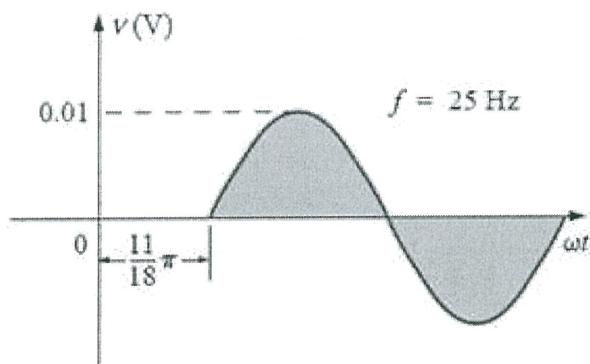

(c)

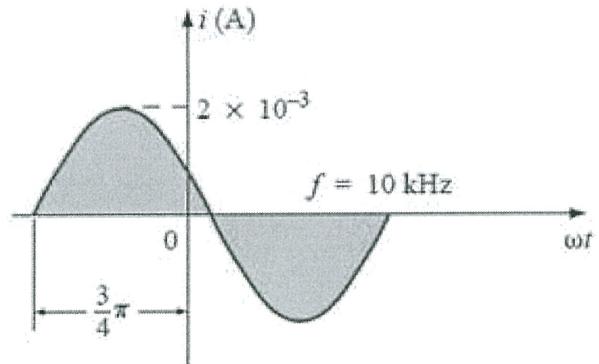

(d)

FIGURE Q7