

**CONFIDENTIAL**



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER I  
SESSION 2015/2016**

COURSE NAME : LOGIC SYSTEMS  
COURSE CODE : DAE 21603  
PROGRAMME : 2 DAE  
EXAMINATION DATE : DECEMBER 2015/ JANUARY 2016  
DURATION : 2 HOURS 30 MINUTES  
INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS  
ONLY

THIS QUESTION PAPER CONSISTS OF **EIGHT (8)** PAGES

**CONFIDENTIAL**

- Q1**
- (a) Explain **two** primary of logic circuit. (3 marks)
  - (b) What is the difference between latche and flip-flop operation. (3 marks)
  - (c) There a **four** primary types of flip-flop,( SR, D, JK and T )
    - (i) Show the symbol and truth table for each type.
    - (ii) Show how to create a T flip-flop from JK flip-flop. (14 marks)
  - (d) Given J, K, Preset, Clear and Clok input for a JK flip-flop in **Figure Q1(d)**.
    - (i) Draw the Q output waveform (5 marks )
- Q2**
- (a) Explain briefly two application of flip-flop. (4 marks)
  - (b) For the circuit in **Figure Q2(b)**:
    - (i) State the function of this circuit.
    - (ii) Determine the external resistors R1 and R2 to give output frequency of 20kHz and duty cycle of 60% if the external capacitor C is 3nF. (7 marks)
  - (c) By using JK flip-flop as a ripple counter to count up counter.
    - (i) Draw the circuit diagram.
    - (ii) Draw the timing diagram as **Figure Q2(c)**.
    - (iii) Modify the circuit to operate as a MOD 6 counter.
    - (iv) If the input klok frequency is 4 kHz, determine the output frequency of the MOD 6 counter. (14 marks)

- Q3** (a) Compare the main features of synchronous and asynchronous counters. (4 marks)
- (b) The logic diagram and Dual-In-Line Package for IC 7493 is given in **Figure Q3(b)**. Draw the connections diagrams for the following 7493-based counters and determine the output frequency if the input clock frequency is 200 kHz. Show all steps and label the input clock as well as the outputs.
- (i) MOD 9 counter
  - (ii) MOD 12 counter
- (6 marks)
- (c) Design a synchronous counter using JK flip-flop to count 4 digits. The count sequence is 0,2,4,6 and repeat. The JK excitation table is shown in **Table Q3(c)**. Show all steps and the design should include the following :
- (i) State diagram
  - (ii) Circuit excitation table used to determine JK flip-flop inputs.
  - (iii) K-maps used to generate minimal expressions for JK inputs.
  - (iv) Logic circuit.
- (15 marks)
- Q4** (a) Explain the data movement in shift registers. (4 marks)
- (b) Determine the number of flip-flops needed to construct a shift register capable of storing :
- (i) a 5-bit binary number
  - (ii) Draw the logic diagram as a serial input/serial output shift register. (6 marks)
- (c) With the aid of logic circuits and tables showing the sequence of states, describe the differences between a Ring counter and a Johnson counter. (15 marks)

- Q5** (a) Describe **five (5)** basic steps taken to create and load a digital circuit into a PLD. (5 marks)
- (b) Name **three (3)** advantages of constructing a digital circuit prototype using a PLD instead of standard logic devices. (3 marks)
- (c) Several types of architecture are used in PLDs. Draw the block diagram of three common types and describe their differences. (6 marks)
- (d) Use the PLA in **Figure Q5(d)** to implement the following functions. Label all inputs and outputs.

(i)  $F1(W, X, Y) = \sum(1,2,3,5,7)$

(ii)  $F2(W, X, Y) = \sum(0,4,6,7)$

(11 marks)

- Q6** (a) **Figure Q6(a)** shows a simplified view of a typical computer system.
- (i) Describe the semiconductor memory devices used.
- (ii) Explain the differences between the **three (3)** storage devices based on the technology each uses.
- (iii) Describe the functions of the **three (3)** buses shown. (13 marks)

- (b) A certain memory has a capacity of 4K x 8, determine
- (i) the number of data inputs and data outputs .
- (ii) the number of address lines.
- (iii) its capacity in bytes. (6 marks)

- (c) List and describe the **three (3)** major operations in a flash memory. (6 marks)

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2015/2016  
 COURSE NAME : LOGIC SYSTEMS

PROGRAMME : 2 DAE  
 COURSE CODE: DAE 21603

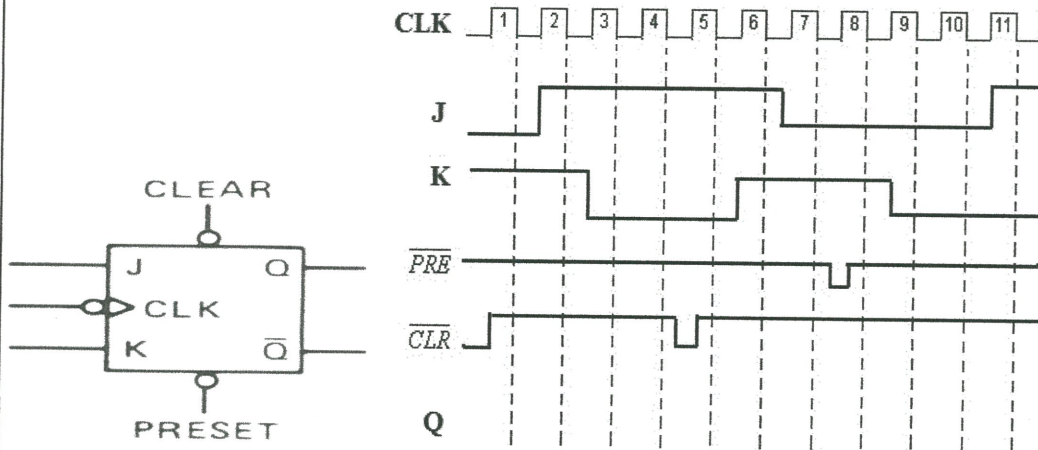


FIGURE Q1(d)


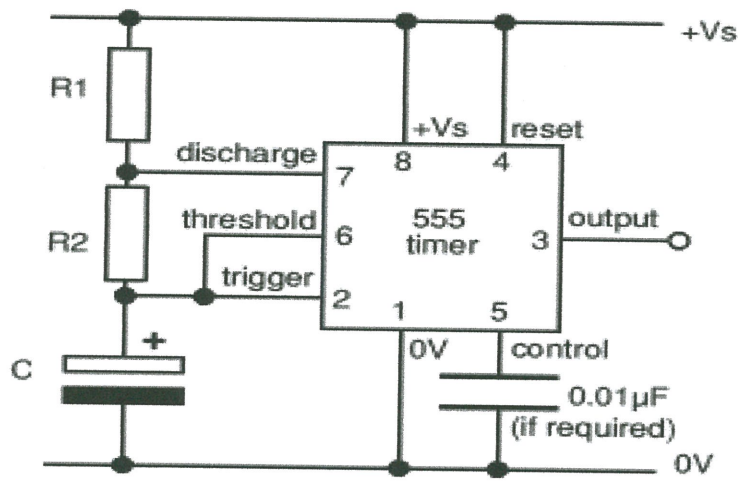


FIGURE Q2(b)


**FINAL EXAMINATION**

SEMESTER/SESSION: SEM I/2015/2016  
 COURSE NAME : LOGIC SYSTEMS


PROGRAMME : 2 DAE  
 COURSE CODE: DAE 21603

 

**FIGURE Q2(c)**

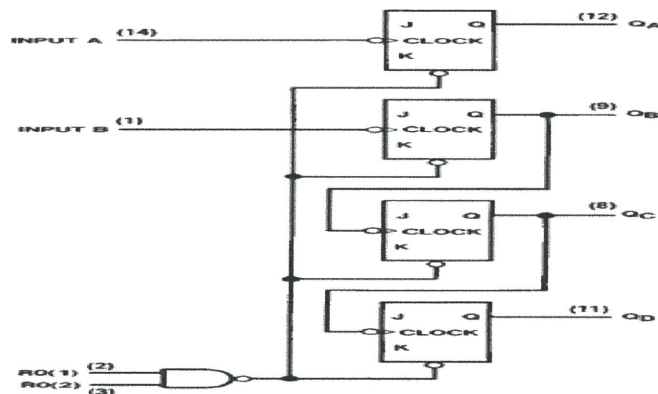

Dual-In-Line Package

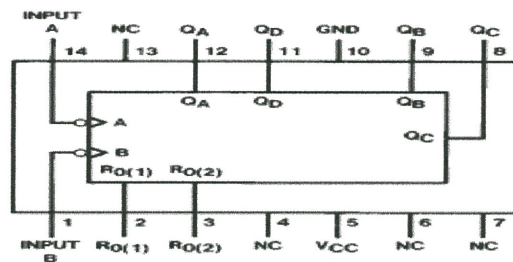

**FIGURE Q3(b)**


**FINAL EXAMINATION**

SEMESTER/SESSION: SEM I/2015/2016  
COURSE NAME : LOGIC SYSTEMS

PROGRAMME : 2 DAE  
COURSE CODE: DAE 21603

**TABLE Q3(c): JK Excitation Table**

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

 


**FIGURE Q5(d)**

**FINAL EXAMINATION**

SEMESTER/SESSION: SEM I/2015/2016  
COURSE NAME : LOGIC SYSTEMS

PROGRAMME : 2 DAE  
COURSE CODE: DAE 21603

 

**FIGURE Q6(a)**