



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER I  
SESSION 2015/2016**

**COURSE NAME** : POLYPHASE CIRCUIT ANALYSIS  
**COURSE CODE** : BEF 23803  
**PROGRAMME** : BACHELOR OF ELECTRICAL  
ENGINEERING WITH HONOURS  
**EXAMINATION DATE** : DECEMBER 2015 / JANUARY 2016  
**DURATION** : 3 HOURS  
**INSTRUCTION** : ANSWER ALL QUESTIONS

**THIS QUESTION PAPER CONSISTS OF SIX (6) PAGES**

- Q1** (a) Explain what is meant by an unbalanced three-phase system. Illustrate your answer with a proper circuit diagram. (3 marks)
- (b) A 210-V balanced three-phase voltage source feeds an unbalanced four-wire, star-connected load. The branch impedances of the load are:  $Z_1 = 10 + j10\Omega$ ,  $Z_2 = 12 + j2\Omega$ ,  $Z_3 = 2 + j2\Omega$ . Assume RYB phase sequence.
- (i) Draw the circuit diagram of load connections (3 marks)
- (ii) Determine the voltage across each phase of the load,  $V_{RN}$ ,  $V_{YN}$ , and  $V_{BN}$ . (3 marks)
- (iii) Find the current through each phase of the load,  $I_R$ ,  $I_Y$ ,  $I_B$  and the neutral current,  $I_N$ . (8 marks)
- (iv) Based on the results obtained from **Q1(b)(iii)**, draw the complete phasor diagram. (3 marks)
- Q2** A  $10\Omega$  resistor, 20mH inductor and  $100\mu\text{F}$  capacitor are connected in series across an ac supply as shown in **Figure Q2**. Given :  $V_S(t) = 220 \cos 1000t$
- (i) Find the load current. (3 marks)
- (ii) Determine the voltage drop across each element,  $V_R$ ,  $V_L$  and  $V_C$ . (6 marks)
- (iii) Calculate the complex power supplied by the source,  $S_V$  and the complex power absorbed of each element,  $S_R$ ,  $S_L$  and  $S_C$ . (8 marks)
- (iv) Calculate the total power absorbed by all three passive elements. (3 marks)
- Q3** **Figure Q3** shows an unbalanced three-wire star load connected to a balanced three-phase, 415V, 50Hz supply. Assume the phase sequence is RYB and take  $V_{RN}$  as the reference phasor. Using Millman's theorem, calculate
- (i) The potential difference between the two star points. (9 marks)

- (ii) Load phase voltages  $V_{RN}$ ,  $V_{YN}$ , and  $V_{BN}$ . (3 marks)
- (iii) Line currents  $I_R$ ,  $I_Y$  and  $I_B$ . (3 marks)
- (iv) The complex power absorbed by each phase load. (3 marks)
- (v) Total complex power supplied to the load. (2 marks)

**Q4** **Figure Q4** shows the single line diagram of an industrial centre. The centre is supplied by a balanced three-phase source with a line voltage of 415 V, 50 Hz and has two balanced three-phase loads as follows:

Load 1: 160 kW at 0.7 pf lagging  
Load 2: 120 kVA at 0.85 pf lagging

Calculate

- (i) The total active consumed by the two loads (4 marks)
- (ii) The total reactive power supplied by the source (3 marks)
- (iii) The system apparent power (1 mark)
- (iv) The system power factor (1 mark)
- (v) The feeder current (1 mark)
- (vi) The size of the shunt capacitor required to raise the system power factor to 0.9 lagging. (8 marks)
- (vii) The feeder current after the power factor correction. (2 marks)

# CONFIDENTIAL

BEF23803

**Q5** (a) A Y-connected 120 MVA, 13.6 kV generator has a phase winding reactance of  $j25\%$ . If the generator above is short-circuited at its terminals, find the short circuit current and the short circuit power delivered by the generator

(i) in p.u.

(6 marks)

(ii) in %,

(2 marks)

(iii) in the actual units.

(2 marks)

(b) **Figure Q5(b)** shows a 400V, 50Hz, single-phase generator supplying power to an impedance  $Z_L$  through a single-phase 30 kVA, 415/110 V, 50 Hz transformer. The transformer has a leakage reactance of  $j0.81 \Omega$  and the load has an impedance  $Z_L = (0.9 + j0.2) \Omega$ .

(i) Draw the per-unit circuit, labeling all values.

(7 marks)

(ii) Using per unit analysis with an  $S_{base}$  of 30 kVA, and voltage base of 415V determine

(a) The per-unit load current

(1 mark)

(b) The actual load current

(1 mark)

(c) The current supplied by the generator

(1 mark)

- END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER/SESSION : I / 2015/2016  
COURSE : POLYPHASE CIRCUIT ANALYSIS

PROGRAMME : 2 BEV  
COURSE CODE : BEF23803

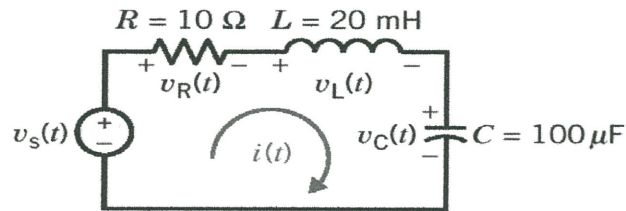


FIGURE Q2


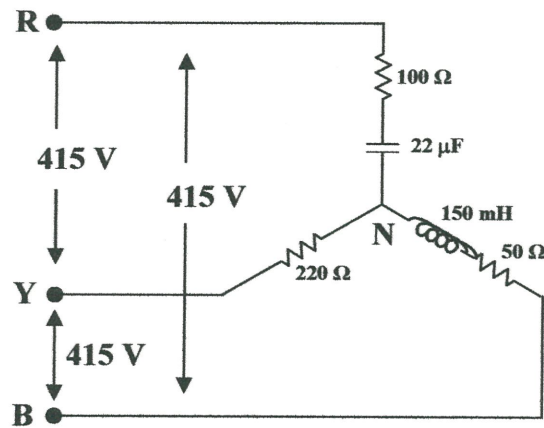


FIGURE Q3


**FINAL EXAMINATION**

SEMESTER/SESSION : I / 2015/2016  
COURSE : POLYPHASE CIRCUIT ANALYSIS

PROGRAMME : 2 BEV  
COURSE CODE : BEF23803

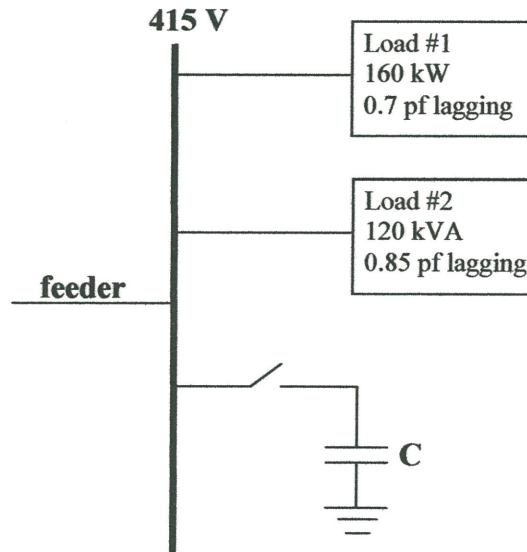

**FIGURE Q4**

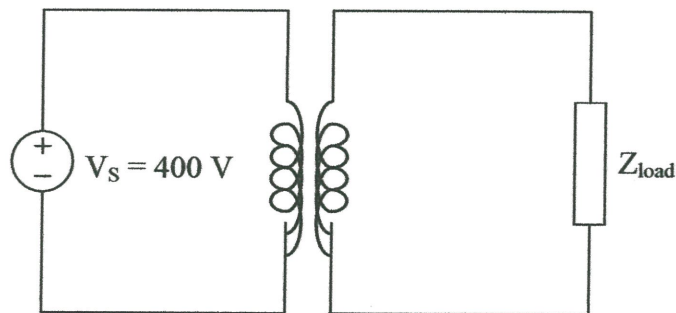

Step-down  
transformer  
30 kVA,  
415/100 V  
 $Z_{eq2} = j0.81\Omega$

**FIGURE Q5(b)**