

**CONFIDENTIAL**



**UTHM**

Universiti Tun Hussein Onn Malaysia

**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESSION 2015/2016**

COURSE NAME : DIGITAL ELECTRONICS  
COURSE CODE : DAE 21203  
PROGRAMME : 1 DAE  
EXAMINATION DATE : JUNE / JULY 2016  
DURATION : 2 HOURS 30 MINUTES  
INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF **SEVEN (7)** PAGES

**CONFIDENTIAL**

- Q1**
- (a) The compact disk (CD) player is an example of a system in which both digital and analog circuits are used. Draw and label clearly the block diagram that represents the basic principles of a CD player. (5 marks)
  - (b) Explain **four (4)** advantages of digital techniques. (4 marks)
  - (c) For the timing diagram in **Figure Q1(c)**:
    - (i) Determine the number of cycles displayed of waveform a, b and c. (3 marks)
    - (ii) For the input signal of a, b and c, find the period, frequency and duty cycle (6 marks)
    - (iii) Build the truth table for the timing diagram showing all inputs and output, a, b, c and F. (4 marks)
  - (d) A pulse waveform with a frequency of 50 kHz is applied to the input of a counter. Determine how many pulses are counted during 100 ms. (3 marks)

- Q2**
- (a) Convert hexadecimal number  $A3_{hex}$  to:
    - (i) Binary number system.
    - (ii) Decimal number system.
    - (iii) BCD code
    - (iv) Gray code
 (8 marks)
  - (b) Given the Boolean expression

$$Z = \overline{\overline{PQ} \cdot (RS + \overline{PS}) \cdot (\overline{PQ} + \overline{RS})}$$

- (i) Design the logic circuit from the Boolean equation. (5 marks)
- (ii) Simplify expression Z using Boolean theorem. (5 marks)
- (iii) Implement the function Z in **Q2 (b) (ii)** using only a 2-input NAND gates. (7 marks)

**Q3.** (a) **Figure Q3 (a)** shows a combinational logic circuit designed to control the operation of a conveyor belt in Factory X.

(i) Simplify the Boolean expression for output Y from this combinational logic circuit.

(7 marks)

(ii) Draw the logic circuit from the simplified expression in **Q3(a)(i)**.

(3 marks)

(b) By using Boolean theorem, prove the following Boolean expressions:

$$\overline{\overline{A.B.A}}.\overline{\overline{A.B.B}} = A \oplus B$$

(5 marks)

(c) For the circuit in **Figure Q3(c)**

(i) Build the truth table

(ii) Write the Boolean expression for the output

(10 marks)

**Q4** (a) Find the simple expression for the output Z base on the truth table below

W	X	Y	Z
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

(4 marks)

(b) For the following function:

$$F(W, X, Y, Z) = \sum(0,5,7,8,10,13,14,15) + d(2,3,4)$$

- (i) Build the truth table (4 marks)
- (ii) Simplify using a Karnaugh map (4 marks)
- (iii) Obtain the minimum sum of product (SOP) expression (2 marks)
- (iv) Implement the simplified expression using basic logic gates (3 marks)

(c) A combinational logic circuit which has one output Z and four (4) inputs (A,B,C,D) representing binary number. Output Z should be **HIGH (1)** if the input is at least 5 but not greater than 11.

- (i) Build the truth table (4 marks)
- (ii) Write the minterm expression for the Z (2 marks)
- (iii) Write the maxterm expression for the Z (2 marks)

**Q5.** (a) Solve the following arithmetics operations. Check the answer with its Decimal equivalent.

- (i)  $101_2 + 100_2$
- (ii)  $110_2 - 101_2$
- (iii)  $1001_2 \times 1011_2$
- (iv)  $+18_{10} - 25_{10}$  using 2's complement (9 marks)

(b) A word length is 6 bits ( including sign bit ), change the binary number into decimal in 2's complement.

- (i)  $100001_2$
- (ii)  $010001_2$  (6 marks)

- (c) A full adder has three (3) inputs A, B and  $C_{in}$  and two (2) outputs SUM and  $C_{out}$ .
- Produce the truth table for the full adder.
  - Write the minimum SUM expression by using Boolean Algebra.
  - Write the minimum  $C_{out}$  expression by using Karnaugh map.

(10 marks)

**Q6.** (a) Consider a half adder :

- Draw the logic symbol
- Build the truth table showing all the inputs and outputs ( SUM and  $C_{out}$  )
- Write the expression for both outputs

(6 marks)

(b) With the aids of diagrams, describe the function of the following device ;

- A decoder
- A encoder

(6 marks)

(c) **Figure Q6(c)** is a logic symbol for the 4 bit 7483 parallel adder . Find the sum S and carry output  $C_{out}$  for the addition below( assume  $C_{in}$  is 0 ):

- $A_1A_2A_3A_4 = 1010$  and  $B_1B_2B_3B_4 = 1101$
- $A_1A_2A_3A_4 = 1110$  and  $B_1B_2B_3B_4 = 0111$

(6 marks)

(d) Design an 8-1 multiplexer using:

- 4-1 multiplexers
- Implement expression  $F(X, Y, Z) = \sum m(0,1,4,7)$
- implement expression  $F(X, Y, Z) = \prod m(0, 2, 5, 6)$

(7 marks)

- END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2015/2016  
 COURSE NAME : DIGITAL ELECTRONICS

PROGRAMME : 2DAE  
 COURSE CODE: DAE 21203

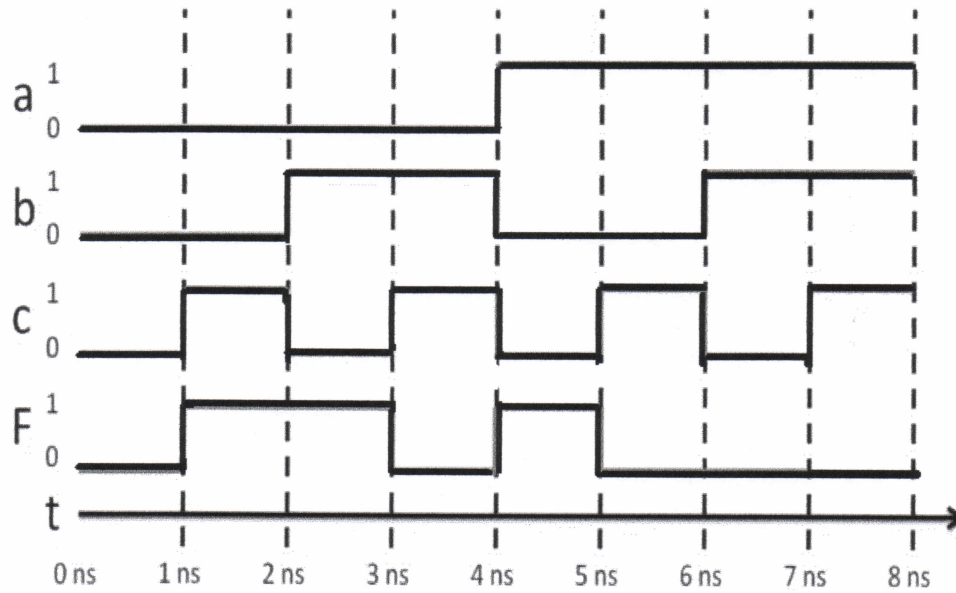


FIGURE Q1(c)

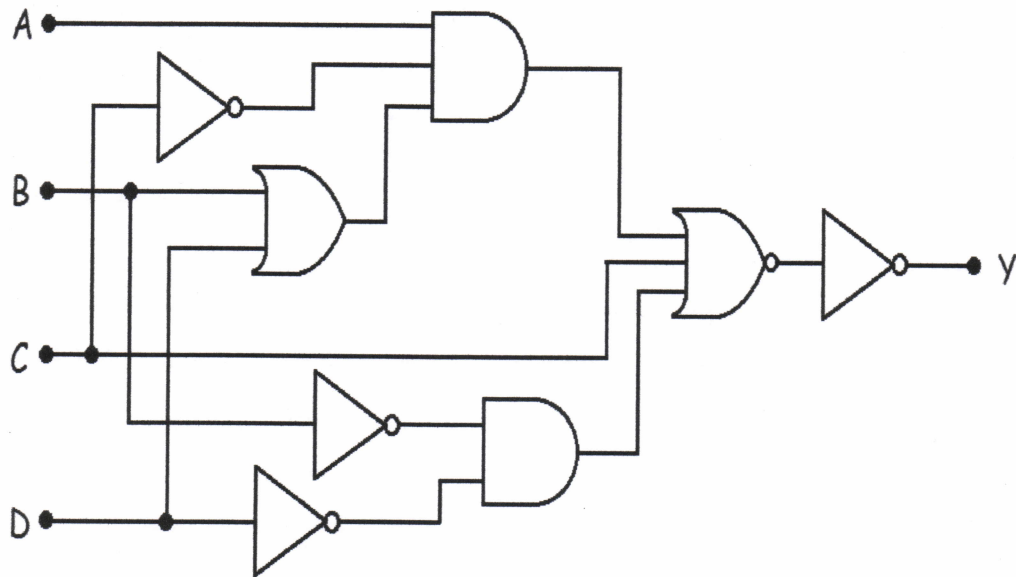


FIGURE Q3(a)

MOHD SABANI BIN HJ. MOHD  
 Puanjil Kurni  
 Pusat Pengajaran Elektronik  
 Universiti Tun Hussein Onn Malaysia

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2015/2016  
COURSE NAME : DIGITAL ELECTRONICS

PROGRAMME : 2DAE  
COURSE CODE: DAE 21203

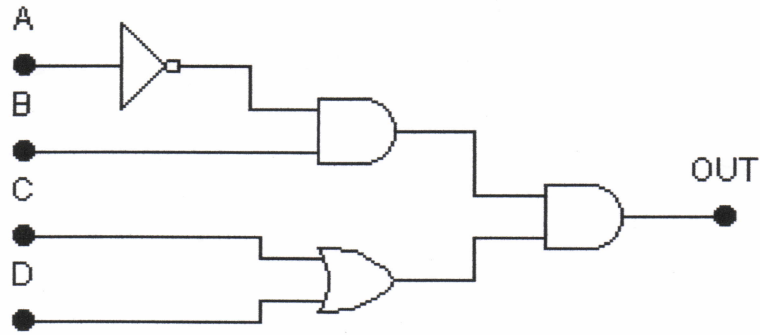


FIGURE Q3(c)

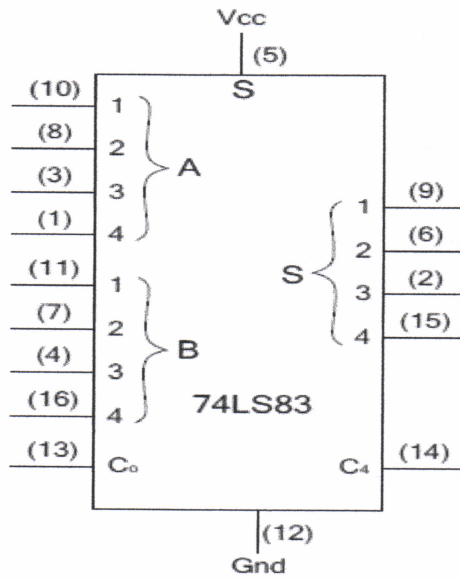


FIGURE Q6(c)