



**UTHM**  
Universiti Tun Hussein Onn Malaysia

**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
(TAKE HOME)  
SEMESTER II  
SESSION 2019/2020**

COURSE NAME : ANALOG ELECTRONICS  
COURSE CODE : BEJ 10503/BEL 10203  
PROGRAMME : BEJ/BEV  
EXAMINATION DATE : JULY 2020  
DURATION : 6 HOURS  
INSTRUCTION : ANSWER ALL QUESTIONS.  
**OPEN BOOK EXAMINATION**

**TERBUKA**

THIS QUESTION PAPER CONSISTS OF **FOUR (4)** PAGES

Q1 The Common-Emitter configuration circuit is shown in **Figure Q1** with  $V_{BE} = 0.7 \text{ V}$ .


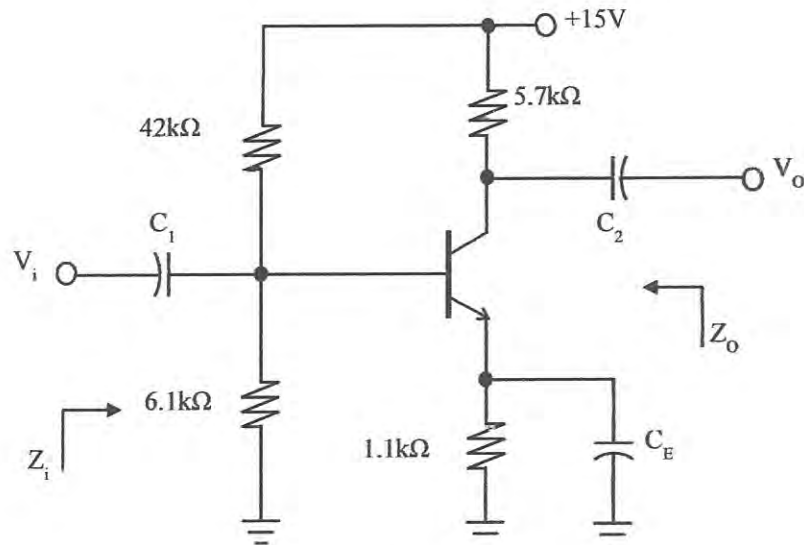


Figure Q1

- Name the type of the biased-circuit shown in **Figure Q1** and give **TWO (2)** advantages of this circuit compared to fixed biased-circuit. (5 marks)
- Analyze the circuit and determine current,  $I_B$ ,  $I_C$  and  $I_E$  and output voltage,  $V_{CE}$ . (15 marks)
- If  $R_E$  is removed from the circuit in **Figure Q1**, draw the small signal AC equivalent circuit using  $r_e$  model for this new circuit. (5 marks)
- Determine the input impedance,  $Z_i$ , output impedance,  $Z_o$  and voltage gain,  $A_v$  for the small signal AC equivalent circuit in part **Q1(c)**. (10 marks)

**Q2** A Field Effect Transistor (FET) circuit has a MATLAB plot of the transfer characteristics curve and the bias line as in **Figure Q2**. Based on the specifications given as follows:

$$V_{DD} = 15 \text{ V}, V_{DS} = 5.475 \text{ V and } I_1 = I_2 = \frac{V_{DD}}{R_1 + R_2} = 16.67 \mu\text{A};$$

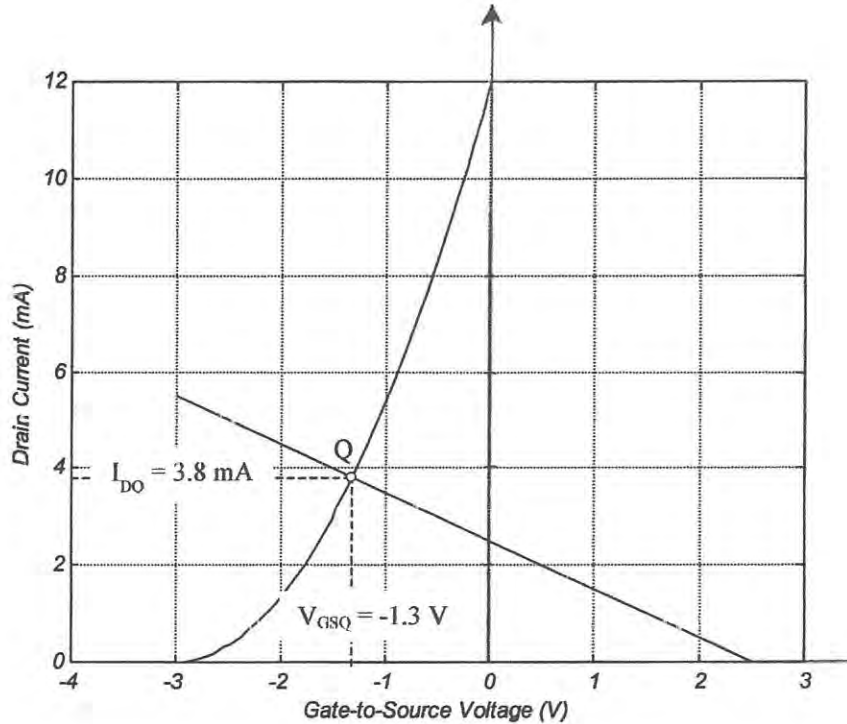

**Figure Q2**

- (a) Design and sketch the Field Effect Transistor (FET) circuit (with bypass capacitor). (10 marks)
- (b) Determine the value of all resistors. (15 marks)
- (c) Draw the AC equivalent of the circuit. (4 marks)
- (d) Calculate its input impedance  $Z_i$ , output impedance  $Z_o$  and voltage gain  $A_v$ . Assume  $r_d \geq 10R_D$ . (6 marks)

**TERBUKA**

**Q3** Figure Q3 is an amplifier circuit that only amplifies the signals of specified frequencies. Assume that the BJT transistor has an infinite value of AC collector resistance,  $r_o$  (or  $r_c$ ) with  $r_e = 28.48 \Omega$ ,  $R_S = 0.82 \text{ k}\Omega$  and  $A_v = -72.91$ ;

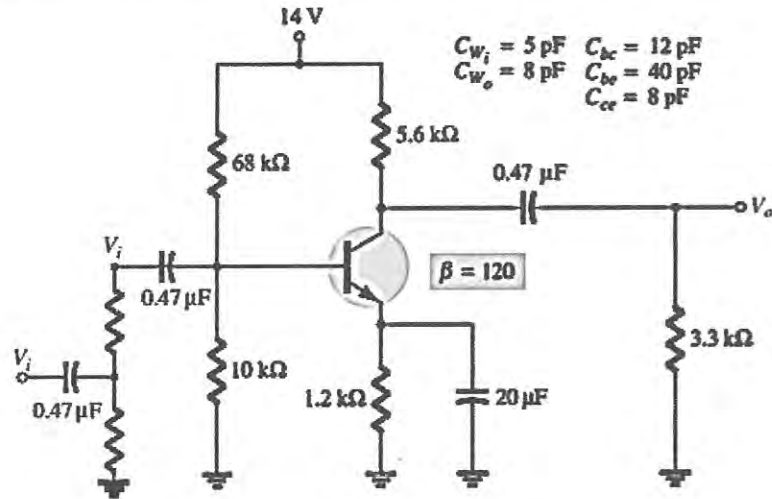


Figure Q3

- (a) Sketch the high- frequency ac equivalent model of Figure Q3. (8 marks)
- (b) Determine the input high cutoff frequency,  $f_{Hi}$  and output high cutoff frequency,  $f_{Ho}$ . (15 marks)
- (c) State the dominant high cut-off frequency,  $f_H$ . (2 marks)
- (d) Sketch the frequency response for high cut-off frequency. (5 marks)

- END OF QUESTIONS -