

**CONFIDENTIAL**



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
(TAKE HOME)  
SEMESTER II  
SESSION 2019/2020**

COURSE NAME : DIGITAL DESIGN  
COURSE CODE : BEC30503  
PROGRAMME CODE : BEJ  
EXAMINATION DATE : JULY 2020  
DURATION : 5 HOURS  
INSTRUCTION : ANSWER ONE QUESTION IN SECTION A AND ALL QUESTIONS IN SECTION B. OPEN BOOK EXAMINATION

**TERBUKA**

THIS QUESTION PAPER CONSISTS OF **SIX (6)** PAGES

**CONFIDENTIAL**

SECTION A

**Q1** The data flow graph (DFG) given in **Figure Q1** shows the operations and data dependencies of a digital system to be designed. *a*, *b*, *c*, *d* and *e* are all 8-bit data inputs that are registered in the initial state and *f* is the output.

- (a) If the design is constrained to three arithmetic units, where each arithmetic unit contains a multiplier and an adder. Construct the schedule of this DFG applying “as soon as possible” (ASAP) scheduling. (8 marks)
- (b) Derive the corresponding RTL code for your design. (6 marks)
- (c) Obtain the fbd of the datapath unit of this digital system. (8 marks)
- (d) Obtain the fbd of the control unit showing all the control signals. (8 marks)
- (e) It is given that the propagation delay of the components are as follows: the adder is 30 ns, multiplier is 130 ns and register is 10 ns. Calculate the maximum operating frequency of your design. (5 marks)

 


Figure Q1

**TERBUKA**

**Q2** A digital system is modelled by the RTL code in **Listing Q2**. Assume that  $a$ ,  $b$  and  $c$  are external 8-bit inputs, and the registers are positive-edge triggered. By using the ALU with the functions given in **Table Q2**, answer the following questions. Note that  $m^*$  denotes  $m$  bitwise inverted.

```

S0: ( ) / R1 ← b;
      ( ) / R2 ← c;
S1: ( ) / R1 ← R1 * R2;
S2: (m) / R2 ← 2R2;
      (m*) / R2 ← R1 - R2;
      ( ) / done = 1;
      ( ) / goto S0;
    
```

**Table Q2: ALU operation**

$f_1f_0$	output	function
00	$X * Y$	Multiply
01	$X + Y$	ADD
10	$X - Y$	SUB
11	Y	PASS Y

**Listing Q2: RTL code**

- (a) Derive the functional block diagram (fbd) of the datapath unit (DU) for the digital system in **Q2**. (8 marks)
- (b) Write the Verilog code to model the datapath in **Q2(a)**. (9 marks)
- (c) Derive the fbd of the control unit (CU) showing the state registers, next state block, output block and all the control signals. Note: Group the control signals as a vector formatted as follows:  $sel1, sel2, selY, ld1, ld2, f1, f0, done$ . (6 marks)
- (d) Write the Verilog code to model the control unit in **Q2(c)**. The control vector must be formatted as in **Q2(c)**. (9 marks)
- (e) If the multiply function is not available in the ALU, suggest an option to implement the operation of  $R2 \leftarrow R1 * R2$  in state S1 if Y input is limited to 2, 4 and 8. (3 marks)

**TERBUKA**

## SECTION B

**Q3** (a) A PLD is a general-purpose chip for implementing logic circuits. It contains a collection of logic circuit elements that can be customized in different ways. Discuss the advantage of FPGA as compared to PLA/PAL/CPLD. (3 marks)

(b) The Verilog code in **Listing Q3(b)** is written using dataflow modelling style. Sketch the respective circuit and rewrite the full Verilog code to describe the circuit by using structural modelling style.

```

module Q3(a, b, c, d, f, g);
  input [1:0] a, b, c, d;
  output f, g;

  assign f = (a & b) | (c & d);
  assign g = (a | c) & (b | d);

endmodule

```

Listing Q3(b)

(7 marks)

(c) Derive the fbd that is described by the Verilog code in **Listing Q3(c)**.

```

module Q3(a, b, m, n, z);
  input [1:0] a, b;
  input m, n;
  output reg [0:3]z;
  reg [1:0] w;

  always@(a, b, m)
    if (m == 0)
      w = a + b;
    else
      w = a - b;

  always@(w, n)
    if (n == 0)
      z = 0;
    else
      case(w)
        2'b00: z = 4'h8;
        2'b01: z = 4'h4;
        2'b10: z = 4'h2;
        2'b11: z = 4'h1;
      endcase

endmodule

```

Listing Q3(c)

(10 marks)

- Q4** (a) Referring to the Verilog code fragment in **Listing Q4(a)**, derive the fbd of the module M\_Q4a. Assuming that A, B, C and D are all 4-bit input signals, complete the input/output declaration for module M\_Q4a.

(10 marks)

```

module M_Q4a (K, L, M, A, B, C, D, R);
    .....
    .....
    always@ (negedge K)
    begin
        if (L == 0)
            case (M)
                2'b00: R <= A;
                2'b01: R <= B;
                2'b10: R <= C;
                2'b11: R <= D;
            endcase
        else R <= R;
    end
endmodule

```

Listing Q4(a)

- (b) By referring to the Verilog code in **Listing Q4(b)**, answer the following questions:

```

module M_Q4b (R, L, w, Clock, Q);
    parameter n = 4;
    input [n-1:0] R;
    input L, w, Clock;
    output reg [n-1:0] Q;
    integer k;
    always @(posedge Clock)
    if (L)
        Q <= R;
    else
        begin
            for (k = 0; k < n-1; k = k+1)
                Q[k] <= Q[k+1];
                Q[n-1] <= w;
        end
    endmodule

```

Listing Q4(b)


- (i) Determine the type of operation perform by the circuit of module M\_Q4b.

(2 marks)

- (ii) Verify that the code in **Listing Q4(b)** implements the operation in **Q4(b)(i)**.

(8 marks)


- Q5** (a) Controller is the sequential circuit that implement Finite State Machine (FSM). The design process of a controller begins with capturing the FSM's behavior and then converting the captured behavior into a circuit. Briefly discuss all substeps required to design a controller. (5 marks)
- (b) Consider the FSM of **Figure Q5(b)** that has an input  $m$  and an output  $n$ . Design a controller to implement the **Figure Q5(b)** using a state register and logic gates. Clearly show all the design steps.

 

**Figure Q5(b)**

(10 marks)

- (c) **Figure Q5(c)** shows a block diagram of a serial adder. Explain the operation of the circuit by using a suitable example. Assume that the operation is 4-bit.

 

**Figure Q5(c)**

(5 marks)

-END OF QUESTIONS -

