



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
(TAKE HOME)
SEMESTER II
SESSION 2019/2020**

COURSE NAME : ELECTRIC CIRCUITS I / ELECTRIC
CIRCUIT ANALYSIS I

COURSE CODE : BEV10303 / BEF12403

PROGRAMME : BEV

EXAMINATION DATE : JULY 2020

DURATION : 4 HOURS

INSTRUCTION : 1) ANSWER ALL QUESTIONS
2) THE ANSWER BOOKLET NEEDS
TO BE SUBMITTED 30 MINUTES
AFTER THE EXAMINATION
PERIOD OF THIS PAPER ENDS
(UPLOAD THEM IN ONE PDF
FILE)

THIS QUESTION PAPER CONSISTS OF FIVE (5) PAGES

- Q1** For the circuit in **Figure Q1(a)**, solve for I_x , I_y and V_z using superposition method. (15 marks)
- Q2** For the circuit shown in **Figure Q2**:
- (i) Convert the delta-connected resistors R_2 - R_3 - R_4 to an equivalent star (wye) connection and redraw the circuit with values indicated. (7 marks)
 - (ii) For the redrawn circuit in **Q2(i)**, replace the current source by a voltage source using source transformation technique. Determine and sketch the Thevenin's equivalent circuit across R_5 . (7 marks)
 - (iii) Using the Thevenin's equivalent circuit in **Q2(ii)**, determine the current in R_5 and the current supplied by the 9V source in the original circuit. (4 marks)
 - (iv) If R_5 is allowed to vary, determine the value of R_5 for maximum power transfer. Compute the value of this maximum power. (2 marks)
- Q3** (a) Describe the relationship between the maximum power transfer theorem and efficiency in an electrical circuit. (3 marks)
- (b) Predict the efficiency of a system if:
- (i) $R_{load} = R_{source}$. (2 marks)
 - (ii) $R_{load} = \infty \Omega$ or $R_{source} = 0 \Omega$. (2 marks)
 - (iii) $R_{load} = 0 \Omega$. (2 marks)
- (c) For the circuit shown in **Figure Q3(c)**:
- (i) Determine the Norton's equivalent circuit across the terminals of R. (5 marks)
 - (ii) Using the equivalent circuit derived in **Q3(c)(i)**, determine the currents I_1 , I_2 , I_3 and I_4 in the original circuit, when $R = 6\Omega$.

(5 marks)

(iii) Determine the power loss in each resistor in the circuit.

(4 marks)

(iv) If R is allowed to vary, determine the value of R for maximum power transfer. Compute the value of this maximum power.

(2 marks)

- END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER/SESSION : II/ 2019/ 2020

PROGRAMME CODE : BEV

COURSE NAME : ELECTRIC CIRCUITS I /
ELECTRIC CIRCUIT ANALYSIS I

COURSE CODE : BEV10303 / BEF12403

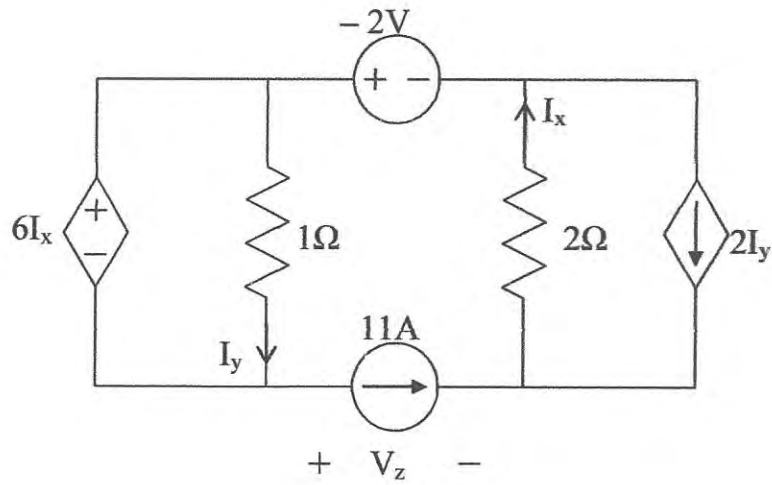


Figure Q1(a)

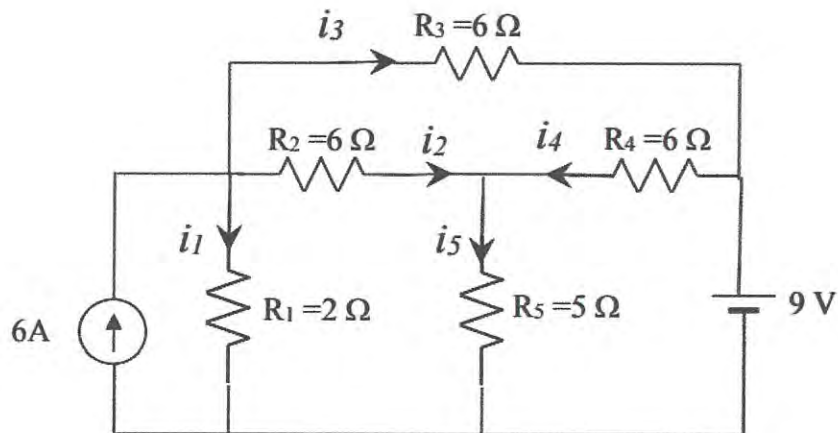


Figure Q2



FINAL EXAMINATION

SEMESTER/SESSION : II/ 2019/ 2020

PROGRAMME CODE : BEV

COURSE NAME : ELECTRIC CIRCUITS I /
ELECTRIC CIRCUIT ANALYSIS I

COURSE CODE : BEV10303 / BEF12403

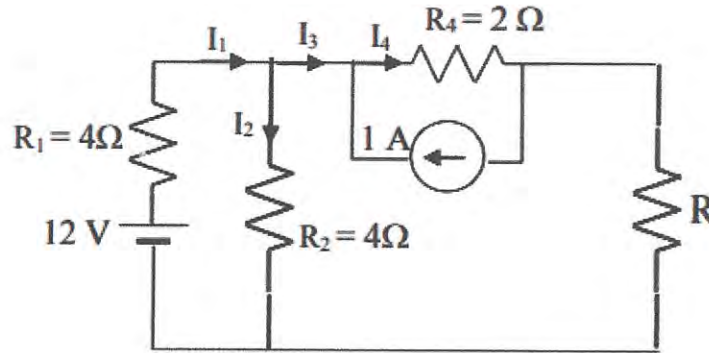


Figure Q3(c)