



UTHM

Universiti Tun Hussein Onn Malaysia

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

FINAL EXAMINATION (TAKE IIOME) SEMESTER II SESSION 2019/2020

COURSE NAME	:	ELECTRIC CIRCUIT II
COURSE CODE	:	BEJ 10403
PROGRAMME	:	BEJ
EXAMINATION DATE	:	JULY 2020
DURATION	:	4 HOURS
INSTRUCTION	:	1. ANSWER ALL QUESTIONS 2. OPEN BOOK EXAMINATION 3. SHOW ALL CALCULATIONS

TERBUKA

THIS QUESTION PAPER CONSISTS OF SEVEN (7) PAGES

Q1 (a) Capacitors in **Figure Q1(a)** has been charged up to its steady state condition. For each of the capacitors, C_1 and C_2 :

(i) Find the voltage, V_1 and V_2 . (4 marks)

(ii) Find the charge, Q_1 and Q_2 . (2 marks)

(iii) Calculate the energy in each capacitor. (4 marks)

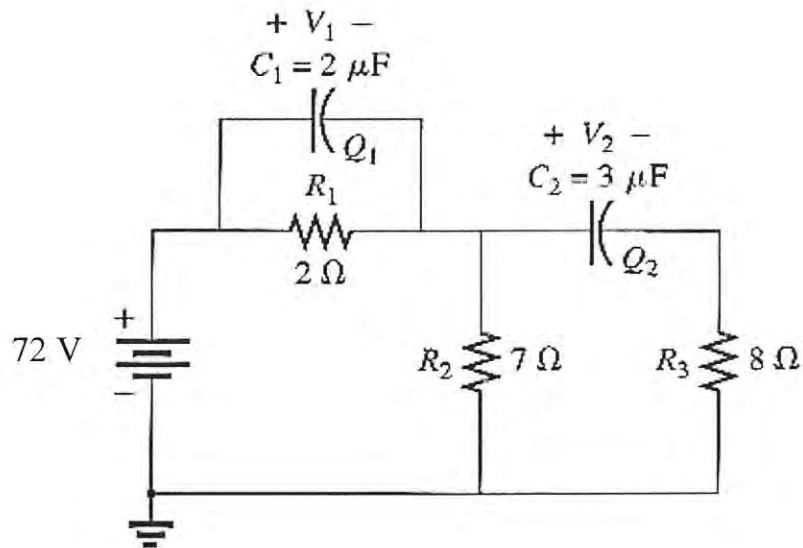


Figure Q1(a)

TERBUKA

- (b) Consider the circuit in **Figure Q1(b)**. Assuming that the switch has been closed for a long time, then at $t = 0$ s, the switch is opened.

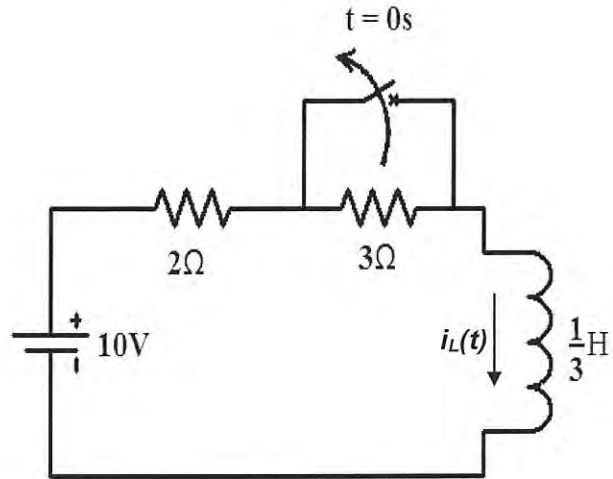


Figure Q1(b)

- (i) Determine the current $i_L(t)$ for $t > 0$. (9 marks)
- (ii) Sketch the current response for $i_L(t)$ by considering it takes 5τ for the circuit to reach its final state. (6 marks)

TERBUKA

Q2 (a) **Figure Q2(a)** is an RLC circuit with $R = 20 \Omega$, $L = 4 \text{ H}$, and $C = 50 \text{ mF}$. Assume the circuit is in steady state at $t = 0^-$ before the switch is moved to position b at $t = 0 \text{ s}$. Based on the circuit,

- (i) determine the initial voltage and current, $v_C(0)$ and $i_L(0)$. (3 marks)
- (ii) identify the type of response for the output voltage, $v(t)$. (3 marks)
- (iii) solve the expression of $v(t)$ for $t > 0 \text{ s}$. (9 marks)

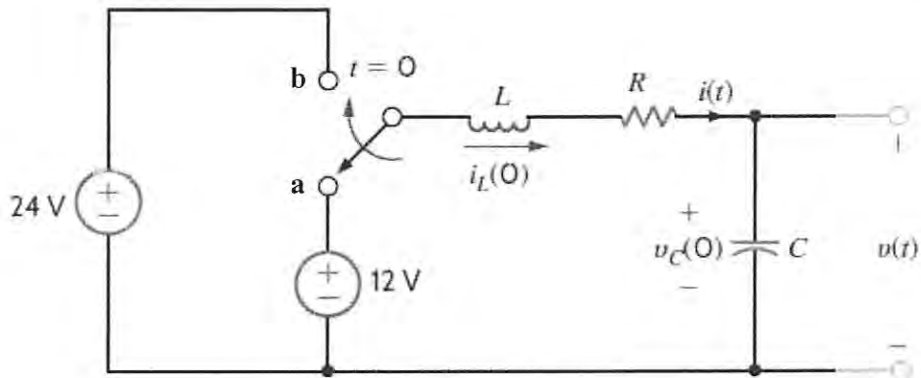


Figure Q2(a)

(b) In an experiment on a two-port network, the following observations are recorded:

$$V_1 = 25 \text{ mV and } I_2 = 5 \text{ mA with port 1 open-circuited and } V_2 = 10 \text{ V}$$

$$I_1 = 10 \text{ mA and } I_2 = 1 \text{ A with port 2 short-circuited and } V_1 = 20 \text{ V}$$

- (i) Obtain the Z-parameter of the two-port network. (8 marks)
- (ii) Based on part **Q2(b)(i)**, determine whether the network is reciprocal or otherwise. (2 marks)

TERBUKA

- Q3** (a) By assuming that the circuit in **Figure Q3(a)** operates at $\omega = 100$ rad/s;
- (i) Find the input impedance, Z_{in} of the circuit. (6 marks)
 - (ii) If an input voltage, $V_i = 10\cos(100t - 15^\circ)V$ is applied to the circuit in **Figure Q3(a)**, determine the current in the circuit. (3 marks)
 - (iii) Calculate the voltage, V_x . Give the answer in time domain. (4 marks)

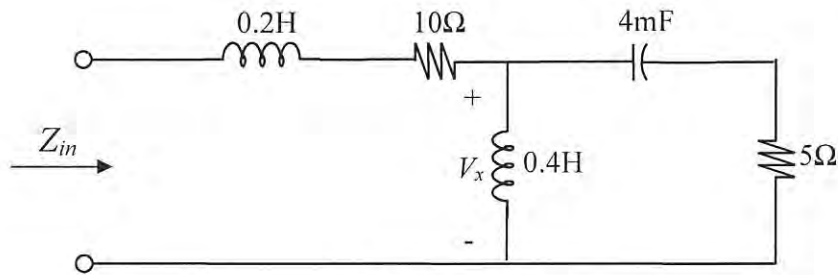


Figure Q3(a)

- (b) Consider the circuit shown in **Figure Q3(b)**.
- (i) Determine the Thevenin impedance, Z_{TH} seen from terminals $a-b$ of the circuit. Show the related circuit diagram in your calculations. (4 marks)
 - (ii) Calculate the Thevenin voltage, V_{TH} across terminals $a-b$ of the circuit. Show the related circuit diagram in your calculations. (4 marks)
 - (iii) Find the value of output current, I_o . (4 marks)

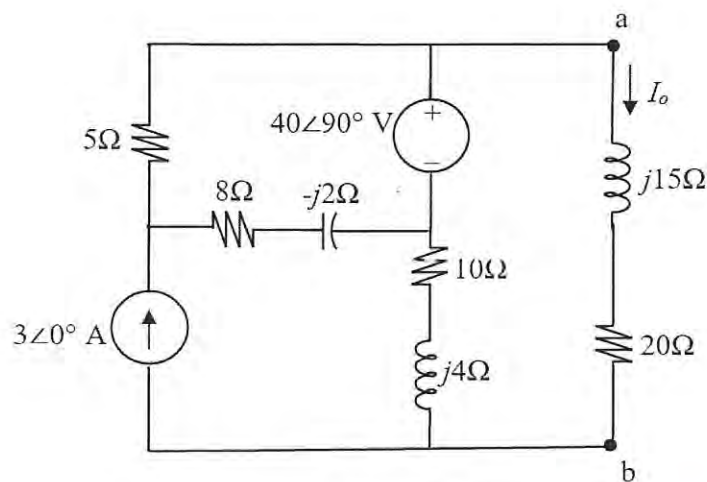


Figure Q3(b)

TERBUKA

Q4 (a) Given a circuit in **Figure Q4(a)**;

- (i) State the condition for maximum average power transfer to the load impedance, Z_L . (2 marks)
- (ii) Determine the load impedance, Z_L . (4 marks)
- (iii) Find the maximum average power. (5 marks)

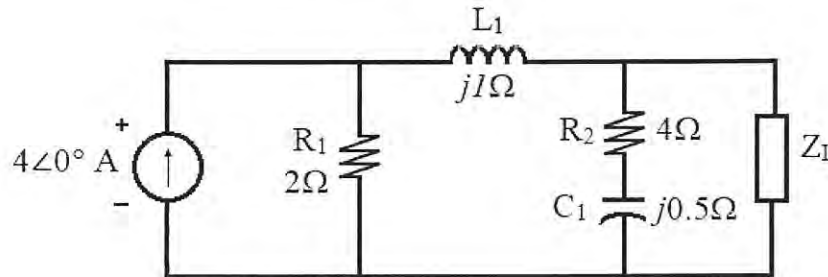


Figure Q4(a)

(b) An air conditioner operates at $240V_{rms}$ at a frequency of 60 Hz. It absorbs an average power of 9 kW at a lagging power factor, Γ_p of 0.75. The power triangle for a load system is shown in **Figure Q4(b)**.

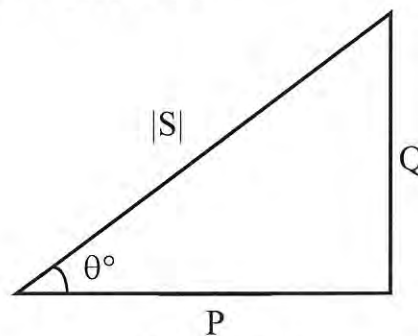


Figure Q4(b)

- (i) Determine the complex power of the load. (4 marks)
- (ii) Determine the capacitive element required to raise the power factor to 0.88. (7 marks)
- (iii) Analyze the effect of power factor correction in part Q4(b)(ii) on the effective current, I_{rms} . (3 marks)

-END OF QUESTIONS-

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/2019/2020
 COURSE NAME : ELECTRIC CIRCUIT II

PROGRAMME CODE : BEJ
 COURSE CODE : BEJ 10403

APPENDIX A

TRIGONOMETRIC EQUATIONS

$$\sin(-x) = -\sin(x)$$

$$\cos(-x) = \cos(x)$$

$$\tan(-x) = -\tan(x)$$

$$\sec x = \frac{1}{\cos x}, \quad \csc x = \frac{1}{\sin x}$$

$$\tan x = \frac{\sin x}{\cos x}, \quad \cot x = \frac{1}{\tan x}$$

$$\sin^2 2x + \cos^2 2x = 1$$

$$\sin(2x) = 2 \sin x \cos x$$

$$\cos(2x) = \cos^2 x - \sin^2 x$$

$$\cos(2x) = 2 \cos^2 x - 1 = 1 - 2 \sin^2 x$$

$$\sin(x \pm 90^\circ) = \pm \cos x$$

$$\cos(x \pm 90^\circ) = \mp \sin x$$

$$\sin(x \pm 180^\circ) = \mp \sin x$$

$$\cos(x \pm 180^\circ) = \mp \cos x$$

$$\cos^2 x + \sin^2 x = 1$$

$$\sin(x \pm y) = \sin x \cos y \pm \cos x \sin y$$

$$\cos(x \pm y) = \cos x \cos y \mp \sin x \sin y$$

$$\tan(x \pm y) = \frac{\tan x \pm \tan y}{1 \mp \tan x \tan y}$$

$$2 \sin x \sin y = \cos(x - y) - \cos(x + y)$$

$$2 \sin x \cos y = \sin(x + y) + \sin(x - y)$$

$$2 \cos x \cos y = \cos(x + y) + \cos(x - y)$$

$$\cos x \cos y = \frac{1}{2} [\cos(x + y) + \cos(x - y)]$$

TERBUKA