



UTHM
Universiti Tun Hussein Onn Malaysia

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
(ONLINE)
SEMESTER II
SESSION 2019/2020**

COURSE NAME : POWER SYSTEM ANALYSIS
COURSE CODE : BEV20703
PROGRAMME CODE : BEV
EXAMINATION DATE : JULY 2020
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS.
OPEN BOOK EXAMINATION

THIS QUESTION PAPER CONSISTS OF FIVE (5) PAGES

- Q1** (a) State **THREE (3)** types of source of energy in power system operation. (3 marks)
- (b) **Figure Q1(b)** shows a single line diagram of a typical power system model. Line 1, Line 2, and Line 3 have reactances of 56.3Ω , 43.2Ω , and 51.6Ω , respectively. Calculate the per-unit (pu) impedance of all components available in the system using a common based of 100MVA and 20kV on the generator G_1 side. (17 marks)
- Q2** (a) Discuss the Gauss-Seidel method utilized in power flow analysis application. (5 marks)
- (b) **Figure Q2(b)** illustrates the single-line diagram of a simple three-bus test system model. There are two generators connected to Bus 1, and Bus 3, respectively. Bus 1 is selected as the slack bus in this analysis. The line impedances are marked in pu on a 100MVA base. For simplification, line susceptances and line charging are neglected. Apply Gauss-Seidel method to determine the value of $V_2^{(1)}$ and $V_3^{(1)}$. Perform **ONE (1)** iteration only. (15 marks)
- Q3** (a) Identify **THREE (3)** factors that influence the operating cost of a thermal plant. (3 marks)
- (b) The fuel-cost function in MYR/h for **THREE (3)** thermal plants are given by:
- $$C_1 = 1470 + 30.24P_1 + 0.0168P_1^2$$
- $$C_2 = 2100 + 30.66P_2 + 0.0105P_2^2$$
- $$C_3 = 2520 + 28.31P_3 + 0.0126P_3^2$$
- P_1 , P_2 , and P_3 are in MW. The total load is set to 750MW. The line losses and generator limits are neglected.
- (i) Calculate the total cost in MYR/h when the generators share the load equally. (3 marks)
- (ii) Apply the iterative method to determine the optimal scheduling of generation using the initial value of $\lambda^1 = 31.5\text{MYR/MWh}$. (10 marks)
- (ii) Evaluate the cost saving gained every hour between the optimal scheduling of generators with the equal load sharing of generators. (4 marks)

- Q4** (a) Summarize the procedure to include the effects of load current in the fault analysis. (5 marks)
- (b) A single-line diagram of a four-bus power system is shown in **Figure Q4(b)**. Each generator is represented by an electromotive force (emf) behind the transient reactance. All impedances are expressed in per unit on a common MVA base. All resistances and shunt capacitances are neglected. The generators operate on no-load at their rated voltage with their emf in phase. A solid three phase fault occurs at Bus 4.
- (i) Determine the impedance to the point of fault, the fault current and current that flows via generators in per unit during fault. (7 marks)
- (ii) Calculate the bus voltages and the line currents during fault. (8 marks)
- Q5** (a) (i) State the definition of power system stability. (2 marks)
- (ii) List **TWO (2)** major categories of power system stability. (2 marks)
- (b) A 60Hz synchronous generator with inertia constant $H = 5.6\text{MJ/MVA}$ is connected to an infinite bus through a purely reactive circuit as shown in **Figure Q5(b)**. The generator is delivering real power $P_3 = 0.85\text{pu}$ and $Q_3 = 0.081\text{pu}$ to the infinite bus at a voltage of $V_3 = 1.0\text{pu}$. A temporary three-phase fault occurs at the sending end of Line 2 at point F. When the fault is cleared, both lines remain following the disturbance. Propose the stability limit of the system by determining the critical clearing angle (δ_c) and the critical fault clearing time (t_c) for the given disturbance. (16 marks)

-END OF QUESTIONS-



FINAL EXAMINATION

SEMESTER/SESSION : II/ 2019/2020

PROGRAMME : BEV

CODE

COURSE NAME : POWER SYSTEM ANALYSIS

COURSE CODE : BEV20703

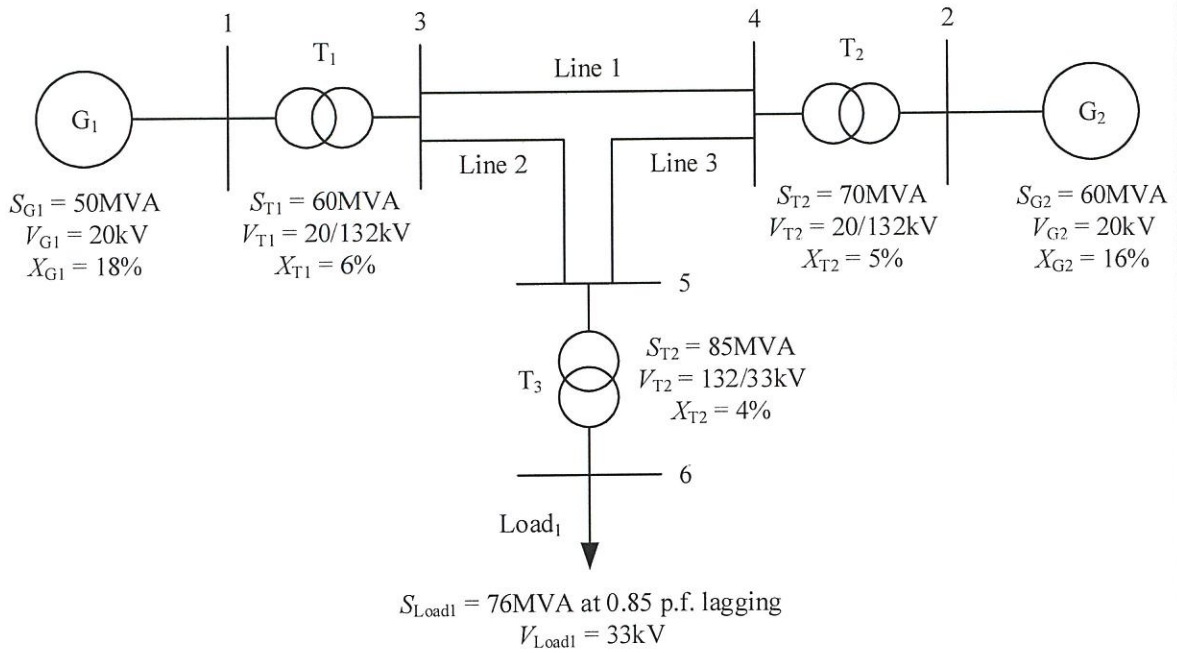


Figure Q1(b)

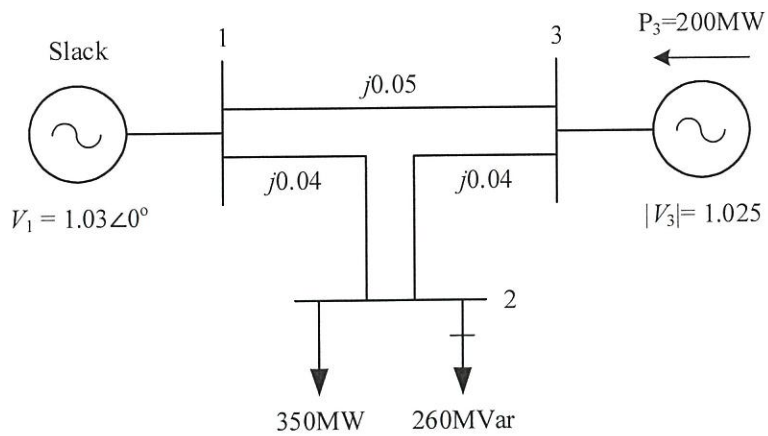


Figure Q2(b)

FINAL EXAMINATION

SEMESTER/SESSION : II/ 2019/2020

PROGRAMME : BEV
 CODE
 COURSE CODE : BEV20703

COURSE NAME : POWER SYSTEM ANALYSIS

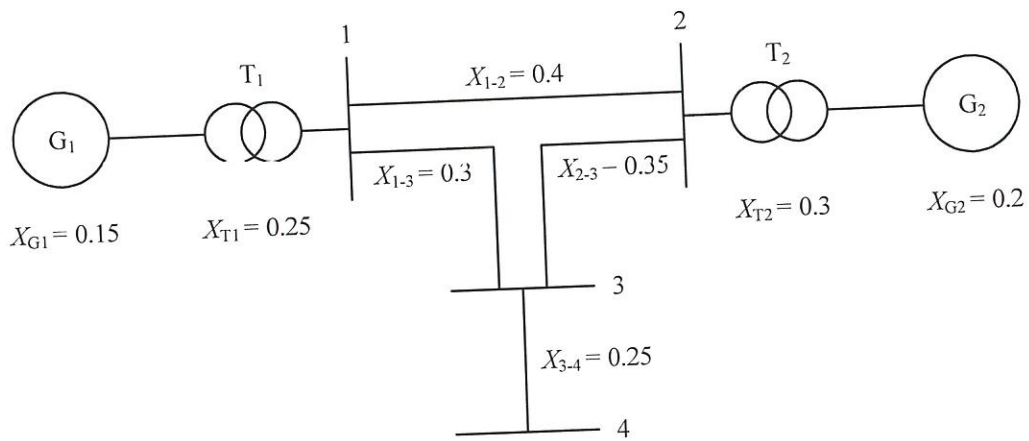


Figure Q4(b)

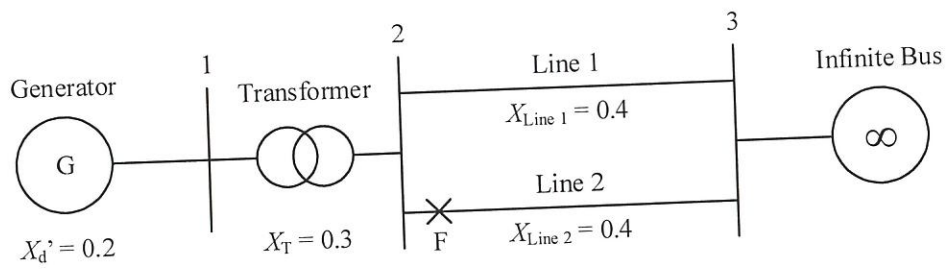


Figure Q5(b)