

**CONFIDENTIAL**



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
(TAKE HOME)  
SEMESTER II  
SESSION 2019/2020**

**COURSE NAME** : RF AND MICROWAVE  
ENGINEERING

**COURSE CODE** : BEB 40803

**PROGRAMME CODE** : BEJ

**EXAMINATION DATE** : JULY 2020

**DURATION** : 3 HOURS

**INSTRUCTION** : 1. ANSWER ALL QUESTIONS  
**OPEN BOOK EXAMINATION**

2. ANSWERS MUST BE  
HANDWRITTEN.

3. MERGE ALL ANSWER SHEETS  
IN **ONE (1) FILE** AND SUBMIT IN  
**PDF** FORMAT.

THIS QUESTION PAPER CONSISTS OF **SIX (6) PAGES**

**CONFIDENTIAL**

**TERBUKA**

**Q1** A transmission line is a distributed parameter network, where voltages and currents can vary in magnitude and phase over its length. Refer to a loaded transmission line in **Figure Q1**,

- (a) Calculate the reflection coefficient of the load (3 marks)
- (b) Calculate the voltage standing wave ratio (VSWR) of the load (3 marks)
- (c) Determine the value of  $V_{\min}$  and  $V_{\max}$ . (5 marks)

**Q2** (a) Show that the S parameter for the circuit in **Figure Q2** is

$$\begin{bmatrix} \frac{Z}{2Z_0+Z} & \frac{2Z_0}{2Z_0+Z} \\ \frac{2Z_0}{2Z_0+Z} & \frac{Z}{2Z_0+Z} \end{bmatrix}$$

(10 marks)

**Q3** Doppler radar can be used for the detection of moving objects and estimating their velocities.

- (a) Draw the schematic diagram of a simple doppler radar using only the components listed in **Table 2**. (6 marks)
- (b) In simple explanation, what is the function of attenuator in this system? (3 marks)
- (c) The system requires an attenuator that need to function at attenuation level of 3dB. Design the attenuator using T-configuration that will match with the 50  $\Omega$  system. (5 marks)

**Q4** A microstrip low-pass filter with cut-off frequency of 2 GHz and 30 dB attenuation at 3.5 GHz is to be designed. The filter has Chebyshev response characteristic with 0.5 dB ripple. The filter is to be implemented on a microstrip board with a relative permittivity,  $\epsilon_r = 9.9$ , thickness,  $h = 0.63$  mm and loss tangent,  $\text{Tan } \delta = 0.001$ .

(i) (a) Sketch the frequency response with complete labelling. (5 marks)

(ii)(b) Design the lumped element circuit prototype of the filter. Show your step by step work clearly by referring to **Figure Q3** and **Table 1**. (10 marks)

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/2019/2020  
COURSE NAME : RF AND MICROWAVE ENGINEERING

PROGRAMME CODE : BEJ  
COURSE CODE: BEB 40803

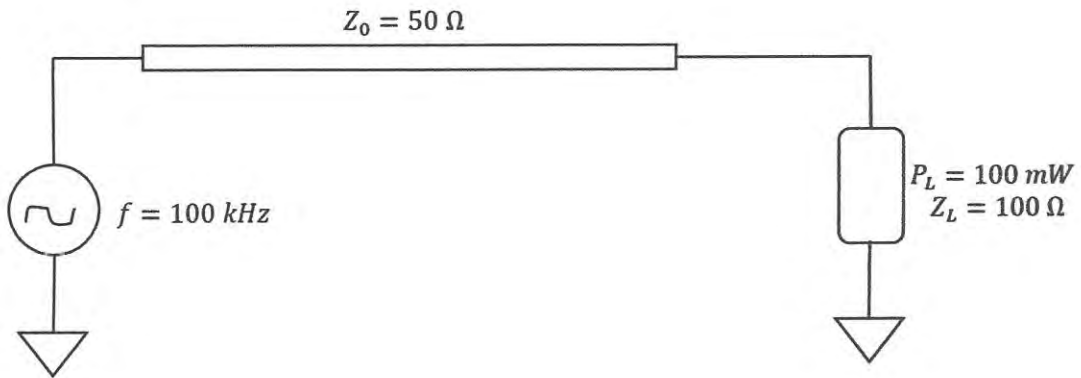


Figure Q1

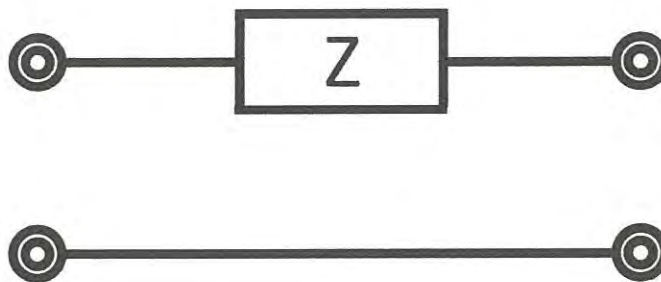


Figure Q2

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/2019/2020  
 COURSE NAME : RF AND MICROWAVE ENGINEERING

PROGRAMME CODE : BEJ  
 COURSE CODE: BEB 40803

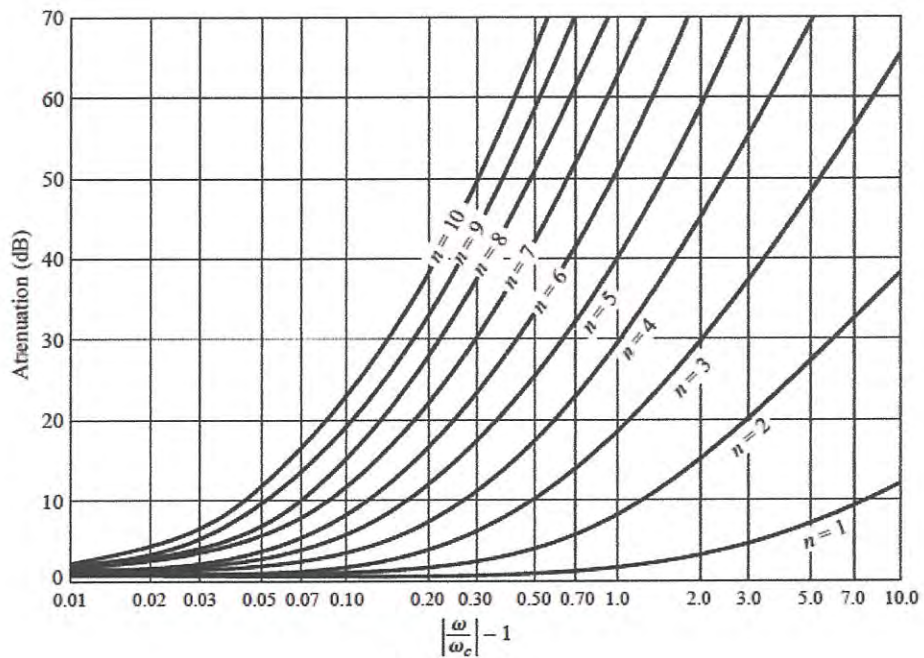


Figure Q3

TABLE 1

0.5 dB Ripple

$N$	$g_1$	$g_2$	$g_3$	$g_4$	$g_5$	$g_6$	$g_7$	$g_8$	$g_9$	$g_{10}$	$g_{11}$
1	0.6986	1.0000									
2	1.4029	0.7071	1.9841								
3	1.5963	1.0967	1.5963	1.0000							
4	1.6703	1.1926	2.3661	0.8419	1.9841						
5	1.7058	1.2296	2.5408	1.2296	1.7058	1.0000					
6	1.7254	1.2479	2.6064	1.3137	2.4758	0.8696	1.9841				
7	1.7372	1.2583	2.6381	1.3444	2.6381	1.2583	1.7372	1.0000			
8	1.7451	1.2647	2.6564	1.3590	2.6964	1.3389	2.5093	0.8796	1.9841		
9	1.7504	1.2690	2.6678	1.3673	2.7239	1.3673	2.6678	1.2690	1.7504	1.0000	
10	1.7543	1.2721	2.6754	1.3725	2.7392	1.3806	2.7231	1.3485	2.5239	0.8842	1.9841

**FINAL EXAMINATION**

SEMESTER/SESSION : SEM II/2019/2020

PROGRAMME CODE : BEJ

COURSE NAME : RF AND MICROWAVE ENGINEERING

COURSE CODE: BEB 40803

**TABLE 2**

<b>Item</b>	<b>Quantity</b>
Voltage Control Oscillator	1
Base band signal generator	1
Low Noise Amplifier	1
Power Amplifier	1
Splitter	1
Mixer	1
Attenuator	1
Reflector antenna	2