



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
(TAKE-HOME)  
SEMESTER I  
SESSION 2020/2021**

COURSE NAME : ELECTRICAL INSTRUMENTATION AND MEASUREMENT  
COURSE CODE : DAE 21403  
PROGRAMME CODE : DAE  
EXAMINATION DATE : JANUARY/FEBRUARY 2021  
DURATION : 6 HOURS  
INSTRUCTION : ANSWER ALL QUESTIONS  
**OPEN BOOK EXAMINATION**

THIS QUESTION PAPER CONSISTS OF SEVEN (7) PAGES



**Q1**

- (a) State the main difference between accuracy and precision. (2 marks)
- (b) List **five (5)** reasons why there are differences between practical values and theoretical values. (5 marks)
- (c) Explain the reasons in determining the mean value of measurement when taking readings from an old instrument. (3 marks)
- (d) Given a four band resistor with the colour coded Red, Black, Orange and Gold.
- (i) Determine the resistance value and expressed the tolerance in relative error.
  - (ii) Calculate an error if the value of the resistor is maximum.
  - (iii) Calculate an error if the value of the resistor is minimum.
- (6 marks)
- (e) State the relationship between quality of instrument, accuracy, cost and quality of results. (3 marks)
- (f) Sketch the construction of a permanent Magnet Moving Coil (PMMC) meter movement. Label your sketching that indicate Permanent Magnet, Scale, Control Spring, Pointer and Moving Coil. Briefly explain the function of each components. (6 marks)

## Q2

- (a) Based on the **Figure Q2(a)**, a PMMC instruments has three Ayrton shunt resistors connected across it to make an ammeter. The meter has  $R_m = 700 \Omega$ ,  $FSD = 50 \mu A$  and ammeter ranges of  $1 A$ ,  $50 mA$  and  $25 \mu A$ .
- (i) Calculate the required values of multiplier resistors for the given circuit configuration. (6 marks)
- (ii) Determine which selector position is to be place for each ammeter range. (3 marks)
- (iii) Discuss the reason why the selector is placed as such condition in **Q2(a)(ii)**. (3 marks)
- (b) List **four (4)** precaution during handling and taking measurement of a multirange DC ammeter. (4 marks)
- (c) Define ohmmeter accuracy and explain which part of the scale gives the most accurate resistance measurement. (3 marks)
- (d) Explain the importance of conducting a zero ohm ( $0 \Omega$ ) adjustment in each resistance range of ohmmeter during resistance measurement. (2 marks)
- (e) A series ohmmeter is made up of supply voltage  $E_b = 3 V$ , series resistor  $R_1 = 30 k\Omega$ , meter shunt resistor  $R_2 = 50 \Omega$ , meter  $FSD = 50 \mu A$  and meter resistance  $R_m = 50 \Omega$ . Determine the new resistance to which  $R_2$  must be adjusted when  $E_b$  falls to  $2.4 V$ . (4 marks)

**TERBUKA**

CONFIDENTIAL

## Q3

- (a) Differentiate the function and application of Wheatstone and Maxwell bridge. (3 marks)
- (b) A Maxwell bridge is designed to measure the unknown impedance ( $R_x, L_x$ ) of a coil, is shown in **Figure Q3(b)**.
- (i) Derive an expression for  $R_x$  and  $L_x$  under balance condition (3 marks)
- (ii) If the fixed bridge component values are  $R_2 = 100 \Omega$  and  $C_1 = 20 \mu F$ , calculate the value of the unknown impedance,  $R_x$  and  $L_x$  if  $R_1 = 3183 \Omega$  and  $R_3 = 50 \Omega$  at balance. (5 marks)
- (c) State **two (2)** conditions that must be met simultaneously when balancing an AC bridge. (2 marks)
- (d) Based on Wheatstone bridge in **Figure Q3(d)**, the resistive components have following nominal values:  
 $V = 5 V, R_1 = 1 k\Omega, R_2 = 1.5 k\Omega, R_3 = 3.9 k\Omega$  and  $R_4 = 7.5 k\Omega$ ,
- (i) Calculate  $V_{TH}$  and  $R_{TH}$ .
- (ii) Draw the Thevenin equivalent circuit.
- (iii) The Galvanometer has a current sensitivity of  $25 mm/\mu A$  and internal resistance of  $75 \Omega$ . Calculate the deflection of the Galvanometer. (12 marks)



**Q4**

- (a) State the importance of calibrating an oscilloscope. (2 marks)
- (b) Sketch and label the waveform completely:
- (i) **Two (2)** cycles of pulse waveform with 10% duty cycle,  $V_P = 5 V$  and  $T = 10 ms$ .
  - (ii)  $1\frac{2}{3}$  cycles of triangle wave with  $V_{P-P} = 200 V$  and  $f = 50 Hz$ . (4 marks)
- (c) Two sine waves of the same phase and amplitude are applied to the input terminals of an oscilloscope operating in the X-Y mode. If the signal applied to the horizontal input is  $5 kHz$  and the frequency of the vertical input signal is  $2 kHz$ , sketch the waveform that will be observed on the oscilloscope screen. (2 marks)
- (d) Name **two (2)** types of signal generator commonly used in audio manufacturing and describe its differences. (4 marks)
- (e) State **two (2)** reasons why the sensory system is very useful and helpful in petrochemical industries. (4 marks)
- (f) Give **two (2)** examples of applications for each of the following sensor or transducer:
- (i) light sensor,
  - (ii) velocity sensor,
  - (iii) pressure transducer. (6 marks)
- (g) State the main difference between sensor and transducer. (3 marks)

**END OF QUESTIONS****TERBUKA**

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2020/2021  
COURSE NAME : ELECTRIC INSTRUMENTATION AND MEASUREMENT  
PROGRAMME CODE : DAE  
COURSE CODE : DAE21403

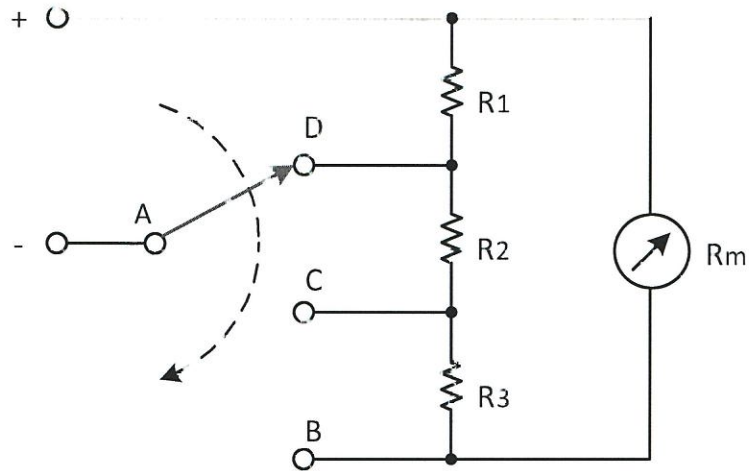


Figure Q2(a)


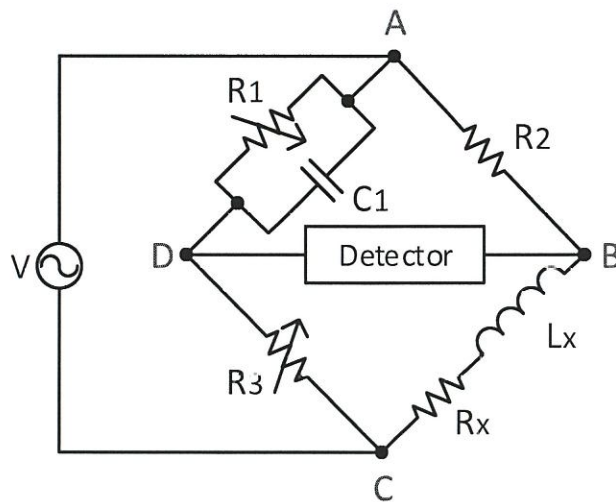


Figure Q3(b)

**TERBUKA**

**FINAL EXAMINATION**

SEMESTER / SESSION : SEM I / 2020/2021  
COURSE NAME : ELECTRIC INSTRUMENTATION AND MEASUREMENT  
PROGRAMME CODE : DAE  
COURSE CODE : DAE21403

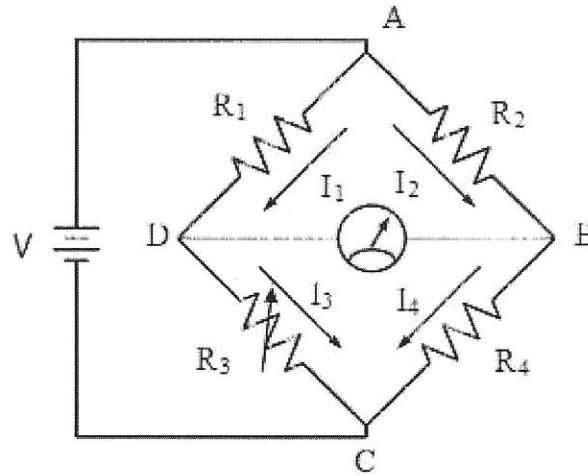

**Figure Q3(d)**