

**CONFIDENTIAL**



**UTHM**  
Universiti Tun Hussein Onn Malaysia

**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**


**FINAL EXAMINATION  
(TAKE HOME)  
SEMESTER I  
SESSION 2020/2021**

COURSE NAME : ELECTRONICS  
COURSE CODE : DAE 21303  
PROGRAMME CODE : DAE  
EXAMINATION DATE : JANUARY / FEBRUARY 2021  
DURATION : 12 HOURS  
INSTRUCTION : ANSWERS ALL QUESTIONS  
OPEN BOOK EXAMINATION

**TERBUKA**

THIS QUESTION PAPER CONSISTS OF SIX (6) PAGES


- Q1** The circuit of **Figure Q1** is a diodes application.  $V_{red}$  is the supply voltage of a home plug. The transformation ratio between the primary and the secondary is  $26:1$  meanwhile  $V_{red} = 220\text{ V}_{rms}$ ,  $f_{in} = 50\text{ Hz}$ ,  $R_L = 300\Omega$  and the first model diode characteristic is practiced.

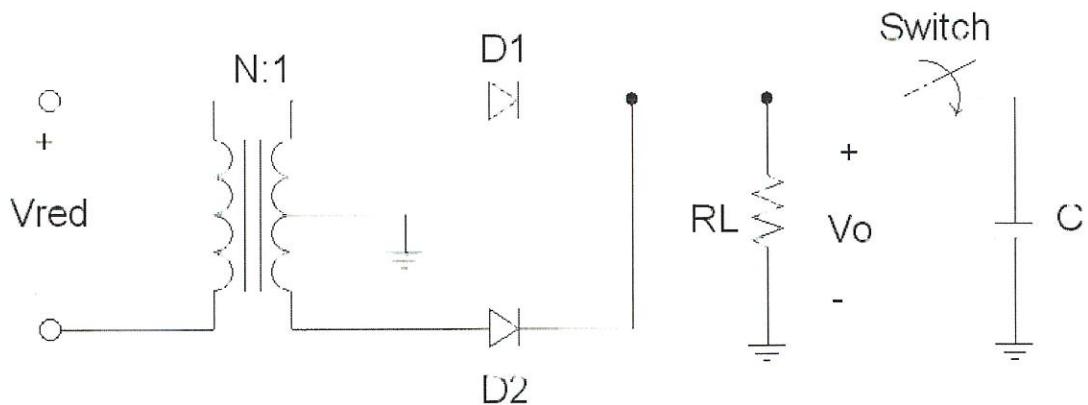**Figure Q1**

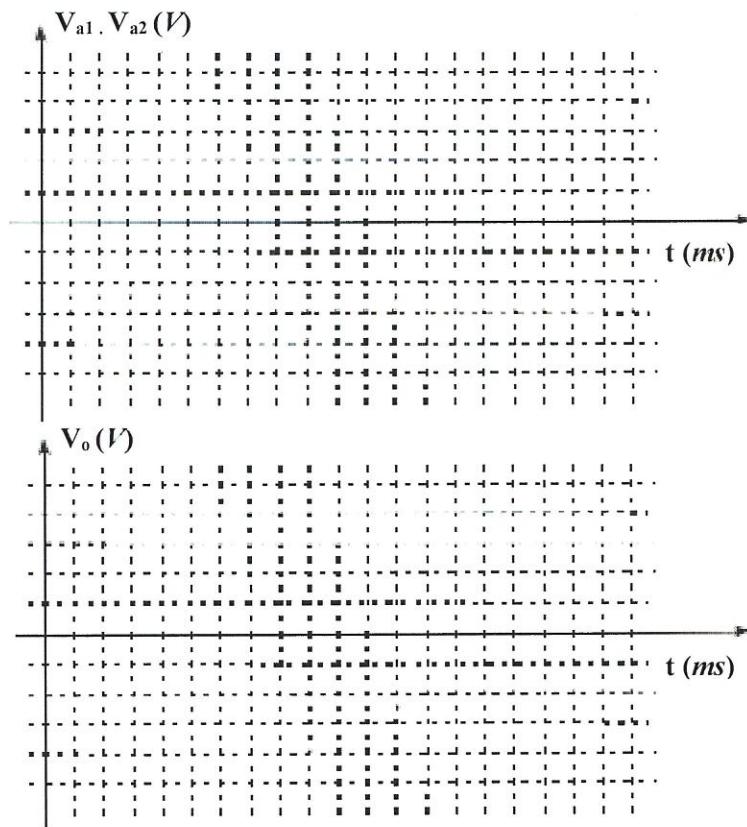
- (a) Consider the switch open initially ( $C$  offline).
- Indicate giving reasons what type of circuit is and propose an application. (2 marks)
  - Plot in **Graph Q1(a)** the following voltage signals: anode voltage of each diode  $V_{a1}$  and  $V_{a2}$  and the output voltage  $V_o$ . State the most significant voltage and time values. Mark in  $V_o$  in which half-wave is ON each diode. (6 marks)
  - Calculate the value of the Peak Inverse Voltage (PIV) in each diode. (2 marks)
- (b) Hereinafter consider the switch closed ( $C$  connected to the circuit).
- Plot in **Graph Q1(b)** the ripple voltage of value  $1V$  peak-peak observed in an oscilloscope in *AC* mode. (6 marks)
  - Calculate the capacitor  $C$  to obtain a ripple voltage up to  $1V$  (*peak-peak*). (2 marks)
  - Calculate the increase of the DC voltage  $V_o$  that is obtained by connecting the capacitor  $C$ . (2 marks)

TERBUKA

Please submit this sheet with the plotted graph.




Graph Q1(a)

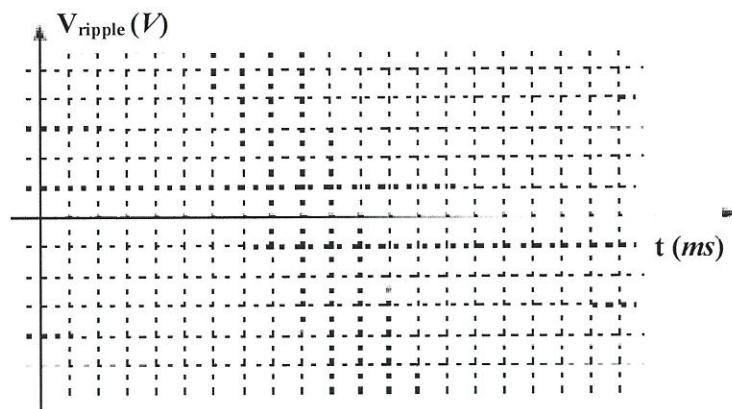

Graph Q1(b)


TERBUKA

- Q2** (a) Each diode in **Figure Q2(a)** is a complete model diode with threshold voltage equal to  $V_D$  and an internal resistance equal to  $r_d$ . Diode  $D_1$  and  $D_2$  are germanium diodes with  $V_D = 0.3V$  and  $r_{d1} = 30\Omega$ , whereas  $D_3$  and  $D_4$  are silicon diodes with  $V_D = 0.7V$  and  $r_{d2} = 20\Omega$ .

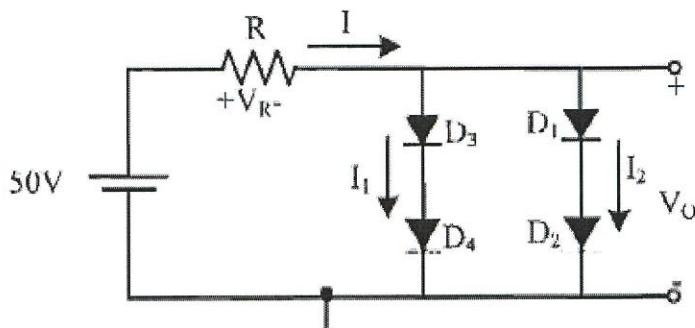**Figure Q2(a)**

- (i) If  $R = 10 k\Omega$ , calculate  $I$ ,  $I_1$ ,  $I_2$ ,  $V_R$  and  $V_o$ . (6 marks)
- (ii) Repeat **Q2(a)(i)** if  $R = 1 k\Omega$ . (3 marks)
- (iii) Predict the condition of circuit when the polarity of the battery reversed. Calculate  $V_o$ . (1 mark)


- (b) **Figure Q2(b)** shows a rectifier circuit connected to a filter capacitor and a zener diode,  $D_1$ . Given that  $I_{zmax} = 60 mA$  and  $I_{zmin} = 3 mA$ . From the circuit, determine the following parameters:

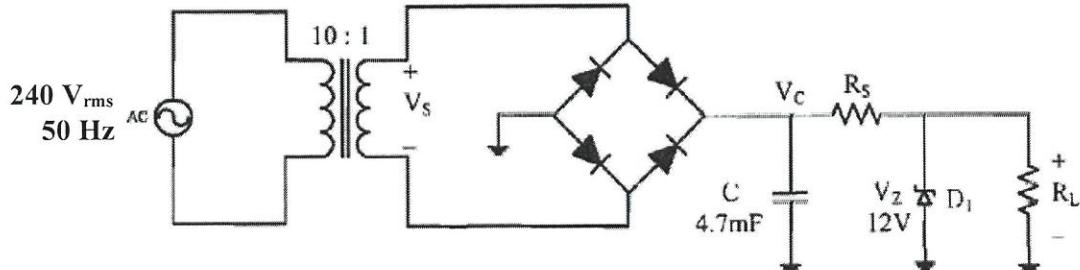**Figure Q2(b)**

- (i) Sketch  $V_c$  with respect to the input signal,  $V_s$ . (2 marks)
- (ii) Average value of  $V_c$  if  $V_{r(p-p)} = 2 V$ . (2 marks)
- (iii) The range of  $R_s$  if  $500 \Omega \leq R_L \leq 1k \Omega$ . (6 marks)

**Q3 (a)** Referring to **Figure Q3(a)**, given  $\beta = 80$  and  $r_o = 40 \text{ k}\Omega$ .

- (i) Draw the AC equivalent circuit using  $r_e$  model. (3 marks)
- (ii) Determine the AC dynamic resistance,  $r_e$ . (9 marks)
- (iii) Determine the input impedance,  $Z_i$  and output impedance,  $Z_o$  for the circuit. (4 marks)
- (iv) Calculate the voltage gain,  $A_v$ . (2 marks)
- (v) If the input voltage,  $V_{in} = 10 \text{ mV}$  is connected to the circuit, find the output voltage,  $V_o$ . (2 marks)

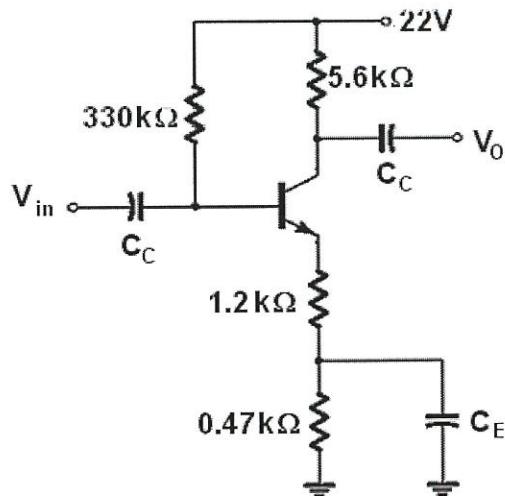

**Figure Q3(a)**

**Q4 (a)** Differentiate between Bipolar Junction Transistor (BJT) and Field Effect Transistor (FET). (4 marks)

- (b) **Figure Q4 (b)(i)** shows a voltage divider bias FET circuit. Find the required values for  $R_S$  and  $R_D$  if the FET transfer characteristics curve with the defined Q-point is as shown in **Figure Q4 (b)(ii)** and the following values are given:  $V_{DD} = +16 \text{ V}$ ,  $R_I = 2.1 \text{ M}\Omega$  and  $R_2 = 270 \text{ k}\Omega$ ,  $V_{DS} = 7 \text{ V}$ . (8 marks)

**TERBUKA**

- (c) Find the input impedance,  $Z_{in}$ , output impedance,  $Z_o$  and the output voltage,  $V_o$  of the amplifier in part Q4(b) if the input signal,  $V_i = 2 \text{ mV}$  and the ac output impedance,  $r_d = \infty$ .

(8 marks)

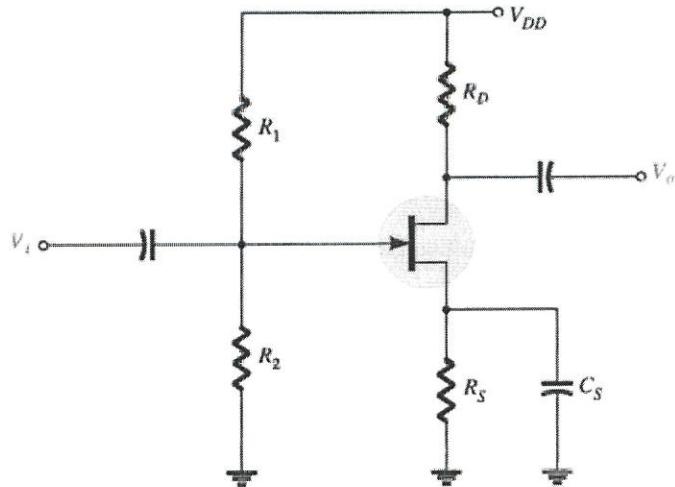


Figure Q4(b)(i)

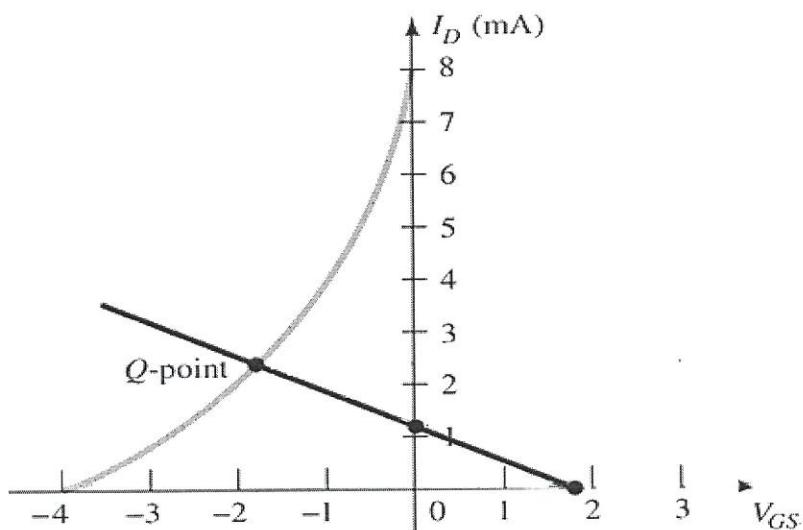


Figure Q4(b)(ii)

-END OF QUESTIONS -

**TERBUKA**