

CONFIDENTIAL



UTHM
Universiti Tun Hussein Onn Malaysia

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
(ONLINE)
SEMESTER II
SESSION 2020/2021**

COURSE NAME : ANALOG ELECTRONICS
COURSE CODE : BEJ 10503
PROGRAMME CODE : BEJ
EXAMINATION DATE : JULY 2021
DURATION : 3 HOURS
INSTRUCTION : ANSWERS ALL QUESTIONS.

TERBUKA

THIS QUESTION PAPER CONSISTS OF SIX (6) PAGES

CONFIDENTIAL

Q1 (a) Explain **TWO (2)** reasons a pure semiconductor behaves like an insulator at absolute zero temperature. (4 marks)

(b) Zener diodes usually operate under reverse biased condition.

(i) Explain the operation of a zener diode. (3 marks)

(ii) Sketch the voltage-current graph for the zener diode. (3 marks)

Q2 (a) A diode labelled as Si has characteristic I - V graphs shown in **Figure Q2(a)**. Obtain the operating point for the diode in the given circuit. (5 marks)

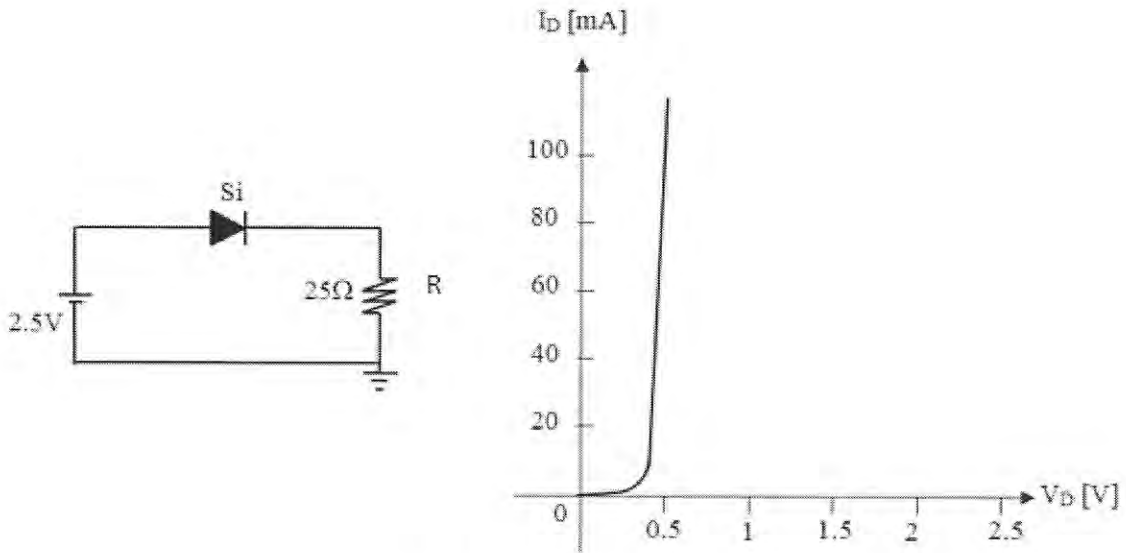


Figure Q2 (a)

(b) Based on **Figure Q2(a)**, if the resistor, R is changed to 50Ω , determine the new current and voltage across the diode. Describe the load line condition. (5 marks)

Q3 (a) Figure Q3(a) shows a BJT amplifier with $I_B = 26 \mu\text{A}$ and $V_{BE} = 0.67 \text{ V}$.

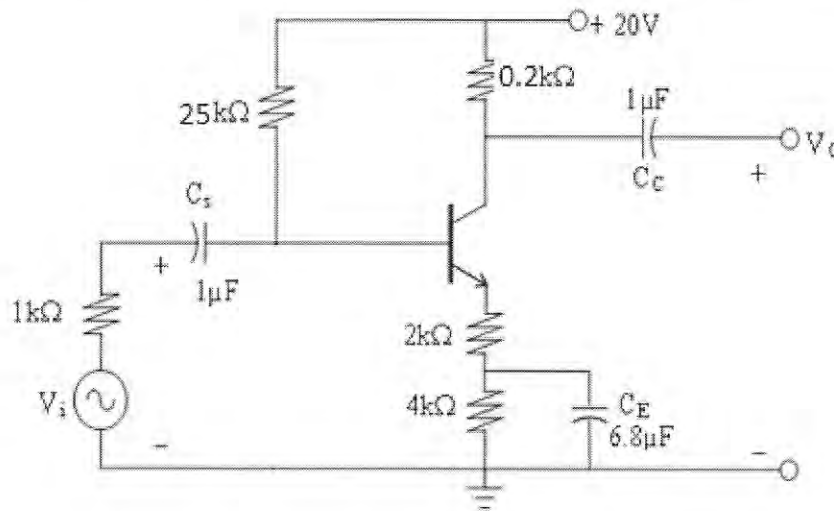


Figure Q3(a)

- (i) What is the function of the emitter resistor in the circuit as shown in **Figure Q3(a)**? (2 marks)
- (ii) Calculate current, β , I_C , I_E and output voltage, V_{CE} for the circuit using exact analysis. (8 marks)
- (iii) Draw the midband AC equivalent circuit using r_e model. (6 marks)
- (iv) Determine the input impedance, Z_i , output impedance, Z_o , voltage gain, A_v , and current gain, A_i , based on the obtained answer in part **Q3(a)(ii)**. (12 marks)

(b) What is the advantage of r_e model? (2 marks)

Q4 (a) Sketch the transfer characteristics curve of JFET, D-MOSFET and E-MOSFET. Then, formulate the drain current, I_D for each curve. (9 marks)

(b) **Figure Q4(b)** shows the JFET self-bias configuration. Determine V_{GSQ} , I_{DQ} , Z_i , Z_o , and A_V for the circuit. Given $I_{DSS} = 9 \text{ mA}$, $V_p = -4.5 \text{ V}$, $r_d = \infty$, and $g_m = 2.4 \text{ mS}$. Show all your calculations with support of sketching diagrams. (Hint: transfer curve and ac analysis) (21 marks)

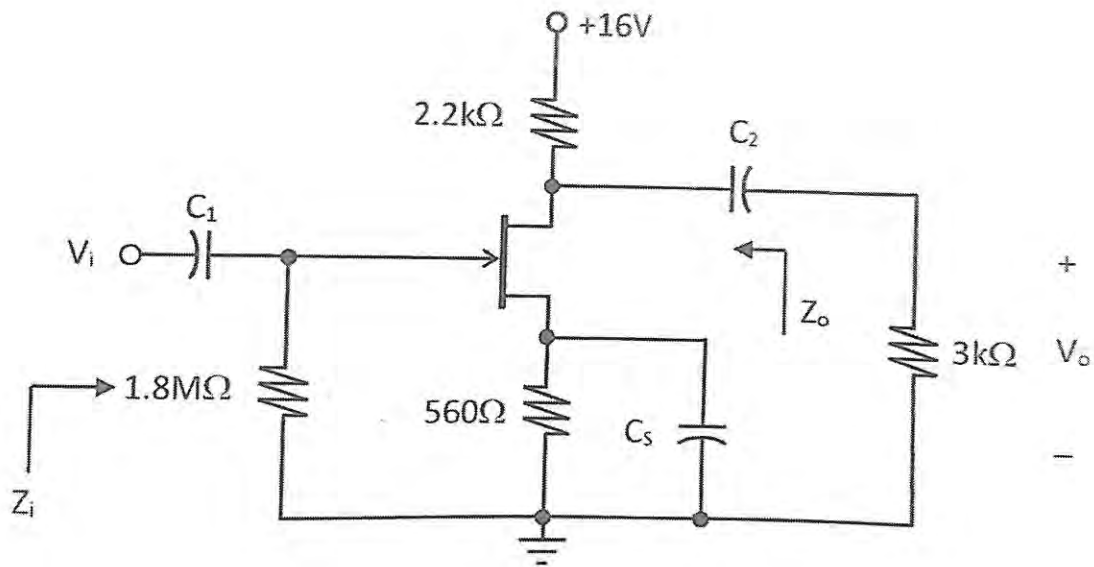


Figure Q4(b)

Q5 (a) **Figure Q5(a)** is a BJT amplifier circuit which has an infinite value of AC collector resistance, r_o (or r_c) with $r_e = 28.48 \Omega$ and $A_v = -72.91$;

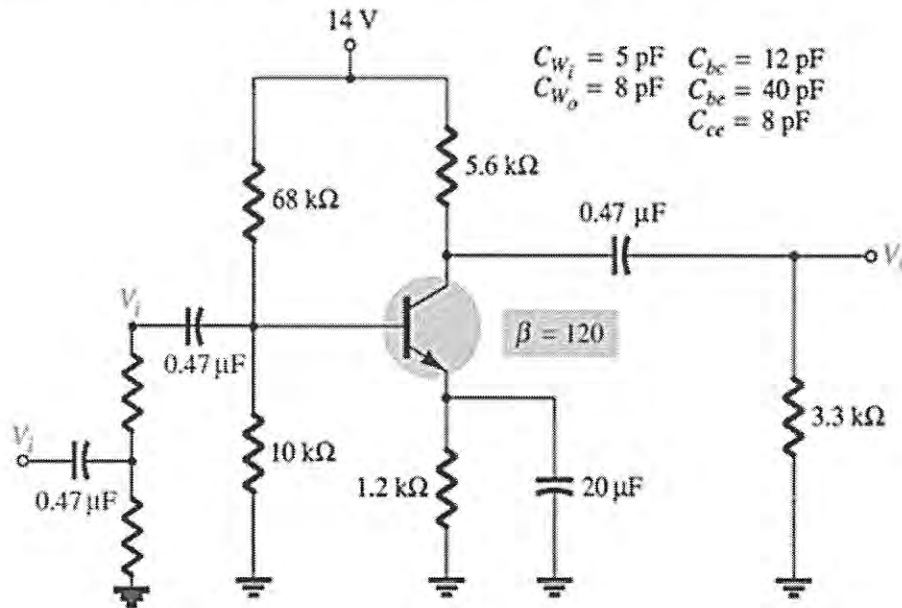


Figure Q5(a)

- (i) Determine the high cut-off frequencies, f_{Hi} and f_{Ho} . (8 marks)
- (ii) The internal capacitors influenced the high frequency response. In your opinion, how to minimize the effect of internal capacitors? (2 marks)

Q6 (a) A class B amplifier with a power supply of $V_{CC} = 30 \text{ V}$ is used to deliver a 25 V peak signal to a 15Ω speaker.

- (i) Propose a circuit diagram for the amplifier. (1 mark)
- (ii) Determine the input power, P_{in} , output power, P_{out} , and circuit efficiency, η for the amplifier. (5 marks)
- (iii) Evaluate the circuit performance in terms of its efficiency as a class B amplifier based on the value obtained in Q6(a)(ii). (1 mark)

TERBUKA

- (b) Analyse the crossover distortion problem that arises in the class B push-pull amplifier by using an appropriate illustration of V_{in} and V_{out} . (3 marks)

-END OF QUESTIONS -