

**CONFIDENTIAL**



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
(TAKE-HOME)  
SEMESTER II  
SESSION 2020/2021**

COURSE NAME : ELECTRONIC CIRCUITS ANALYSIS  
AND DESIGN

COURSE CODE : BEJ 30403

PROGRAMME CODE : BEJ

EXAMINATION DATE : JULY 2021

DURATION : 4 HOURS

INSTRUCTION : ANSWERS ALL QUESTIONS.  
**OPEN BOOK EXAMINATION**  
PLEASE UPLOAD YOUR ANSWER  
IN PDF FORM TO AUTHOR  
(UTHM LMS) WITHIN THE  
SPECIFIED TIME GIVEN.

THIS QUESTION PAPER CONSISTS OF FIVE (5) PAGES

**TERBUKA**

**CONFIDENTIAL**

- Q1 (a) Explain **TWO (2)** main characteristics of operational amplifier. (4 marks)
- (b) Calculate the output voltage,  $V_o$  for the circuit in **Figure Q1(b)** given that  $V_{D1} = 2\text{ V}$ . (6 marks)

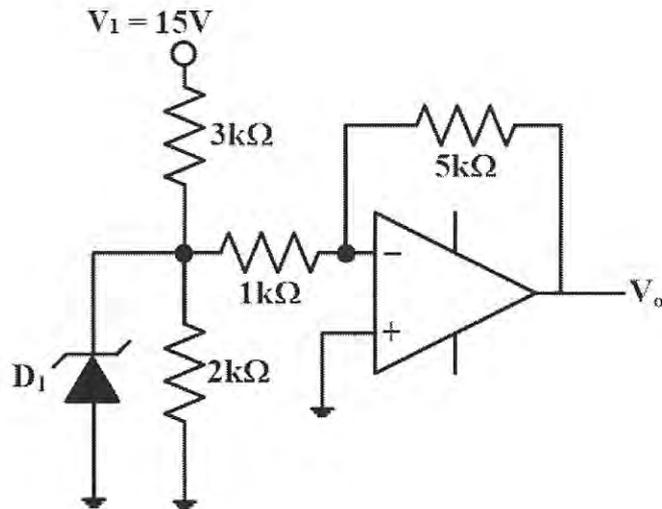


Figure Q1(b)

- (c) The values of both  $V_1$  and  $V_{D1}$  in **Figure Q1(b)** are changed to  $V_1 = 12\text{ V}$  and  $V_{D1} = 4\text{ V}$ , find the new output voltage,  $V_o$ . (6 marks)
- (d) Analyse **TWO (2)** factors that made the comparator is less suitable for system that involves noisy signal. (4 marks)
- Q2 Filter is an important system in most of the electronic applications. It is normally used to eliminate noise and maintain the integrity of transmitted signal.
- (a) Differentiate between Butterworth, Chebychev and Bessel response of a filter. (6 marks)
- (b) A differentiator circuit has the values of  $R_1 = 5\text{ k}\Omega$ ,  $R_2 = 10\text{ k}\Omega$  and  $C = 0.02\text{ }\mu\text{F}$ .
- (i) Draw the circuit and label accordingly. (2 marks)
- (ii) Derive the transfer function. (6 marks)
- (iii) Prove that the differentiator circuit is actually a high pass filter. (4 marks)

(iv) Determine the cut off frequency.

(2 marks)

**Q3** An amplifier circuit shown in **Figure Q3** has the following characteristic: voltage gain,  $A = 100$ , input impedance  $Z_i = 100 \text{ k}\Omega$ , output impedance  $Z_o = 1 \text{ k}\Omega$ , and gain-bandwidth product  $AB = 5000$ .

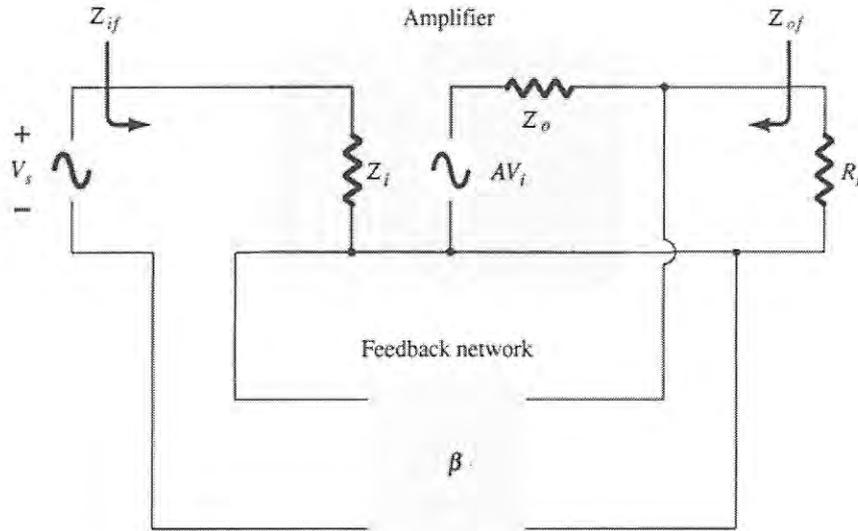


Figure Q3

- (a) Explain **THREE (3)** immediate improvements when employing negative feedback in an amplifier circuit. (6 marks)
- (b) Analyse **Figure Q3** to determine the feedback topology and amplifier type of the circuit. (2 marks)
- (c) Given the feedback factor,  $\beta = 0.1$ , calculate:
  - (i) the voltage gain with feedback,  $A_f$  (3 marks)
  - (ii) the input impedance with feedback,  $Z_{if}$  (3 marks)
  - (iii) the output impedance,  $Z_{of}$  (3 marks)
  - (iv) the gain-bandwidth product with feedback,  $A_f B_f$  (3 marks)

Q4 (a) By assuming all the diodes in **Figure Q4(a)** are ideal,

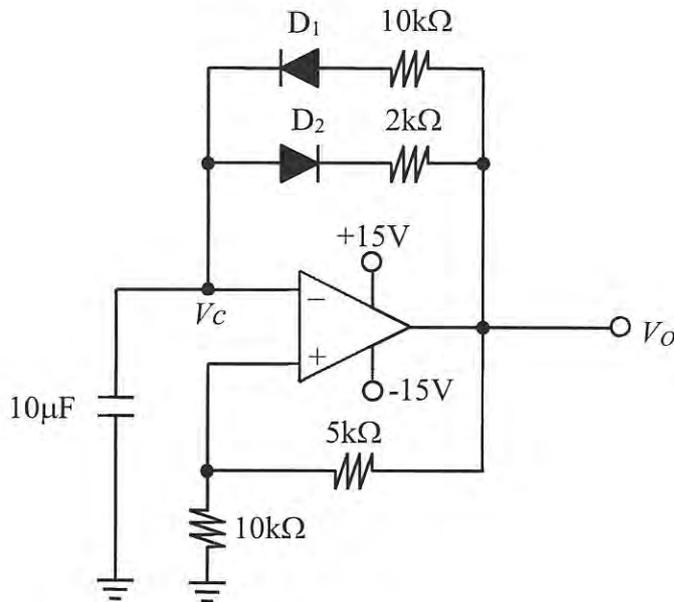


Figure Q4(a)

- (i) Analyse the frequency of the output waveform,  $V_O$ . (7 marks)
  - (ii) Illustrate the output waveform,  $V_O$  and the voltage of the capacitor,  $V_C$ . Draw both waveforms parallel at x-axis and show clearly the relationship between these two waveforms. Also clearly label the waveforms. (6 marks)
- (b) Design a circuit using 555 timer that will produce an output as shown in **Figure Q4(b)**. Show the complete circuitry with labels. Use a capacitor value of 0.01μF. (7 marks)

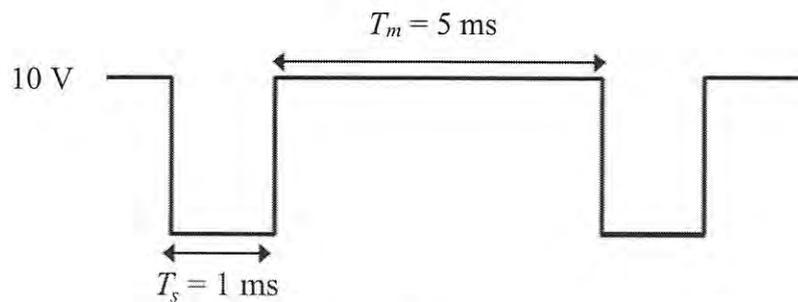


Figure Q4(b)

- Q5** (a) Examine the voltage regulator circuit in **Figure Q5** to find the value for the resistors  $R_S$  and  $R_I$ , such that the regulated output voltage is at 20 V and  $I_{Lmax} = 50$  mA. Also determine the power rating for the transistor to be used in the circuit. For the Zener diode,  $V_Z = 5$  V and  $I_Z = 10$  mA when  $V_i = 50$  V.

(8 marks)

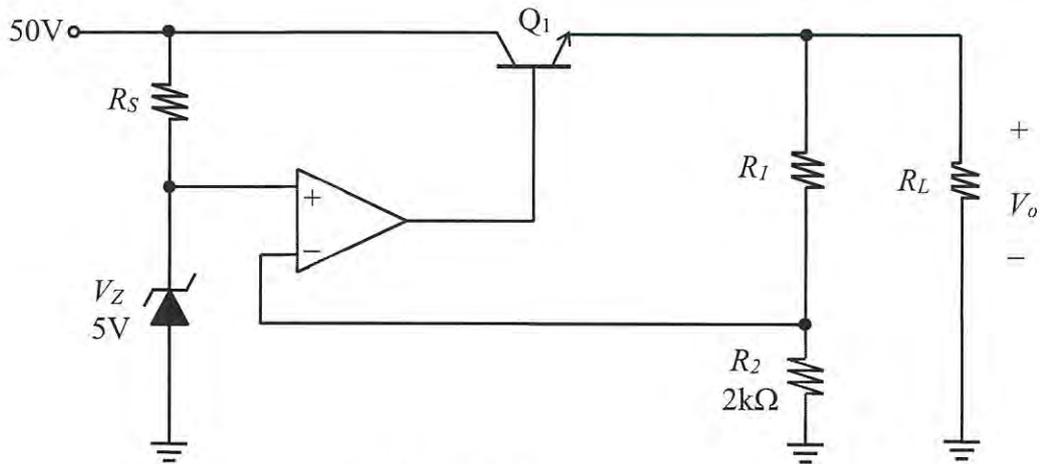


Figure Q5

- (b) Calculate the minimum value of the load resistance ( $R_L$ ) in **Figure Q5**. Explain what will happen if a load with a resistance value less than the  $R_{L(min)}$  is used in the circuit. (4 marks)
- (c) Relate how the circuit in **Figure Q5** works as a voltage regulator if the output voltage is slightly dropped below the regulated output value. (4 marks)
- (d) Modify the circuit in **Figure Q5**, such that it will have a current limiter to protect the circuit in case of a short circuit and describe how the new circuit works. (4 marks)

- END OF QUESTIONS -

TERBUKA