



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
(ONLINE)
SEMESTER II
SESSION 2020/2021**

COURSE NAME : POWER SYSTEM

COURSE CODE : BEJ20603

PROGRAMME CODE : BEJ

EXAMINATION DATE : JULY 2021

DURATION : 3 HOURS

INSTRUCTION :
1) ANSWER ALL QUESTIONS
2) **OPEN BOOK EXAMINATION**
3) PLEASE SUBMIT THE ANSWER BOOKLET AND THE DECLARATION FORM WITHIN 15 MINUTES AFTER THE EXAMINATION ENDS
4) SUBMIT ALL OF THE DOCUMENTS IN PDF FILES

THIS QUESTION PAPER CONSISTS OF **FIVE (5)** PAGES

CONFIDENTIAL

TERBUKA

- Q1** (a) Based on the circuit in **Figure Q1(a)**:
- (i) Calculate the current, the true power, the reactive power and the apparent power for the load. (5 marks)
 - (ii) Determine the power factor of the circuit. (2 marks)
- (b) With the help of appropriate diagram, differentiate between the lagging power factor and leading power factor. (4 marks)
- (c) An AC generator whose emf is given by $v(t) = 4 \sin(1 \times 10^4)t$ (V), is connected to an *RLC* circuit for which $L = 2$ mH, $C = 4$ μ F, and $R = 5$ Ω .
- (i) Determine the r.m.s. voltage across the generator. (1 mark)
 - (ii) Calculate the impedance of the circuit. (3 marks)
 - (iii) Sketch the impedance triangle of the circuit. (2 marks)
 - (iv) Calculate the average power transmitted to the circuit. (4 marks)
- (d) Differentiate between the instantaneous power and the average power. Write the appropriate formula that articulate the instantaneous power and the average power respectively. (4 marks)
- Q2** (a) A three-phase load of identical impedances, that can be Y-connected or Δ -connected, is composed of two 200 Ω resistors in parallel connection. Determine which connection will absorb lesser average power from the three-phase source with a line voltage of 400 V. Assume zero line impedance. (12 marks)

- (b) In a balanced three-phase Δ -Y circuit, the source is connected in negative sequence with $V_{bc} = 120 \angle 20^\circ$ V. The line impedance, Z_L is $2 + j1 \Omega$ whilst the load impedance, Z_Y is $18 + j14 \Omega$ respectively. Calculate the line currents. (4 marks)
- (c) Three identical Y-connected loads, each having a resistance of 20Ω in parallel with an inductor, are connected to a three phase supply of 400 V and 50 Hz frequency. The power absorb by the load is 8 kW and power factor at the load is 0.9919.
- (i) Determine the current that flows through the inductor. Please state the assumptions used to solve the question. (7 marks)
- (ii) Calculate load inductance in Henry (H). (2 marks)
- Q3** (a) A three-phase transmission line has a per phase impedance of 1Ω resistor that is in series connection with 3Ω inductor. The line feeds a balanced Δ -connected load, with a total reactive power of 5 kVAR and power factor angle of 22.62° . If the line voltage across the load terminal has a magnitude of 240 V :
- (i) Calculate the magnitude of the line voltage and the phase voltage at the source end. (8 marks)
- (ii) Determine the complex power of the source. (2 marks)
- (iii) Calculate the source power factor. (2 marks)
- (b) A balanced three-phase Y-connected generator with $V_{bc} = 440 \angle 20^\circ$ V supplies an unbalanced Δ -connected load with $Z_{AB} = -j5 \Omega$, $Z_{BC} = j10 \Omega$ and $Z_{CA} = 20 \Omega$.
- (i) Determine the line currents. (9 marks)
- (ii) Calculate the total complex power supplied by the source. (4 marks)

- Q4** (a) Describe the formula to calculate a power factor of a non-linear load. (5 marks)
- (b) State **THREE (3)** example of loads that will caused low power factor in an industry. (3 marks)
- (c) A 230 V, 50 Hz power source is connected to the some loads, where:
- Load-1: $R = 4.5 \Omega$ and in series connection with $L = 8 \text{ mH}$.
 - Load-2: 10 kVA of power factor 0.6 lagging.
 - Load-3: 5 kVAR of power factor 0.5 lagging.
- (i) Determine the active power and reactive power of the Load-1. (5 marks)
- (ii) Determine the total current delivers by the supply and the total power factor. (8 marks)
- (iii) Calculate the required capacitor in order to increase the power factor to unity. (4 marks)

– END OF QUESTIONS–

FINAL EXAMINATION

SEMESTER/SESSION : SEM II / 2020/2021
COURSE NAME : POWER SYSTEM

PROGRAMME CODE : BEJ
COURSE CODE : BEJ 20603

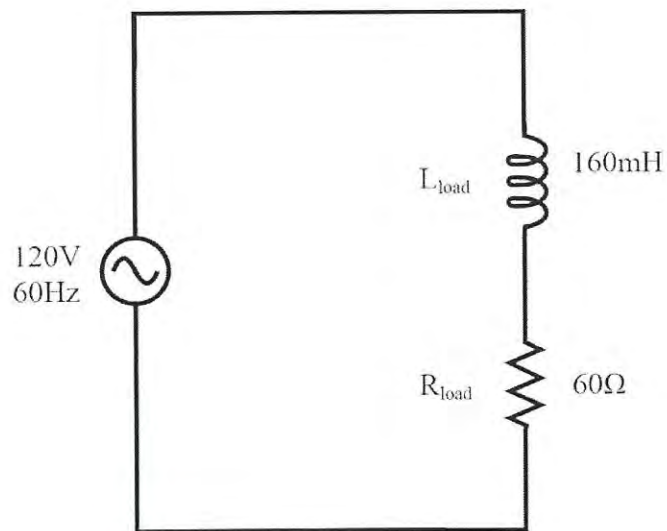


Figure Q1(a)

TERBUKA