



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
(ONLINE)
SEMESTER II
SESSION 2020/2021**

COURSE NAME : ELECTRIC AND ELECTRONIC TECHNOLOGY

COURSE CODE : BDA 14303

PROGRAMME CODE : BDD

EXAMINATION DATE : JULY 2021

DURATION : 3 HOURS

INSTRUCTION : PART A: ANSWER **ONE(1)** FROM **TWO(2)** QUESTIONS **ONLY**
PART B: ANSWER **ALL** QUESTIONS

THIS QUESTION PAPER CONSISTS OF **FOURTEEN (14)** PAGES

CONFIDENTIAL

PART A: ANSWER ONE(1) FROM TWO(2) QUESTIONS ONLY

- Q1** (a) Solve the value of v_1 , i_1 , v_2 and i_2 in the circuit of **Figure Q1(a)**.
(Use A = your first two number of your identification number/ passport number and use B = your last two number of your identification number/ passport number).
(Use 10 if your number for A and B are 00).
(For example if your number is 991030-03-5344 : A is 99 and B is 44)
- (5 marks)
- (b) A student sets up an electric circuit like the one shown in **Figure Q1(b)**.
- i) Describe how a student would measure the current and voltage value for each component in the circuit in a laboratory.
- (2 marks)
- ii) By using nodal analysis method determine the value of current and voltage across the 4Ω resistor?
- (4 marks)
- iii) From the result obtained in **Q1(b)(ii)** please do explain why.
- (4 marks)
- (c) Using superposition theorem to determine the voltage V_a in the network shown in **Figure Q1(c)**.
- (10 marks)

TERBUKA

CONFIDENTIAL

- Q2** (a) Solve the value of I_1 , I_2 and I_3 in the circuit of **Figure Q2(a)**.
(Use A = your first two number of your identification number/ passport number and use B = your last two number of your identification number/ passport number. Use 10 if your number for A and B are 00).
(For example if your number is 991030-03-5344 : A is 99 and B is 44)
(5 marks)
- (b) A student sets up an electric circuit like the one shown in **Figure Q2(b)**.
- i) Describe how a student would measure the current and voltage value for each component in the circuit in a laboratory.
(2 marks)
- ii) By using mesh analysis method determine the value of current and voltage across the 10Ω resistor?
(4 marks)
- iii) From the result obtained in **Q2(b)(ii)** please do explain why.
(4 marks)
- (c) Find the resistor R_L value that can provide maximum power transfer from the circuit shown in **Figure Q2(c)**.
(10 marks)

TERBUKA

PART B: ANSWER ALL QUESTIONS

- Q3** (a) Calculate the current waveform, if the voltage across a $4\mu\text{F}$ is show in **Figure Q3(a)**.
 X – The last two digit of your matrix number. (Use 10 if your number are 00).
(For example if your number is CD150072: X is 72)
(4 marks)
- (b) Find the equivalent inductance of the circuit in **Figure Q3(b)**.
(4 marks)
- (c) Solve the value of v_c , i_L and the energy stored in the capacitor and inductor in the circuit of **Figure Q3(c)** under dc condition.
(Use A = your first two number of your matric number and use B = your last two number of your matric number. Use 10 if your number for A and B are 00).
(For example if your number is CD150072: A is 15 and B is 72)
(7 marks)
- (d) **Figure Q3(d)** shows that the switch in the circuit has been closed for a long time. It is opened at $t = 0$. Find the capacitor voltage, $V(t)$ for $t > 0$.
(10 marks)
- Q4** (a) Calculate the rms value of waveform in **Figure Q4(a)**.
 X – The last digit of your matrix number. (Use 1 if your number are 0).
(For example if your number is CD150072: X is 2)
(5 marks)

TERBUKA

CONFIDENTIAL

- (b) A series RLC circuit with $L = 160 \text{ mH}$, $C = 100 \text{ }\mu\text{F}$, and $R = (X+10)\Omega$ is connected to a sinusoidal voltage $V(t) = (X+10)V \sin\omega t$, with $\omega = 200 \text{ rad/s}$.

X – The last digit of your matrix number. For example, a student with the matrix number CD150072 will have the values of $X = 2$, therefore $X+10=12V$.

- i) Calculate the impedance of the circuit.

(5 marks)

- ii) Let the current at any instant in the circuit be $I(t) = I_o \sin(\omega t - \phi)$. Find I_o .

(2 marks)

- iii) What is the phase ϕ ?

(4 marks)

- (c) Write down the equation for a sinusoidal voltage of 50 Hz and its peak value is 20 V. Draw the corresponding voltage versus time graph.

(5 marks)

- (d) The equation for an alternating current is given by $i = 77 \sin 314t$. Find the peak value, frequency, time period and instantaneous value at $t = 2 \text{ ms}$.

(4 marks)

- Q5** (a) Explain the **three (3)** main differences between AC and DC motors?

(5 marks)

- (b) An ideal transformer is rated at 2400/120V, 9.6kVa, and has 50 turns on the secondary side. Calculate:

- i) The turn ratio

(2 marks)

TERBUKA

CONFIDENTIAL

CONFIDENTIAL

- ii) The number of turn on the primary side
(2 marks)
- iii) The current rating for primary and secondary winding
(2 marks)
- (c) **Figure Q5(c)** shows a logic circuit which has three inputs A, B, C and two outputs F and G.
- i) Obtain the logic expression for the outputs G and F.
(2 marks)
- ii) Redesign the circuit using only 3-to-8 decoder (with active high outputs) and OR gates.
(6 marks)
- (d) Find the Boolean expression for the Boolean function below by using Karnaugh Map.
$$F(W, X, Y, Z) = \sum m(0,1,2,4,5,6,8,9,12,13,14)$$

(6 marks)

-END OF QUESTIONS -

TERBUKA

CONFIDENTIAL

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2020/2021
 COURSE NAME : ELECTRICAL AND ELECTRONIC TECHNOLOGY

PROGRAMME CODE : BDD
 COURSE CODE : BDA 14303

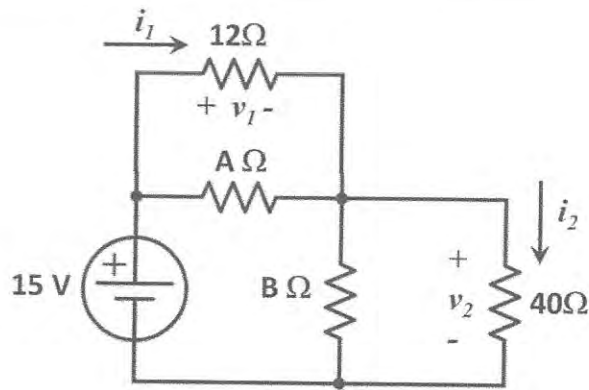


Figure Q1(a)

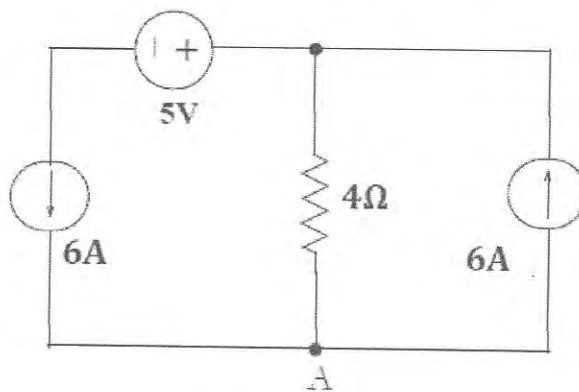


Figure Q1(b)

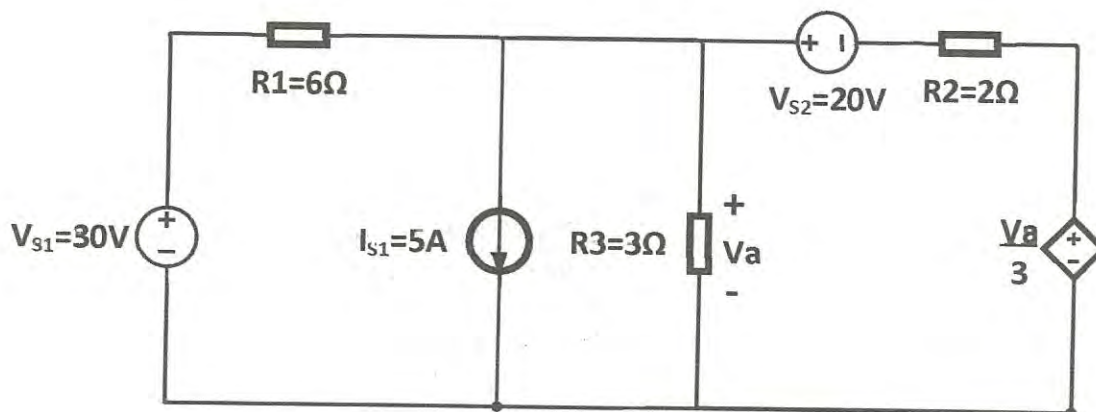


Figure Q1(c)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2020/2021

COURSE NAME : ELECTRICAL AND ELECTRONIC TECHNOLOGY

PROGRAMME CODE : BDD

COURSE CODE : BDA 14303

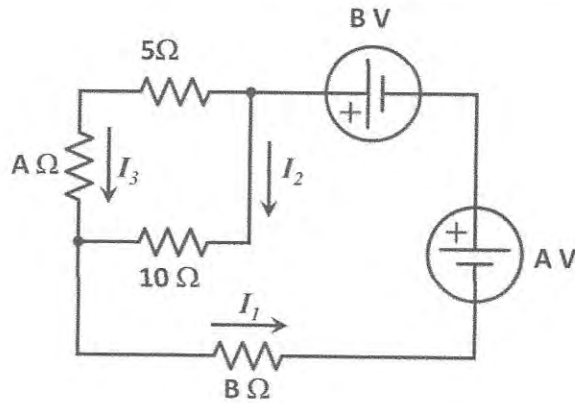


Figure Q2(a)

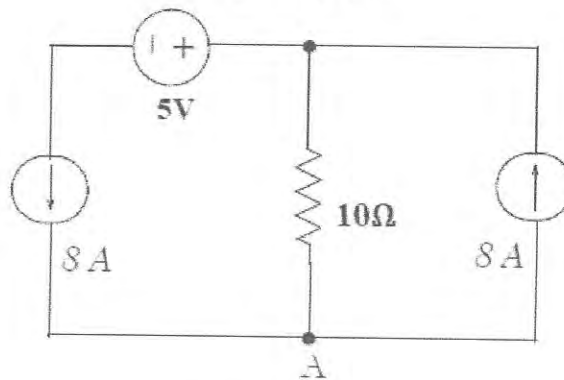


Figure Q2(b)

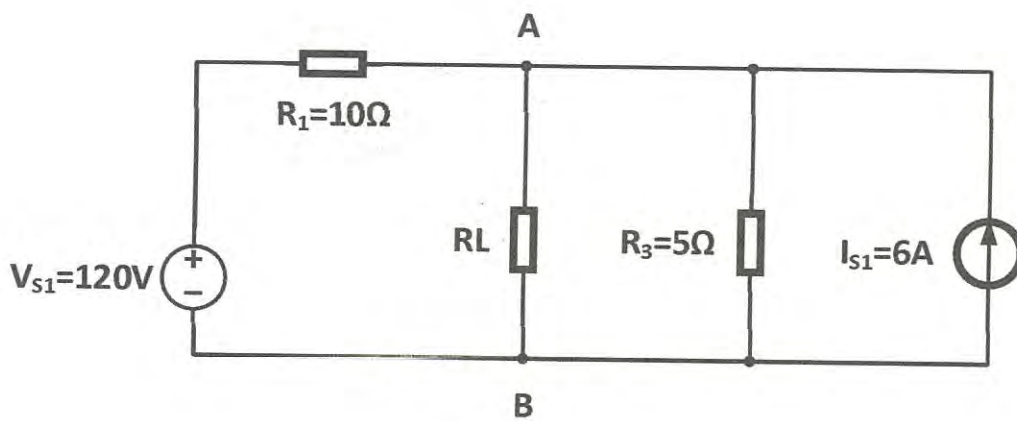


Figure Q2(c)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2020/2021

COURSE NAME : ELECTRICAL AND ELECTRONIC TECHNOLOGY

PROGRAMME CODE : BDD

COURSE CODE : BDA 14303

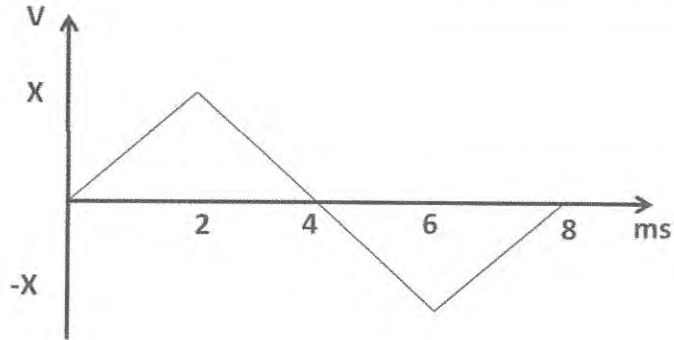


Figure Q3(a)

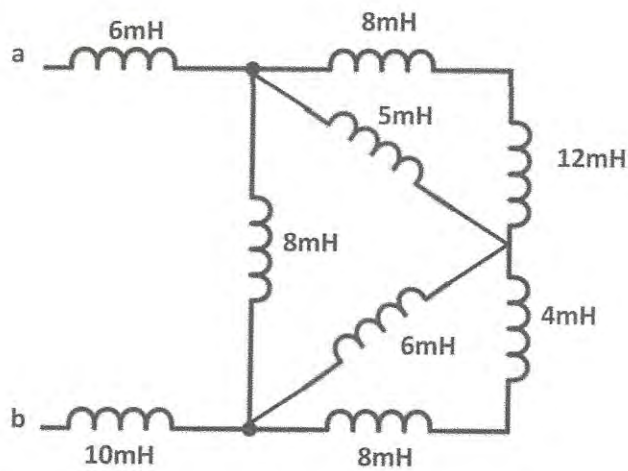


Figure Q3(b)

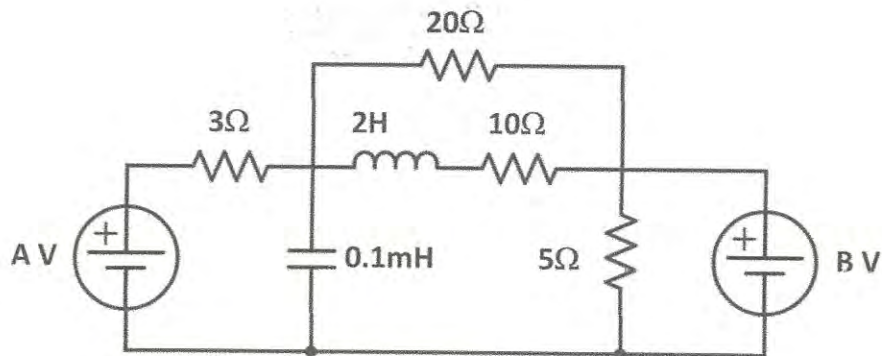


Figure Q3(c)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2020/2021

PROGRAMME CODE : BDD

COURSE NAME : ELECTRICAL AND ELECTRONIC TECHNOLOGY

COURSE CODE : BDA 14303

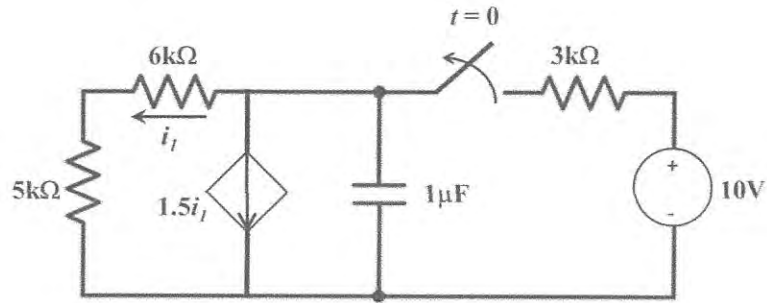


Figure Q3(d)

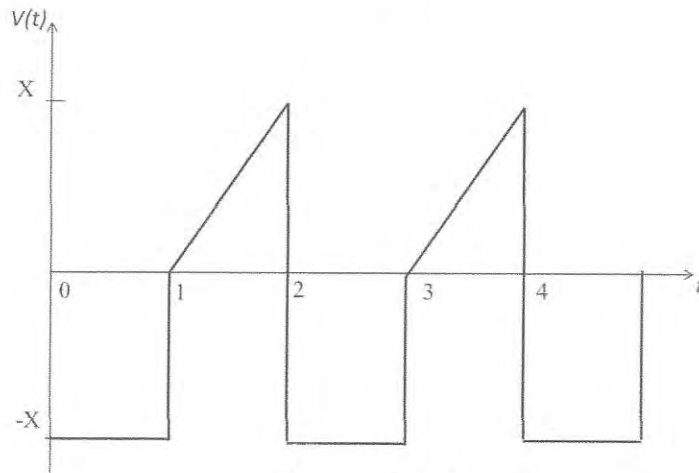


Figure Q4(a)

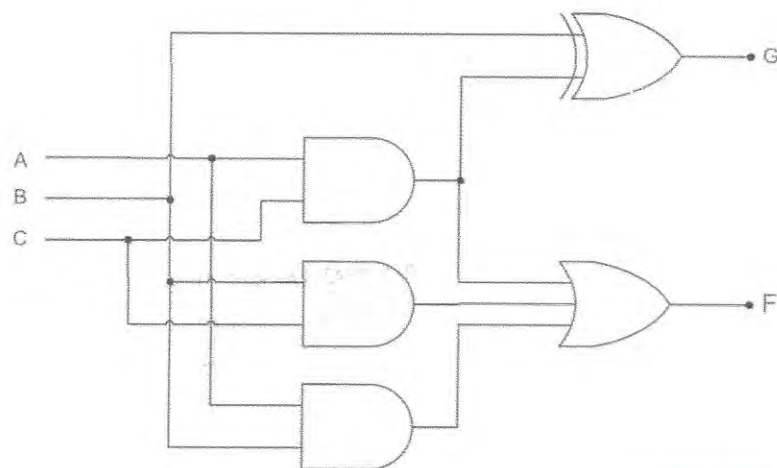


Figure Q5(c)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2020/2021

COURSE NAME : ELECTRICAL AND ELECTRONIC TECHNOLOGY
TECHNOLOGY

PROGRAMME CODE : BDD

COURSE CODE : BDA 14303

LIST OF FORMULA

OHMS LAW

$$V = IR$$

JOULE'S LAW


$$P = IV$$

KIRCHHOFF LAW

$$\sum_{k=1}^n i_k = 0$$

$$\sum_{v=1}^n v_k = 0$$

WYE-DELTA TRANSFORMATION

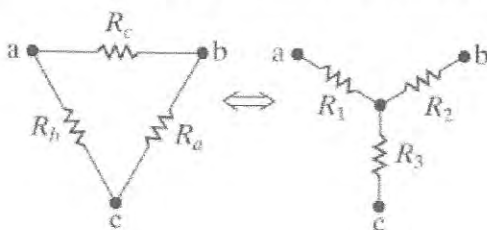

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

SOURCE TRANSFORMATION

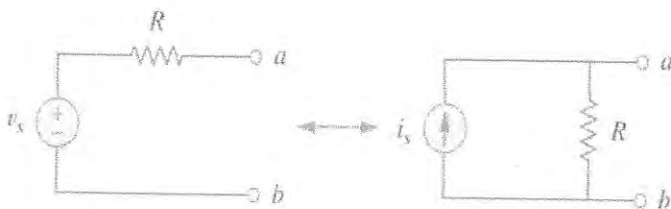

$$V_s = I_s R$$

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2020/2021

PROGRAMME CODE : BDD

COURSE NAME : ELECTRICAL AND ELECTRONIC TECHNOLOGY

COURSE CODE : BDA 14303

THEVENIN AND NORTON EQUIVALENT CIRCUIT

$$R_{TH} = R_N$$

$$I_N = \frac{V_{TH}}{R_{TH}}$$


$$P = i^2 R_L = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

When $R_L \neq R_{TH}$

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}}$$

When $R_L = R_{TH}$

MAXIMUM POWER TRANSFER

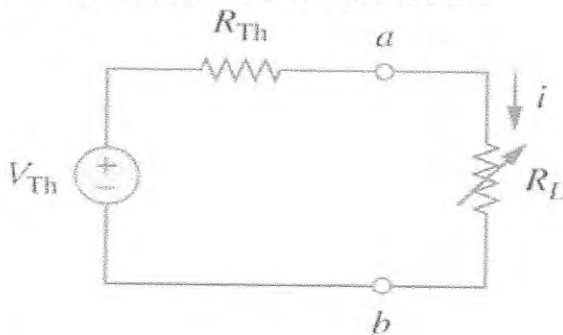

$$P = i^2 R_L = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

CAPACITOR AND INDUCTOR

$$C = \frac{\epsilon A}{d}$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt + v(t_0)$$

$$i = C \frac{dv}{dt}$$

$$w = \frac{1}{2} C v^2$$

$$L = \frac{N^2 \mu A}{l}$$

$$v = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

$$w = \frac{1}{2} L i^2$$

$$\tau = RC$$

$$\tau = \frac{L}{R}$$

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2020/2021

PROGRAMME CODE : BDD

COURSE NAME : ELECTRICAL AND ELECTRONIC TECHNOLOGY
TECHNOLOGY

COURSE CODE : BDA 14303

ALTERNATING CURRENT POWER CALCULATION

$$P(t) = v(t)i(t)$$

Instantaneous power

$$P = \frac{1}{2} \operatorname{Re}[VI^*] = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

Average power

$$i_{RMS} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

$$P_{RMS} = I_{RMS}^2 R = \frac{V_{RMS}^2}{R}$$

TRANSFORMERS

$$\frac{V_P}{V_S} = \frac{N_P}{N_S}$$

TERBUKA

FINAL EXAMINATION








SEMESTER / SESSION : SEM II / 2020/2021
 COURSE NAME : ELECTRICAL AND ELECTRONIC TECHNOLOGY
 TECHNOLOGY

PROGRAMME CODE : BDD
 COURSE CODE : BDA 14303

STANDARD RESISTOR VALUES AND COLOR

Color	Digit	Multiplier	Tolerance (%)
Black	0	10^0 (1)	
Brown	1	10^1	1
Red	2	10^2	2
Orange	3	10^3	
Yellow	4	10^4	
Green	5	10^5	0.5
Blue	6	10^6	0.25
Violet	7	10^7	0.1
Grey	8	10^8	
White	9	10^9	
Gold		10^{-1}	5
Silver		10^{-2}	10
(none)			20

LOGIC GATES

Name	NOT	AND	NAND	OR	NOR	XOR	XNOR																																																																																
Alg. Expr.	\bar{A}	AB	\overline{AB}	$A+B$	$\overline{A+B}$	$A \oplus B$	$\overline{A \oplus B}$																																																																																
Symbol																																																																																							
Truth Table	<table border="1"> <thead> <tr> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	X	0	1	1	0	<table border="1"> <thead> <tr> <th>B</th> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	B	A	X	0	0	0	0	1	0	1	0	0	1	1	1	<table border="1"> <thead> <tr> <th>B</th> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	B	A	X	0	0	1	0	1	1	1	0	1	1	1	0	<table border="1"> <thead> <tr> <th>B</th> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	B	A	X	0	0	0	0	1	1	1	0	1	1	1	1	<table border="1"> <thead> <tr> <th>B</th> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	B	A	X	0	0	1	0	1	0	1	0	0	1	1	0	<table border="1"> <thead> <tr> <th>B</th> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	B	A	X	0	0	0	0	1	1	1	0	1	1	1	0
A	X																																																																																						
0	1																																																																																						
1	0																																																																																						
B	A	X																																																																																					
0	0	0																																																																																					
0	1	0																																																																																					
1	0	0																																																																																					
1	1	1																																																																																					
B	A	X																																																																																					
0	0	1																																																																																					
0	1	1																																																																																					
1	0	1																																																																																					
1	1	0																																																																																					
B	A	X																																																																																					
0	0	0																																																																																					
0	1	1																																																																																					
1	0	1																																																																																					
1	1	1																																																																																					
B	A	X																																																																																					
0	0	1																																																																																					
0	1	0																																																																																					
1	0	0																																																																																					
1	1	0																																																																																					
B	A	X																																																																																					
0	0	0																																																																																					
0	1	1																																																																																					
1	0	1																																																																																					
1	1	0																																																																																					

TERBUKA