



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2021/2022**

- COURSE NAME : ELECTRICAL TECHNOLOGY
- COURSE CODE : DAE 11003
- PROGRAMME CODE : DAE
- EXAMINATION DATE : JANUARY / FEBRUARY 2022
- DURATION : 3 HOURS
- INSTRUCTION : 1. ANSWER **FOUR (4)** QUESTIONS ONLY FROM **FIVE (5)** QUESTIONS PROVIDED.
2. THIS FINAL EXAMINATION IS AN **ONLINE ASSESSMENT** AND CONDUCTED VIA **CLOSE BOOK**.

THIS QUESTION PAPER CONSISTS OF TEN (10) PAGES

- Q1**
- (a) Describe the relationship between protons and atomic number. (2 Marks)
 - (b) Determine the minimum and maximum resistance value of a four (4) band resistor which has the first band - Green, the second band - Blue, the third band - Orange, the fourth band - Gold. (3 Marks)
 - (c) Identify the color code of $33 \text{ k}\Omega$, $\pm 5\%$ four (4) band resistor. (4 Marks)
 - (d) Calculate resistor value that would produce a current flow of 5 Amps with a battery voltage of 12.6 volts. (2 Marks)
 - (e) If the current through a circuit is 2 Amps and the resistance of a light bulb in the circuit is 10 Ohms, find the voltage difference across the light bulb and the power usage of the circuit. (4 Marks)
 - (f) Referring to **Figure Q1(f)**, sketch the connections of the ammeter and the voltmeter in measuring current and voltage across the load R_1 . (2 Marks)
 - (g) Describe the linear relationship between current and voltage. (2 Marks)
 - (h) Design an electric circuit schematic and illustrate the current flow direction for a DC lamp with a switch (Single Pole Single Throw -SPST) and a 9V battery. (4 Marks)
 - (i) A battery is a type of voltage source that converts chemical energy into electrical energy. If the battery supplies 10 joules of energy per coulomb. Find the voltage of the battery. (2 Marks)
- Q2**
- (a) Express Kirchhoff's Voltage Law (KVL) equivalence for the circuit referring to **Figure Q2(a)**. (2 marks)
 - (b) Define the voltage divider in the series circuit. (3 marks)
 - (c) Show the formula of the voltage divider for the circuit referring to **Figure Q2(c)**. (2 marks)

- (d) Consider a **three (3)** resistor in series (referring to **Figure Q2(d)**). Given, $V_1 = 0.2V_x$, $V_2 = 0.5V_x$ and $R_T = 40 \Omega$. Obtain design values for:
- (i) R_1 (2 marks)
 - (ii) R_2 (2 marks)
 - (iii) R_3 (1 mark)
- (e) Referring to **Figure Q2(e)**, determine the following items when $R_2 = 19 \text{ k}\Omega$, $R_3 = 30 \text{ k}\Omega$ and the $I_s = 8 \text{ mA}$.
- (i) *Requivalent* (2.5 marks)
 - (ii) V_1 (2 marks)
 - (iii) I_2 (2 marks)
 - (iv) I_3 (2 marks)
 - (v) Power supplied by the source (1.5 marks)
- (f) Summarize the total power obtained in series and parallel circuits. (3 marks)

- Q3** (a) Referring to **Figure Q3(a)**:
- (i) Identify the bleeder current in **Figure Q3(a)**. Provide statement and equivalent equation to support your answer. (3 Marks)
 - (ii) Find load currents at I_{RL1} and I_{RL2} (8 Marks)
 - (iii) Determine value of bleeder current (2 Marks)
- (b) Based on **Figure Q3(b)**, define:
- (i) Ohm's Law for Magnetic Circuits with aids of related equivalent. (2 marks)
 - (ii) Magnetomotive force (m.m.f) (2 marks)
 - (iii) Reluctance of the circuit if the flux is $834 \mu\text{Wb}$. (2 marks)



- (c) (i) Explain the effect for material below on a magnetic field. Support your statement with related diagram.
 (a) iron
 (b) wood
 (4 marks)

- (ii) Illustrate the north and south poles of the magnet.
 (2 marks)

- Q4.** (a) (i) Define 'Period' of a sine wave.
 (1 mark)

- (ii) Illustrate 5 cycles of sine wave.
 (2 marks)

- (b) Convert the following angular values from degrees to radians:
 (i) 45°
 (2 marks)

- (ii) 200°
 (2 marks)

- (c) A sine wave has a peak value of 20V. Determine the following values:
 (i) V_{rms}
 (2 marks)

- (ii) V_{pp}
 (2 marks)

- (iii) V_{avg} (over a half cycle)
 (2 marks)

- (d) Solve the following operations:
 (i) $\frac{2.5\angle 65^{\circ} - 1.8\angle -23^{\circ}}{1.2\angle 37^{\circ}}$
 (4 marks)

- (ii) $\frac{(100\angle 15^{\circ})(85 - j150)}{25 + j45}$
 (3 marks)

- (e) Design a simple AC generator complete with magnetic poles, anchor, load, carbon brushes and slip rings.
 (5 marks)

- Q5** (a) Define:
 (i) *Primary winding*
 (1 mark)

- (ii) *Secondary winding.*
 (1 mark)



- (b) Identify **three (3)** types of self-excited DC generators. (3 marks)
- (c) Determine the maximum power that can be delivered to the 10Ω speaker referring to **Figure Q5(C)**. (12 marks)
- (d) Identify the parts labelled as i, ii, iii, iv and v of a DC machines referring to **Figure Q5(d)**. (5 marks)
- (e) Construct *Short Shunt Compound Wound DC Generator* circuit. (3 marks)

-END OF QUESTIONS -

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2021/2022
COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : DAE
COURSE CODE : DAE 11003

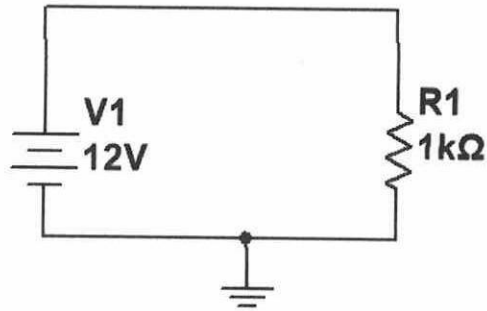


Figure Q1(f)

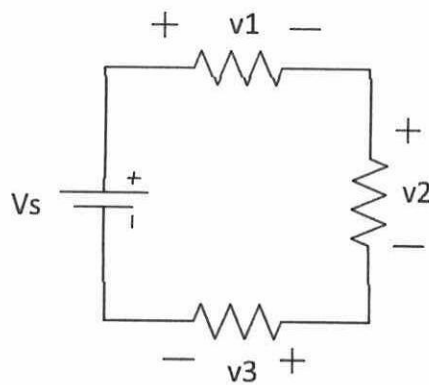


Figure Q2(a)

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2021/2022
COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : DAE
COURSE CODE : DAE 11003

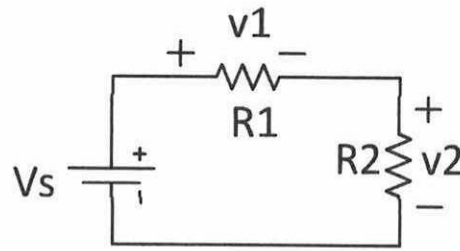


Figure Q2(c)

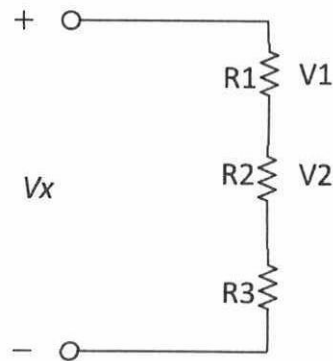


Figure Q2(d)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2021/2022
COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : DAE
COURSE CODE : DAE 11003

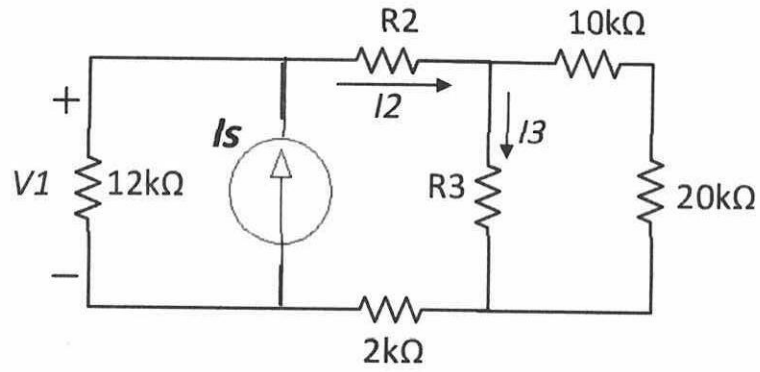


Figure Q2(e)

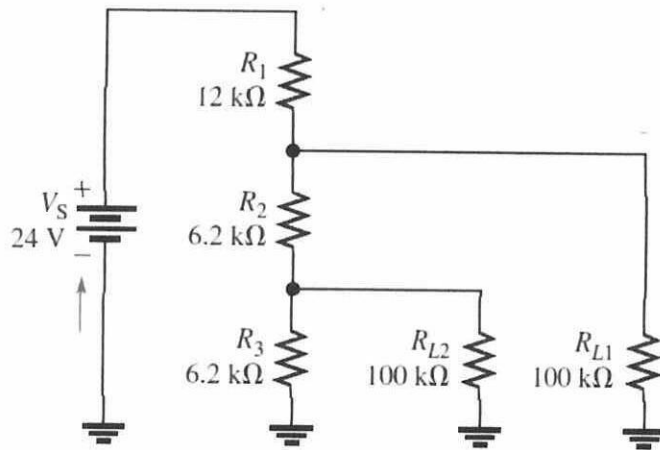


Figure Q3(a)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2021/2022
COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : DAE
COURSE CODE : DAE 11003

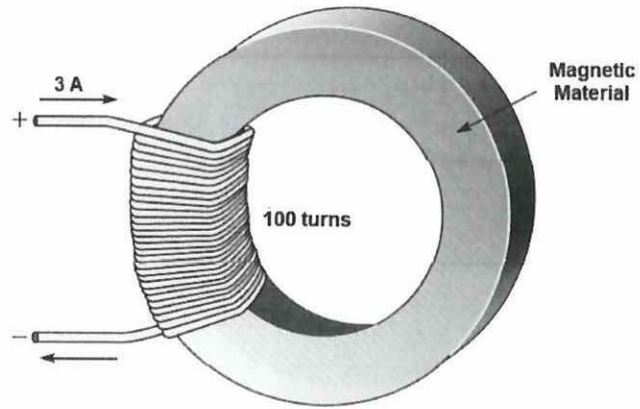


Figure Q3(b)

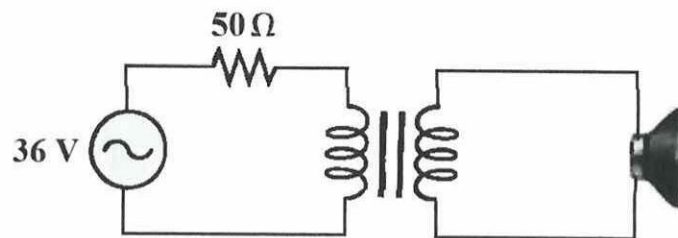


Figure Q5(c)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2021/2022
COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : DAE
COURSE CODE : DAE 11003

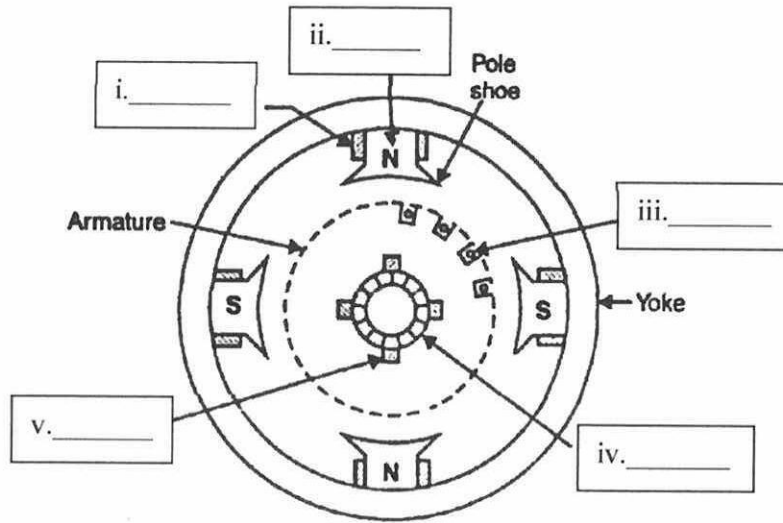


Figure Q5(d)

TERBUKA