

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2022/2023**

COURSE NAME : ELECTRONICS

COURSE CODE : DAE 21303

PROGRAMME CODE : DAE

EXAMINATION DATE : FEBRUARY 2023

DURATION : 2 HOURS 30 MINUTES

INSTRUCTION : 1. ANSWERS ALL QUESTIONS.

2. THIS FINAL EXAMINATION IS CONDUCTED VIA **CLOSED BOOK**.

3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES DURING THE EXAMINATION CONDUCTED VIA **CLOSED BOOK**.

THIS QUESTION PAPER CONSISTS OF **EIGHT (8)** PAGES

CONFIDENTIAL

TERBUKA

Q1 (a) In your own words, define briefly:

- (i) Extrinsic semiconductor. (2 marks)
- (ii) Forward bias and reverse bias. (2 marks)
- (iii) Depletion region. (2 marks)

(b) A centre-tapped full wave rectifier with a load, R_L is driven by a transformer with $N_{pri} : N_{sec}$ turn ratio. The primary transformer is connected to a 120 V_{rms}, 50 Hz. The average voltage, V_{dc} that is produced by this rectifier is 27 V. Assuming diodes are ideal.

- (i) Draw the schematic diagram of the circuit. (2 marks)
- (ii) Determine the transformer turns ratio. (4 marks)
- (ii) Sketch and label with values the input voltage, V_{in} and output voltage, V_o waveform of the rectifier. (4 marks)
- (iii) Calculate the Peak Inverse Voltage, PIV of each diode in the circuit. (2 marks)

(c) Based on question **Q1(b)**, a 1.0 mF capacitor filter is now connected to the output of the rectifier circuit. If the dc current through the load is 0.1 A,

- (i) Determine the filtered output ripple voltage, $V_{r(p-p)}$ and the average voltage, $V_{r(dc)}$. (4 marks)
- (ii) Sketch and clearly label the output ripple voltage from the filter. (3 marks)

- Q2** (a) A voltage regulator circuit in **Figure Q2(a)** will maintain an output voltage of 20 V across a 1 k Ω load, R_L with an input, V_s varies between 30 V and 50 V. Determine:
- (i) The minimum, I_{ZMin} and the maximum zener current, I_{ZMax} for the network if $R_{in} = 100 \Omega$.
(10 marks)
 - (ii) The zener power rating, P_{zmin} and P_{zmax} .
(2 marks)
- (b) The applications of the diode are shown in **Figure Q2(b)** with two different types of network.
- (i) Determine the output voltage, V_o .
(8 marks)
 - (ii) Draw the waveform for each network.
(5 marks)
- Q3** (a) **Figure Q3(a)(i)** depicts the load line and device characteristics of a fixed-bias network of Calculate the following based on the **Figure Q3(a)(ii)**.
- (i) The common collector voltage, V_{cc}
(2 marks)
 - (ii) The base resistor, R_B
(2 marks)
 - (iii) The collector resistor, R_C
(2 marks)
- (b) Determine the dc bias characteristics for the voltage-divider configuration of **Figure Q3(b)**.
- (i) The dc base current, I_B
(6 marks)
 - (ii) The dc collector current, I_C
(1 mark)
 - (iii) The dc bias voltage, V_{CE}
(2 marks)

(c) Refer to the amplifier network in **Figure Q3 (c)**.

- (i) Sketch the ac equivalent circuit using r_e model. (4 marks)
- (ii) Determine the ac dynamic resistance, r_e if the dc base current, $I_B = 34.51 \mu\text{A}$. (2 marks)
- (iii) Calculate the input impedance, Z_i and the output impedance, Z_o . (4 marks)

Q4 (a) Determine the pinch-off voltage, V_P for a specific JFET if the drain current, $I_D = 4\text{mA}$ when the gate to source, $V_{GS} = -3\text{V}$ and the maximum drain current, $I_{DSS} = 12\text{mA}$. (3 marks)

(b) For the self-bias configuration of **Figure Q4(b)**, solve the following if given Shockley's equation:

$$I_D = I_{DSS} \left(1 - \frac{V_{GSQ}}{V_P} \right)^2$$

- (i) The *quiescent*, Q-points (drain current, I_{DQ} and gate to source voltage, V_{GSQ}) by using graphical approach method. (8 marks)
- (ii) The drain to source voltage, V_{DS} , drain voltage, V_D , gate voltage, V_G and gate to source voltage, V_{GS} . (7 marks)
- (c) The fixed-bias configuration of **Figure Q4(c)** had an operating point defined by the gate to source voltage, $V_{GSQ} = -2.5\text{V}$ with the maximum drain current, $I_{DSS} = 10\text{mA}$, the pinch-off voltage, $V_P = -4\text{V}$, and the drain resistance, $r_d = 20\text{k}\Omega$. Determine:
- (i) The input impedance Z_i . (1 mark)
- (ii) The output impedance Z_o . (2 marks)
- (iii) The voltage gain A_v . (4 marks)

-END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER / SESSION : SEM 1 2022/2023
 COURSE NAME : ELECTRONICS

PROGRAMME CODE : DAE
 COURSE CODE : DAE 21303



 


Figure Q2(a)

 

(i) Clipper Network

 


(ii) Clamper Network

Figure Q2(b)


FINAL EXAMINATION

SEMESTER / SESSION : SEM 1 2022/2023
COURSE NAME : ELECTRONICS

 PROGRAMME CODE : DAE
COURSE CODE : DAE 21303



(i)

 

(ii)

Figure Q3(a)

 


Figure Q3(b)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM 1 2022/2023
 COURSE NAME : ELECTRONICS

PROGRAMME CODE : DAE
 COURSE CODE : DAE 21303

 


Figure Q3(c)

 


Figure Q4(b)

FINAL EXAMINATION

SEMESTER / SESSION : SEM 1 2022/2023
COURSE NAME : ELECTRONICS

PROGRAMME CODE : DAE
COURSE CODE : DAE 21303

 


Figure Q4(c)