

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2022/2023**

COURSE NAME : POWER SYSTEM
COURSE CODE : BEJ 20603 / BEF 25503
PROGRAMME CODE : BEV
EXAMINATION DATE : FEBRUARY 2023
DURATION : 3 HOURS
INSTRUCTION : :
1. ANSWER ALL QUESTIONS
2. THIS FINAL EXAMINATION IS CONDUCTED VIA **CLOSED BOOK**.
3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES DURING THE EXAMINATION CONDUCTED VIA CLOSED BOOK

THIS QUESTION PAPER CONSISTS OF FOUR (4) PAGES

TERBUKA

CONFIDENTIAL

- Q1**
- (a) The increasing electricity demand has led to significant interest in distributed generation. Give **three (3)** impacts of implementing distributed generation in modern power systems. (3 marks)
- (b) Describe **three (3)** ways of defining the power factor. (3 marks)
- (c) The heating element in a soldering iron has a resistance of $0.8 \text{ k}\Omega$. It is connected to an AC voltage source with peak to peak voltage of 651 V .
- (i) Find the average power dissipated in the soldering iron. (3 marks)
- (ii) Calculate the current that flows into the heating element. (2 marks)
- (d) A current source, $i(t) = 5 \sin(120\pi t) - 2 \cos(120\pi t - 50^\circ) \text{ A}$ is connected to a $10 \text{ }\Omega$ resistor.
- (i) Determine the average power delivered to the resistor. (4 marks)
- (ii) Deduce the instantaneous voltage, $v(t)$ across the resistor. (4 marks)
- (iii) Establish the instantaneous power, $p(t)$ equation of the resistor. (6 marks)
- Q2**
- (a) A three-phase load consists of three $100 \text{ }\Omega$ resistors that can be either Y-connected or Δ -connected with a line voltage of 400 V . Prove that the Δ -connected load will absorb higher average power. Assume zero line impedance. (11 marks)
- (b) In a balanced three-phase Δ -Y circuit, the source is connected in the negative sequence with $V_{ab} = 220 \angle 20^\circ \text{ V}$ and $Z_Y = 20 + j15 \text{ }\Omega$.
- (i) Calculate the line currents. (3 marks)
- (ii) Define the balanced system based on your answers in **Q2(b)(i)**. (1 mark)

- (c) Three identical Y-connected loads, each having a resistance of 150Ω in series with an inductance of 0.5 H , are connected to a three-phase supply of 400 V with 50 Hz frequency. Sketch the circuit connection and determine the load's real power and power factor.

(10 marks)

- Q3** (a) A three-phase line has an impedance of $1 + j3 \Omega$ per phase. The line feeds a balanced Δ -connected load, which absorbs a total complex power of $12 + j5 \text{ kVA}$. The line voltage at the load end has a magnitude of 240 V .

(i) Sketch the equivalent circuit.

(3 marks)

(ii) Calculate the magnitude of the line voltage at the source end.

(7 marks)

(iii) Find the complex power of the source.

(2 marks)

- (b) A three-phase supply of 400 V is connected across a balanced Δ -connected load of each consisting of 32Ω resistance and 24Ω inductive reactance. Sketch the three-phase connection and determine the current drawn from the supply. Use VRY as a reference in the RYB sequence.

(9 marks)

- (c) List **four (4)** possible connections of a balanced three-phase system.

(4 marks)

- Q4** (a) Most of the loads in the electrical distribution systems are inductive. Hence, the system possesses a low power factor, which is highly undesirable. States **five (5)** disadvantages of having poor power factor within the electrical distribution system.

(5 marks)

- (b) A $230 \text{ V}_{\text{rms}}$ 50 Hz source supplies a parallel combination of a 5 kW heater and a 30 kVA induction motor whose power factor is 0.7 .

(i) Determine the complex power of the system.

(11 marks)

(ii) Find the power factor of the system.

(2 marks)

- (iii) Calculate the kVA rating of a capacitor required to adjust the system power factor to 0.9 lagging. (3 marks)
- (iii) Deduce the value of the capacitor required. (2 marks)
- (iv) Compute the new reactive power of the system. (2 marks)

- END OF QUESTIONS -