



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2022/2023**

COURSE NAME : ELECTRIC CIRCUITS 1
COURSE CODE : BEJ 10303
PROGRAMME CODE : BEJ
EXAMINATION DATE : FEBRUARY 2023
DURATION : 3 HOURS
INSTRUCTION : 1. ANSWER ALL QUESTIONS
2. THIS FINAL EXAMINATION IS CONDUCTED VIA **CLOSED BOOK**.
3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES DURING THE EXAMINATION CONDUCTED VIA CLOSED BOOK

THIS QUESTION PAPER CONSISTS OF **EIGHT (8) PAGES**.

TERBUKA

CONFIDENTIAL

- Q1** (a) For the circuit in **Figure Q1(a)**, find voltage, V_x and the power absorbed by the $12\ \Omega$ resistor. (8 marks)
- (b) Calculate the source current, I_S in the circuit of **Figure Q1(b)** by using delta-to-wye transformation. By aid of diagrams, show all related circuits involved during the transformation. (7 marks)
- (c) Referring to the circuit in **Figure Q1(c)**,
- (i) Determine the value of voltages, v_1 and v_2 , using nodal analysis. (7 marks)
- (ii) Calculate the power dissipated in all the resistors in the circuit. (3 marks)
- Q2** (a) By using the mesh analysis, compute the value of i_B and v_O for the circuit shown in **Figure Q2(a)**. (12 marks)
- (b) Nodal and mesh analysis provide a systematic way of analyzing a complex network. Describe the difference between these two analyses. (4 marks)
- (c) Use superposition to find V_O in the circuit of **Figure Q2(b)**. (9 marks)
- Q3** (a) By aid of the diagram, explain the Thevenin's theorem. (3 marks)
- (b) Refer to the circuit in **Figure Q3(a)**,
- (i) Obtain the Thevenin equivalent at terminals a-b. (11 marks)
- (ii) Determine the Norton current, I_N and draw its Norton equivalent circuit. (3 marks)

TERBUKA

- (c) The variable resistor, R in **Figure Q3(b)** is adjusted until it absorbs the maximum power from the circuit.
- (i) Calculate the value of R for maximum power. (3 marks)
- (ii) Determine the maximum power, P_{max} absorbed by R . (5 marks)
- Q4** (a) Given that, $v(t) = 120 \cos(377t + 45^\circ)$ V and $i(t) = 10 \cos(377t - 10^\circ)$ A.
- (i) Find the instantaneous power and average power absorbed by the passive linear network. (8 marks)
- (ii) Explain what is instantaneous power and average power. (4 marks)
- (b) A current flowing through a 9Ω resistor has a periodic triangular waveform as shown in **Figure Q4(a)**.
- (i) Find the rms value of the current waveform (7 marks)
- (ii) Find the average value of the current waveform. (4 marks)
- (iii) Calculate the power absorbed by the 9Ω resistor. (2 marks)

-END OF QUESTIONS -

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2022/2023
COURSE NAME : ELECTRIC CIRCUITS 1

PROGRAMME CODE : BEJ
COURSE CODE : BEJ 10303

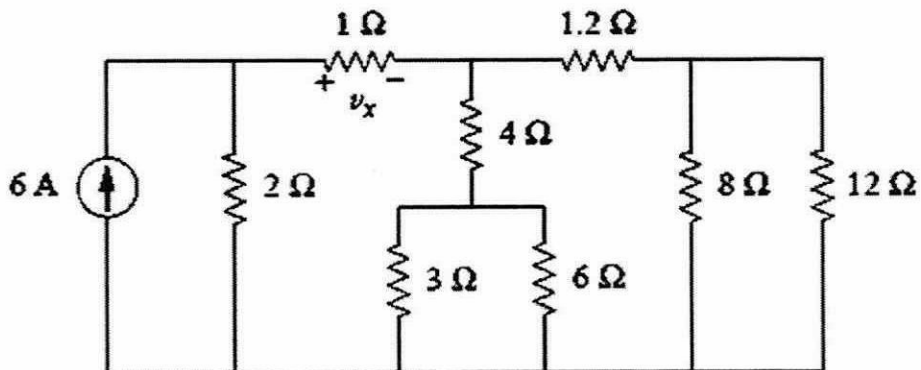


Figure Q1(a)

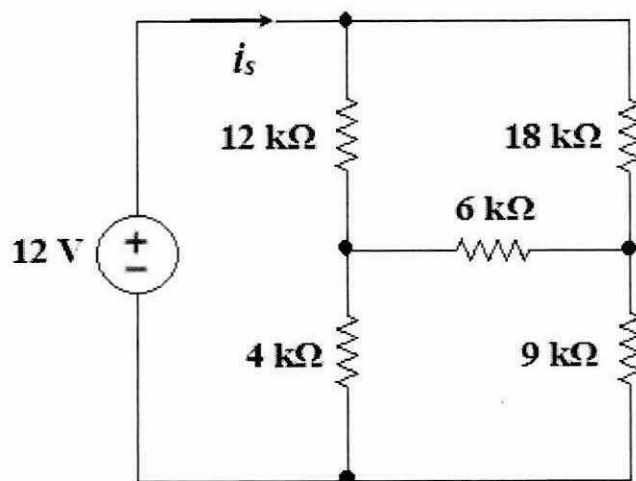


Figure Q1(b)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2022/2023
COURSE NAME : ELECTRIC CIRCUITS 1

PROGRAMME CODE : BEJ
COURSE CODE : BEJ 10303

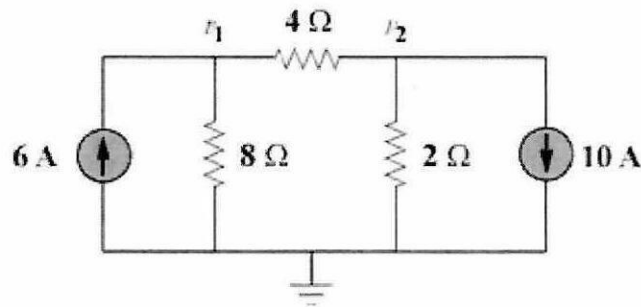


Figure Q1(c)

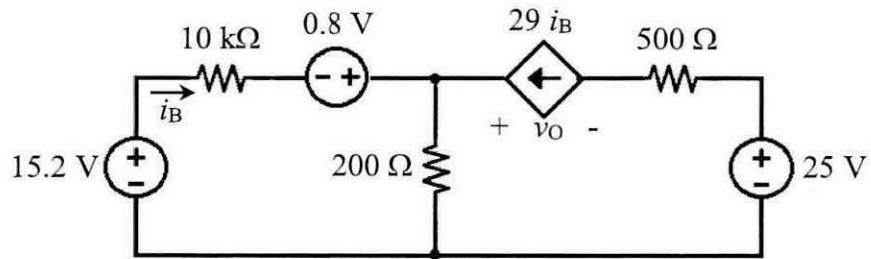


Figure Q2(a)

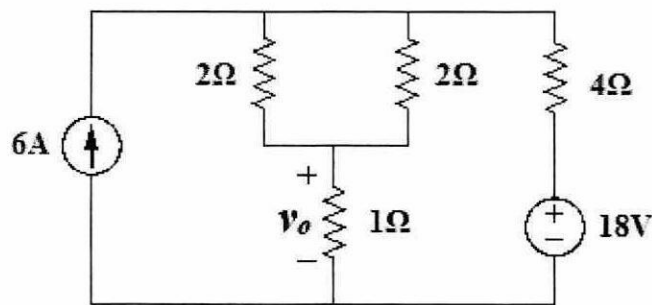


Figure Q2(b)

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2022/2023
COURSE NAME : ELECTRIC CIRCUITS 1

PROGRAMME CODE : BEJ
COURSE CODE : BEJ 10303

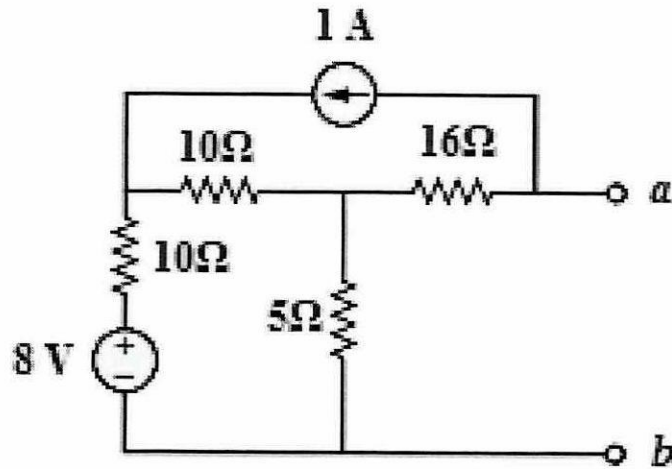


Figure Q3(a)

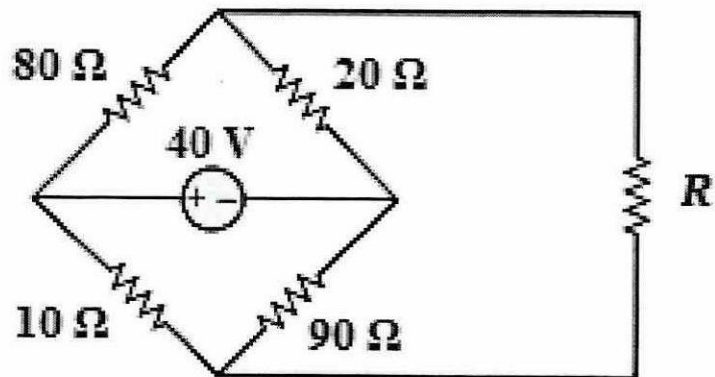


Figure Q3(b)

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2022/2023
COURSE NAME : ELECTRIC CIRCUITS 1

PROGRAMME CODE : BEJ
COURSE CODE : BEJ 10303

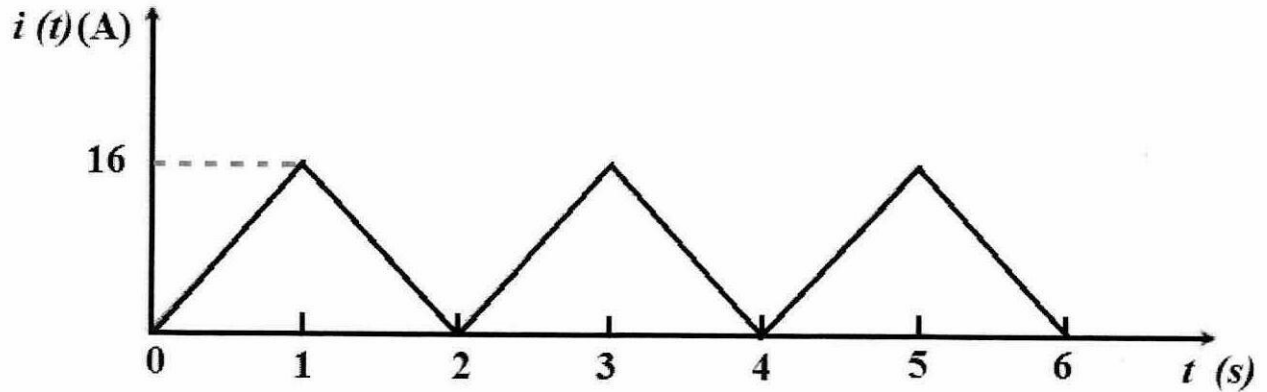


Figure Q4(a)

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2022/2023
 COURSE NAME : ELECTRIC CIRCUITS 1

PROGRAMME CODE : BEJ
 COURSE CODE : BEJ 10303

APPENDIX A

TRIGONOMETRIC EQUATIONS

$$\sin(-x) = -\sin(x)$$

$$\cos(-x) = \cos(x)$$

$$\tan(-x) = -\tan(x)$$

$$\sec x = \frac{1}{\cos x}, \quad \csc x = \frac{1}{\sin x}$$

$$\tan x = \frac{\sin x}{\cos x}, \quad \cot x = \frac{\cos x}{\sin x}$$

$$\sin^2 2x + \cos^2 2x = 1$$

$$\sin(2x) = 2 \sin x \cos x$$

$$\cos(2x) = \cos^2 x - \sin^2 x$$

$$\cos(2x) = 2 \cos^2 x - 1 = 1 - 2 \sin^2 x$$

$$\sin(x \pm 90^\circ) = \pm \cos x$$

$$\cos(x \pm 90^\circ) = \mp \sin x$$

$$\sin(x \pm 180^\circ) = \mp \sin x$$

$$\cos(x \pm 180^\circ) = \mp \cos x$$

$$\cos^2 x + \sin^2 x = 1$$

$$\sin(x \pm y) = \sin x \cos y \pm \cos x \sin y$$

$$\cos(x \pm y) = \cos x \cos y \mp \sin x \sin y$$

$$\tan(x \pm y) =$$

$$\frac{\sin(x \pm y)}{\cos(x \pm y)} = \frac{\sin x \cos y \pm \cos x \sin y}{\cos x \cos y \mp \sin x \sin y}$$

$$2 \sin x \cos y = \sin(x+y) + \sin(x-y)$$

$$2 \cos x \cos y = \cos(x+y) + \cos(x-y)$$

$$\cos x \cos y = \frac{1}{2} [\cos(x+y) + \cos(x-y)]$$