

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2022/2023**

COURSE NAME : DIGITAL DESIGN
COURSE CODE : BEJ 30503 / BEC 30503
PROGRAMME CODE : BEJ
EXAMINATION DATE : FEBRUARY 2023
DURATION : 3 HOURS
INSTRUCTION :
1. ANSWER ALL QUESTIONS IN PART A AND ONE (1) QUESTION IN PART B.
2. THIS FINAL EXAMINATION IS CONDUCTED VIA **CLOSED BOOK**.
3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES DURING THE EXAMINATION CONDUCTED VIA CLOSED BOOK.

THIS QUESTION PAPER CONSISTS OF **EIGHT (8)** PAGES

CONFIDENTIAL

TERBUKA

PART A

- Q1**
- (a) List four principles in digital design to achieve the design objectives effectively and quickly. (4 marks)
 - (b) Compare the digital system with the analog system. Thus, explain one advantage of digital signal. (5 marks)
 - (c) Explain what digital design is, how it differs from designing an application by using a general-purpose processor? (4 marks)
 - (d) The Verilog program in **Figure Q1(d)** is written in behavioral modelling, name the circuit that is described by the codes and rewrite the program by using the dataflow modelling. (7 marks)
- Q2**
- (a) **Figure Q2(a)** shows a 2-to-4 decoder and its truth table.
 - (i) Write a Verilog program to describe the given decoder. (4 marks)
 - (ii) Design a 3-to-8 decoder by using the decoder in **Figure Q2(a)**. *Hint*: Derive the 3-to-8 decoder truth table based on the given 2-to-4 truth table, then draw the block diagram showing the interconnection of the designed module. (6 marks)
 - (b) A combinational logic module, *Sub_Core1* is described by the Verilog program in **Figure Q2(b)**. It is made up of logic component, *Core1_slice*.
 - (i) Sketch the logic circuit of *Core1_slice* component. (3 marks)
 - (ii) Draw the functional block diagram (FBD) of the *Sub_Core1* module, showing how the *Core1_slice* components are interconnected. (5 marks)
 - (iii) If the input vector, (*in3*, *in2*, *in1*, *in0*) is 0101, what is the value of the output vector, (*flag*, *out3*, *out2*, *out1*, *out0*)? (2 marks)

- Q3** (a) Convert the decimal numbers -100 into a signed 8-bit number in the following representations:
- (i) Sign and magnitude (1 mark)
 - (ii) 1's complement (1 mark)
 - (iii) 2's complement (1 mark)
- (b) Explain why the 2's complement representation is used to represent a signed number in a computer system instead of sign and magnitude or 1's complement representations. (4 marks)
- (c) **Figure Q3(c)** shows a functional block diagram (FBD) of a 4-bit arithmetic comparator. Based on the diagram, answer the following questions:
- (i) What is the logic that should be applied to Cin ? Explain your answer. (3 marks)
 - (ii) Write a full Verilog program to model the given circuit by using the FA module given in **Figure Q3(c)(ii)**. (7 marks)
 - (iii) If the input $x = -4$, $y = 5$ and $Cin = 1$, determine the values of b , N , Z , V and $Cout$. (3 marks)
- Q4** (a) Derive the circuit that is synthesized from the Verilog program in **Figure Q4(a)**. (6 marks)
- (b) Explain the differences between the blocking assignment and the non-blocking assignment in describing the sequential circuits. (4 marks)
- (c) A sequence detector to detect a sequence 101 is to be designed using a Finite State Machine (FSM).
- (i) Sketch the state diagram for the FSM by using the Moore model. (6 marks)
 - (ii) Draw the FBD of the FSM. (4 marks)

PART B

- Q5** A digital system is modelled by the register transfer level (RTL) codes in **Figure Q5**. Given that the registers are positive-edge-triggered and $*a$ denotes a bitwise inverted. The adder-subtractor unit is performing an add operation when $f=0$, or a subtraction operation when $f=1$.
- (a) From the RTL codes, derive the datapath unit of the digital system. Given A and B are registers and Acc is a load-shift register. (7 marks)
- (b) Design an FBD of the control unit for the digital system. (6 marks)
- (c) Derive the RTL Control Sequence (RTL-CS) table, applying the control vector format $LdA, LdB, LdAcc, f, S$ and $done$. (7 marks)
- Q6** The data flow graph (DFG) given in **Figure Q6** shows the operations and data dependencies of a digital system to be designed. a, b, c, d and e are all 8-bit data inputs, while x and y are the outputs.
- (a) If the design is constrained to one multiplier and one adder. Construct the schedule of this DFG applying “as late as possible” (ALAP) scheduling. (7 marks)
- (b) Derive the corresponding RTL code for your design. (6 marks)
- (c) Obtain the FBD of the datapath unit of this digital system. (7 marks)

-END OF QUESTIONS-

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2022/2023
 COURSE NAME : DIGITAL DESIGN

PROGRAMME CODE : BEJ
 COURSE CODE : BEJ 30503 /
 BEC 30503


```

module CircuitQ1d(a, b, c, d, S, X);
    input a, b, c, d;
    input [1:0] S;
    output X;
    reg X;

    always@ (a or b or c or d or S)
        if (S == 0) X = a;
        else if (S == 1) X = b;
        else if (S == 2) X = c;
        else X = d;

endmodule
    
```

Figure Q1(d)

 

(i)

En	w1	w0	y0	y1	y2	y3
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	1	0	0	0	1	0
0	1	1	0	0	0	1
1	X	X	0	0	0	0

(ii)

Figure Q2(a)

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2022/2023
 COURSE NAME : DIGITAL DESIGN

PROGRAMME CODE : BEJ
 COURSE CODE : BEJ 30503 /
 BEC 30503

```

module Sub_Core1(in3, in2, in1, in0, flag, out3, out2, out1, out0);
  input in3, in2, in1, in0;
  output flag, out3, out2, out1, out0;
  wire co0, co1;

  Core1_slice slice0(in3, in0, in3, out0, co0);
  Core1_slice slice1(in3, in1, co0, out1, co1);
  Core1_slice slice2(in3, in2, co1, out2, flag);
  assign out3 = in3;

endmodule

module Core1_slice(in3, ini, bi, s, co);
  input in3, ini, bi;
  output s, co;
  wire ai;

  assign ai = in3 ^ ini;
  assign s = ai ^ bi;
  assign co = ai & bi;

endmodule

```

Figure Q2(b)

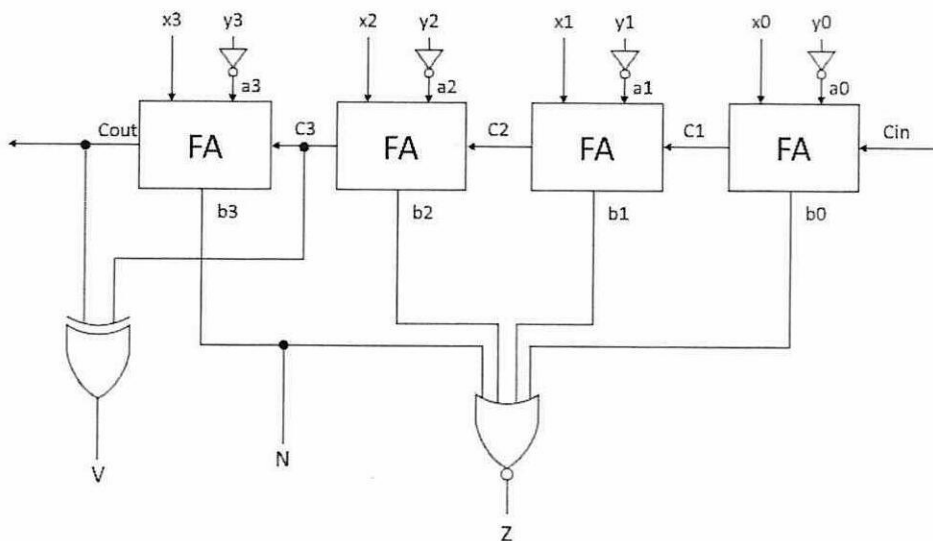


Figure Q3(c)

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2022/2023
COURSE NAME : DIGITAL DESIGN

PROGRAMME CODE : BEJ
COURSE CODE : BEJ 30503 /
BEC 30503

```
module FA (x, y, cin, cout, s);  
    input x, y, cin;  
    output cout, s;  
  
    assign s = x ^ y ^ cin;  
    assign cout = x & y | x & cin | y & cin;  
endmodule
```

Figure Q3(c)(ii)

```
module CircuitQ4(a, b, c, f, g);  
    input a, b, c;  
    output reg f, g;  
  
    always@ (posedge Clk, posedge Rst)  
        if (Rst) begin f = 0; g = 0; end  
        else  
            begin  
                f = a & b;  
                g = f ^ c;  
            end  
endmodule
```

Figure Q4(a)

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2022/2023
COURSE NAME : DIGITAL DESIGN

PROGRAMME CODE : BEJ
COURSE CODE : BEJ 30503 /
BEC 30503

```
S0: A ← In  
S1: (*a) Acc ← A + B;  
    (a) Acc ← A - B;  
S2: (*a) Acc ← B + B;  
    (a) Acc ← B - B;  
S3: B ← (Acc >> 1);  
done;
```

Figure Q5

 


Figure Q6

TERBUKA