

**CONFIDENTIAL**



**UTHM**  
Universiti Tun Hussein Onn Malaysia

**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER I  
SESSION 2022/2023**

COURSE NAME : ELECTRIC CIRCUITS II  
COURSE CODE : BEJ 10403  
PROGRAMME CODE : BEJ  
EXAMINATION DATE : FEBRUARY 2023  
DURATION : 3 HOURS  
INSTRUCTION :  
1. ANSWER ALL QUESTIONS  
2. THIS FINAL EXAMINATION IS CONDUCTED VIA **CLOSED BOOK**.  
  
3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES DURING THE EXAMINATION CONDUCTED VIA CLOSED BOOK


THIS QUESTION PAPER CONSISTS OF SIX (6) PAGES

**TERBUKA**

**CONFIDENTIAL**


**Q1 (a)** Based on **Figure Q1(a)**, determine:

- (i)  $v(0^+)$  and  $i(0^+)$  (4 marks)
- (ii)  $\frac{dv(0^+)}{dt}$  and  $\frac{di(0^+)}{dt}$  (4 marks)
- (iii)  $v(\infty)$  and  $i(\infty)$  (2 marks)

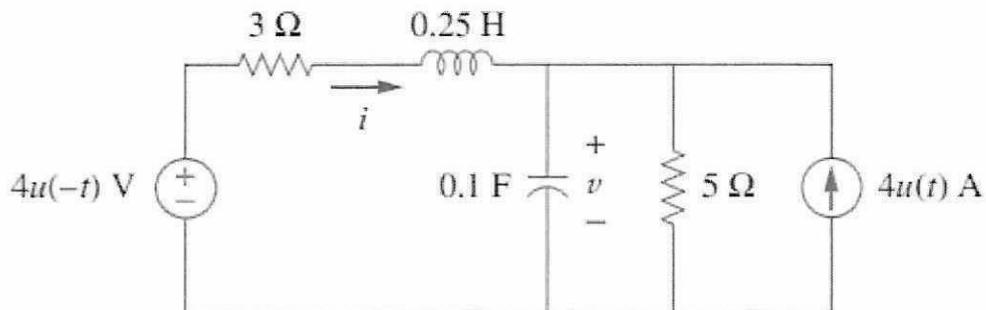

**Figure Q1(a)**

- (b) Based on the circuit in **Figure Q1(b)**, calculate the value of resistor,  $R$  that is needed to have a critically damped response.

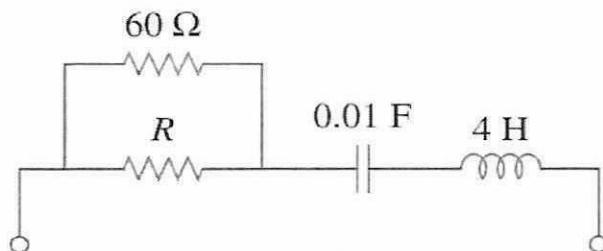


**Figure Q1(b)**

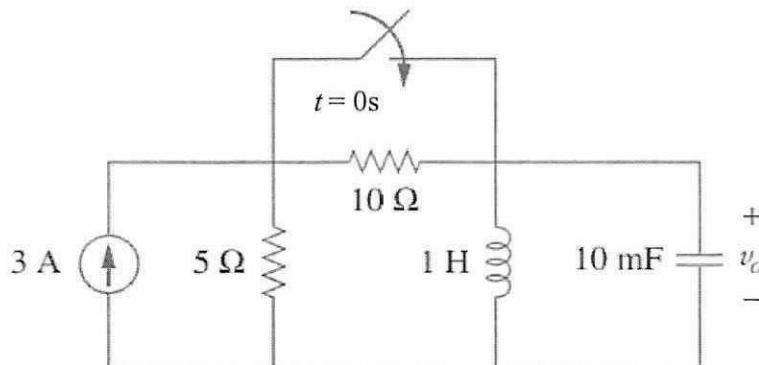(4 marks)

- (c) Determine the output voltage,  $v_o(t)$  for the circuit in **Figure Q1(c)**.

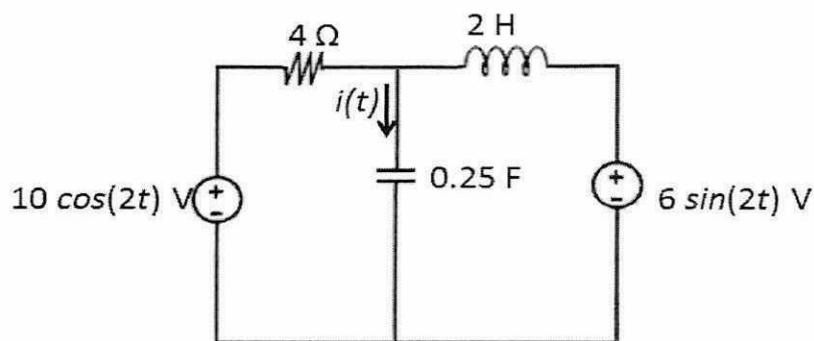
(11 marks)



**Figure Q1(c)**

**Q2 (a)** Solve the current,  $i(t)$  for the circuit in **Figure Q2(a)**. Hint: use mesh analysis.

(10 marks)

**Figure Q2(a)**


(b) For the circuit in **Figure Q2(b)**,

(i) determine the value of voltage,  $V_x$ .

(12 marks)

(ii) find the current,  $i(t)$ .

(3 marks)

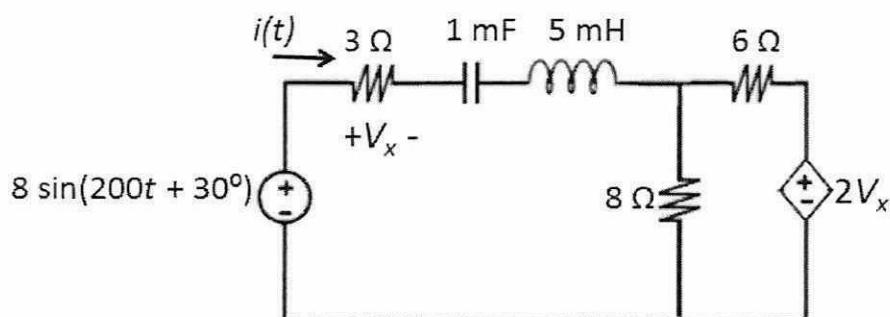**Figure Q2(b)**


- Q3 (a)** A voltage source,  $V_s = 20 \cos(2t)$  V and current source,  $I_s = 4 \cos(2t)$  A are applied for the circuit in **Figure Q3(a)**.

(i) Find the Thevenin equivalent circuits at terminals  $a-b$ .

(8 marks)

(ii) An impedance  $Z_L$  is placed across terminals  $a-b$ , find the maximum power that can be transferred to the load.

(4 marks)

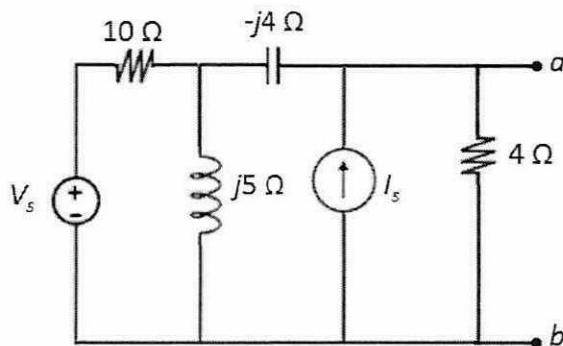

**Figure Q3 (a)**

- (b) For the power system in **Figure Q3(b)**,

(i) find the average power

(5 marks)

(ii) find the reactive power

(2 marks)


(iii) find the power factor

(2 marks)

(iv) find the parallel element required that will give a unity power factor when connected to the system.

(4 marks)

220 Vrms, 50 Hz

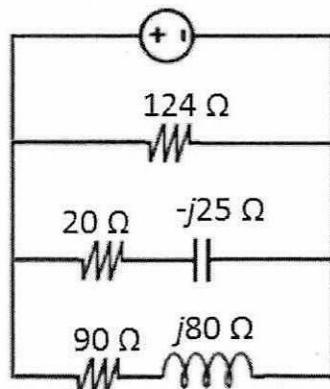

**Figure Q3(b)**

**Q4 (a)** Figure Q4(a) shows a two-port network circuit.

- (i) Calculate the admittance parameters of the circuit. (10 marks)
- (ii) If given that  $I_1 = 1 \text{ A}$  and  $I_2 = -0.5 \text{ A}$ , find  $V_1$  and  $V_2$ . (3 marks)

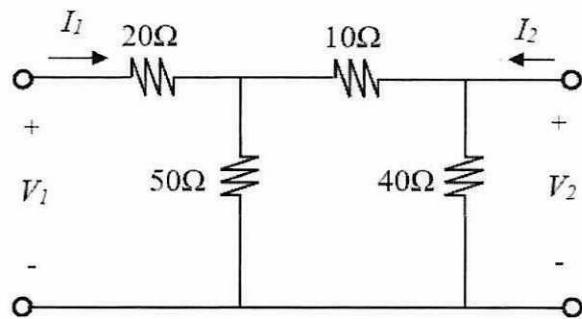


Figure Q4(a)

(b) For circuit in Figure Q4(b),

- (i) calculate  $I_1$ ,  $I_2$ ,  $V_1$  and  $V_2$ . (9 marks)
- (ii) determine the power dissipated in  $10 \Omega$  resistor. (3 marks)

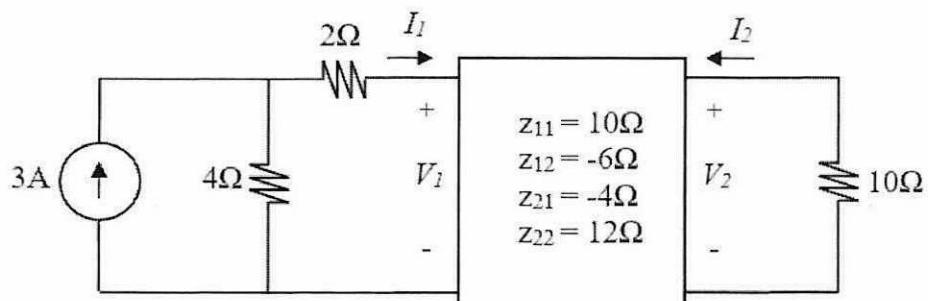


Figure Q4(b)

-END OF QUESTIONS -

## FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2022/2023  
 COURSE NAME : ELECTRIC CIRCUITS II

PROGRAMME CODE : BEJ  
 COURSE CODE : BEJ10403

## Mathematical Formula

$\sin(x) = -\sin(-x)$	$e^{jx} = \cos x + j \sin x$ (Euler's formula)
$\cos(-x) = \cos(x)$	$\cos x = \frac{e^{jx} + e^{-jx}}{2}$
$\tan(-x) = -\tan(x)$	$\sin x = \frac{e^{jx} - e^{-jx}}{2j}$
$\sin 2x + \cos 2x = 1$	
$\sin(2x) = 2 \sin x \cos x$	If $U = U(x)$ , $V = V(x)$ , and $a = \text{constant}$ ,
$\cos(2x) = \cos 2x - \sin 2x$	$\frac{d}{dx}(aU) = a \frac{dU}{dx}$
$\cos(2x) = 2 \cos^2 x - 1 = 1 - 2 \sin^2 x$	$\frac{d}{dx}(UV) = U \frac{dV}{dx} + V \frac{dU}{dx}$
$\sin(x \pm 90^\circ) = \pm \cos x$	$\frac{d}{dx}(aU^n) = naU^{n-1}$
$\cos(x \pm 90^\circ) = \mp \sin x$	$\frac{d}{dx}(a^U) = a^U \ln a \frac{dU}{dx}$
$\sin(x \pm 180^\circ) = \mp \sin x$	$\frac{d}{dx}(e^U) = e^U \frac{dU}{dx}$
$\cos(x \pm 180^\circ) = \mp \cos x$	$\frac{d}{dx}(\sin U) = \cos U \frac{dU}{dx}$
$\cos^2 x + \sin^2 x = 1$	$\frac{d}{dx}(\cos U) = -\sin U \frac{dU}{dx}$
$\sin(x \pm y) = \sin x \cos y \pm \cos x \sin y$	If $U = U(x)$ , $V = V(x)$ , and $a = \text{constant}$ ,
$\cos(x \pm y) = \cos x \cos y \mp \sin x \sin y$	$\int a dx = ax + C$
$\tan(x \pm y) = \frac{\tan x \pm \tan y}{1 \mp \tan x \tan y}$	$\int U dV = UV - \int V dU$
$2 \sin x \sin y = \cos(x - y) - \cos(x + y)$	$\int \frac{dU}{U} = \ln U + C$
$2 \sin x \cos y = \sin(x + y) + \sin(x - y)$	$\int \ln x dx = x \ln x - x + C$
$2 \cos x \cos y = \cos(x + y) + \cos(x - y)$	$\int \sin ax dx = -\frac{1}{a} \cos ax + C$
$\cos x \cos y = \frac{1}{2} [\cos(x + y) + \cos(x - y)]$	$\int \cos ax dx = \frac{1}{a} \sin ax + C$
$j^2 = -1$	
$z = x + jy = r(\cos \phi + j \sin \phi)$	
$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$	
$x(t) = (A_1 + A_2 t)e^{-\alpha t}$	
$x(t) = (A_1 \cos \omega_d t + A_2 \sin \omega_d t)e^{-\alpha t}$	
$a^2 + bx + c = 0$	
$x_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$	