



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2022/2023**

- COURSE NAME : POWER SYSTEMS
- COURSE CODE : BEJ 20603
- PROGRAMME CODE : BEJ
- EXAMINATION DATE : JULY/AUGUST 2023
- DURATION : 3 HOURS
- INSTRUCTION : 1. ANSWER ALL QUESTIONS.
2. THIS FINAL EXAMINATION IS CONDUCTED VIA **CLOSED BOOK**.
3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES DURING THE EXAMINATION CONDUCTED VIA CLOSED BOOK.

THIS QUESTION PAPER CONSISTS OF FIVE (5) PAGES

- Q1** (a) (i) Define electric power system. (2 marks)
- (ii) State **THREE (3)** main elements of an electric power system. (3 marks)
- (iii) State **THREE (3)** advantages of a high voltage transmission line power system. (3 marks)
- (iv) State **THREE (3)** types of electric loads. (3 marks)
- (b) (i) State **TWO (2)** of the renewable power plants. (2 marks)
- (ii) Draw and state **FOUR (4)** elements of a photovoltaic power system. (8 marks)
- (c) (i) List **TWO (2)** hydropower stations in peninsular Malaysia. (2 marks)
- (ii) List **TWO (2)** power stations in Sarawak, Malaysia. (2 marks)
- Q2** (a) A current source is expressed as:
$$i(t) = 15\cos(377t - 45^\circ) A$$
- (i) Find the rms value of the current. (2 marks)
- (ii) Find the period of the current. (2 marks)
- (iii) Find the phase value of the current. (1 mark)
- (b) An equivalent AC circuit is shown in **Figure Q2(b)** consist of a single-phase input voltage, a transmission line as Z_{AB} and a load as Z_{BC} . Given the input voltage $V_{in} = 240 V_{rms}$ at a frequency of 50 Hz.
- (i) Determine the current that flows in the transmission line. (5 marks)
- (ii) Determine the power factor at the source. (2 marks)

- (iii) Determine power losses at the transmission line. (3 marks)
- (iv) If a $50 \mu\text{F}$ capacitor is connected in parallel with the Z_{BC} load, calculate the new power losses in the transmission line and find the reduction of the losses. (10 marks)
- Q3** (a) A balanced three phase Y-connected source, is connected to a balanced three phase delta-connected load. If the phase sequence is positive or ABC-sequence,
- (i) Draw and label the circuit configuration. (3 marks)
- (ii) Calculate the phase current of the loads. (5 marks)
- (iii) Calculate the line currents. (4 marks)
- (b) A balanced Y-connected ABC-sequence source, $V_{AN} = 230V_{rms}$ is connected to a Y-connected unbalanced load; $Z_{AN} = 10 + j3 \Omega$, $Z_{BN} = 8 + j4 \Omega$, and $Z_{CN} = 5 + j2 \Omega$. Assume phase A as reference,
- (i) Find the phase voltage across each load. (3 marks)
- (ii) Calculate the line current and neutral current. (5 marks)
- (iii) Calculate the total complex power supply by the source. (5 marks)
- Q4** (a) Explain the formula for power factor calculation of a non-linear load system. (5 marks)
- (b) With the help of a power triangle diagram, explain the difference between lagging and leading power factor. (4 marks)
- (c) Describe the effect of low power factor to the rating and size of electrical machines. (3 marks)

- (d) A $230 V_{rms}$ 50 Hz source supplies a 4 kVA machine with power factor 0.8 leading parallel with a 25 kVA induction motor with power factor 0.7 lagging.
- (i) Determine the total apparent power of the system. (6 marks)
- (ii) Find the power factor of the system and draw the power diagram. (2 marks)
- (iii) Calculate the value of capacitor required to adjust the power factor to 0.95 lagging. (5 marks)

- END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER / SESSION : SEM II 2022/2023
COURSE NAME : POWER SYSTEMS

PROGRAMME CODE : BEJ
COURSE CODE : BEJ 20603

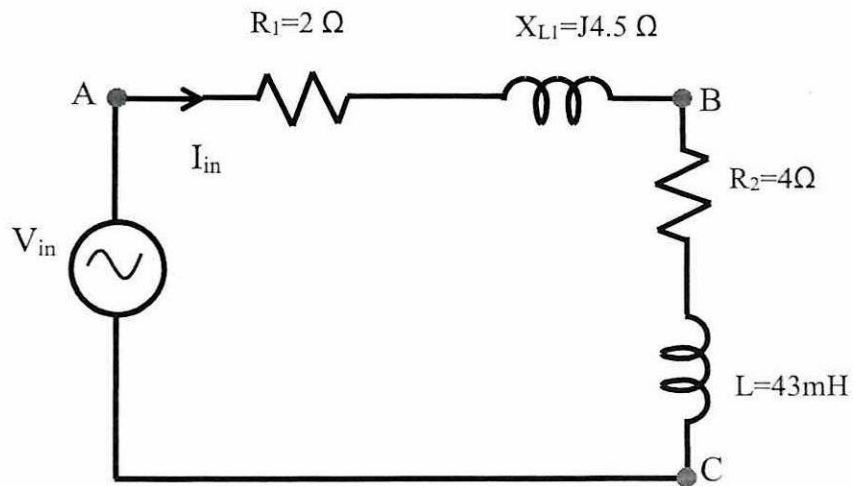


Figure Q2(b)

TERBUKA