

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2022/2023**

- COURSE NAME : ELECTRIC CIRCUIT 1
- COURSE CODE : BEV 10303
- PROGRAMME CODE : BEV
- EXAMINATION DATE : JULY/ AUGUST 2023
- DURATION : 3 HOURS
- INSTRUCTION :
1. ANSWER ALL QUESTIONS
 2. THIS FINAL EXAMINATION IS CONDUCTED VIA **CLOSED BOOK**.
 3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES DURING THE EXAMINATION CONDUCTED VIA CLOSED BOOK

THIS QUESTION PAPER CONSISTS OF **FIVE (5)** PAGES

TERBUKA

CONFIDENTIAL

- Q1** (a) Define the following terms (8 marks)
- (i) Ohm's law.
 - (ii) Branch.
 - (iii) Loop.
 - (iv) Node.
- (b) Analyze how many branches, nodes, and elements are in series and in parallel with the circuit (see **Figure Q1 (b)**). (4 marks)
- (c) Suppose it is more convenient to work with a Wye network in a place where the circuit contains a delta configuration. Show Delta to Wye conversion. (13 marks)
- Q2** (a) By using mesh analysis, solve to find the current I_0 in the circuit (see **Figure Q2(a)**). (13 marks)
- (b) By using nodal analysis, solve the nodal voltages in the circuit (see **Figure Q2(b)**). (12 marks)
- Q3** (a) Use the superposition theorem, to identify the current i in the circuit (see **Figure Q3 (a)**). (12 marks)
- (b) Solve the given circuit (see **Figure Q3 (b)**) for the Thevenin equivalent circuit, to the left of the terminals a-b. Then find the current through $R_L = 6 \Omega$, 16Ω , and 36Ω . (13 marks)
- Q4** (a) Define the instantaneous current. (4 marks)
- (b) Define the instantaneous voltage. (4 marks)
- (c) Recall instantaneous power $p(t)$. (3 marks)

- (d) Differentiate how resistive load and reactive load absorbing the power. (2 marks)
- (e) Identify the average power supplied by the source and the average power absorbed by the resistor (see **Figure Q4(e)**). (12 marks)

-END OF QUESTIONS –

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM II 2022/2023
 COURSE NAME : ELECTRIC CIRCUIT 1

PROGRAMME CODE : BEV
 COURSE CODE : BEV 10303

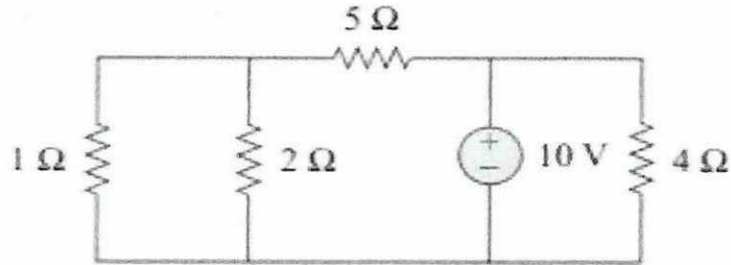


Figure Q1(b)

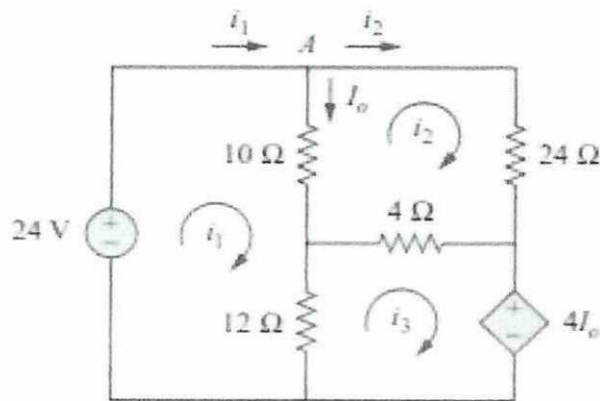


Figure Q2(a)

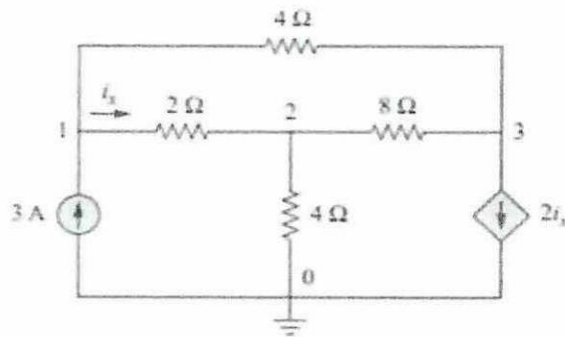


Figure Q2(b)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II 2022/2023
 COURSE NAME : ELECTRIC CIRCUIT 1

PROGRAMME CODE : BEV
 COURSE CODE : BEV 10303

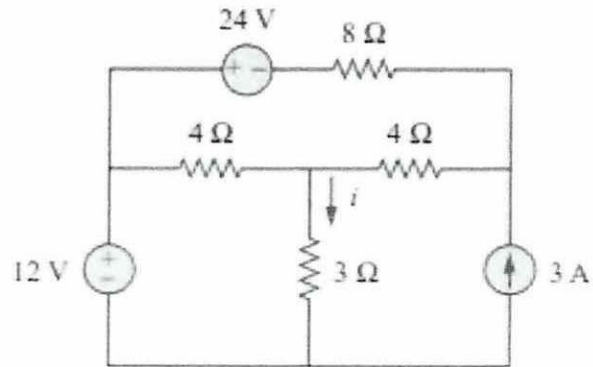


Figure Q3(a)

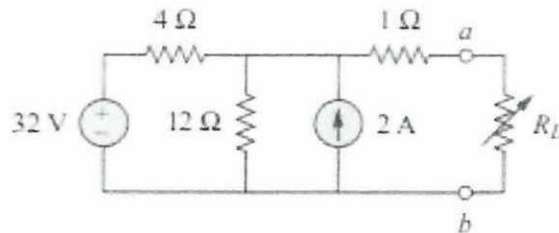


Figure Q3(b)

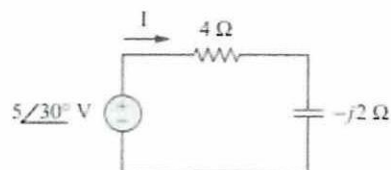


Figure Q4(e)