

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2014/2015**

COURSE NAME : ELECTRICAL MACHINES &
DRIVES
COURSE CODE : DAE 32303
PROGRAMME : 2 DAE
EXAMINATION DATE : JUNE 2015 / JULY 2015
DURATION : 2 ½ HOURS
INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS
ONLY

THIS QUESTION PAPER CONSISTS OF **SIX (6)** PAGES

CONFIDENTIAL

CONFIDENTIAL

- Q1**
- a) With the aid of an appropriate diagram, briefly describe the generation of Direct Current (DC) Signal in DC machines. (3 marks)
- b) Name **three (3)** types of DC motors and draw their schematic diagrams. (3 marks)
- c) A compound DC motor rated at 440 V, 10 HP, 2000 rpm has armature resistance 0.21Ω , series field resistance 0.5Ω and shunt field resistance 150Ω . The rotational losses are 220 W. The full load line current is 45 A.
- (i) Compute the developed mechanical power. (5 marks)
- (ii) Indicate the output power. (2 marks)
- (iii) Identify the load torque. (2 marks)
- (iv) Find the efficiency of the motor. (4 marks)
- d) A DC series generator delivers 150 kW at 11 kV to a load. The armature resistance is 25Ω and the field resistance is 60Ω .
- (i) Calculate the generated emf, E_g (3 marks)
- (ii) Identify the input power if the stray and friction losses are 350 W. (3 marks)
- Q2** The purpose of open circuit test and short circuit test is to determine the shunt and series branch parameter of a practical transformer.
- (a) Briefly explain with the aid of an appropriate circuit configuration, the open circuit test procedures. (3 marks)
- (b) Briefly describe with the aid of an appropriate circuit configuration, the short circuit test procedures. (3 marks)

CONFIDENTIAL

- (c) Short-circuit and open-circuit tests were performed on a 150kVA transformer, 50 Hz, rated at 220V/2400V, and the results are listed as follows:

$$\begin{array}{ll} V_{sc} = 44 \text{ V} & V_{oc} = 220 \text{ V} \\ I_{sc} = 43.57 \text{ A} & I_{oc} = 8 \text{ A} \\ P_{sc} = 480 \text{ W} & P_{oc} = 60 \text{ W} \end{array}$$

Construct the equivalent circuit with the necessary parameters of the transformer referred to the low voltage side.

(14 marks)

- (d) An ideal-transformer having 100 turns on the primary and 2250 turns on the secondary is connected to a 220 V, 50 Hz source. The load across the secondary draws a current of 3 A at a power factor of 0.78 lagging.

- (i) Calculate the effective value of the primary current. (2 marks)
- (ii) Indicate the primary current if the secondary current is 100 mA. (1 marks)
- (iii) Estimate the peak flux linked by the secondary winding. (2 marks)

- Q3** (a) State **two (2)** advantages and **two (2)** disadvantages of an Induction machines. (4 marks)

- (b) You have been requested to analyze the data for an induction motor in order to determine its performance. The following data are given to you at 440 V , 50 Hz , 6 poles, Y connected, rated at 100 hp, the equivalent parameter for the motor are which referred to the stator are given below;

$$\begin{array}{ll} R_s = 0.084 \Omega/\text{phase} & X_s = 0.20 \Omega/\text{phase} \\ R_R = 0.066 \Omega/\text{phase} & X_R = 0.165 \Omega/\text{phase} \\ R_C = \infty & X_m = 6.9 \Omega/\text{phase} \end{array}$$

Losses in the motor are identified as follows:

$$\begin{array}{ll} \text{Windage \& friction losses} & = 1.5 \text{ kW} \\ \text{Stray losses} & = 120 \text{ W} \\ \text{Core losses} & = 100 \text{ W} \end{array}$$

Using approximate and actual equivalent circuit with a slip of 0.05, determine the following;

- (i) Sketch a complete equivalent circuit. (2 marks)
- (ii) Calculate the line current. (4 marks)
- (iii) Estimate the stator copper loss. (2 marks)
- (iv) Indicate the air gap power. (3 marks)
- (v) Identify the developed power. (3 marks)
- (vi) Solve the induced torque (3 marks)
- (vii) Calculate the load torque (2 marks)
- (viii) Identify the efficiency of the motor. (2 marks)

Q4 (a) A 3-phase Y-connected synchronous generator supplies a load of 15 MW at power factor 0.85 lagging and the terminal voltage is 11 kV. The armature resistance is 0.2 ohm/phase and synchronous reactance of 0.76 ohm/phase.

- (i) Calculate the armature current (2 marks)
- (ii) Indicate the internal generated voltage (2 marks)
- (iii) Estimate the voltage regulation. (1 marks)
- (iv) Draw the phasor diagram. (2 marks)

b) A 2400 V, 60 kW, 50 Hz, 6 poles, delta-connected synchronous motor has a synchronous reactance of 4 Ω /phase and armature resistance of 2 Ω /phase. At full load, the efficiency is 92 %. Find the following requirements for this machine when it is operating at full load at rated power factor of 0.85 lagging.

CONFIDENTIAL

- (i) Sketch the phasor diagram to represent back emf, (2 marks)
- (ii) Calculate the supply voltage , E_A (3 marks)
- (iii) Indicate the armature current. (3 marks)
- (iv) Indicate the voltage regulation. (2 marks)
- (v) Estimate the input power (2 marks)
- (vi) Solve the developed mechanical power (4 marks)
- (vii) Sketch the power flow diagram (2 marks)

Q5 (a) Briefly describe the following aspect of a Stepper motor.

- (i) The physical construction of the motor (4 marks)
- (ii) The performance of the motor (4 marks)
- (iii) The characteristics of the motor (4 marks)

(b) State the **three (3)** main types of Stepper motor (3 marks)

(c) Describe in details any **one (1)** of the following motors by considering its design and its operating fundamentals.

- (i) Universal motor
- (ii) Servo motor
- (iii) Reluctance motor

(10 marks)

- Q6**
- (a) What is the main difference between DC motor and DC generator.
(2 marks)
 - (b) State **three (3)** advantages of DC motors
(3 marks)
 - (c) Illustrate the **two (2)** types of DC motor equivalent circuits.
(3 marks)
 - (d) Illustrate the **two (2)** types of DC generator equivalent circuits.
(3 marks)
 - (e) A separately excited dc motor turns at 1500 r/min when the armature is connected to a 240 V source. Calculate the armature voltage required so that the motor runs at :
 - (i) 2500 r/min
(2 marks)
 - (ii) 200 r/min
(2 marks)
 - (f) A three phase, Y connected synchronous generator is rated 120 kVA, 2.0 kV, 50 Hz, 0.85 pf lagging. Its synchronous inductance is 2.5 mH and effective resistance is 2.5 Ω .
 - (i) Solve the voltage regulation at this frequency.
(5 marks)
 - (ii) Solve the rated voltage and apparent power if the supply frequency is going to be twice.
(5 marks)

- END OF QUESTION -