



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2022/2023**

- COURSE NAME : ANALOG ELECTRONICS
- COURSE CODE : BEJ 10503 / BEV 10503
- PROGRAMME CODE : BEJ / BEV
- EXAMINATION DATE : JULY / AUGUST 2023
- DURATION : 3 HOURS
- INSTRUCTION
1. ANSWER ALL QUESTIONS
 2. THIS FINAL EXAMINATION IS CONDUCTED VIA **CLOSED BOOK**.
 3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES DURING THE EXAMINATION CONDUCTED VIA CLOSED BOOK

THIS QUESTION PAPER CONSISTS OF FIVE (5) PAGES

TERBUKA

- Q1** (a) (i) In your own words, define the intrinsic semiconductor and acceptor atoms. (2 marks)
- (ii) Differentiate between p-type semiconductors and n-type semiconductors. (4 marks)
- (iii) Show how to forward-bias a diode and draw the direction of the current flow. (2 marks)
- (b) The input voltage, $V_i(t) = 5\sin(\omega t)$ V, is applied to the circuit shown in **Figure Q1(b)**. Assume the diodes are ideal.
- (i) Calculate the output voltage, $V_o(t)$ during positive and negative cycles. Show all steps clearly. (9 marks)
- (ii) Sketch the output voltage, $V_o(t)$ with respect to the input voltage, $V_i(t)$. (4 marks)
- (c) For the circuit shown in **Figure Q1(c)**, assume that the diode is ideal and $V_{DC} = 2$ V.
- (i) Calculate the output voltage V_o and the capacitor voltage, V_c for the input shown. (8 marks)
- (ii) Sketch and label the output voltage, V_o waveform. (2 marks)
- Q2** A common emitter voltage divider bias amplifier circuit is depicted in **Figure Q2**. Given that $\beta = 150$, $V_{CC} = 20$ V, $V_{BE} = 0.7$ V, $R_1 = 15$ k Ω , $R_2 = 5$ k Ω , $R_C = 3$ k Ω and $R_E = 1.5$ k Ω .
- (a) By using approximate analysis, determine the operating points I_{BQ} , I_{CQ} , I_{EQ} , V_{CEQ} , V_B , and r_e . Show all the calculations. (13 marks)
- (b) Sketch and label clearly the AC equivalent circuit of **Figure Q2** using r_e model. Assume that $r_o = \infty$. (3 marks)
- (c) Based on **Q2(b)**, calculate the input impedance, Z_i , output impedance, Z_o and voltage gain, A_v . (9 marks)
- (d) Determine the current gain, A_i if $r_o = 50$ k Ω . (4 marks)

- Q3** A self-bias circuit configuration of a depletion n-channel MOSFET is shown in **Figure Q3**.
- (a) Find the operating points of the transistor, I_{DQ} and V_{GSQ} using a graphical method. (Draw the transfer characteristics and the network equation on the same graph paper).
(11 marks)
 - (b) Obtain V_{DSQ} .
(3 marks)
 - (c) Calculate the transconductance, g_m .
(2 marks)
 - (d) Sketch the AC small-signal equivalent circuit of **Figure Q3** with bypass source resistance, R_s .
(3 marks)
 - (e) Assuming the admittance equivalent circuit parameter $y_{os} = 20 \mu S$, calculate the input impedance, Z_i , output impedance, Z_o and voltage gain, A_v .
(8 marks)
- Q4**
- (a) Draw a basic Class B push-pull amplifier that uses two dc power supplies of $\pm 16 V$ and a load resistor of 20Ω .
(2 marks)
 - (b) If the output signal in **Q4(a)** has a peak value of $12 V$, determine:
 - (i) The efficiency.
(5 marks)
 - (ii) The dissipated power.
(2 marks)
 - (c) The output waveform in the Class B amplifier in **Q4(a)** will have crossover distortion. Illustrate and explain the crossover distortion and suggest a method to minimize or eliminate it.
(4 marks)

- END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER / SESSION : SEM II 2022/2023
 COURSE NAME : ANALOG ELECTRONICS

PROGRAMME CODE : BEJ/BEV
 COURSE CODE : BEJ10503/BEV10503

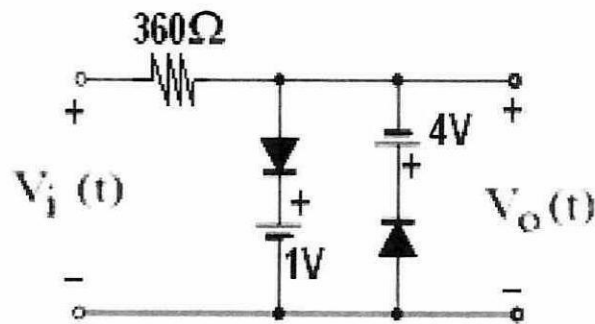


Figure Q1(b)

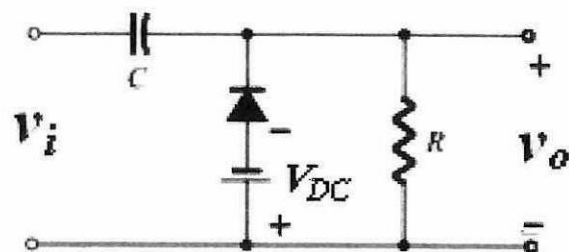
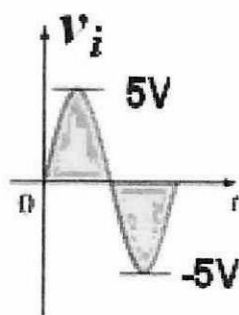


Figure Q1(c)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II 2022/2023
COURSE NAME : ANALOG ELECTRONICS

PROGRAMME CODE : BEJ/BEV
COURSE CODE : BEJ10503/BEV10503

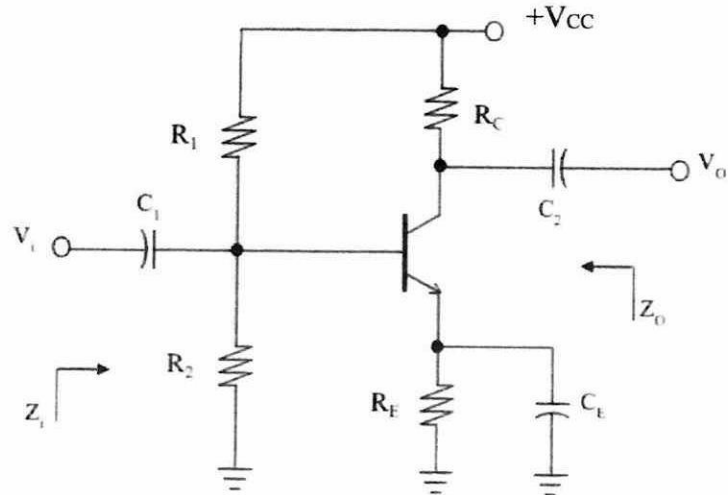


Figure Q2

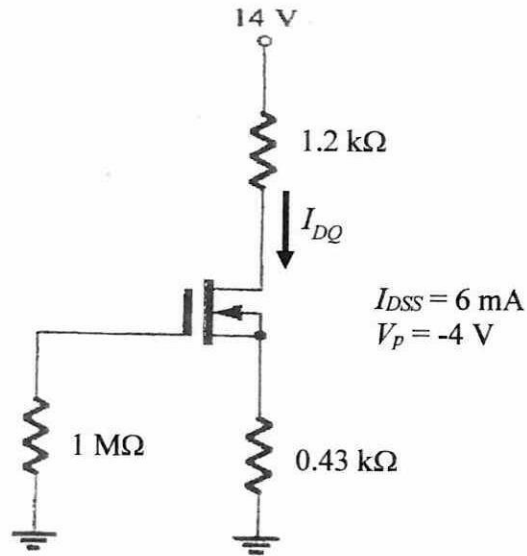


Figure Q3