

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2022/2023**

COURSE NAME : ELECTRIC CIRCUITS II

COURSE CODE : BEJ 10403

PROGRAMME CODE : BEJ

EXAMINATION DATE : JULY/ AUGUST 2023

DURATION : 3 HOURS

INSTRUCTION :

1. ANSWER ALL QUESTIONS.
2. THIS FINAL EXAMINATION IS CONDUCTED VIA **CLOSED BOOK**.
3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES DURING THE EXAMINATION CONDUCTED VIA CLOSED BOOK.

THIS QUESTION PAPER CONSISTS OF **SEVEN (7)** PAGES

TERBUKA

CONFIDENTIAL

- Q1** (a) For the circuit in **Figure Q1(a)**, assume the circuit is in steady state at $t = 0^-$, before the switch is moved position **b** at $t = 0$ s. Based on the circuit, solve the expression $V(t)$ for $t > 0$ s. (10 marks)
- (b) Referring to the circuit in **Figure Q1(b)**,
- (i) Find the value of $v(0)$ and $dv(0)/dt$. (5 marks)
 - (ii) Calculate the roots of the characteristics of the circuit. State the response type of the circuit. (5 marks)
 - (iii) Determine $v(t)$ for $t > 0$. (5 marks)
- Q2** (a) Given a circuit in **Figure Q2(a)**.
- (i) Determine and draw the equivalent circuit in frequency domain. (3 marks)
 - (ii) Determine the value of voltage, V and currents, i_1 and i_2 . (6 marks)
 - (iii) Draw a phasor diagram to illustrate all currents and voltages for the circuit. (2 marks)
- (b) Based on the circuit shown in **Figure Q2(b)**,
- (i) Calculate the total impedance, Z_{eq} seen from the input terminal. (5 marks)
 - (ii) Analyze the output voltage, V_o when the input is $120\angle 30^\circ$ V. (7 marks)
 - (iii) From your answer in part **Q2(b)(ii)**, identify whether the phase shift is leading or lagging. (2 marks)
- Q3** (a) For the circuit shown in **Figure Q3(a)**, Calculate:
- (i) The average power delivered by the source. (2 marks)
 - (ii) The apparent power. (2 marks)
 - (iii) The reactive power. (1 mark)

- (b) Based on the waveform in **Figure Q3(b)**,
- (i) Calculate the effective value of the current waveform. (5 marks)
 - (ii) Calculate the average power delivered to a $12\ \Omega$ resistor when the current runs through the resistor. (2 marks)
- (c) An electrical hair dryer has the following specifications:
- Line voltage: 120 V rms
 - Line frequency: 60 Hz
 - Power: 600 W
 - Power factor: 0.92 (lagging)
- (i) Calculate the rms-value current (I_{rms}) drawn by the dryer. (7 marks)
 - (ii) Find the value of capacitance that must be connected across the dryer to raise the power factor to 0.95. (6 marks)


- Q4** (a) A two-port network is an electrical network with two separate ports for input and output. Compare between one-port network and two-port network by drawing those two networks respectively. (3 marks)
- (b) For circuit in **Figure Q4(b)**,
- (i) Calculate I_1, I_2, V_1 and V_2 . (10 marks)
 - (ii) Determine the power dissipated in the $10\ \Omega$ resistor. (4 marks)
- (c) Hybrid parameters (h-parameter) are very useful for describing electronic devices such as transistors.
- (i) State all FOUR (4) values of h-parameters available. (2 marks)
 - (ii) Determine the h-parameters for the circuit in **Figure Q4(c)(ii)**. (6 marks)

-END OF QUESTIONS -


FINAL EXAMINATION

SEMESTER / SESSION : SEM II 2022/2023
COURSE NAME : ELECTRIC CIRCUITS II

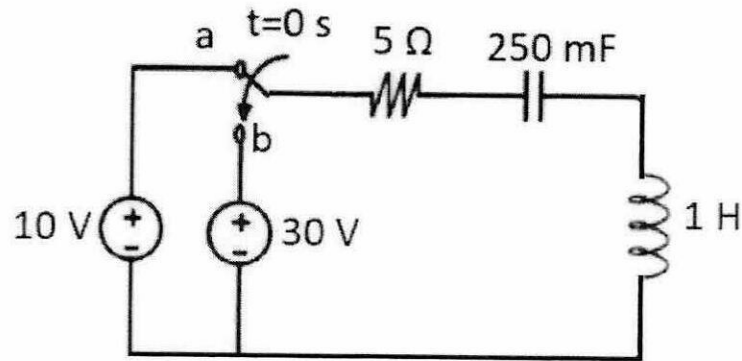PROGRAMME CODE : BEJ
COURSE CODE : BEJ 10403



FigureQ1(a)

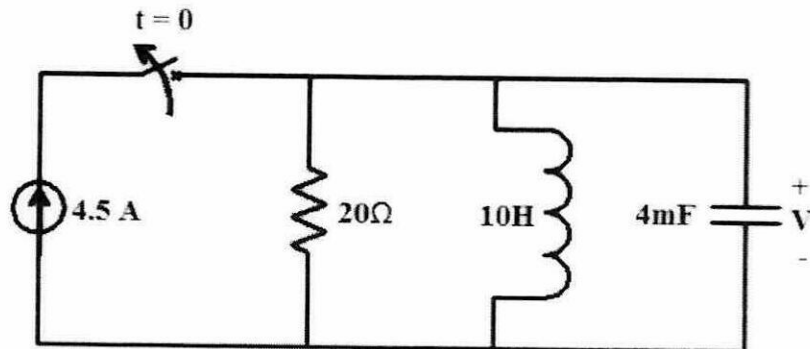

FigureQ1(b)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM II 2022/2023
 COURSE NAME : ELECTRIC CIRCUITS II

PROGRAMME CODE : BEJ
 COURSE CODE : BEJ 10403

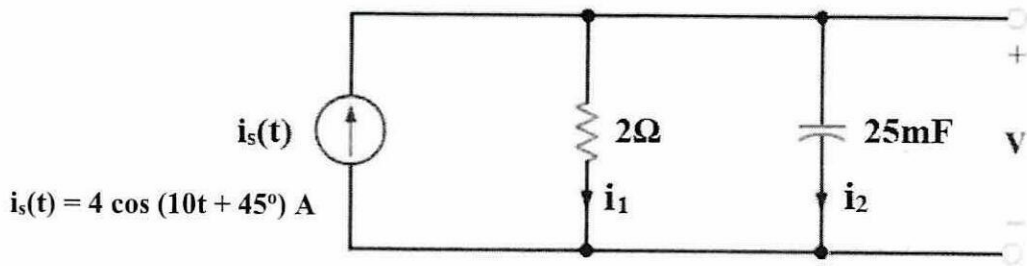


Figure Q2(a)

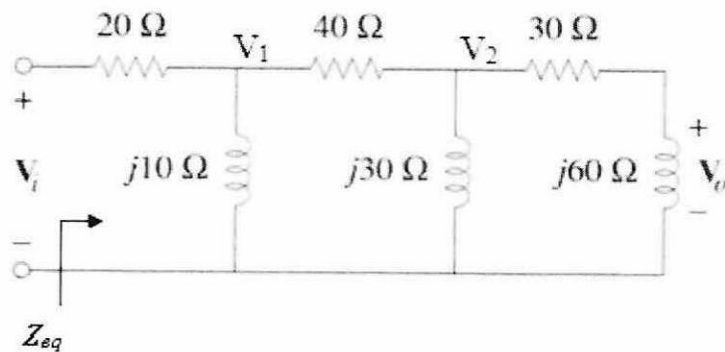


Figure Q2(b)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II 2022/2023
COURSE NAME : ELECTRIC CIRCUITS II

PROGRAMME CODE : BEJ
COURSE CODE : BEJ 10403

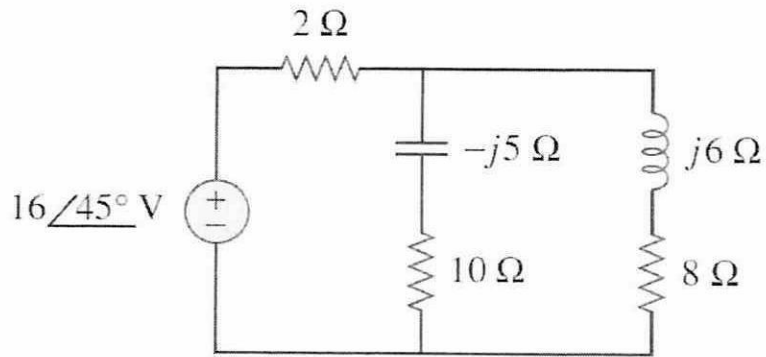


Figure Q3(a)

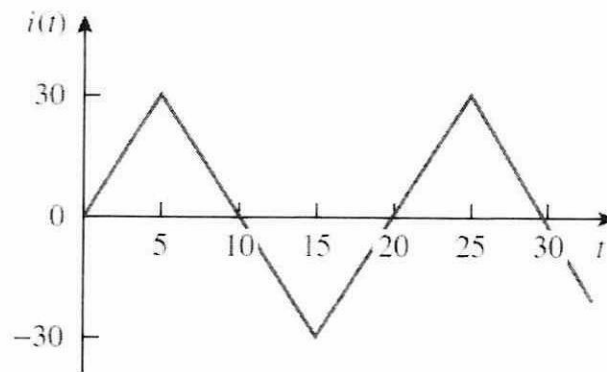


Figure Q3(b)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II 2022/2023
 COURSE NAME : ELECTRIC CIRCUITS II

PROGRAMME CODE : BEJ
 COURSE CODE : BEJ 10403

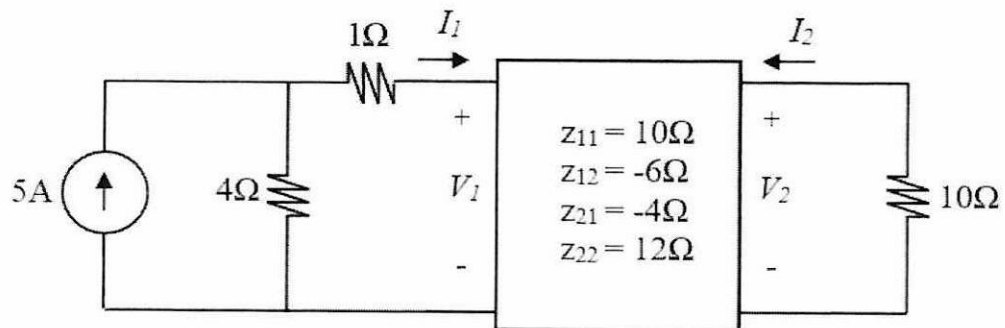


Figure Q4(b)

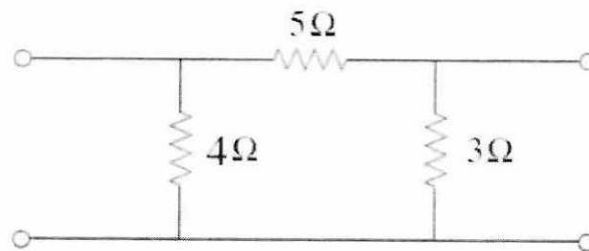


Figure Q4(c)(ii)