

**CONFIDENTIAL**



**UTHM**  
Universiti Tun Hussein Onn Malaysia

**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESSION 2022/2023**

COURSE NAME : ELECTRIC AND ELECTRONIC TECHNOLOGY

COURSE CODE : BDA 14303

PROGRAMME CODE : BDD

EXAMINATION DATE : JULY/AUGUST 2023

DURATION : 3 HOURS

INSTRUCTION : 1. PART A: ANSWER **ONE(1)** QUESTION **ONLY**.  
PART B: ANSWER **ALL** QUESTIONS.  
2. THIS FINAL EXAMINATION IS CONDUCTED VIA **CLOSED BOOK**.  
3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES DURING THE EXAMINATION CONDUCTED VIA CLOSED BOOK.

THIS QUESTION PAPER CONSISTS OF **TEN (10)** PAGES

**TERBUKA**

**CONFIDENTIAL**

## PART A

- Q1** (a) Nodal analysis is a technique to find currents and voltage between nodes in a circuit. Kindly explain the steps to conduct nodal analysis. (4 marks)
- (b) Calculate the value of  $V_1$ ,  $V_2$  and power dissipated in the  $8\Omega$  resistor as shown in **Figure Q1(b)** using nodal analysis method. (8 marks)
- (c) Given a circuit in **Figure Q1(c)**, using Thevenin Theorem to analyse  $V_{th}$ ,  $R_{th}$  at AB point. Then, determine the value of current  $I_{R4}$ . (13 marks)
- Q2** (a) With the assistance of a diagram, explain what is Norton Theorem?. (5 marks)
- (b) Find the Norton equivalent with respect to terminals a-b in the circuit shown in **Figure Q2(b)**. (10 marks)
- (c) As shown in **Figure Q2(c)**, use mesh analysis to determine  $I_b$  and the current through resistor of  $50\Omega$ . (10 marks)

## PART B

- Q3** (a) Find the equivalent inductance of the circuit at **Figure Q3(a)**, in which,  $L1 = L2 = 10\text{mH}$ ,  $L3 = L4 = 20\text{mH}$ , and  $L5 = 5\text{mH}$ . (8 marks)
- (b) Find the equivalent capacitance of the circuit at **Figure Q3(b)**. (7 marks)
- (c) Obtain the energy stored in the capacitor  $C1$  and the inductor  $L1$  of circuit showed in **Figure Q3(c)** when  $V_s = 6\text{V}$ . (10 marks)

**Q4** A series RLC circuit containing a resistance of  $15\Omega$ , an inductance of  $0.2\text{H}$  and a capacitor of  $50\mu\text{F}$  are connected in series across alternative power supply,  $V_s = 100\sin(50\pi t)$ .

- (a) Calculate
- (i) the frequency of the power supply. (2 marks)
  - (ii) the total circuit impedance. (6 marks)
  - (iii) the total effective current,  $I_{\text{rms}}$ . (4 marks)
  - (iv) the power factor. (3 marks)
- (b) Sketch the voltage phasor diagram. (8 marks)
- (c) Explain the relationship between the total current and the voltage supply. (2 marks)

**Q5** (a) (i) Compare the difference between AC Motor and DC Motor. (5 marks)

- (ii) **Figure Q5(a)** shows a transformer. The primary coil of transformer has 8000 turns is connected to the 240 V mains supply and has current of 0.050 A. The secondary coil supplies 6.0 V to a lamp. Calculate the number of turns in the secondary coil, output current and power from the transformer to the lamp. (5 marks)

(b) Explain briefly **1 (ONE)** advantage and **1 (ONE)** limitation of digital system compared to analog system. (4 marks)

(c) Analyze the logic circuit in **Figure Q5(c)** and obtain:

- (i) The Boolean expression for X (3 marks)
- (ii) The truth table for the logic circuit (8 marks)

-END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2022/2023  
COURSE NAME: ELECTRIC AND ELECTRONIC TECHNOLOGY

PROGRAMME CODE : BDD  
COURSE CODE : BDA 14303

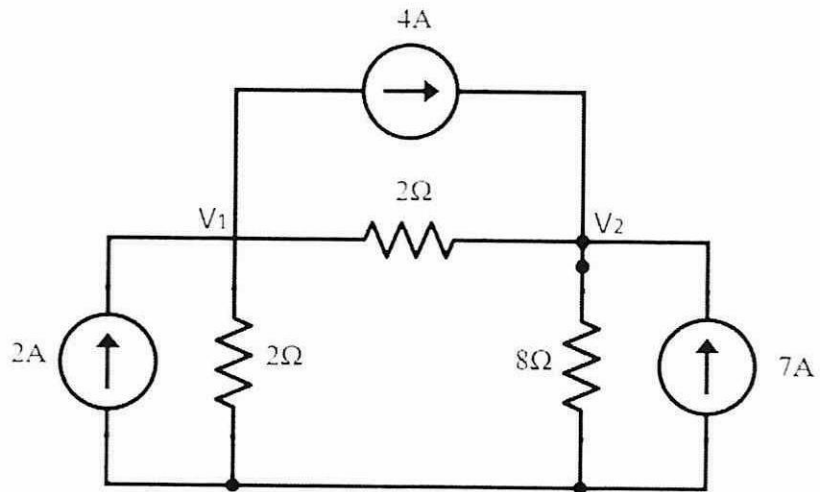


Figure Q1(b)


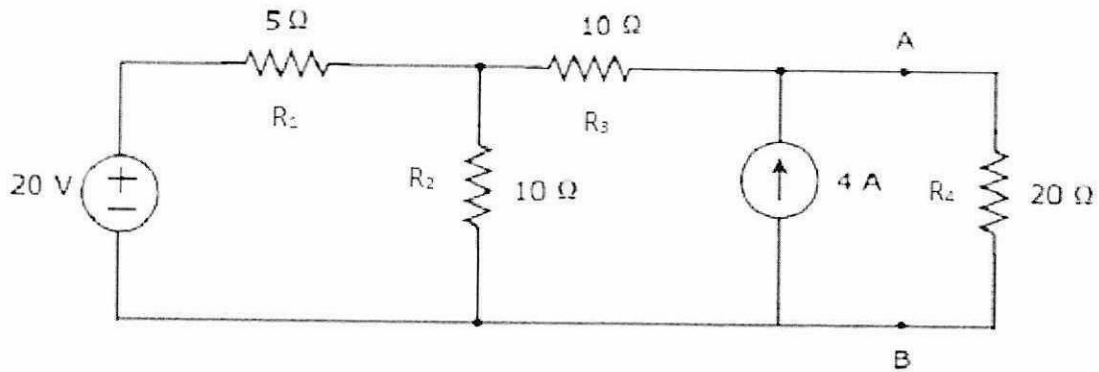


Figure Q1(c)


**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2022/2023  
COURSE NAME: ELECTRIC AND ELECTRONIC TECHNOLOGY

PROGRAMME CODE : BDD  
COURSE CODE : BDA 14303

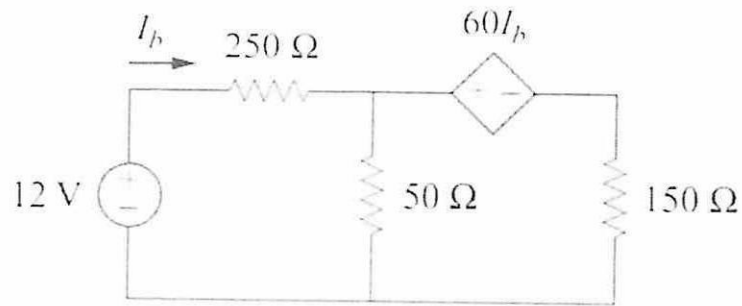

**Figure Q2(b)**

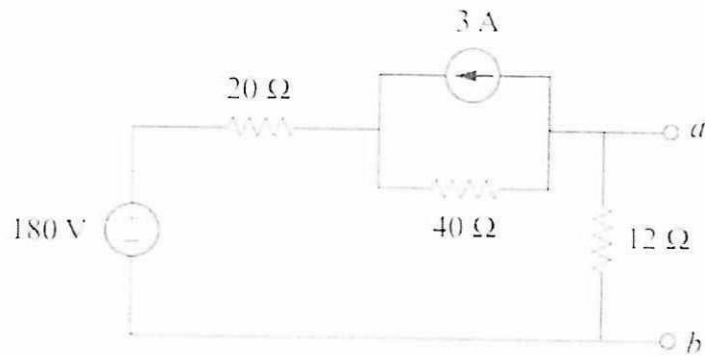

**Figure Q2(c)**

**TERBUKA**



FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2022/2023  
COURSE NAME: ELECTRIC AND ELECTRONIC TECHNOLOGY

PROGRAMME CODE : BDD  
COURSE CODE : BDA 14303

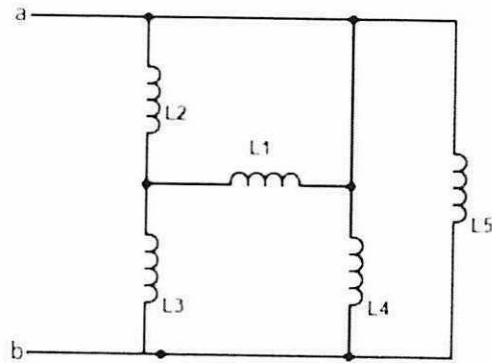


Figure Q3(a)

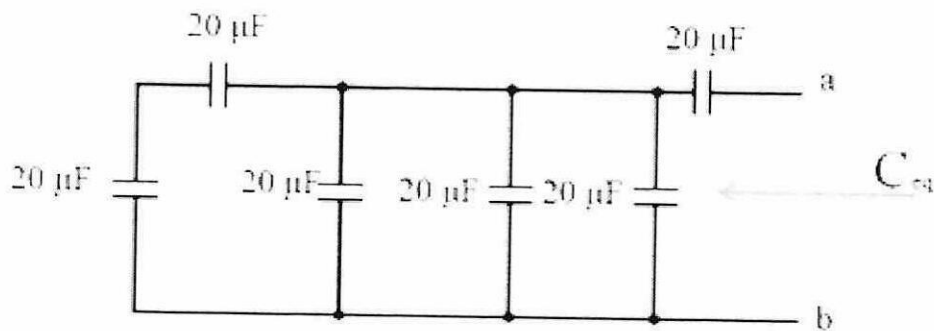


Figure Q3(b)

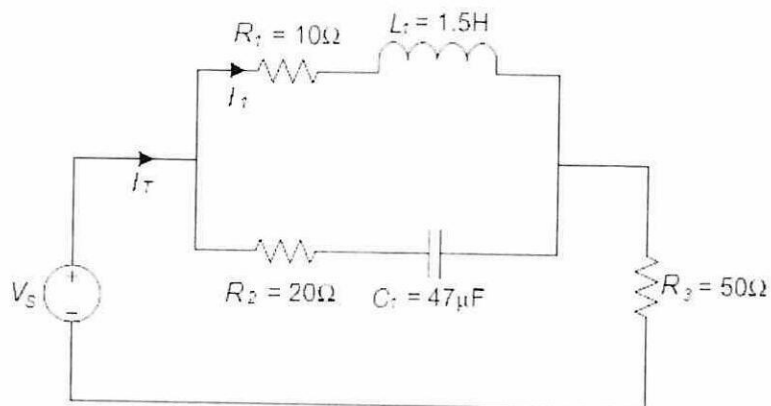


Figure Q3(c)

**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2022/2023  
COURSE NAME: ELECTRIC AND ELECTRONIC TECHNOLOGY

PROGRAMME CODE : BDD  
COURSE CODE : BDA 14303

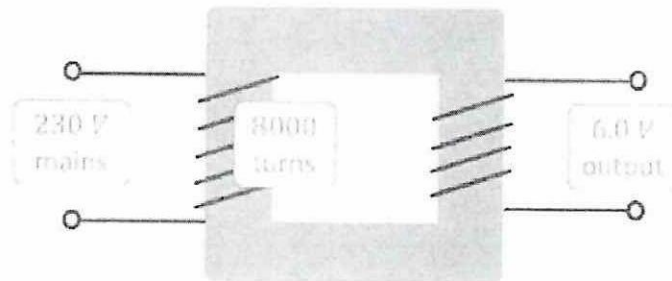


Figure Q5(a)

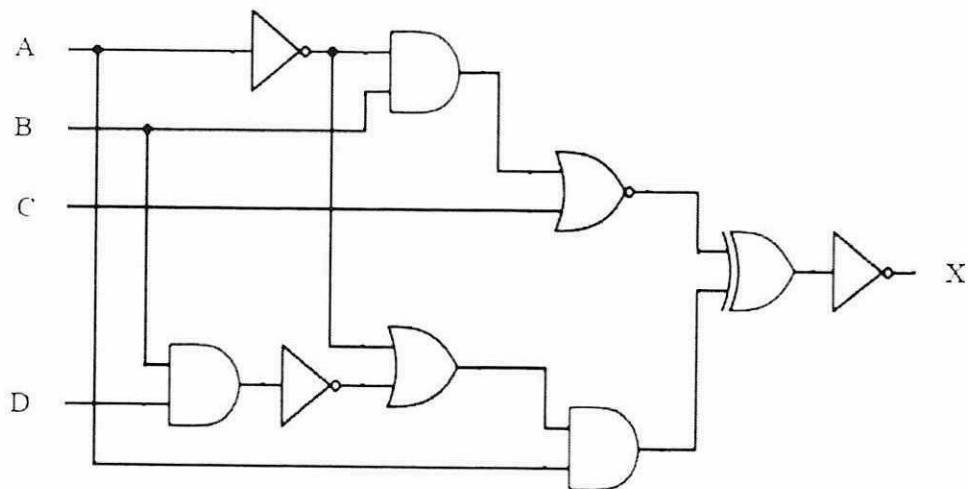


Figure Q5(c)

**TERBUKA**

**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2022/2023  
 COURSE NAME: ELECTRIC AND ELECTRONIC TECHNOLOGY

PROGRAMME CODE : BDD  
 COURSE CODE : BDA 14303

**LIST OF FORMULA**

**OHMS LAW**

$$V = IR$$

**JOULE'S LAW**


$$P = IV$$

**KIRCHHOFF LAW**

$$\sum_{k=1}^n i_k = 0$$

$$\sum_{v=1}^n v_k = 0$$

**WYE-DELTA TRANSFORMATION**

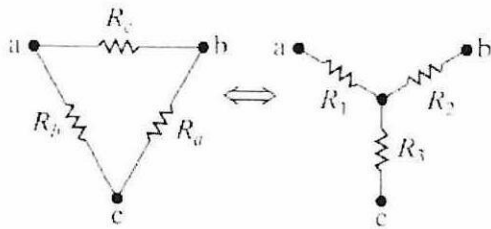

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

**SOURCE TRANSFORMATION**

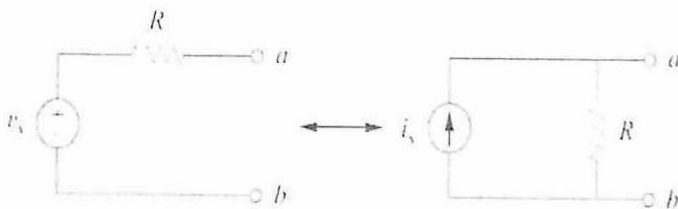

$$V_S = I_s R$$

**TERBUKA**



**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2022/2023  
 COURSE NAME: ELECTRIC AND ELECTRONIC TECHNOLOGY

PROGRAMME CODE : BDD  
 COURSE CODE : BDA 14303

**THEVENIN AND NORTON EQUIVALENT CIRCUIT**

$$R_{TH} = R_N$$

$$I_N = \frac{V_{TH}}{R_{TH}}$$


$$P = i^2 R_L = \left( \frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

When  $R_L \neq R_{TH}$

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}}$$

When  $R_L = R_{TH}$

**MAXIMUM POWER TRANSFER**

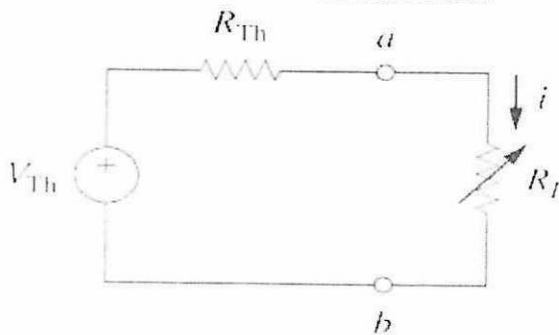

$$P = i^2 R_L = \left( \frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

**CAPACITOR AND INDUCTOR**

$$C = \frac{\epsilon A}{d}$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt + v(t_0)$$

$$i = C \frac{dv}{dt}$$

$$w = \frac{1}{2} C v^2$$

$$L = \frac{N^2 \mu A}{l}$$

$$v = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

$$w = \frac{1}{2} L i^2$$

$$\tau = RC$$

$$\tau = \frac{L}{R}$$

**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2022/2023  
 COURSE NAME: ELECTRIC AND ELECTRONIC TECHNOLOGY

PROGRAMME CODE : BDD  
 COURSE CODE : BDA 14303

**ALTERNATING CURRENT POWER CALCULATION**

$$P(t) = v(t)i(t)$$

$$P = \frac{1}{2} \operatorname{Re}[VI^*] = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$i_{RMS} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

$$P_{RMS} = I_{RMS}^2 R = \frac{V_{RMS}^2}{R}$$

**TRANSFORMERS**

$$\frac{V_P}{V_S} = \frac{N_P}{N_S}$$

**LOGIC GATES**

Name	NOT	AND	NAND	OR	NOR	XOR	XNOR																																																																																																
Alg. Expr.	$\bar{A}$	$AB$	$\overline{AB}$	$A+B$	$\overline{A+B}$	$A \oplus B$	$\overline{A \oplus B}$																																																																																																
Symbol																																																																																																							
Truth Table	<table border="1"> <tr><td>A</td><td>X</td></tr> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </table>	A	X	0	1	1	0	<table border="1"> <tr><td>B</td><td>A</td><td>X</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	B	A	X	0	0	0	0	1	0	1	0	0	1	1	1	<table border="1"> <tr><td>B</td><td>A</td><td>X</td></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	B	A	X	0	0	1	0	1	1	1	0	1	1	1	0	<table border="1"> <tr><td>B</td><td>A</td><td>X</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	B	A	X	0	0	0	0	1	1	1	0	1	1	1	1	<table border="1"> <tr><td>B</td><td>A</td><td>X</td></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	B	A	X	0	0	1	0	1	0	1	0	0	1	1	0	<table border="1"> <tr><td>B</td><td>A</td><td>X</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	B	A	X	0	0	0	0	1	1	1	0	1	1	1	0	<table border="1"> <tr><td>B</td><td>A</td><td>X</td></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	B	A	X	0	0	1	0	1	0	1	0	0	1	1	1
A	X																																																																																																						
0	1																																																																																																						
1	0																																																																																																						
B	A	X																																																																																																					
0	0	0																																																																																																					
0	1	0																																																																																																					
1	0	0																																																																																																					
1	1	1																																																																																																					
B	A	X																																																																																																					
0	0	1																																																																																																					
0	1	1																																																																																																					
1	0	1																																																																																																					
1	1	0																																																																																																					
B	A	X																																																																																																					
0	0	0																																																																																																					
0	1	1																																																																																																					
1	0	1																																																																																																					
1	1	1																																																																																																					
B	A	X																																																																																																					
0	0	1																																																																																																					
0	1	0																																																																																																					
1	0	0																																																																																																					
1	1	0																																																																																																					
B	A	X																																																																																																					
0	0	0																																																																																																					
0	1	1																																																																																																					
1	0	1																																																																																																					
1	1	0																																																																																																					
B	A	X																																																																																																					
0	0	1																																																																																																					
0	1	0																																																																																																					
1	0	0																																																																																																					
1	1	1																																																																																																					

**TERBUKA**