

**CONFIDENTIAL**



## **UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

### **FINAL EXAMINATION SEMESTER I SESSION 2023/2024**

COURSE NAME : CIRCUIT THEORY

COURSE CODE : DAE 11103

PROGRAMME CODE : DAE

EXAMINATION DATE : JANUARY/FEBRUARY 2024

DURATION : 3 HOURS

INSTRUCTION :  
1. ANSWER ALL QUESTIONS  
2. THIS FINAL EXAMINATION IS CONDUCTED VIA **CLOSED BOOK**.  
3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES DURING THE EXAMINATION CONDUCTED VIA CLOSED BOOK

THIS QUESTION PAPER CONSISTS OF **10** PAGES

**CONFIDENTIAL**

**TERBUKA**

**Q1** (a) For the circuit shown in **Figure Q1(a)**, compute the total resistance  $R_T$  with terminals  $a$  and  $b$  being:

(i) Open-circuited. (3 marks)

(ii) Short-circuited. (3 marks)

(b) Apply nodal analysis for the circuit with supernode condition in **Figure Q1(b)**.

(i) Write the support equation. (2 marks)

(ii) Determine the supernode equation. (4 marks)

(iii) Compute  $V$ . (6 marks)

(iv) Compute  $i$ . (2 marks)

**Q2** (a) Use the mesh analysis for the circuit in **Figure Q2(a)**.

(i) Write the mesh equations for each loop. (3 marks)

(ii) Determine the branch current controlling the dependent voltage source. (2 marks)

(iii) Compute the current in the  $4 \Omega$  resistor. (7 marks)

(iv) Compute the power dissipated in the  $4 \Omega$  resistor. (2 marks)

(b) (i) Explain the superposition theorem. (4 marks)

(ii) Justify why the superposition theorem can be applied to passive direct current (DC) circuits. (2 marks)

**TERBUKA**

- Q3** (a) Compute the maximum power delivered to the resistor  $R$  in **Figure Q3(a)**.  
(8 marks)
- (b) For a  $200 \mu\text{F}$  capacitor, the voltage is shown in **Figure Q3(b)**.
- (i) Calculate the current.  
(8 marks)
  - (ii) Sketch the current.  
(4 marks)
- Q4** (a) At  $t = 3 \text{ s}$ , the current through a  $10-\text{mH}$  inductor is  $6e^{-t/2} \text{ A}$ . Find:
- (i) Voltage.  
(4 marks)
  - (ii) Power.  
(4 marks)
- (b) For  $t > 0$  of the free-source RC circuit in **Figure Q4(b)**, if  $V_c(0) = 15 \text{ V}$ , compute:
- (i)  $V_c$   
(6 marks)
  - (ii)  $V_x$   
(3 marks)
  - (iii)  $i_x$   
(3 marks)

**TERBUKA**

**Q5** (a) The circuit in **Figure Q5(a)** is connected to 20 A source for a long time. At  $t = 0$ , the switch is opened. For  $t > 0$ , compute:

- (i)  $i_L(t)$  (5 marks)
- (ii)  $i_o(t)$  (2 marks)
- (iii)  $v_o(t)$  (2 marks)
- (iv) Power dissipated in 10  $\Omega$  resistor. (2 marks)
- (v) Energy stored in 2 H inductor. (2 marks)



(b) For the following sinusoid, find:



$$v(t) = 12 \cos(50t + 10^\circ)$$



- (i) Amplitude. (1 mark)
- (ii) Phase. (1 mark)
- (iii) Angular frequency. (1 mark)
- (iv) Period. (1 mark)
- (v) Frequency. (2 marks)
- (v) Frequency. (2 marks)


**END OF QUESTIONS**

**TERBUKA**

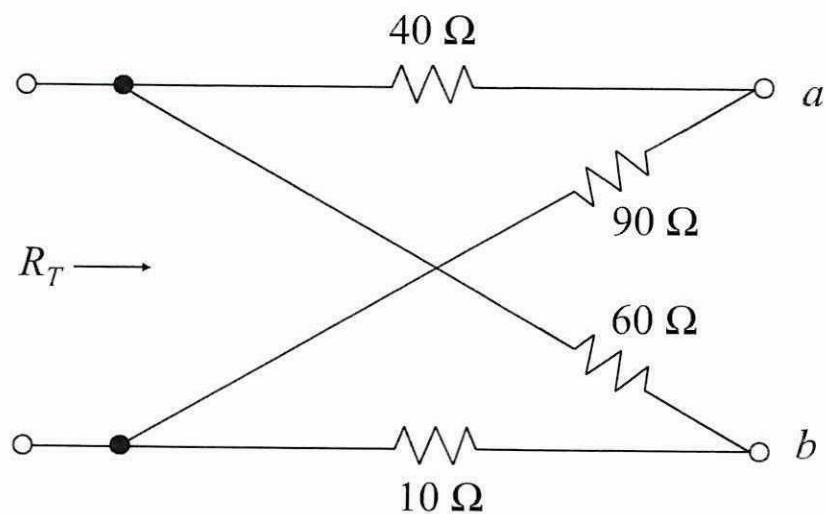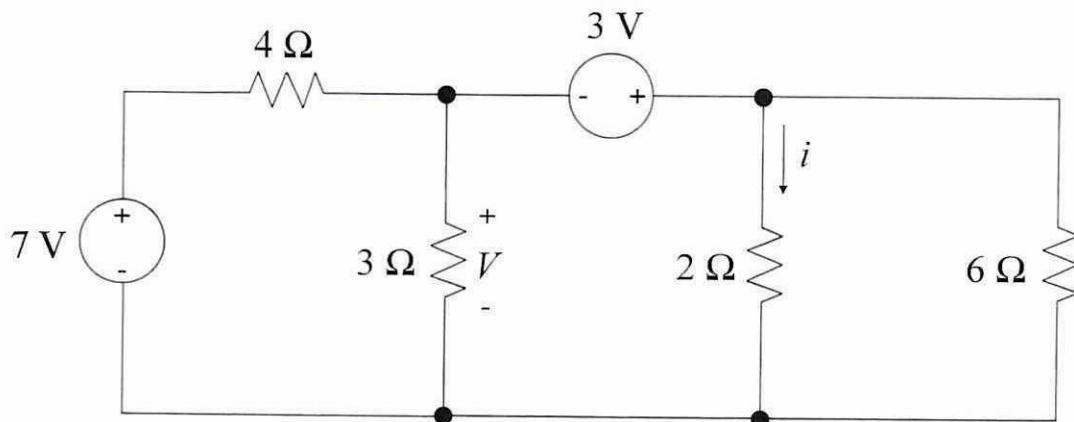**FINAL EXAMINATION**SEMESTER / SESSION : SEM I / 2023/2024  
COURSE NAME : CIRCUIT THEORYPROGRAMME CODE : DAE  
COURSE CODE : DAE 11103**Figure Q1(a)****Figure Q1(b)****TERBUKA**

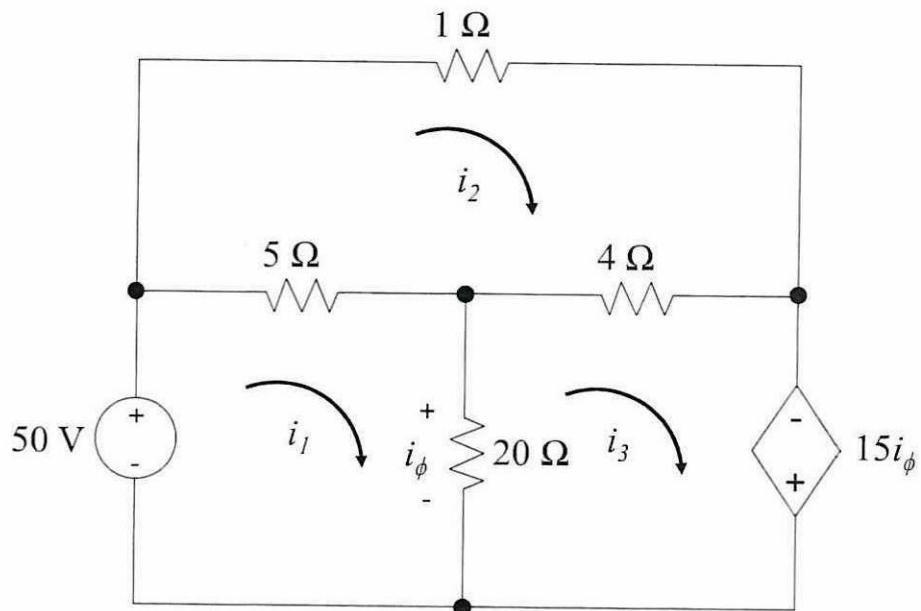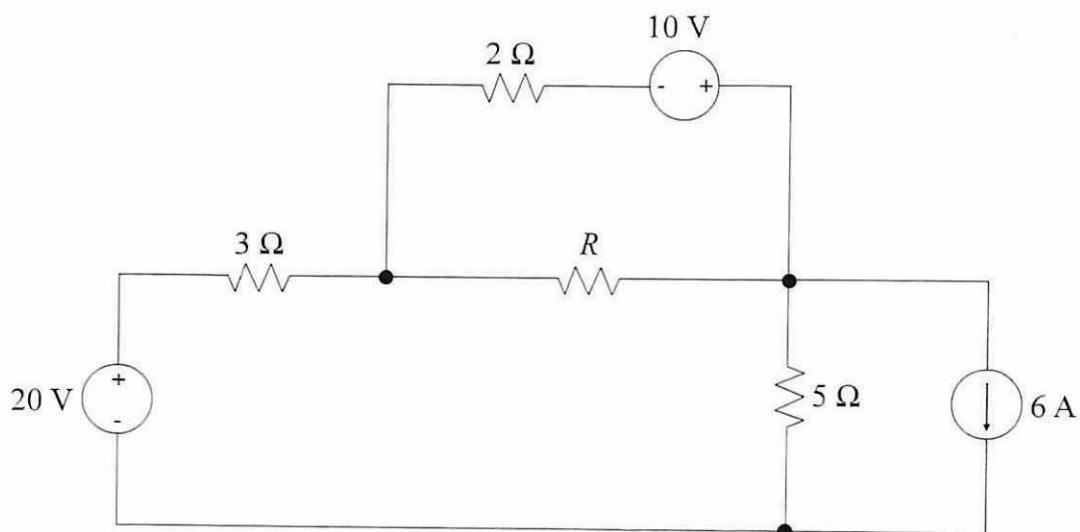**FINAL EXAMINATION**SEMESTER / SESSION : SEM I / 2023/2024  
COURSE NAME : CIRCUIT THEORYPROGRAMME CODE : DAE  
COURSE CODE : DAE 11103**Figure Q2(a)****Figure Q3(a)**

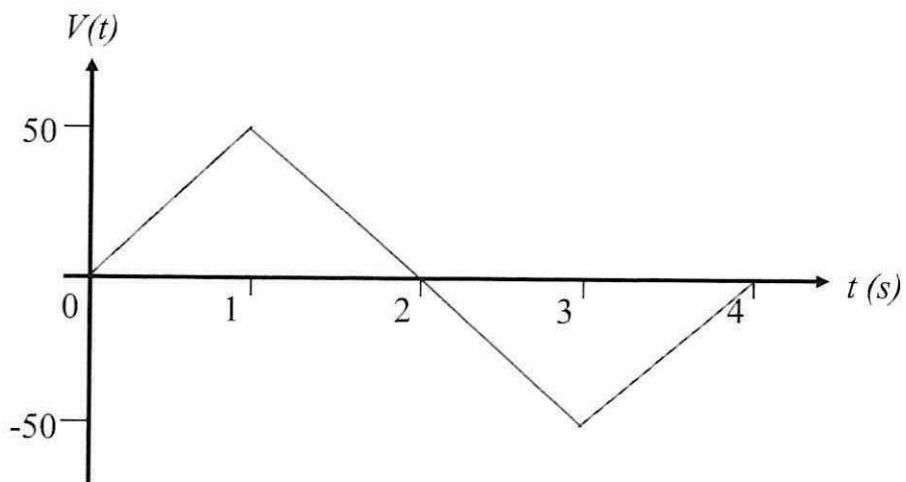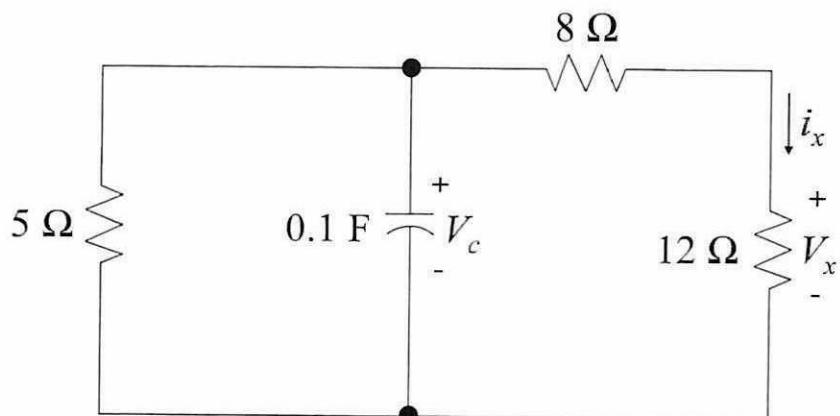**FINAL EXAMINATION**SEMESTER / SESSION : SEM I / 2023/2024  
COURSE NAME : CIRCUIT THEORYPROGRAMME CODE : DAE  
COURSE CODE : DAE 11103**Figure Q3(b)****Figure Q4(b)****TERBUKA**

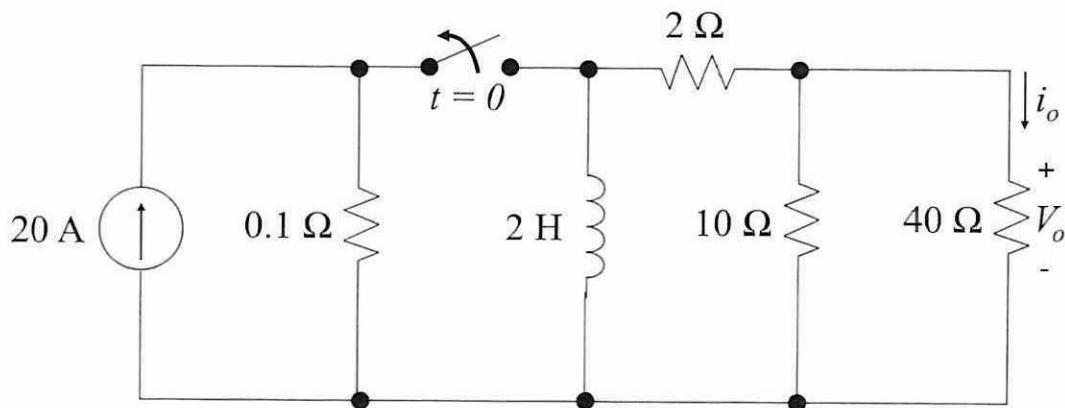**FINAL EXAMINATION**SEMESTER / SESSION : SEM I / 2023/2024  
COURSE NAME : CIRCUIT THEORYPROGRAMME CODE : DAE  
COURSE CODE : DAE 11103**Figure Q5(a)****TERBUKA**

## FINAL EXAMINATION



SEMESTER / SESSION : SEM I / 2023/2024  
 COURSE NAME : CIRCUIT THEORY

PROGRAMME CODE : DAE  
 COURSE CODE : DAE 11103
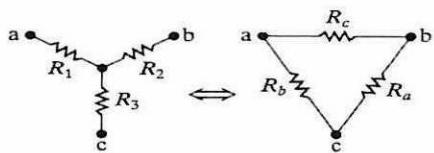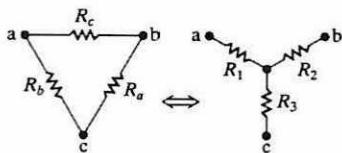
## List of Formulae

$$i = \frac{dq}{dt} \quad q = \int_{t_o}^t idt \quad v_{ab} = \frac{dw}{dq} \quad p = Vi = \frac{dw}{dt}$$

$$R = \rho \frac{l}{A} \quad G = \frac{1}{R} \quad \sum_{n=1}^N i_n = 0 \quad \sum_{n=1}^N V_n = 0$$



$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_1 = R_a + R_c + \frac{R_a R_c}{R_b}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_2 = R_a + R_b + \frac{R_a R_b}{R_c}$$

$$R_c = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

$$R_3 = R_b + R_c + \frac{R_b R_c}{R_a}$$

$$P_L = i^2 R = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

$$C = \frac{\varepsilon A}{d}$$

$$i = C \frac{dv}{dt}$$

$$V(t) = \frac{1}{C} \int_{t_o}^t i dt + V(t_o)$$

$$P = \frac{dw}{dt} = CV \frac{dv}{dt}$$

$$w = \frac{1}{2} CV^2(t)$$

**TERBUKA**

**FINAL EXAMINATION**

SEMESTER / SESSION : SEM I / 2023/2024  
 COURSE NAME : CIRCUIT THEORY

PROGRAMME CODE : DAE  
 COURSE CODE : DAE 11103

$$v = L \frac{di}{dt} \quad i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0) \quad w = \frac{1}{2} Li^2$$

$$V(t) = V_o e^{-\frac{t}{RC}} \quad \tau = RC \quad i(t) = I_0 e^{-\frac{t}{\tau}} \quad \tau = \frac{L}{R}$$

$$v(t) = V_m \sin(\omega t + \varphi) \quad f = \frac{1}{T} \quad \omega = 2\pi f$$

$$z = x + jy = r\angle\varphi$$

Addition

$$z_1 = x_1 + jy_1 = r_1\angle\varphi$$

$$z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

$$z_2 = x_2 + jy_2 = r_2\angle\varphi$$

Subtraction

$$z_3 = x_3 + jy_3 = r_3\angle\varphi$$

$$z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

Division

$$\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle\varphi_1 - \varphi_2$$

Reciprocal

$$\frac{1}{z} = \frac{1}{r} \angle -\varphi$$

Multiplication

$$z_1 \cdot z_2 = r_1 r_2 \angle\varphi_1 + \varphi_2$$

Square Root

$$\sqrt{z} = \sqrt{r} \angle \left( \frac{\varphi}{2} \right)$$

Complex Conjugate

$$z^* = x - jy = r \angle -\varphi = r e^{-j\varphi}$$

**TERBUKA**