

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2014/2015**

COURSE NAME : DIGITAL ELECTRONICS
COURSE CODE : DAR 21303
PROGRAMME : 2 DAR
EXAMINATION DATE : JUNE 2015 / JULY 2015
DURATION : 2 ½ HOURS
INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF **NINE (9)** PAGES

CONFIDENTIAL

- Q1** (a) Perform the following arithmetic operations. Check the answer with its decimal equivalent.
- (i) $1001_2 + 1101_2 + 1010_2$
 - (ii) $100101010_2 + 001011011_2$
 - (iii) $+ 26_{10} - 35_{10}$ using 2's complement
- (7 marks)
- (b) Show that a full adder can be implemented using two half adders by doing the following:
- (i) Produce a truth table for the full adder
 - (ii) Write the output expression for Sum and Carry
 - (iii) Use Boolean algebra theorem to simplify the output expression for Sum and Carry.
 - (iv) Draw and label all inputs and outputs of the logic circuit for the full adder.
- (15 marks)
- (c) Convert 439_{10} to hexadecimal.
- (3 marks)

Q2 (a) Explain the importance of Boolean theorems in digital systems. Write **four (4)** examples of Boolean algebra rules.

(4 marks)

(b) Simplify the following Boolean expression using Boolean algebra and verify the result using a Karnaugh map.

$$Z = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}B\overline{C}D$$

(7 marks)

(c) Waveforms A, B and C of **Figure Q2(c)** are applied to a logic circuit. The output waveform, D, from the circuit is also shown in **Figure Q2(c)**.

- (i) Obtain the truth table and Boolean expression of the logic circuit.
- (ii) Simplify the Boolean expression and implement the logic circuit using NAND gates

(14 marks)

Q3 (a) For the following function:

$$f(A, B, C, D) = \sum m(0, 5, 8, 10, 13, 14) + d(1, 6, 12)$$

- (i) Simplify using a Karnaugh map.
- (ii) Obtain the minimum sum of product (SOP) expression
- (iii) Implement the simplified expression using basic logic gates.

(9 marks)

(b) Design a comparator circuit to compare two 2-bit numbers (A1, A0 and B1, B0). The circuit will have two output signals, GE and LT. GE will be HIGH to indicate that the 2-bit A value is equal to or greater than the 2-bit B value. LT will be HIGH if A<B.

- (i) Obtain the truth table of the circuit.

(5 marks)

- (ii) Simplify the output function for GE and LT.

(5 marks)

- (iii) Draw the simplified logic diagram of this circuit using NAND gates only.

(6 marks)

Q4 (a) Briefly describe the difference between a multiplexer and a demultiplexer with the aid of block diagrams.

(6 marks)

(b) Use the 74138 IC in **Figure Q4(b)** to implement the following function:

- (i) $F(X, Y, Z) = X + YZ$
- (ii) $W(X, Y, Z) = XY + Y\bar{Z} + \bar{X}Y\bar{Z}$

(10 marks)

(c) The logic diagram and Dual-In-Line Package (DIL) for IC 7493 is given In **Figure Q4(c)**. Do the following and show all steps.

- (i) Name the three standard MOD counters that can be implemented.
- (ii) Design a 7493-based Mod-10 counter. Label the input clock and outputs clearly.
- (iii) If the input clock frequency is 2 kHz, determine the output frequency of this counter.

(9 marks)

- Q5** (a) With the aid of truth tables, describe the differences between the following flip flops:
- (i) RS flip flop
 - (ii) JK flip flop
 - (iii) D flip flop
- (9 marks)
- (b) **Figure Q5(b)(i)** shows a latch and 2 different flip-flops. The waveforms given in **Figure Q5(b)(ii)** are applied to the pins labeled. Sketch the waveforms that appear at the Q terminal of each circuit.
- (6 marks)
- (c) State **two (2)** differences between synchronous and asynchronous counters.
- (4 marks)
- (d) For the counter circuit in **Figure Q5(d)**
- (i) Construct a table to show the counting sequence.
 - (ii) Describe its operation.
- (6 marks)
- Q6** (a) The 4-bit serial input register in **Figure Q6(a)** has 1011 (Q,R,S,T) stored in it and data inputs are low. Show the register operations for four clock transitions by doing the following:
- (i) Draw a table showing the state sequence
 - (ii) Draw the timing diagram.
- (10 marks)
- (b) Briefly explain **two (2)** advantages of digital techniques over analog. Give **one (1)** major drawback of digital techniques.
- (4 marks)
- (c) Two conversion are necessary to interface real world, analog signals with a digital circuit. Name dan describe briefly the function of the two circuits used.
- (3 marks)
- (d) The circuit in **Figure Q6(d)(i)** is used in digital and analog interface.
- (i) State the function of this circuit.
 - (ii) Determine the output V_{out} and record its value in **Table Q6(d)** if the 4-bit numbers D_3, D_2, D_1 and D_0 are applied to the inputs.
- (8 marks)

- END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2014/2015
COURSE NAME : DIGITAL ELECTRONICS

PROGRAMME : 2DAR
COURSE CODE: DAR 21303

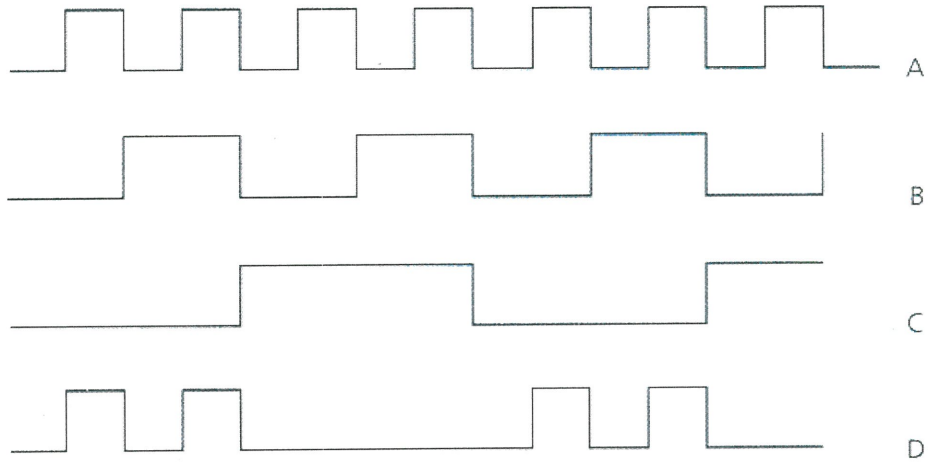


FIGURE Q2(c)


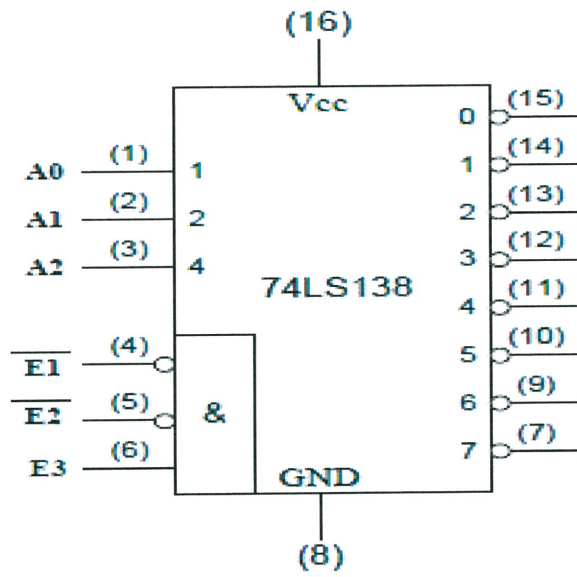


FIGURE Q4(b)

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2014/2015
 COURSE NAME : DIGITAL ELECTRONICS

PROGRAMME : 2DAR
 COURSE CODE: DAR 21303

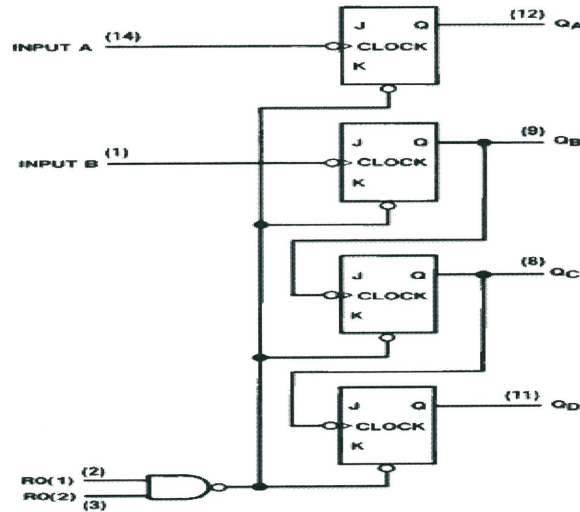

Dual-In-Line Package

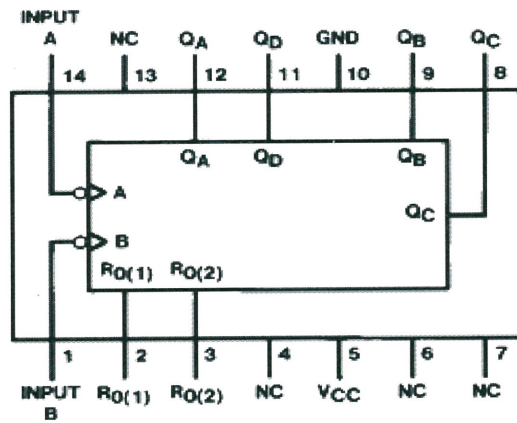


FIGURE Q4(c)

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2014/2015
 COURSE NAME : DIGITAL ELECTRONICS

PROGRAMME : 2DAR
 COURSE CODE: DAR 21303

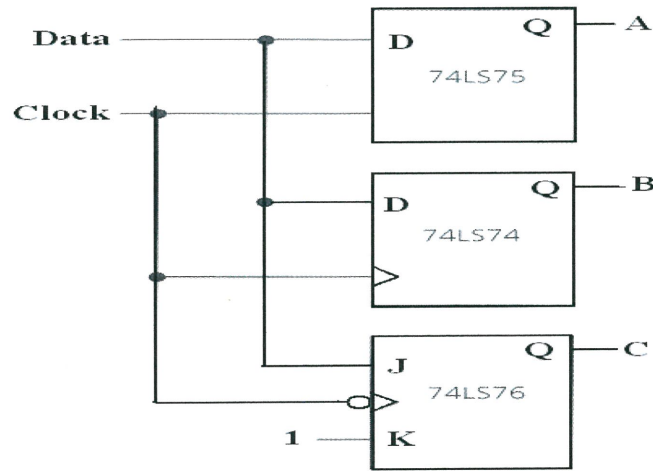


FIGURE Q5(a)(i)

[Preset and Clear Inputs disabled.]

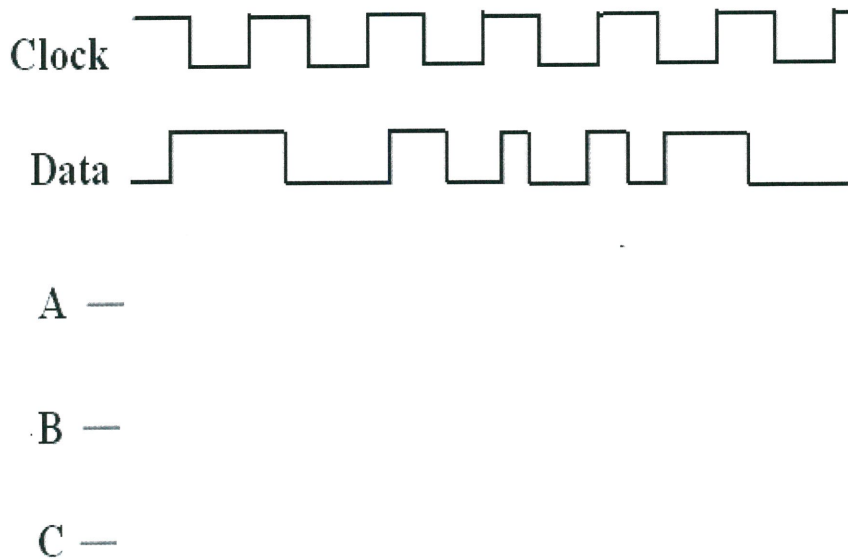


FIGURE Q5(b)(ii)

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2014/2015
 COURSE NAME : DIGITAL ELECTRONICS

PROGRAMME : 2DAR
 COURSE CODE: DAR 21303

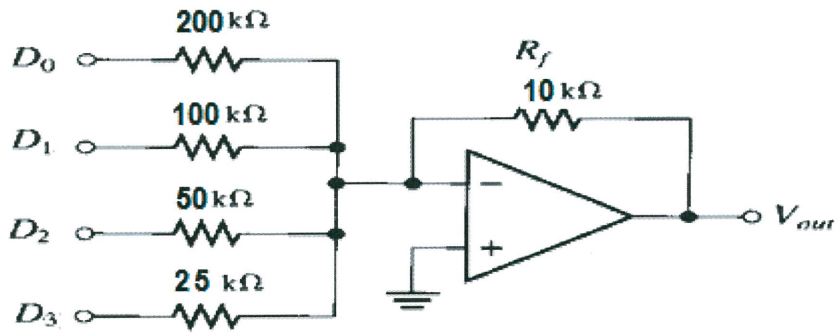


FIGURE Q6(d)(i)

Table Q6(d)

D_3	D_2	D_1	D_0	V_{out} (V)
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	