



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER I  
SESSION 2016/2017**

COURSE NAME : ELECTRICAL TECHNOLOGY  
COURSE CODE : DAE 11003  
PROGRAMME CODE : DAE  
EXAMINATION DATE : DECEMBER 2016 / JANUARY 2017  
DURATION : 2 HOURS 30 MINUTES  
INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS ONLY

**TERBUKA**

THIS QUESTION PAPER CONSISTS OF **TEN (10)** PAGES

- Q1**
- (a) List **three (3)** particles contained in the atomic structure according to the classic Bohr Model. (3 marks)
- (b) Illustrate the placement of an ammeter and a voltmeter to measure the current and the source voltage in **Figure Q1(b)**. (4 marks)
- (c) Determine the resistance values for the following:
- (i) Red, violet, orange, gold  
(ii) Brown, gray, red, silver (6 marks)
- (d) Determine the color bands for each of the following values:
- (i)  $330\Omega$   
(ii)  $2.2k\Omega$   
(iii)  $56k\Omega$  (9 marks)
- (e) Explain **three (3)** basic functions of multimeter. (3 marks)
- Q2**
- (a) Define Ohm's Law (3 marks)
- (b) Referring to the circuit in **Figure Q2(b)**, determine the followings:
- (i) Calculate the current if the voltage ranging from 10V to 100V (10V intervals). Construct the table of voltage, V and current, I.
- (ii) Plot a graph of current, I versus voltage, V. (Plot a graph for 10 points).
- (iii) Give a conclusion based on your answer in **Q2(b)(ii)**. (12 Marks)
- (c) Determine the total resistance ( $R_T$ ) for circuit of **Figure Q2(c)**. (3 Marks)
- (d) Find  $R_1$ ,  $R_2$  and  $R_3$  in **Figure Q2(d)**. (7 Marks)

TERBUKA

- Q3.** (a) Define:
- (i) Kirchoff's voltage law.
  - (ii) Kirchoff's current law.
- (6 marks)
- (b) Give **two (2)** examples of voltage divider applications. (4 marks)
- (c) In the circuit of **Figure Q3(c)**, determine the resistance  $R_2$ ,  $R_3$  and  $R_4$ . (10 marks)
- (d) Determine the current in each branch of the current dividers in **Figure Q3(d)**. (5 marks)
- 
- Q4.** (a) Describe the series-parallel combinations between terminal A and D in **Figure Q4(a)**. (4 marks)
- (b) A Wheatstone bridge circuit consists of **four (4)** resistors and a dc voltage source which look alike a 'diamond' configuration.
- (i) Draw the Wheatstone bridge (complete with  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ , dc source and  $V_{out}$  terminals).
  - (ii) Explain the condition of the balanced Wheatstone bridge. (8 Marks)
- (c) Referring to **Figure Q4(c)**, determine the followings:
- (i) Magnetizing force ( $H$ )
  - (ii) Magnetic flux ( $\Phi$ )
  - (iii) Magnetic flux density ( $B$ )
- (13 marks)
- 
- Q5.** (a) Draw two sine waves as follows: Sine wave A is the reference, and sine wave B lags A by  $90^\circ$ . Both have equal amplitudes. (4 marks)
- (b) Convert the following angular values from degrees to radians:
- (i)  $30^\circ$
  - (ii)  $45^\circ$
- (4 marks)

**TERBUKA**

- (c) A sinusoidal voltage is applied to the resistive circuit in **Figure Q5(c)**. Determine the following:
- (i)  $I_{rms}$
  - (ii)  $I_{avg}$
  - (iii)  $I_p$
  - (iv)  $I_{pp}$
  - (v)  $i$  at the positive peak
- (10 marks)

- (d) Find the half-cycle average values of the voltages across  $R_1$  and  $R_2$  in **Figure Q5(d)**. All values shown are rms.
- (7 marks)

- Q6** (a) Draw a phasor diagram to represent the sine wave in **Figure Q6(a)** with respect to a  $0^0$  reference.
- (5 marks)

- (b) Convert each of the following rectangular numbers to polar form:
- (i)  $40 - j40$
  - (ii)  $50 - j200$
- (4 marks)

- (c) Solve the following equations:
- (i)  $(9 + j3) + (5 + j8)$
  - (ii)  $(4.5 \angle 48^0) \times (3.2 \angle 90^0)$
  - (iii)  $\frac{8 \angle 50^0}{2.5 \angle 39^0}$
- (6 marks)

- (d) Determine  $I_s$  in **Figure Q6(d)**. What is the value of  $R_L$ ?
- (10 marks)

-END OF QUESTIONS -

**TERBUKA**

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2016/2017  
COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : DAE  
COURSE CODE : DAE 11003

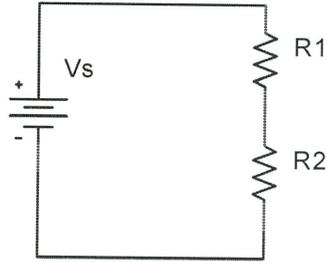


Figure Q1(b)

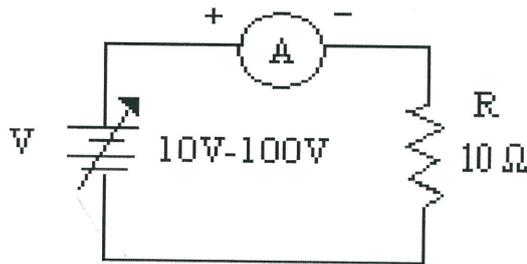


Figure Q2(b).

**TERBUKA**

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2016/2017  
COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : DAE  
COURSE CODE : DAE 11003

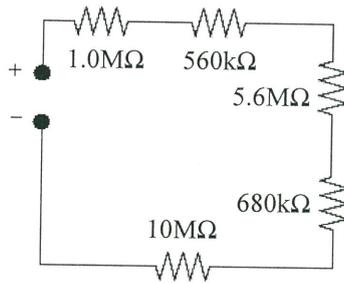


Figure Q2(c)

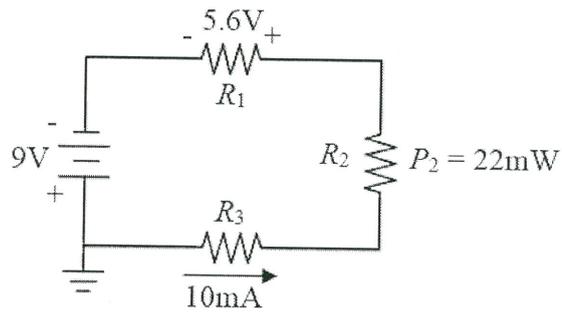


Figure Q2(d)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2016/2017  
COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : DAE  
COURSE CODE : DAE 11003

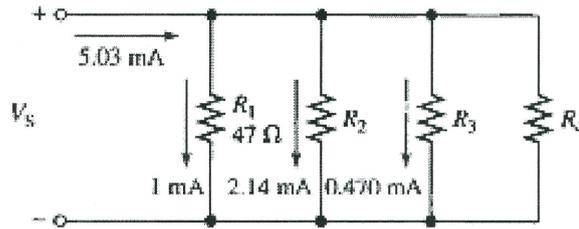


Figure Q3(c)

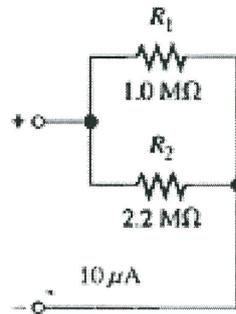


Figure Q3(d)

**TERBUKA**

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2016/2017  
COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : DAE  
COURSE CODE : DAE 11003

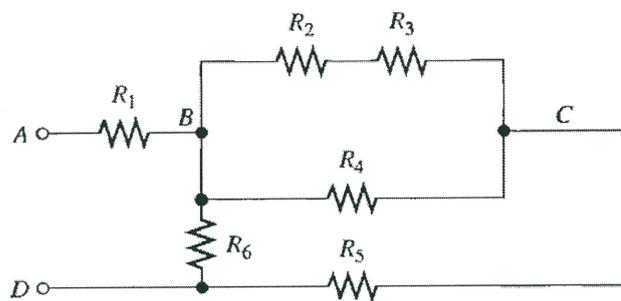


Figure Q4(a)

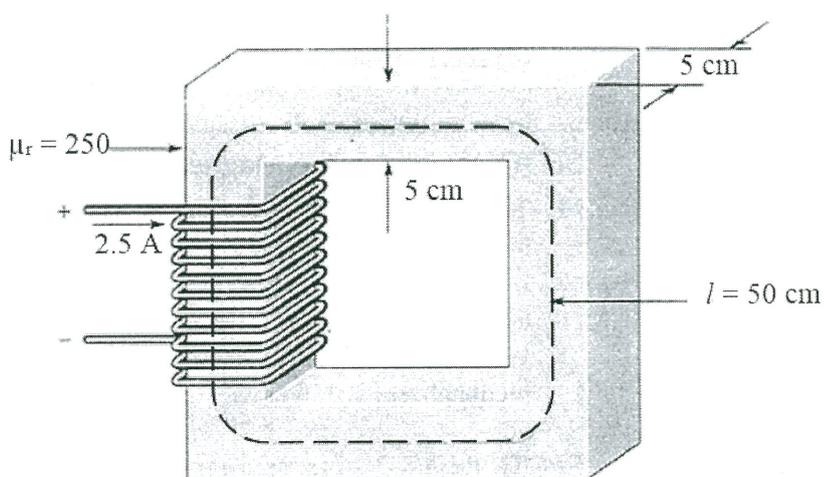


Figure Q4(c)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2016/2017  
COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : DAE  
COURSE CODE : DAE 11003

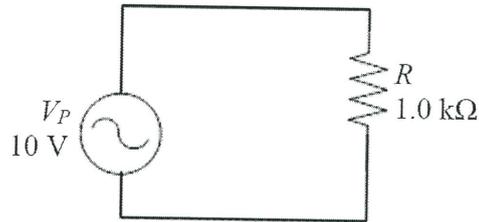


Figure Q5(c)

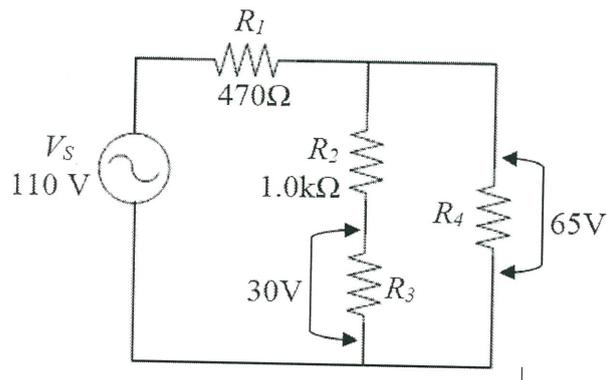


Figure Q5(d)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2016/2017  
COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : DAE  
COURSE CODE : DAE 11003

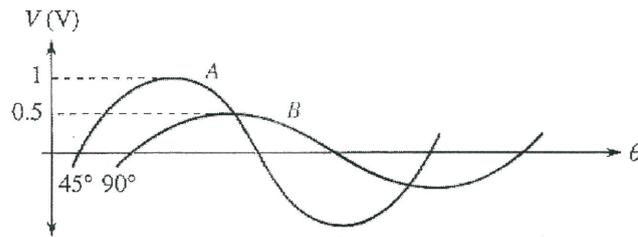


Figure Q6(a)

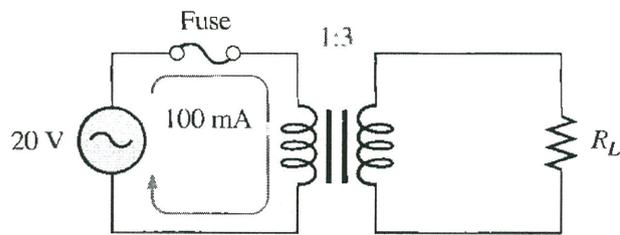


Figure Q6(d)

TERBUKA