

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2016/2017**

COURSE NAME : LOGIC SYSTEMS
COURSE CODE : DAE 21603
PROGRAMME : 2 DAE
EXAMINATION DATE : DECEMBER 2016/ JANUARY 2017
DURATION : 2 HOURS AND 30 MINUTES
INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS ONLY

TERBUKA

THIS QUESTION PAPER CONSISTS OF NINE (9) PAGES

CONFIDENTIAL

UNIVERSITI TUN HUSSEIN ONN MALAYSIA
JALAN SEMBANG, 41200 SEMBANG, SELANGOR
TEL: 03-5080 8888 FAX: 03-5080 8889
WWW.UTHM.MY

- Q1**
- (a) Explain **two** primary of logic circuit. (3 marks)
 - (b) What is the difference between latch and flip-flop operation. (3 marks)
 - (c) With the aid of truth tables, describe the differences between the following flip-flops
 - (i) RS flip flop.
 - (ii) JK flip-flop.
 - (iii) D flip-flop.(12 marks)
 - (d) Given D, $\overline{\text{Preset}}$, $\overline{\text{Clear}}$ and Clok input for a D flip-flop in **Figure Q1(d)**.
 - (i) Draw the Q output waveform
 - (ii) Draw the \overline{Q} output waveform(7 marks)
- Q2**
- (a) Explain briefly two application of flip-flop. (4 marks)
 - (b) For the circuit in **Figure Q2(b)**:
 - (i) State the function of this circuit. (2 marks)
 - (ii) Determine the external resistors R1 and R2 to give output frequency of 20kHz and duty cycle of 60% if the external capacitor C is 3nF. (6 marks)
 - (c) **Figure Q2(c)** show JK flip-flop as a ripple counter to count up counter.
 - (i) Draw the timing diagram as **Figure Q2(c)**. (9 marks)
 - (ii) Modify the circuit to operate MOD 7 counter. (4 marks)

TERBUKA

Q3 (a) The logic diagram and Dual-In-Line Package for IC 7493 is given in **Figure Q3(a)**. Draw the connections diagrams for the following 7493-based counters and determine the output frequency if the input clock frequency is 200 kHz. Show all steps and label the input clock as well as the outputs.

- (i) MOD 9 counter
- (ii) MOD 12 counter
- (iii) MOD 16 counter

(15 marks)

(b) For the **Figure Q3(b)**, the propagation delay, t_{pd} for each flip-flop is 50ns And t_{pd} for AND gate is 20ns.

- (i) Determine the maximum input clock frequency (f_{max}) for the Counter.
- (ii) Determine the maximum input clock frequency (f_{max}) with a MOD-16 ripple counter.

(10 marks)

Q4 (a) Design a synchronous counter using JK flip-flop to count 4 digits. The count sequence is 0,2,4,6 and repeat. The JK excitation table is shown in **Table Q4(a)**. Show all steps and the design should include the following :

- (i) State diagram
- (ii) Circuit excitation table used to determine JK flip-flop inputs.
- (iii) K-maps used to generate minimal expressions for JK inputs.
- (iv) Logic circuit.

(15 marks)

(b) Explain 4 mode data movement in shift register.

(4 marks)

(c) Determine the number of flip-flops needed to construct a shift register capable of storing :

- (i) a 4-bit binary number
- (ii) Draw the logic diagram as a serial input/serial output shift register.

(6 marks)

TERBUKA

- Q5** (a) List **three (3)** advantages of constructing a digital circuit prototype using a PLD instead of standard logic devices. (3 marks)
- (b) Several types of architecture are used in PLDs. Draw the block diagram of three common types and describe their differences. (6 marks)
- (c) List **five (5)** limitations of PLAs. (5 marks)
- (d) Use the PLA in **Figure Q5(d)** to implement the following functions. Label all inputs and outputs.
- (i) $F1(W, X, Y) = \Sigma(1,2,3,5,7)$
 - (ii) $F2(W, X, Y) = \Sigma(0,4,6,7)$
- (11 marks)

- Q6** (a) Define each basic memory operations terms below.
- (i) Write
 - (ii) Read.
 - (iii) Address.
- (6 marks)
- (b) A certain memory has a capacity of 2K x 8, determine
- (i) the number of data inputs and data outputs .
 - (ii) the number of address lines.
 - (iii) its capacity in bytes.
- (9 marks)
- (c) Define each of the following terms.
- (i) RAM
 - (ii) ROM
 - (iii) EPROM
 - (iv) Internal Memory
- (10 marks)



- END OF QUESTION -

CONFIDENTIAL
DAE 21603
QUESTION 5
QUESTION 6

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2016/2017
 COURSE NAME : LOGIC SYSTEMS

PROGRAMME : 2 DAE
 COURSE CODE: DAE 21603

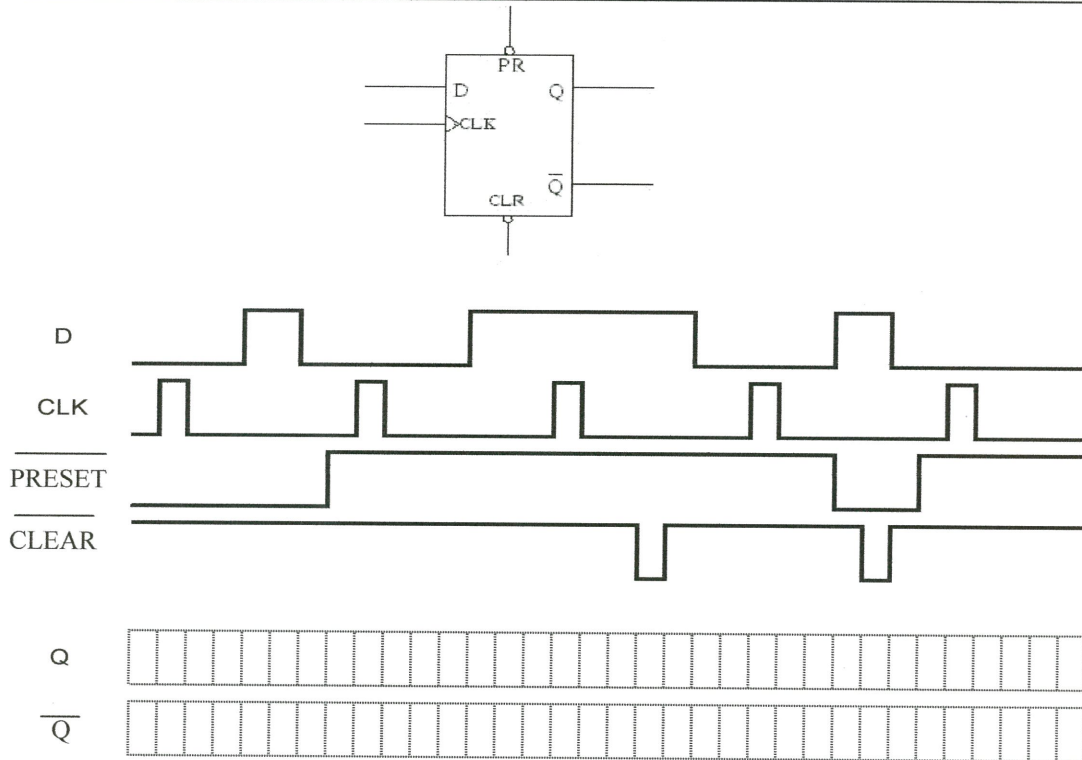


FIGURE Q1(d)

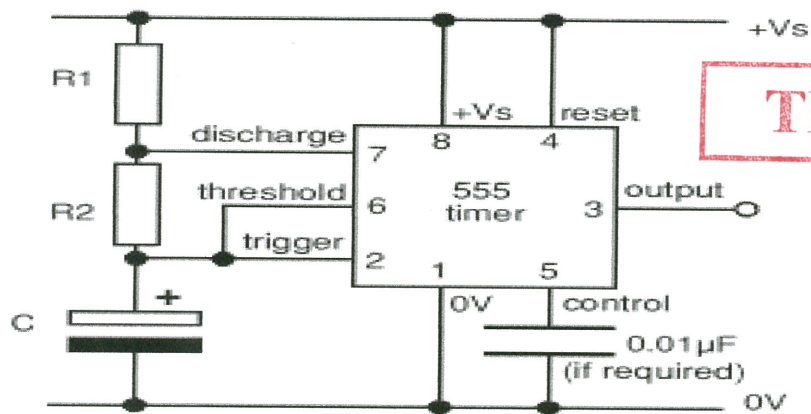


FIGURE Q2(b)

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2016/2017
COURSE NAME : LOGIC SYSTEMS

PROGRAMME : 2 DAE
COURSE CODE: DAE 21603

 



FIGURE Q2(c)

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2016/2017
COURSE NAME : LOGIC SYSTEMS

PROGRAMME : 2 DAE
COURSE CODE: DAE 21603

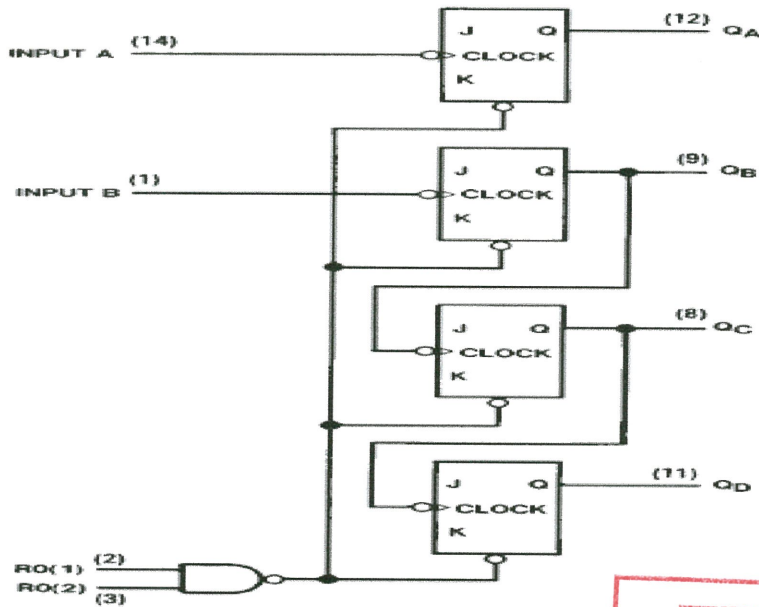

TERBUKA

Dual-In-Line Package

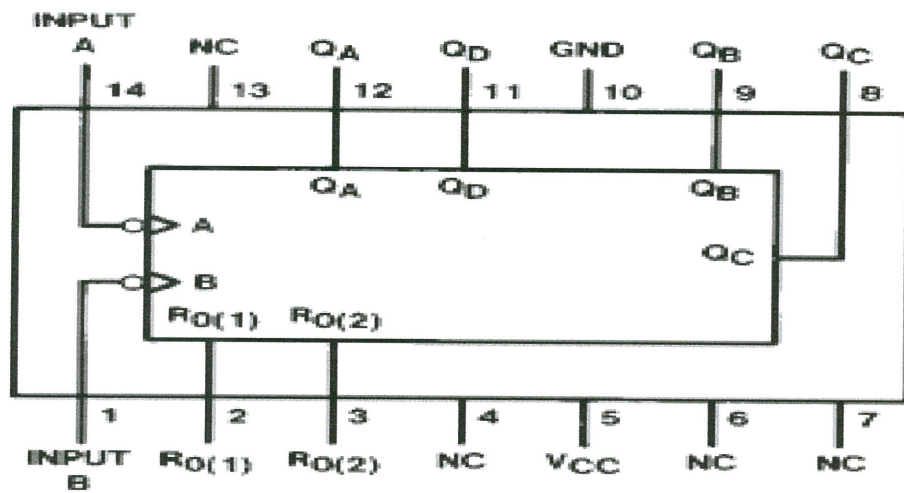


FIGURE Q3(a)

Handwritten text at the bottom left corner, likely a student's name or ID, which is mostly illegible due to blurring and low resolution.

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2016/2017
 COURSE NAME : LOGIC SYSTEMS

PROGRAMME : 2 DAE
 COURSE CODE: DAE 21603

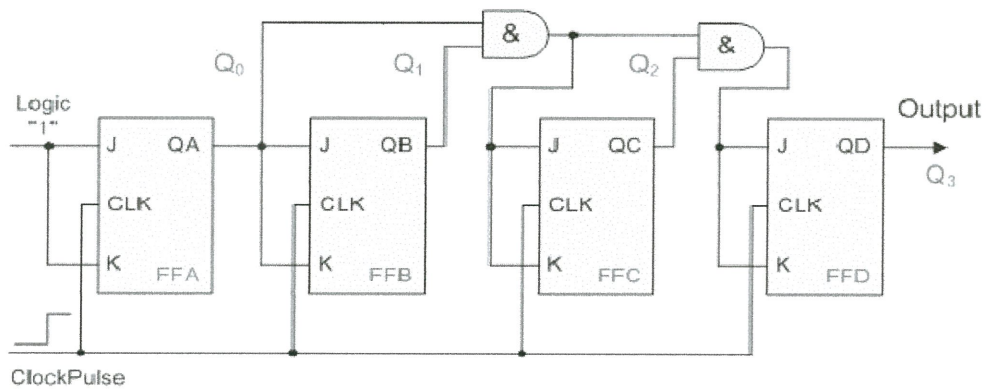


FIGURE Q3(b)

TERBUKA

TABLE Q4(a): JK Excitation Table

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Handwritten notes:
 This is a shift register
 with 4 bits
 and the output is Q₃

