



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2023/2024**

- COURSE NAME : ANALOG ELECTRONICS
- COURSE CODE : BEJ10503
- PROGRAMME CODE : BEJ
- EXAMINATION DATE : JULY 2024
- DURATION : 3 HOURS
- INSTRUCTIONS :
1. ANSWER ALL QUESTIONS
 2. THIS FINAL EXAMINATION IS CONDUCTED VIA
 - Open book
 - Closed book
 3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES DURING THE EXAMINATION CONDUCTED VIA CLOSED BOOK

THIS QUESTION PAPER CONSISTS OF FIVE (5) PAGES

- Q1** A common emitter voltage divider bias amplifier circuit is depicted in **Figure Q1.1**. Given $\beta = 100$, $R_1 = 15 \text{ k}\Omega$, $R_2 = 6 \text{ k}\Omega$, $R_C = 2 \text{ k}\Omega$, $R_E = 1.5 \text{ k}\Omega$ and $r_o = \infty$. shows a BJT amplifier circuit with $\beta = 75$ and $V_{BE} = 0.7 \text{ V}$.

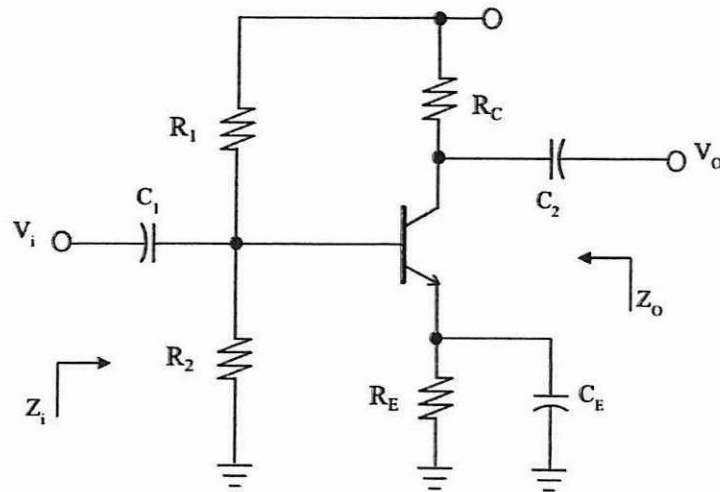


Figure Q1.1 BJT amplifier circuit

- (a) Analyze the circuit and determine Q-point current and voltage, (I_{BQ} , I_{CQ} and output voltage, V_{CEQ}) using exact analysis. (15 marks)
- (b) From the results obtained in **Q1(a)**, find the r_e value. (1 mark)
- (c) Sketch the small signal AC equivalent circuit using r_e model for the circuit in **Figure Q1.1**. (3 marks)
- (d) Determine the input impedance, Z_i and output impedance, Z_o for the small signal AC equivalent circuit in part **Q1(b)**. (2 marks)
- (e) Calculate the voltage gain, A_v and the current gain, A_i . (4 marks)

TERBUKA

Q2 Based on the FET amplifier circuit shown in Figure Q2.1;

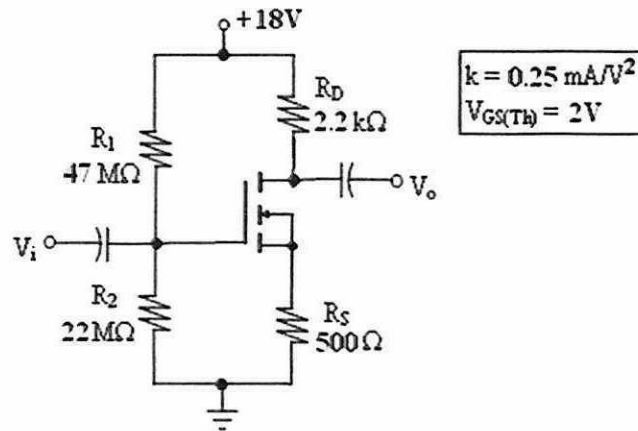


Figure Q2.1 FET amplifier circuit

- (a) name the transistor and its configuration. (2 marks)
- (b) plot the transfer characteristics of the transistor. (12 marks)
- (c) determine the operating point, V_{GSQ} and I_{DQ} of the amplifier from the graph obtained in Q2(b). (2 marks)
- (d) if the amplifier has an applied load resistance, R_L of 10 kΩ and a source resistance, R_{sig} of 1 kΩ, sketch the AC small-signal equivalent circuit of the FET amplifier circuit. (3 marks)
- (e) assuming the transistor AC output resistance $r_o = \infty$ (infinity), calculate the input impedance, Z_i , output impedance, Z_o and voltage gain, A_v . (11 marks)

TERBUKA

Q3 Figure Q3.1 shows a common emitter amplifier network. Given the $\beta = 100$, $r_o = \infty \Omega$, junction capacitances, $C_{be} = 35 \text{ pF}$, $C_{bc} = 4 \text{ pF}$, $C_{ce} = 1 \text{ pF}$, and wiring capacitances, $C_{wi} = 5 \text{ pF}$, $C_{wo} = 8 \text{ pF}$. Based on this figure;

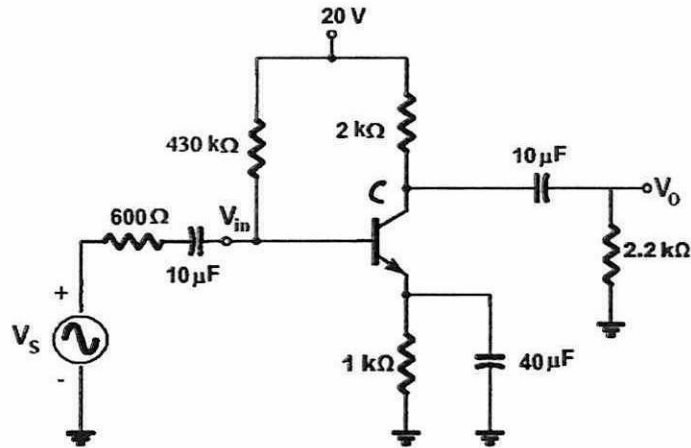


Figure Q3.1 Common emitter amplifier

- (a) conduct a DC analysis and determine the I_B , I_C , V_{CE} and r_e . (6 marks)
- (b) draw the low frequency ac equivalent model. (3 marks)
- (c) calculate the lower cutoff frequencies f_{LS} , and f_{LC} due to coupling capacitors. (6 marks)
- (d) draw the high frequency ac equivalent model. (3 marks)
- (e) calculate the high input and high output cut-off frequencies, f_{Hi} and f_{Ho} , respectively. Show all calculations. (7 marks)

TERBUKA

- Q4** There are different ways to describe amplifiers. For instance, they can be described by their class of operation, inter-stage coupling, or frequency range.
- (a) Explain the signal cycle and efficiency of the Class A and Class B amplifiers.
(5 marks)
 - (b) Determine the input power, output power and circuit efficiency of a class B amplifier providing a 25 V peak signal to a 15 Ω load and a power supply of $V_{cc} = 30$ V. Sketch the circuit diagram for the amplifier.
(8 marks)
 - (c) Analyze the circuit performance in terms of its efficiency as a class B amplifier based on the value obtained in **Q4(b)**.
(2 marks)
 - (d) Crossover distortion is seen as a problem arising from a class B push-pull amplifier. Analyse the crossover distortion problem that arises in the class B push-pull amplifier by using an appropriate illustration of V_{in} and V_{out} .
(5 marks)

- END OF QUESTIONS -

TERBUKA