



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

FINAL EXAMINATION
SEMESTER II
SESSION 2023/2024

- COURSE NAME : ANALOG IC DESIGN
- COURSE CODE : BEJ43903
- PROGRAMME CODE : BEJ
- EXAMINATION DATE : JULY 2024
- DURATION : 3 HOURS
- INSTRUCTIONS :
1. ANSWER ALL QUESTIONS
 2. THIS FINAL EXAMINATION IS CONDUCTED VIA
 - Open book
 - Closed book
 3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES DURING THE EXAMINATION CONDUCTED VIA CLOSED BOOK

THIS QUESTION PAPER CONSISTS OF TEN (10) PAGES

Q1 (a) A MOS differential pair is shown in Figure Q1.1.

- (i) Design the MOS differential pair for a voltage gain of 5 and a power dissipation of 1 mW if the equilibrium overdrive must at least 150 mV. Assume $\gamma = \lambda = 0$, $\mu_n C_{ox} = 100 \mu A/V^2$, $V_{TH} = 0.6 V$ and $V_{DD} = 1.8 V$. (8 marks)

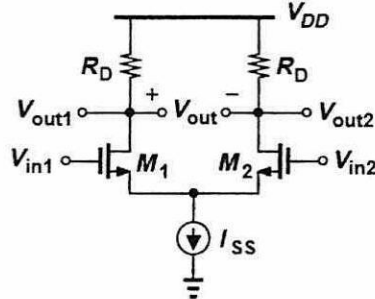


Figure Q1.1

- (ii) Determine the maximum allowable input CM level if $V_{TH} = 0.4 V$ is applied to the same circuit in Figure Q1.1.

(2 marks)

- (b) Figure Q1.2 shows the differential amplifier that uses a resistor rather than a current source to define a tail current of 1 mA. Assuming that the circuit is symmetrical and $\gamma = \lambda = 0$, $(W/L)_{1,2} = 20/0.5$, $\mu_n C_{ox} = 100 \mu A/V^2$, $V_{TH} = 0.6 V$ and $V_{DD} = 3 V$.

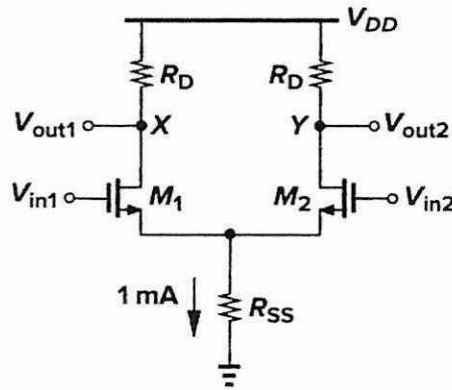


Figure Q1.2

- (i) Determine the required input CM voltage for which R_{SS} sustains 0.5 V and calculate the R_{SS} value.

(8 marks)

- (ii) Calculate R_D for a differential gain of 20.

(4 marks)

- (iii) Draw the small-signal equivalent circuit for this amplifier.

(3 marks)

- Q2 (a) A current mirror circuit senses the reference current and generates the copy of reference current with the same characteristics. **Figure Q2.1** shows a basic block diagram for current mirror circuit.

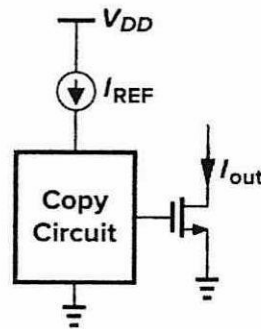


Figure Q2.1

- (i) Complete the circuit by drawing the 'copy circuit'. Using the complete circuit, prove that $I_{out} = \frac{(W/L)_2}{(W/L)_1} I_{REF}$. (4 marks)
- (ii) Modify the circuit in **Figure Q2.1** such that the body effect can be ignored and constant output voltage. (3 marks)
- (b) The common-source stage depicted in **Figure Q2.2** must be designed for a voltage gain of 20 and a power budget of 2 mW. Assume the following:
 $\mu_n C_{ox} = 100 \mu A/V^2, (W/L)_1 = 20/0.18, \lambda_n = 0.1 V^{-1}, \lambda_p = 0.2 V^{-1}, \gamma = 0$.

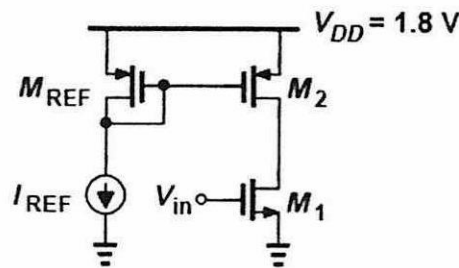


Figure Q2.2

- (i) Determine the V_{GS1} and I_{D1} . (5 marks)
- (ii) Find I_{REF} and $\frac{(W/L)_2}{(W/L)_{REF}}$ if M_{REF} has $(W/L)_{REF}$. (3 marks)

- (c) A current source circuit is shown in **Figure Q2.3**. Given the following parameters, $(W/L)_1 = 2$, $(W/L)_2 = 10$, $V_{DD} = 2.5\text{ V}$, $\mu_n C_{ox} = 100\mu\text{A}/\text{V}^2$, $V_{TH,n} = 0.5\text{ V}$, $\lambda_n = 0.05\text{ V}^{-1}$, $\gamma = 0$.

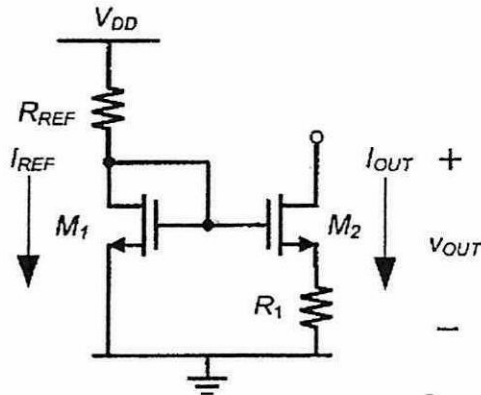


Figure Q2.3

- (i) Find the value of R_{REF} such that $I_{REF} = 100\mu\text{A}$.
(3 marks)
- (ii) Determine the value of R_1 that gives $I_{OUT} = 40\mu\text{A}$. Assume that M_2 is in saturation.
(4 marks)
- (iii) Determine the lowest output voltage, V_{OUT} for which the circuit still acts as a current source.
(3 marks)

Q3 (a) Operation amplifiers (also known as op-amps) are key elements in analogue processing systems.

- (i) Compare **TWO (2)** advantages of single stage amplifier and two stage amplifiers.
(4 marks)
- (ii) Determine the input common-mode voltage range and the closed-loop output impedance of the unity-gain buffer depicted in **Figure Q3.1**. Assume the threshold voltage, $V_{TH} = 0.7\text{ V}$ with supply voltage of 3 V .
(4 marks)

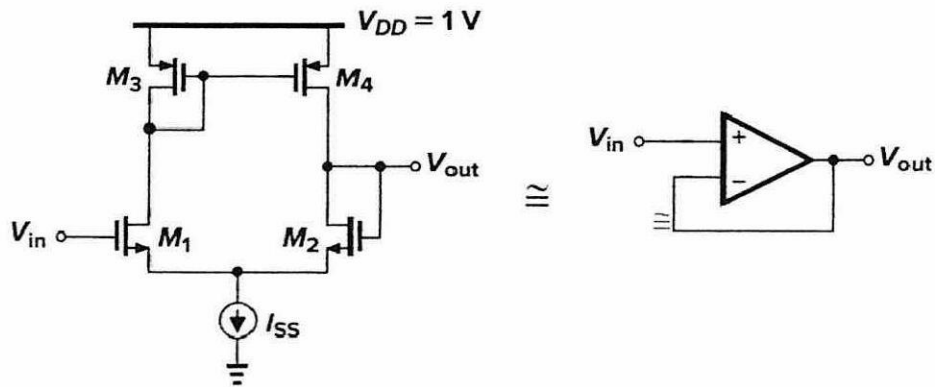


Figure Q3.1

- (b) An amplifier circuit depicted in **Figure Q3.2** is designed based on the following specification. Assume M_1 operates at the edge of saturation if the input common-mode level is 1 V.

$$A_v = 10, P = 2\text{ mW}, \mu_n C_{ox} = 2\mu_p C_{ox} = 100\ \mu\text{A}/\text{V}^2,$$

$$V_{DD} = 1.8\text{ V}, V_{TH,n} = 0.6\text{ V}, V_{TH,p} = -0.4\text{ V}, \lambda_n = 0.1\text{ V}^{-1}, \lambda_p = 0.2\text{ V}^{-1}$$

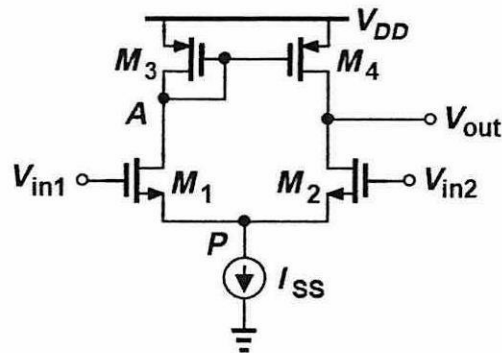


Figure Q3.2

- (i) Find the I_{SS} and $g_{m(n)}$. (5 marks)
- (ii) Determine $(W/L)_{1-2}$ and $(W/L)_{3-4}$. (4 marks)

- (c) A simple implementation of a two-stage op amp is shown in **Figure Q3.3**. Assume the following parameters: $(W/L)_{1-8} = 100/0.5$, $I_{SS} = 1\text{ mA}$, $V_{DD} = 3\text{ V}$, $V_{TH} = 0.7\text{ V}$, $\mu_n C_{ox} = 100\ \mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 50\ \mu\text{A}/\text{V}^2$, $\gamma = 0$.

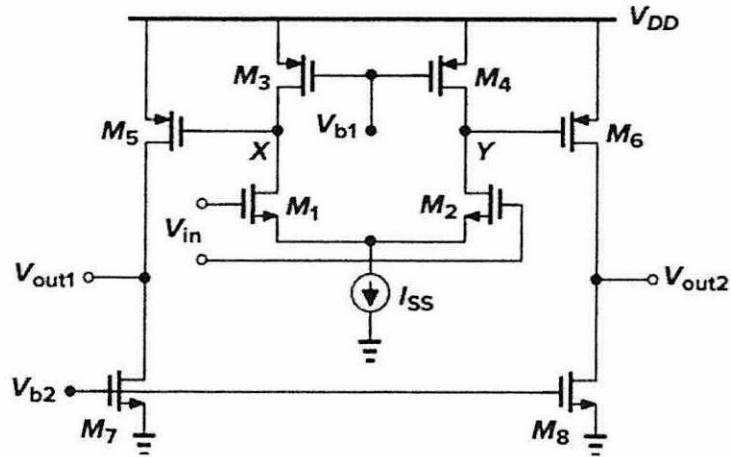


Figure Q3.3

- (i) Analyse the CM level that must be established at the drains of M_3 and M_4 so that $I_{D5} = I_{D6} = 1\text{ mA}$. (4 marks)
- (ii) Based on part **Q3(c)(i)**, calculate the overall voltage gain and the maximum output swing. (4 marks)
- Q4** (a) A comparator detects if its input (voltage or current) is higher or lower than a reference level. Discuss **TWO (2)** key stage issues in comparator design and suggest the solution for each issue. (4 marks)
- (b) Find the propagation delay time of an open-loop comparator has a dominant pole at 10^3 rad/s , DC gain of 10^4 , slew rate $1\text{ V}/\mu\text{s}$, and a binary output voltage swing of 1 V for an applied input voltage 10 mV . (8 marks)

TERBUKA

APPENDIX A

Constants

- $kT = 0.026 \text{ eV}$, at room temperature
- $k = 8.62 \times 10^{-5} \text{ eV/K}$, Boltzman's constant
- $V_T = 0.026 \text{ V}$, thermal voltage
- $q = 1.6 \times 10^{-19} \text{ C}$ (coulombs)
- $n_i = 1.45 \times 10^{10} \text{ cm}^{-3}$, Si at room temperature
- $\epsilon_0 = 8.85 \times 10^{-14} \text{ F/cm}$
- $\epsilon_{OX} = (3.9) 8.85 \times 10^{-14} \text{ F/cm}$
- $\epsilon_{si} = (11.8) 8.85 \times 10^{-14} \text{ F/cm}$

N-channel MOSFET:

Cut-off	$V_{GS} \leq V_T$	$I_{DS} = 0$
Linear	$V_{GS} \leq V_T, V_{DS} \leq V_{SG} - V_T$	$I_{DS} = \mu_n C_{OX} \frac{W}{L} \left[(V_{SG} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right] (1 + \lambda V_{DS})$
Saturation	$V_{GS} > V_T, V_{DS} > V_{SG} - V_T$	$I_{DS} = \frac{1}{2} \mu_n C_{OX} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$
		$g_m = \mu_n C_{OX} \frac{W}{L} (V_{GS} - V_T) (1 + \lambda V_{DS})$
		$g_m = \mu_n C_{OX} \frac{W}{L} (V_{GS} - V_T) = \sqrt{2 \mu_n C_{OX} \frac{W}{L} I_D} = \frac{2I_D}{V_{GS} - V_T} \quad (\text{for } \lambda = 0)$

P-channel MOSFET:

Cut-off	$V_{SG} \leq V_T $	$I_{SD} = 0$
Linear	$V_{SG} > V_T , V_{SD} \leq V_{SG} - V_T $	$I_{SD} = \mu_p C_{OX} \frac{W}{L} \left[(V_{SG} - V_T) V_{SD} - \frac{V_{SD}^2}{2} \right] (1 + \lambda V_{SD})$
Saturation	$V_{SG} > V_T , V_{SD} > V_{SG} - V_T $	$I_{SD} = \frac{1}{2} \mu_p C_{OX} \frac{W}{L} (V_{SG} - V_T)^2 (1 + \lambda V_{SD})$

Diff.Amp :

$$|V_{in1} - V_{in2}| \ll \frac{4I_{SS}}{\mu_n C_{OX} \frac{W}{L}}$$

$$I_{D1} - I_{D2} \approx \frac{1}{2} \mu_n C_{OX} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{OX} \frac{W}{L}}} = \sqrt{\mu_n C_{OX} \frac{W}{L} I_{SS}} (V_{in1} - V_{in2})$$

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) \quad K_n = \mu_n C_{OX} \frac{W}{L}$$

$$g_m = \sqrt{2 \mu_n C_{OX} \left(\frac{W}{L_{eff}} \right) I_D} = \sqrt{2 K_n I_D (1 + \lambda V_{DS})}$$

TERBUKA

$$r_o = \frac{\lambda^{-1} + V_{DS}}{I_D} \approx \frac{1}{\lambda I_D} \quad r_{oN} = \frac{1}{\lambda_n \frac{I_{SS}}{2}} (r_{oN} || r_{oP})$$

$$A_v = g_m (r_{oN} || r_{oP}) \quad g_m = r_{oN} || r_{oP}$$

$$2 \text{ stage: } A_v = \frac{2 I_D}{V_{GS5} - V_{TH}} \cdot \left[\frac{1}{\lambda_n I_{D5}} || \frac{1}{\lambda_p I_{D6}} \right] \text{ where } r_{oi} = \frac{1}{\lambda_n I_{Di}}$$

$$\beta = \text{feedback factor} = \frac{V_2}{V_1} \Big|_{I_2=0} = -(g_{m7} + g_{m8})(R_{oN7} || R_{oN8})$$

$$g_{m7} + g_{m8} = \mu_n C_{OX} \left(\frac{W}{L} \right)_{7,8} V_{DS7,8} \cdot \frac{1}{2 \mu_n C_{OX} \left(\frac{W}{L} \right)_{7,8} (V_{GS7,8} - V_{T7,8})}$$

$$= -2 \mu_n C_{OX} \left(\frac{W}{L} \right)_{7,8} V_{DS7,8} \cdot \frac{1}{2 \mu_n C_{OX} \left(\frac{W}{L} \right)_{7,8} (V_{GS7,8} - V_{T7,8})}$$

$$= - \frac{V_{DS7,8}}{V_{GS7,8} - V_{T7,8}}$$

Power dissipated:

$$P_D = V_{DS} \times I_D$$

$$P = I_{SS} \cdot V_{DD}$$

$$V_{CM,out} = V_{DD} \cdot \frac{I_{SS} R_D}{2 V_{DD}} = \frac{P_{RD}}{2 V_{DD}}$$

$$R_D = \left[2 V_{DD} \left(\frac{V_{DD} - V_{CM,out}}{P} \right) \right]$$

$$|A_v| = g_m R_D = \sqrt{\frac{W}{L} \mu_n C_{ox} I_{SS} R_D} = \sqrt{\frac{W}{L} \mu_n C_{ox} I_{SS} \frac{P}{V_{DD}} \left[2 V_{DD} \left(\frac{V_{DD} - V_{CM,out}}{P} \right) \right]}$$

Unbuffered Op-Amp:

$$ICMR_{(max)} = \left(\frac{W}{L} \right)_3 = \left(\frac{W}{L} \right)_4 = \frac{I_5}{K'_3 [V_{DD} - V_{in(max)} - |V_{T3}| + V_{T1}]^2}$$

$$g_m = GB \cdot C_C \quad \left(\frac{W}{L} \right)_3 = \left(\frac{W}{L} \right)_2 = \frac{(g_{m1})^2}{K'_1 I_5}$$

$$ICMR_{(min)} = \left(\frac{W}{L} \right)_5 = \frac{2 I_5}{K'_5 V_{DS5} [sat]^2}, \quad \left(\frac{W}{L} \right)_6 = \frac{g_{m6}}{g_{m4}} \cdot \left(\frac{W}{L} \right)_4$$

$$I_i = \frac{g_{m,i}^2}{2 K'_i \left(\frac{W}{L} \right)_i}$$

Two-stage Op-Amp:

$$SR = \frac{I_5}{C_C} \text{ where } I_7 \gg I_5 \text{ and } C_L > C_C$$

$$A_{v1} = \frac{g_{m1}}{g_{ds2} + g_{ds4}} = \frac{2g_{m1}}{I_5(I_2 + I_4)} \quad A_{v2} = \frac{g_{m6}}{g_{ds6} + g_{ds7}} = \frac{g_{m6}}{I_6(I_6 + I_7)}$$

$$GB = \frac{g_{m1}}{C_C} \quad p_2 = -\frac{g_{m6}}{C_L} \quad z_1 = \frac{g_{m6}}{C_C}$$

$$g_{m6} = 2.2 g_{m2} (C_L / C_C)$$

$$\text{Positive ICMR } V_{in(max)} = V_{DD} - \sqrt{\frac{I_5}{b_3}} - |V_{T03}|_{(max)} + V_{T1(min)}$$

$$\text{Negative ICMR } V_{in(max)} = V_{SS} + \sqrt{\frac{I_5}{b_1}} + V_{T1(max)} + V_{DS5(sat)}$$

Comparator

$$V_{OH} = V_{DD} - (V_{DD} - V_{G6(min)} - |V_{TP}|) \left[1 - \sqrt{1 - \frac{8I_7}{\beta_6 (V_{DD} - V_{G6(min)} - |V_{TP}|)^2}} \right]$$

$$V_{OL} = V_{SS}$$

$$A_v(0) = \left(\frac{g_{m1}}{g_{ds2} + g_{ds4}} \right) \left(\frac{g_{m6}}{g_{ds6} + g_{ds7}} \right) \quad A_v(s) = \frac{A_v(0)}{\left(\frac{s}{p_1} + 1 \right) \left(\frac{s}{p_2} + 1 \right)}$$

$$\text{Poles: } p_1 = -\frac{1}{C_I(g_{ds2} + g_{ds4})} \quad p_2 = -\frac{1}{C_{II}(g_{ds6} + g_{ds7})}$$

$$v_{in} = V_{TRP} = V_{DD} - |V_{TP}| - \sqrt{\frac{K_N(W/L)_7}{K_P(W/L)_6}} (V_{Bias} - V_{SS} - V_{TN})$$

Slew rate:

$$SR = \frac{I_{tail}}{C_L} \quad GBW = \frac{g_{m1} r_{o2}}{r_{o2} C_L} = \frac{g_{m1}}{C_L}$$

$$\tau = R_{out} \times C_{out} = R_{out} \times \left(C_{gd2} + C_{gd1} \left(1 - \frac{1}{A_v} \right) \right)$$

Propagation time delay:

$$\frac{V_{OH} - V_{OL}}{2} = A_v(0) [1 - e^{-t_p / \tau_c}] V_{in}$$

$$t_p = \Delta T = \frac{\Delta V}{SR} = \frac{V_{OH} - V_{OL}}{2 \cdot SR} = \tau_c \ln \frac{1}{1 - \frac{V_{OH} - V_{OL}}{2A_v(0)V_{in}}}$$

$$V_{in(min)} = \frac{V_{OH} - V_{OL}}{A_v(0)} \text{ where } t_p = \tau_c \ln \frac{1}{1 - \frac{V_{in(min)}}{2V_{in}}} \quad k = \frac{V_{in}}{V_{in(min)}}$$