



UNIVERSITI TUN HUSSEIN ONN MALAYSIA


FINAL EXAMINATION  
SEMESTER II  
SESSION 2023/2024

- COURSE NAME : ELECTRIC CIRCUITS II
- COURSE CODE : BEV10403
- PROGRAMME CODE : BEV
- EXAMINATION DATE : JULY 2024
- DURATION : 3 HOURS
- INSTRUCTIONS :
1. ANSWER ALL QUESTIONS
  2. THIS FINAL EXAMINATION IS CONDUCTED VIA
    - Open book
    - Closed book
  3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES DURING THE EXAMINATION CONDUCTED VIA CLOSED BOOK

THIS QUESTION PAPER CONSISTS OF SIX (6) PAGES

- Q1** (a) An electrical system is modelled by a series second-order RLC circuit with a capacitor valued at 47 nF and an inductor valued at 47 mH. Determine the range of resistor values for the circuit to exhibit an underdamped response. (4 marks)

- (b) Consider the second-order circuit shown in **Figure Q1.1**.

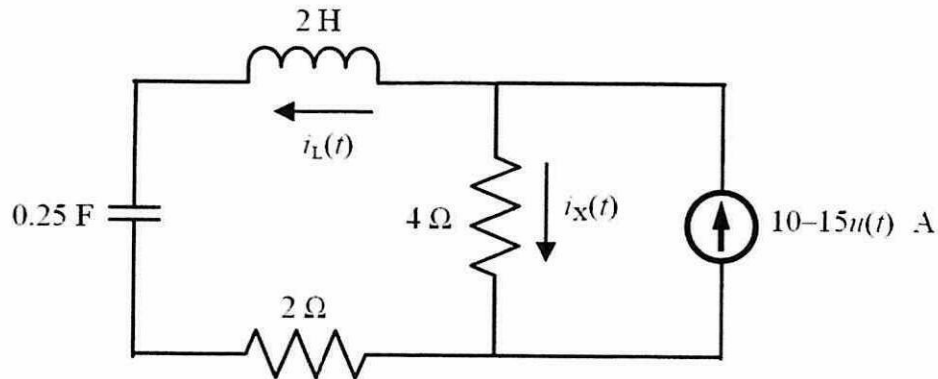

**Figure Q1.1**

- (i) Apply source transformation and determine the mathematical equation of the voltage supply for  $t < 0$  and  $t > 0$ . (2 marks)
- (ii) Determine the roots,  $s_1$  and  $s_2$ , of the characteristic equation for the RLC circuit during  $t > 0$ . (5 marks)
- (iii) Based on the results in **Q2(b)(ii)**, determine the general mathematical expression of the inductor current  $i_L(t)$  for  $t > 0$ . Represents the unknown constant coefficients accordingly, as  $A_1$  and  $A_2$ . (2 marks)
- (iv) Solve for the unknown constant coefficient values of the  $i_L(t)$  expression in **Q2(b)(iii)** using the initial and final conditions. (9 marks)
- (v) Determine the complete expression for the current  $i_x(t)$  for  $t > 0$ . (3 marks)

- Q2 (a) A circuit consisting of a resistor and an inductor is connected in parallel with a capacitor across a supply voltage ( $V_s$ ) with a frequency ( $f$ ), as shown in Figure Q2.1.

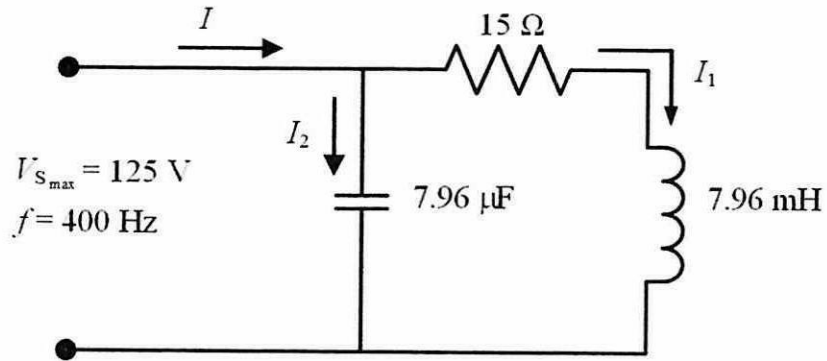


Figure Q2.1

- (i) Convert and draw the circuit into a phasor domain equivalent circuit. (3 marks)
  - (ii) Determine the current in each branch ( $I_1$  and  $I_2$ ) and the current from the supply ( $I$ ) with its phase relative to the supply voltage ( $V_s$ ). (7 marks)
  - (iii) Sketch the phasor diagram of the circuit that includes the supply voltage ( $V_s$ ), the supply current ( $I$ ), and the current in each branch ( $I_1$  and  $I_2$ ). Point out the power factor angle. (5 marks)
- (b) Solve the current  $I_0$  in the circuit of Figure Q2.2 using any analysis technique.


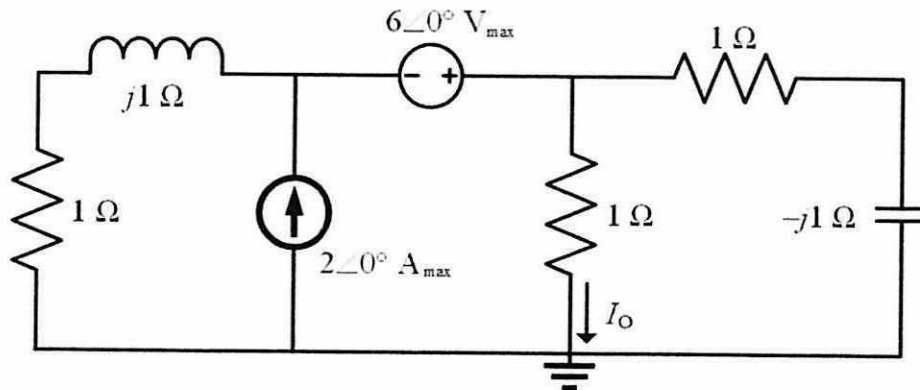


Figure Q2.2

(10 marks)

**Q3** (a) Based on the circuit shown in **Figure Q3.1**.

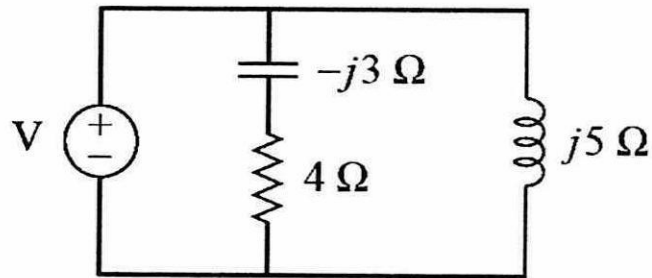

**Figure Q3.1**

- (i) Calculate the complex power (S), real power (P) and reactive power (Q), supplied by the source,  $V = 230\angle 15^\circ \text{ V}_{\text{rms}}$ . (6 marks)
- (ii) Calculate and draw the power triangle of the loads. (4 marks)
- (b) Three loads consisting of 20 kW (resistive), 25 kVAR (inductive) and 10 kVAR (capacitive) are connected to a 230  $\text{V}_{\text{rms}}$ , 50 Hz source. Calculate,
  - (i) The total complex power and power factor of the loads. (3 marks)
  - (ii) The current drawn from the supply. (2 marks)
  - (iii) The value of capacitance required to improve the power factor to 0.95 lagging. (7 marks)
  - (iv) The current drawn from the supply after improving the power factor to 0.95 lagging. (3 marks)

Q4 (a) Define the two-port network.

(2 marks)

(b) Determine the z parameters for the circuit in Figure Q4.1.

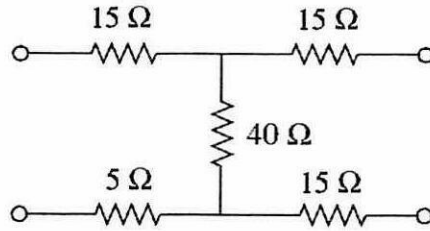


Figure Q4.1

(7 marks)

(c) Refer to the circuit shown in Figure Q4.2.

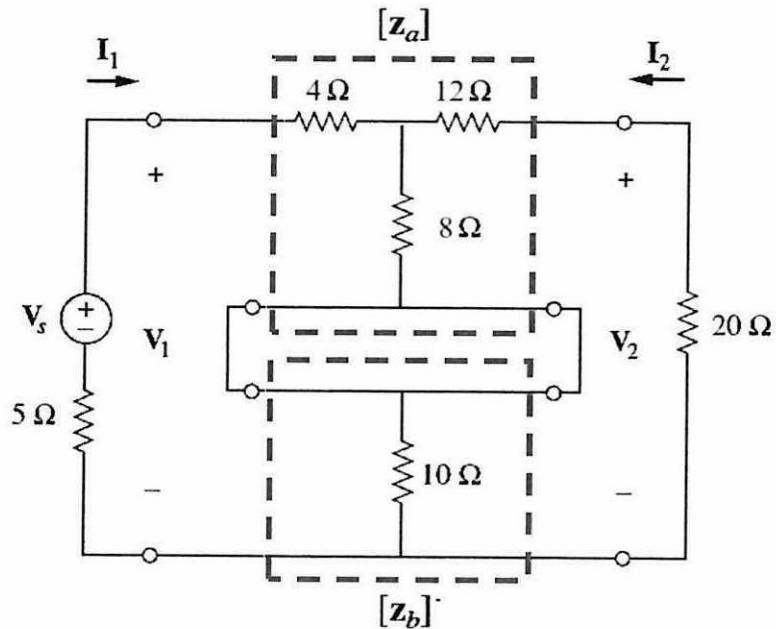


Figure Q4.2

(i) State the types of two-port interconnection configurations of the circuit.

(1 mark)

(ii) Determine  $\frac{V_s}{V_2}$ .

(15 marks)

- END OF QUESTIONS -

**APPENDIX A**

**Table APPENDIX A.1**

System parameter	Type of RLC circuit	
	Series RLC circuit	Parallel RLC circuit
Damping factor	$\alpha = \frac{R}{2L}$	$\alpha = \frac{1}{2RC}$
Resonant frequency	$\omega_o = \frac{1}{\sqrt{LC}}$	$\omega_o = \frac{1}{\sqrt{LC}}$
Damping frequency	$\omega_d = \sqrt{\omega_o^2 - \alpha^2}$	$\omega_d = \sqrt{\omega_o^2 - \alpha^2}$
Roots of the characteristic equation	$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2}$	$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2}$

**Table APPENDIX A.2**

Type of response	Condition
Overdamped	$\alpha > \omega_o$
Critically Damped	$\alpha = \omega_o$
Underdamped	$\alpha < \omega_o$

**Table APPENDIX A.3**

The z parameters for series connection of two two-port networks	$[z] = [z_a] + [z_b]$
The y parameters for parallel connection of two two-port networks	$[y] = [y_a] + [y_b]$
The T parameters for cascade connection of two two-port networks	$[T] = [T_a][T_b]$

**TERBUKA**