



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESSION 2023/2024**

- COURSE NAME : DIGITAL DESIGN
- COURSE CODE : BEJ 30503
- PROGRAMME CODE : BEJ
- EXAMINATION DATE : JULY 2024
- DURATION : 3 HOURS
- INSTRUCTIONS :
1. ANSWER ALL QUESTIONS FROM PART A AND ONE QUESTION FROM PART B
  2. THIS FINAL EXAMINATION IS CONDUCTED VIA
    - Open book
    - Closed book
  3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES

THIS QUESTION PAPER CONSISTS OF **EIGHT (8)** PAGES

**CONFIDENTIAL**

**TERBUKA**

## PART A

**Q1** Digital design is a process of designing a digital system from specifications rather than by using a general-purpose processor.

- (a) Discuss the advantage of digital design as compared to general-purpose processors in specific application such as video processing.

(4 marks)

- (b) Computer-Aided Design (CAD) tools not only simplifies the design process but also allows for designing complex digital systems. However, explain why the designer must have an in-depth understanding of the relevant theories and design methodologies to design a circuit effectively rather than only relying on CAD tools.

(4 marks)

- (c) Field Programmable Gate-Array (FPGA) is very popular for fast prototyping of digital circuits as it supports the implementation of relatively large logic circuits. In FPGA, the logics are implemented using the Look-up Table (LUT). Explain the advantage of using LUT instead of using the AND or the OR planes.

(2 marks)

**Q2** Verilog HDL is a hardware description language used to model and design digital systems. It's widely used in digital design, particularly for describing and simulating electronic systems at the register-transfer level (RTL) of abstraction.

- (a) With a suitable example, explain Verilog modelling styles in describing digital circuits.

(9 marks)

- (b) **Figure Q2.1** shows the Verilog program describing a digital circuit. Rewrite the program by using behavioural modelling.

```
module Q2b(En, w, y);
    input En;
    input [1:0]w;
    output [0:3]y;

    and(y[0], En, ~w[1], ~w[0]);
    and(y[1], En, ~w[1], w[0]);
    and(y[2], En, w[1], ~w[0]);
    and(y[3], En, w[1], w[0]);
endmodule
```

**Figure Q2.1**

(8 marks)

- (c) A combinational logic module, **Q2c**, is described by the Verilog code in **Figure Q2.2**. It comprises a logic component, **Q2slice**.

```

module Q2c(in3, in2, in1, in0, flag, out3, out2, out1, out0);
  input in3, in2, in1, in0;
  output flag, out3, out2, out1, out0;
  wire co0, co1;

  Q2slice M0(in3, in0, in3, out0, co0);
  Q2slice M1(in3, in1, co0, out1, co1);
  Q2slice M2(in3, in2, co1, out2, flag);

  assign out3 = in3;
endmodule

module Q2slice(in3, ini, bi, s, co);
  input in3, ini, bi;
  output s, co;
  wire ai;
  assign ai = in3 ^ ini;
  assign s = ai ^ bi;
  assign co = ai & bi;
endmodule

```

**Figure Q2.2**

- (i) Sketch the logic circuit of **Q2slice** component. (4 marks)
- (ii) Draw the Functional Block Diagram (FBD) of module **Q2c**, showing how the **Q2slice** components are interconnected. (7 marks)
- (iii) If the input vector, ( $in3, in2, in1, in0$ ) is 0101, what is the value of the output vector, ( $flag, out3, out2, out1, out0$ )? (2 marks)

**Q3** **Figure Q3.1** shows an adder-subtractor circuit, where FA is a full adder module. From the figure, answer the following questions:

- (a) Explain how the addition or subtraction is implemented. (4 marks)
- (b) Given  $a = 1011$ ,  $b = 0001$  and  $c_{in} = 1$ , determine the value of  $s$  and  $c_{out}$ . Furthermore, verify your answer by providing the calculation in decimal. (3 marks)

(c) From the circuit, explain how to generate the overflow signal.

(3 marks)

 


Figure Q3.1

**Q4** Figure Q4.1 shows a Verilog program describing a sequential circuit. By referring to the program, answer questions Q4(a) to Q4(c):

(a) Name the assignment type (*blocking* or *non-blocking*) that is used in the code, i.e., in the “Q1 <= D” statement.

(2 marks)

(b) Draw the circuit that is synthesized from the codes.

(6 marks)

(c) Draw the output signal at Q1, Q2 and Q3 based on the timing diagram given in Figure Q4.2.

(6 marks)

```

module Q4c(clk, D, Q1, Q2, Q3);
  input clk, D;
  output reg Q1, Q2, Q3;
  always@(posedge clk)
  begin
    Q1 <= D;
    Q2 <= Q1;
    Q3 <= Q2;
  end
endmodule

```

Figure Q4.1

 


Figure Q4.2

- (d) **Figure Q4.3** shows a Verilog program describing an 8-bit register with synchronous reset signal. A timing diagram in **Figure Q4.4** showing the input data at *A*. Based on the timing diagram, draw the output signal *Q*.

```

module Q4d(clk, rst, A, Q);
  input clk, rst;
  input [7:0] A;
  output reg [7:0] Q;

  always@(posedge clk)
    if (rst)
      Q <= 0;
    else
      Q <= A;
endmodule

```

Figure Q4.3

 


Figure Q4.4

(4 marks)

- (e) For the circuit in **Figure Q4.5**, determine the output  $Q$  at the next positive clock edge if  $L = 1$ ,  $w = 1$ , and  $R = 1011$ .

 


Figure Q4.5

(2 marks)

PART B

**Q5** Figure Q5.1 shows a datapath and a controller of a digital system, containing two 8-bit registers *R0* and *R1*, an Adder-Subtractor circuit, and a 1KB memory. The controller is used to control the operation of the datapath. The *start* signal is asserted to start the operation, while the *done* signal is used to indicate the completion of the operation.

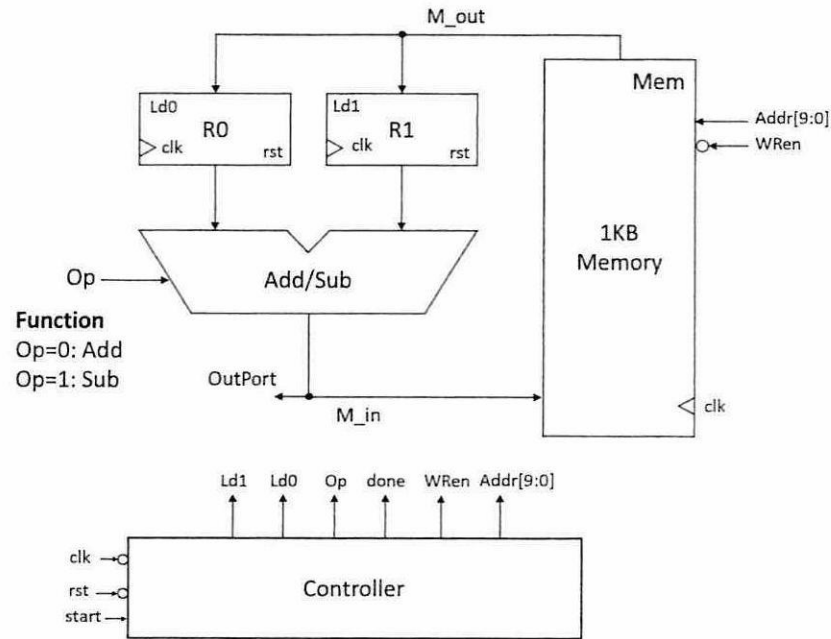


Figure Q5.1

- (a) Write a Verilog program to describe the datapath circuit. (10 marks)
  
- (b) Derive the RTL codes to represent the operations below:
  1. Load the data from memory location 0x100 into *R0*.
  2. Load the data from memory location 0x200 into *R1*.
  3. Add the content of *R1* and *R2* and the result is then stored in memory location 0x100.(5 marks)
  
- (c) Derive the Algorithmic State Diagram (ASM) chart to implement the operation in Q5(b). (8 marks)
  
- (d) Draw the functional block diagram (FBD) of the controller by showing the state register, input, and output signals. (7 marks)

- Q6** A fully dedicated architecture (FDA) that implement the following computation is to be designed.

$$y = \sum_{i=1}^4 c_i x_i$$

- (a) Draw the data flow graph for the FDA. (5 marks)
- (b) Derive the as-late-as-possible (ALAP) schedule, and resource allocation for a minimum hardware implementation. (10 marks)
- (c) Derive the RTL codes for your design. (7 marks)
- (d) From the RTL codes in **Q6(c)**, draw and label the FBD of the datapath of the design. (8 marks)

- END OF QUESTIONS -