



**UTHM**  
Universiti Tun Hussein Onn Malaysia

**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESSION 2023/2024**

- COURSE NAME** : TRANSFORM CIRCUIT
- COURSE CODE** : BEV 20203
- PROGRAMME CODE** : BEV
- EXAMINATION DATE** : JULY 2024
- DURATION** : 3 HOURS
- INSTRUCTIONS** :
1. ANSWER ALL QUESTIONS
  2. THIS FINAL EXAMINATION IS CONDUCTED VIA
    - Open book
    - Closed book
  3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES DURING THE EXAMINATION CONDUCTED VIA CLOSED BOOK

THIS QUESTION PAPER CONSISTS OF EIGHT (8) PAGES

**TERBUKA**

**CONFIDENTIAL**

**PART A**


**Q1** (a) Consider the following function.

$$f(t) = u(t - 1) - u(t - 3)$$

(i) Sketch the graph of the function. (2 marks)

(ii) Write the piecewise function. (2 marks)

(b) Consider the two signals shown in **Figure Q1(b)**. where  $y(t) = x_1(t) * x_2(t)$ .

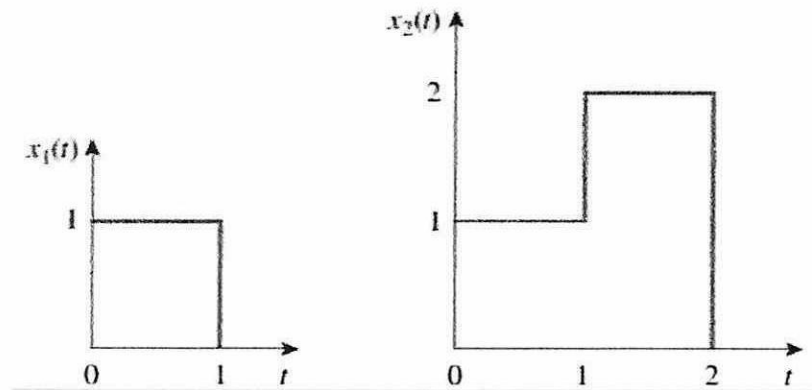

**Figure Q1(b)**

(i) Convolve  $x_1(t)$  and  $x_2(t)$  Graphically. Show step by step of the convolution to determine output signal,  $y(t)$ . (12 marks)

(ii) Write the piecewise function,  $y(t)$ . (2 marks)

(iii) Sketch the output signal. (2 marks)


(c) Please refer to **APPENDIX B**, determine the Inverse Laplace Transformation of the following functions.

(i)  $F(s) = 5 + \frac{6}{s+4} - \frac{7s}{s^2+25}$  (2 marks)

(ii) 
$$F(s) = \frac{3}{s} - \frac{5}{s+1} + \frac{6}{s^2+4}$$

(3 marks)

- Q2** (a) Consider the circuit shown in **Figure Q2(a)**. Since the input voltage is multiplied by  $u(t)$ , the voltage source is a short for all  $t < 0$  and  $i_L(0) = 0$  A.

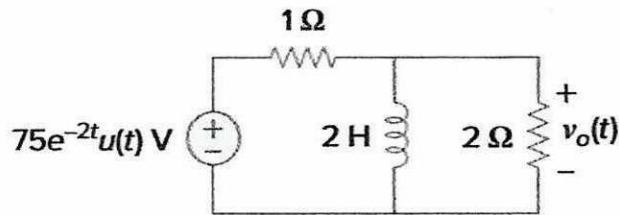

**Figure Q2(a)**

- (i) Draw the circuit in s-domain. (2 marks)
  - (ii) Determine  $V_o(s)$ . (4 marks)
  - (iii) Find  $v_o(t)$ . (4 marks)
- (b) Considering  $i_L(0) = 1$  A in **Q2(a)**,
- (i) Draw the circuit in s-domain. (2 marks)
  - (ii) Determine  $V_o(s)$ . (8 marks)
- (c) The output of a linear system is  $y(t) = 10e^{-t} \cos 4t u(t)$  when the input is  $x(t) = e^{-t} u(t)$ . Calculate:
- (i) Transfer function,  $H(s)$  of the system. (4 marks)
  - (ii) Impulse response,  $h(t)$ . (1 mark)

TERBUKA

**Q3** Bode plots show the frequency response, that is, the changes in magnitude and phase as a function of frequency. This is done on two semi-log scale plots. The top plot is typically magnitude or “gain” in dB. The bottom plot is phase, most commonly in degrees.

- (a) Draw the magnitude and phase plots (Bode plot) of the following transfer function using the logarithmic graph paper provided.

$$H(s) = \frac{800s}{(s + 20)(s + 400)}$$

(15 marks)

- (b) In Fourier series circuit analysis, voltage and current source is given in periodic function. Draw one (1) odd symmetric periodic function and one (1) even symmetric periodic function.

(4 marks)

- (c) Fourier series of a periodic signal is given as below, plot the amplitude and phase spectra for  $n = 1, 3$  and  $5$ .

$$f(t) = \sum_{n=\text{odd}}^{\infty} \frac{2}{n\pi} \cos(n\pi t - 90^\circ)$$

(6 marks)

**Q4** The Fourier Series Equation is given as:

$$f(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t)$$

$$a_0 = \frac{1}{T} \int_0^T f(t) dt, \quad a_n = \frac{2}{T} \int_0^T f(t) \cos n\omega_0 t dt, \quad b_n = \frac{2}{T} \int_0^T f(t) \sin n\omega_0 t dt,$$

where  $a_0, a_n$  and  $b_n$  are Fourier coefficients.

- (a) Determine the Fourier series expansion of the backward sawtooth waveform of **Figure Q4(a)**.

(6 marks)

TERBUKA



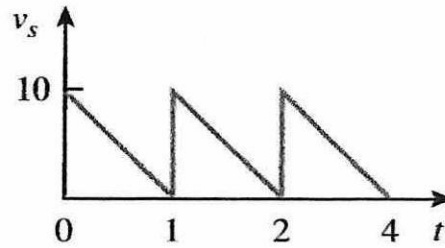


Figure Q4(a)

- (b) The voltage source of the circuit in **Figure Q4(b)** is  $v_s(t) = 5 + \sum_{n=1}^{\infty} \frac{10}{n\pi} \sin 2n\pi t$ , determine the response  $i_o(t)$  of the circuit.

(10 marks)

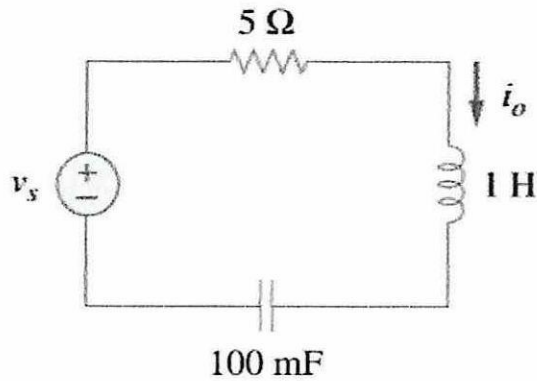


Figure Q4(b)

- (c) The input currents of the circuit in **Figure Q4(c)** is  $i(t) = 20 + 16 \cos(10t + 45^\circ)$ . Calculate the resistor voltage,  $v(t)$  and average power dissipated in the resistor,  $P$  [W].

(9 marks)

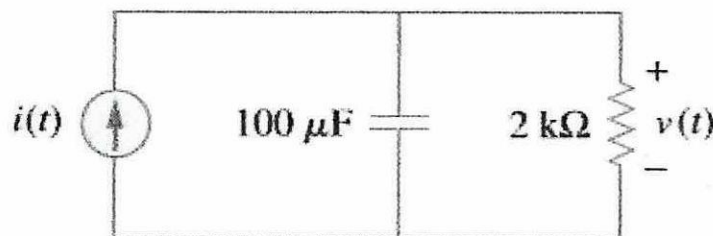


Figure Q4(c)

TERBUKA

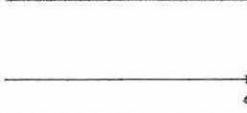
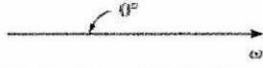
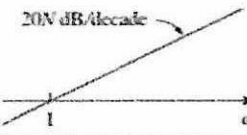

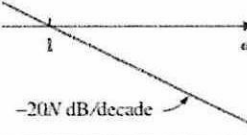
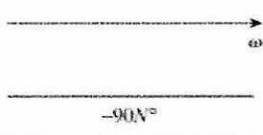
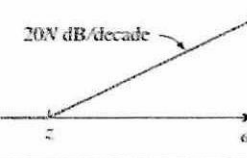
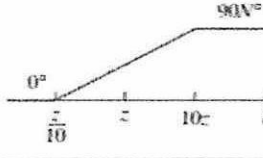
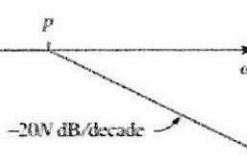
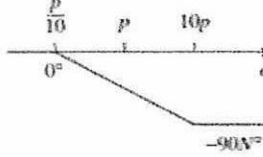
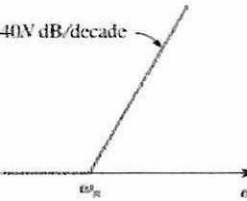
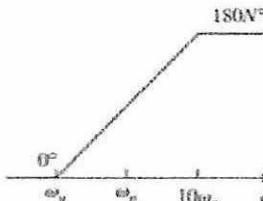
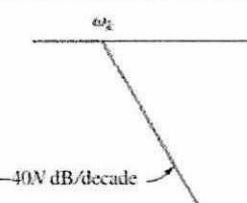
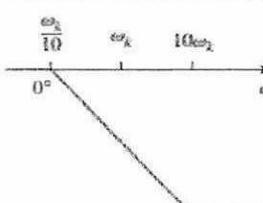
**- END OF QUESTIONS -**

**TERBUKA**

Handwritten text, possibly a signature or date, located in the bottom right area of the page.

APPENDIX A

Table APPENDIX A.1

Factor	Magnitude	Phase
$K$	$20 \log_{10} K$ 	$0^\circ$ 
$(j\omega)^N$	$20N \text{ dB/decade}$ 	$90N^\circ$ 
$\frac{1}{(j\omega)^N}$	$-20N \text{ dB/decade}$ 	$-90N^\circ$ 
$\left(1 + \frac{j\omega}{z}\right)^N$	$20N \text{ dB/decade}$ 	$0^\circ$ to $90N^\circ$ 
$\frac{1}{(1 + j\omega/p)^N}$	$-20N \text{ dB/decade}$ 	$0^\circ$ to $-90N^\circ$ 
$\left[1 + \frac{2j\omega\zeta}{\omega_n} + \left(\frac{j\omega}{\omega_n}\right)^2\right]^N$	$40N \text{ dB/decade}$ 	$0^\circ$ to $180N^\circ$ 
$\frac{1}{[1 + 2j\omega\zeta/\omega_k + (j\omega/\omega_k)^2]^N}$	$-40N \text{ dB/decade}$ 	$0^\circ$ to $-180N^\circ$ 

TERBUKA

**APPENDIX B**

**Table APPENDIX B.1**

$f(t)$	$F(s)$	$f(t)$	$F(s)$
$\delta(t)$	1	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
$u(t)$	$\frac{1}{s}$	$\sin(\omega t + \theta)$	$\frac{s \sin \theta + \omega \cos \theta}{s^2 + \omega^2}$
$e^{-at}$	$\frac{1}{s + a}$	$\cos(\omega t + \theta)$	$\frac{s \cos \theta - \omega \sin \theta}{s^2 + \omega^2}$
$t$	$\frac{1}{s^2}$	$e^{-at} \sin \omega t$	$\frac{\omega}{(s + a)^2 + \omega^2}$
$t^n$	$\frac{n!}{s^{n+1}}$	$e^{-at} \cos \omega t$	$\frac{s + a}{(s + a)^2 + \omega^2}$
$te^{-at}$	$\frac{1}{(s + a)^2}$		
$t^n e^{-at}$	$\frac{n!}{(s + a)^{n+1}}$		
$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$		

*\*Defined for  $t \geq 0$ ;  $f(t) = 0$ , for  $t < 0$ .*

**TERBUKA**

CONFIDENTIAL