

**CONFIDENTIAL**



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESSION 2023/2024**

- COURSE NAME : ELECTRIC AND ELECTRONICS TECHNOLOGY
- COURSE CODE : BDA 14303
- PROGRAMME CODE : BDD
- EXAMINATION DATE : JULY 2024
- DURATION : 3 HOURS
- INSTRUCTIONS :
1. PART A: ANSWER **ONE (1)** QUESTION FROM TWO (2) QUESTIONS ONLY.  
PART B: ANSWER ALL QUESTIONS.
  2. THIS FINAL EXAMINATION IS CONDUCTED VIA  
 Open book  
 Closed book
  3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES

THIS QUESTION PAPER CONSISTS OF **TEN (10)** PAGES

**TERBUKA**

**CONFIDENTIAL**

**PART A: ANSWER ONE QUESTION ONLY**

**Q1** Mesh and nodal analysis are two methods used in electrical engineering to analyse circuits.

(a) As shown in **Figure APPENDIX A.1** use mesh analysis to find  $V_o$ .  
(10 marks)

(b) Explain the purpose of nodal analysis in electrical circuits.  
(2 marks)

(c) Using nodal analysis, determine the voltage across the resistor  $R_2$  as shown in **Figure APPENDIX B.1**.  
(8 marks)

**Q2** Please answer the following questions.

(a) As shown in **Figure APPENDIX C.1** calculate the current  $I_x$  and  $I_y$  in the following circuit using mesh analysis.  
(10 marks)

(b) Based on **Figure APPENDIX D.1**, find  $V_o$  using nodal analysis.  
(10 marks)

**PART B: ANSWER ALL QUESTIONS**

**Q3** Please answer the following questions

(a) Calculate the current flowing through  $20\Omega$  as shown in **Figure APPENDIX E.1** using the superposition principle.  
(10 marks)

(b) Based on **Figure APPENDIX F.1**:

(i) Determine the equivalent circuit to the left of the terminals a-b in the circuit using Thevenin's theorem.  
(8 marks)

(ii) Identify the current through  $R_L$ .  
(2 marks)

**TERBUKA**

- Q4** Capacitors and inductors are electronic components that can store energy.
- (a) Identify the capacitance of the single capacitor which is equal to the equivalent to the capacitance of the circuit in Figure **APPENDIX G.1**.  
(5 marks)
  - (b) Find  $V_c$ ,  $i_L$  and the energy stored in the capacitor and inductor in the circuit of **Figure APPENDIX H.1** under DC condition.  
(7 marks)
  - (c) The switch in **Figure APPENDIX I.1** has been closed for a long time, and it is opened at  $t=0$ . Determine  $V(t)$  for  $t \geq 0$ .  
(8 marks)
- Q5** Refer to **Figure APPENDIX J.1**, a  $50 \Omega$  resistor (R), a 0.1 H inductor (L) and a  $50 \mu\text{F}$  capacitor (C) are connected in series to a 50 Hz source (V). The RMS current,  $I_{\text{RMS}}$  in the circuit is 2A.
- (a) Determine the total circuit impedance.  
(7 marks)
  - (b) Identify the rms voltage across the resistor, inductor, capacitor and the RLC combination.  
(5 marks)
  - (c) Calculate the power factor.  
(2 marks)
  - (d) Sketch the phasor diagram for this circuit.  
(4 marks)
  - (e) Explain the relationship between the total current and the voltage supply.  
(2 marks)
- Q6** Please answer the following questions.
- (a) State two (2) differences between AC motor and DC motor.  
(4 marks)
  - (b) An ideal transformer is rated at 2400/120V, 9.6kVa and has 50 turns on the secondary side. Calculate:
    - (i) The turn ratio.  
(2 marks)

**TERBUKA**

- (ii) The number of turn on the primary side. (2 marks)
- (iii) The current rating for primary and secondary winding. (2 marks)
- (c) Construct the truth table describing the output of the circuit described by the logic diagram in **Figure APPENDIX K.1** and write the Boolean expression. (10 marks)

- END OF QUESTIONS -

**TERBUKA**



APPENDIX A

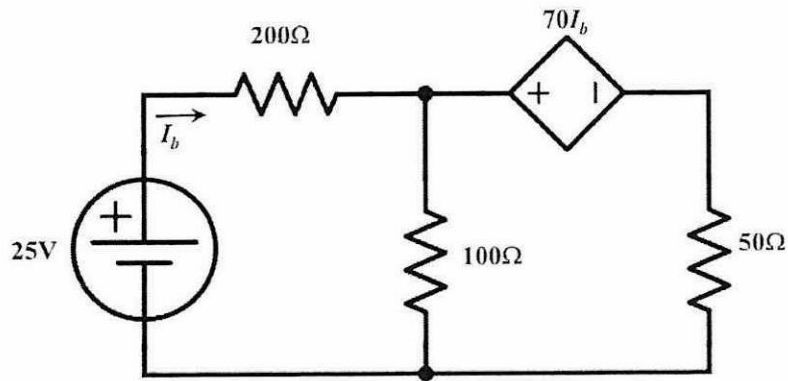


Figure APPENDIX A.1

APPENDIX B

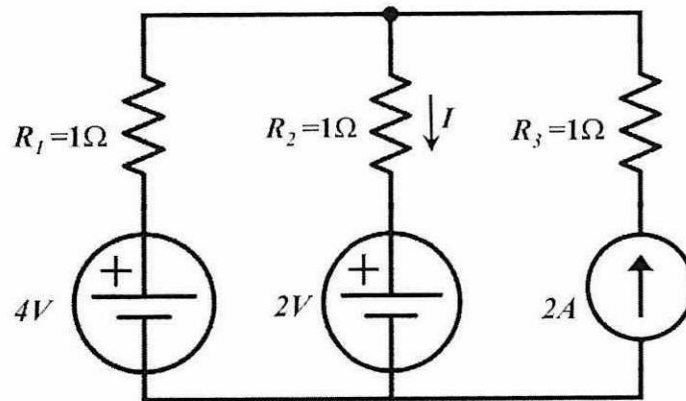


Figure APPENDIX B.1

APPENDIX C

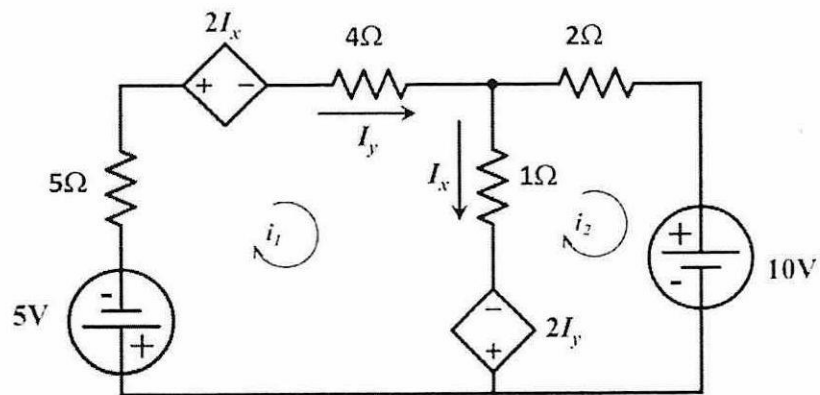


Figure APPENDIX C.1

APPENDIX D

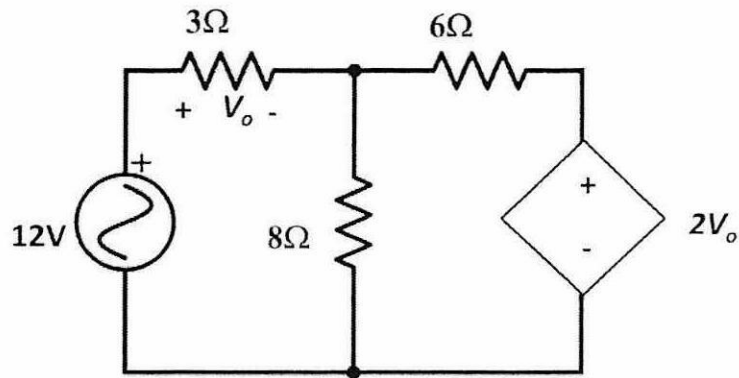


Figure APPENDIX D.1

APPENDIX E

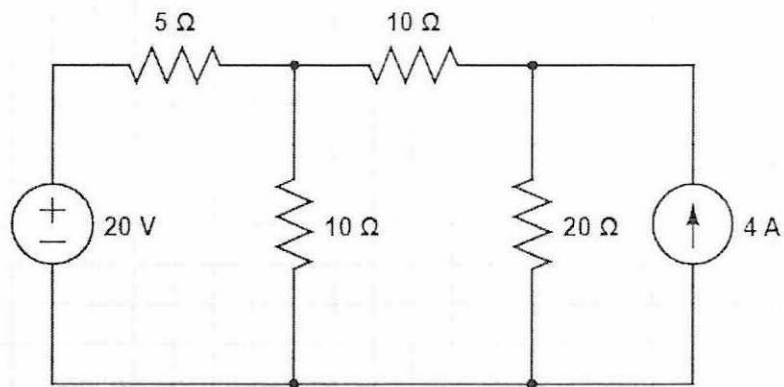


Figure APPENDIX E.1

APPENDIX F

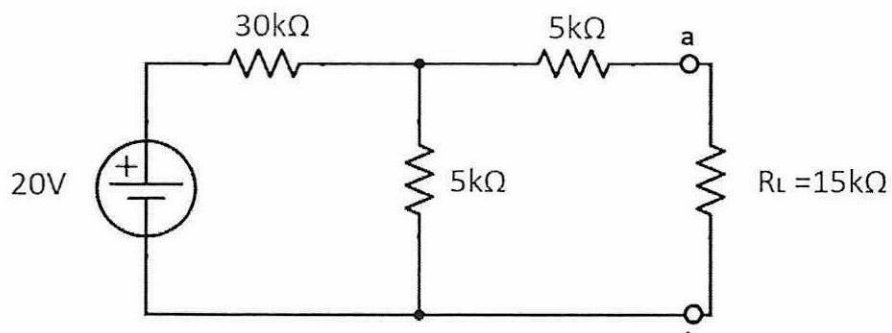


Figure APPENDIX F.1

APPENDIX G

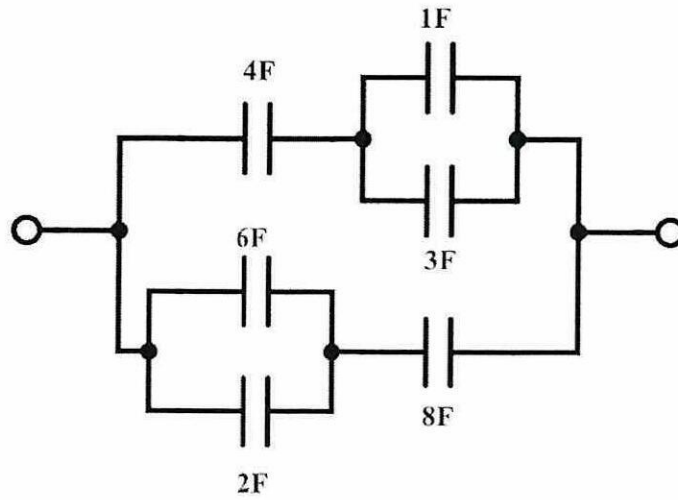


Figure APPENDIX G.1

APPENDIX H

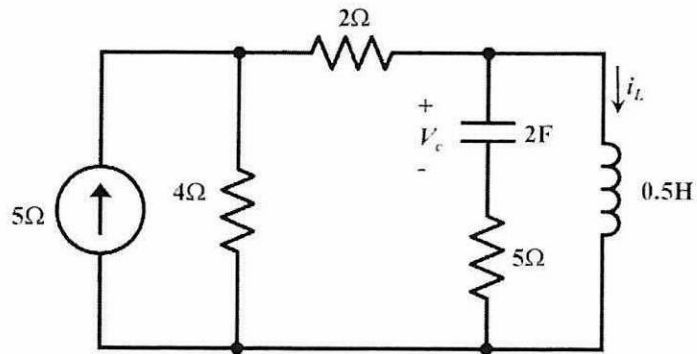


Figure APPENDIX H.1

APPENDIX I

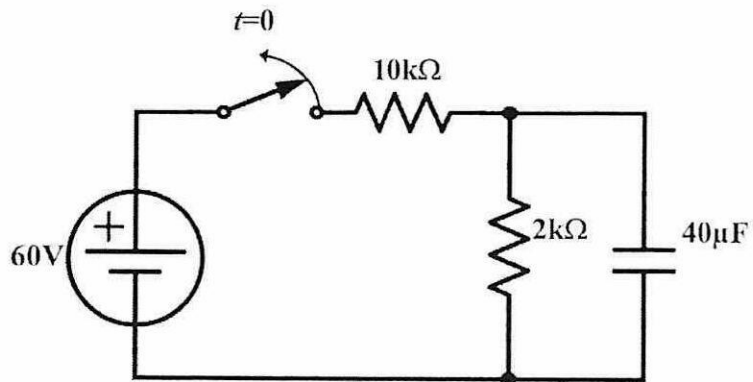


Figure APPENDIX I.1

APPENDIX J

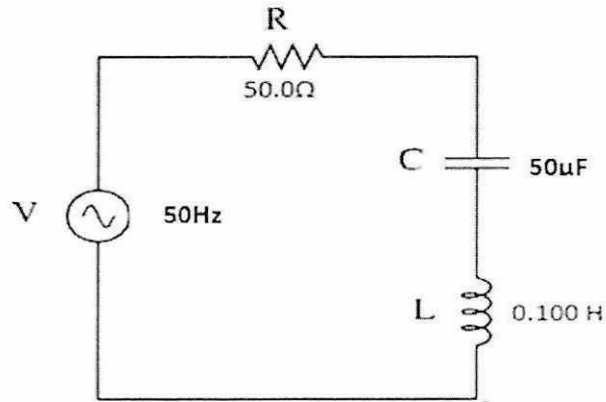


Figure APPENDIX J.1

APPENDIX K

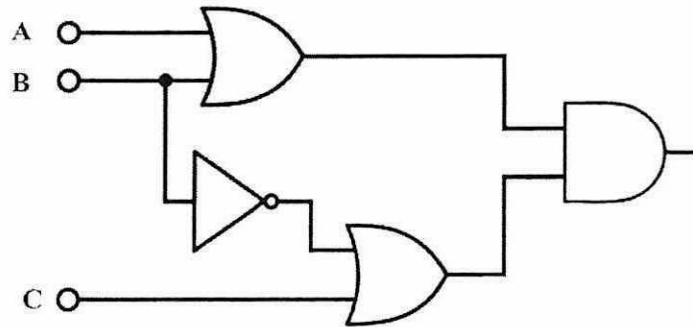


Figure APPENDIX K.1

**TERBUKA**



APPENDIX L

LIST OF FORMULA


**OHMS LAW**  
 $V = IR$

**JOULE'S LAW**  
 $P = IV$

**KIRCHHOFF LAW**  $\sum_{k=1}^n i_k = 0$

$\sum_{v=1}^n v_k = 0$

**WYE-DELTA TRANSFORMATION**

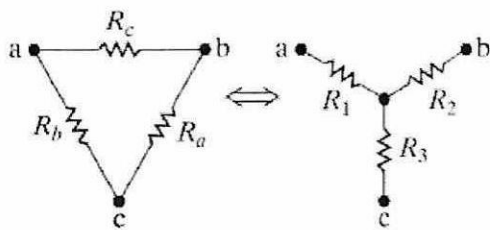


$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} \quad R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} \quad R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} \quad R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

**SOURCE TRANSFORMATION**

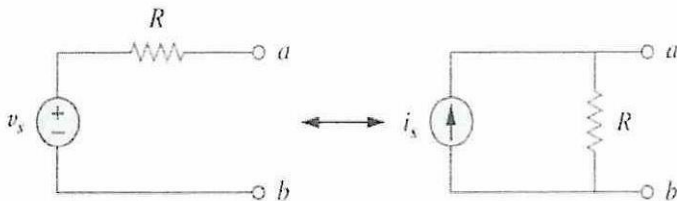

$V_S = I_S R$

**THEVENIN AND NORTON EQUIVALENT CIRCUIT**

$R_{TH} = R_N$

$I_N = \frac{V_{TH}}{R_{TH}}$

$P = i^2 R_L = \left( \frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$

When  $R_L \neq R_{TH}$

$P_{max} = \frac{V_{TH}^2}{4R_{TH}}$

When  $R_L = R_{TH}$

**TERBUKA**

## CAPACITOR AND INDUCTOR

$$C = \frac{\epsilon A}{d}$$

$$i = C \frac{dv}{dt}$$

$$L = \frac{N^2 \mu A}{l}$$

$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

$$\tau = RC$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt + v(t_0)$$

$$w = \frac{1}{2} C v^2$$

$$v = L \frac{di}{dt}$$

$$w = \frac{1}{2} L i^2$$

$$\tau = \frac{L}{R}$$

## ALTERNATING CURRENT POWER CALCULATION

$$P(t) = v(t)i(t)$$

Instantaneous power

$$P = \frac{1}{2} \operatorname{Re}[VI^*] = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

Average power

$$i_{RMS} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

$$P_{RMS} = I_{RMS}^2 R = \frac{V_{RMS}^2}{R}$$

## TRANSFORMERS

$$\frac{V_P}{V_S} = \frac{N_P}{N_S}$$

TERBUKA