

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2017/2018**

COURSE NAME : ELECTRICAL TECHNOLOGY
COURSE CODE : DAE 11003
PROGRAMME CODE : DAE
EXAMINATION DATE : JUNE / JULY 2018
DURATION : 2 HOURS 30 MINUTES
INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS ONLY

TERBUKA

THIS QUESTION PAPER CONSISTS OF **ELEVEN (11)** PAGES

CONFIDENTIAL

UNIVERSITI TUN HUSSEIN ONN MALAYSIA
JALAN BINA 1
75450 KAMPUNG BANGSA
SEREMBAN, NEGERI SEMBILAN
75000
TEL: 06-733 3111
FAX: 06-733 3112
WWW.UTHM.MY

- Q1**
- (a) List **three (3)** particles in an atom (3 marks)
 - (b) The amount of electrons that flow through a wire in 50 ms is 6.87×10^8 C. Calculate the current in amperes. (2 marks)
 - (c) Find the total conductance, G for each of the following resistances values:
 - (i) 2 k Ω resistor and 4 k Ω resistor connected in series. (2 marks)
 - (ii) 10 Ω resistor and 20 Ω resistor connected in parallel. (2 marks)
 - (d) Determine the voltage of a battery that uses 1000 J of energy to move 25C of charge through a resistor. (2 marks)
 - (e) A portable player of MP3 using a 12 V, 4.5 Ah rechargeable battery. It can operate for a period of 6.5 hours.
 - (i) Find the current drawn from the battery during this period. (2½ marks)
 - (ii) Determine the amount of charge delivered by the battery in Coulombs. (2½ marks)
 - (f) Referring to **Figure Q1(f)**,
 - (i) Calculate the currents i, i_1 , and i_2 . (4 marks)
 - (ii) Determine the voltages at V_1 , V_2 , V_3 , V_4 and V_5 using current and voltage divider formulas. (5 marks)

TERBUKA

- Q2** (a) Three resistors R_1 , R_2 and R_3 are connected in series with a 20 V source. The value of resistor R_1 is 4 k Ω , the voltage across resistor R_2 is 10 V and the current flowing through resistor R_3 is 2 mA.
- (i) Draw the circuit. (1 mark)
 - (ii) Determine the value of voltage across resistor R_1 . (1½ marks)
 - (iii) Calculate the value of resistors R_2 and R_3 . (3½ marks)
- (b) A parallel combination of two 50 Ω resistors and a resistor R_1 , is connected in series with a 10 Ω resistor. A 20 V supply is applied across the circuit and 1.5 A of current is measured flowing out of the voltage supply.
- (i) Draw the circuit. (1½ marks)
 - (ii) Calculate the values of resistor R_1 . (4½ marks)
- (c) Referring to **Figure Q2(c)**, Calculate the values of currents I_R , I_{2R} , I_{3R} and I_{4R} . (9 marks)
- (d) Determine the minimum value of 100 Ω rheostat in **Figure Q2(d)** that can be adjusted before the fuse of 0.5 A blows. (4 marks)
- Q3** (a) Four batteries which are connected in series produce 20 mA in the circuit. Each of the battery has the voltage of 9 V. Determine the power in the circuit. (3 marks)
- (b) Referring to the circuit in **Figure Q3(b)**, determine the followings:
- (i) Construct the table for 10 sets of values for resistance, R and current, I. (5 marks)
 - (ii) Sketch a graph of current, I versus resistance, R based on your answer in **Q3(b)(i)** above. (4 marks)
 - (iii) Write the conclusion based on your answer in **Q3(b)(ii)**. (4 marks)

TERBUKA

1. A. 11003/11003
2. A. 11003/11003
3. A. 11003/11003
4. A. 11003/11003
5. A. 11003/11003

- (c) Referring to **Figure Q3(c)**, given that the total power, $P_T = 24.5 \text{ mW}$, the total resistance, $R_T = 8 \text{ k}\Omega$, and the currents, $I_4 = 0.8 \text{ mA}$, $I_3 = 0.4 \text{ mA}$, $I_2 = 0.25 I_1$. Calculate the values of resistance, R_1 , R_2 , R_3 and R_4 .
(9 marks)

Q4 (a) A magnetic field has the cross-sectional area of 1.9 m^2 and the magnetic flux is $1300 \text{ }\mu\text{Wb}$. Calculate the flux density.
(2 marks)

(b) The current flowing through 15 turns of wire is 6 A. Determine the following:

(i) Magnetomotive force (m.m.f) (2 marks)

(ii) Reluctance of the circuit if the flux is $500 \text{ }\mu\text{Wb}$
(2 marks)

(c) By referring to **Figure Q4(c)**, determine the followings:

(i) Magnetizing force (H) (4 marks)

(ii) Magnetic flux (Φ) (7 marks)

(iii) Magnetic flux density (B) (2 marks)

(d) Determine the flux established in the magnetic path of **Figure Q4(d)**, if the reluctance of the material is $28 \times 10^3 \text{ At/Wb}$.
(2 marks)

(e) By Referring to **Figure Q4(e)**, determine the following:

(i) Flux density in the core.
(2 marks)

(ii) Show the north and south poles of the magnet
(2 marks)

TERBUKA

- Q5** (a) Determine the turns ratio of the transformer having 150 turns in its primary winding and 600 turns in its secondary winding. (2 marks)
- (b) The primary winding of a transformer has 1500 V across it. Calculate the secondary voltage if the turns ratio is 0.125. (2 marks)
- (c) Given a transformer with the input power to the primary is 150 W. If 10.5 W are dissipated in the winding resistances, calculate the output power to the load. Neglecting any other losses. (2 marks)
- (d) Determine the value to which R_L must be adjusted in **Figure Q5(d)** for maximum power transfer. The internal resistance of the source is 100Ω . (3 marks)
- (e) Determine the phase of the primary voltage with respect to the secondary voltage for each transformer in **Figure Q5(e)(i), (ii) and (iii)** (4 marks)
- (f) Complete the following questions:
- (i) Calculate the mutual inductance (L_M) when $k = 0.5$, $L_1 = 2.5 \mu\text{H}$ and $L_2 = 8 \mu\text{H}$. (2 marks)
- (ii) Calculate the coefficient of coupling (k), when $L_M = 2 \mu\text{H}$, $L_1 = 6 \mu\text{H}$ and $L_2 = 3.5 \mu\text{H}$. (2 marks)
- (f) Determine the following quantities by referring to **Figure Q5(g)** :
- (i) Primary current, I_P . (2 marks)
- (ii) Secondary current, I_S . (2 marks)
- (iii) Secondary voltage, V_S . (2 marks)
- (iv) Power in load, P_L . (2 marks)

TERBUKA

Q6 (a) Determine the frequency for the following angular velocity:

- (i) 1256 rad/s
- (ii) 68 rad/s

(2 marks)

(b) Solve the following complex numbers in rectangular form:

(i) $\frac{25\angle 60^\circ}{3 - j4} + j8$

(2 marks)

(ii) $21 + (8\angle 30^\circ)(5 - j10)$

(2 marks)

(iii) $3 + \frac{4 + j5}{5 - j8}$

(2 marks)

(c) In the linear circuit, the voltage source is $V_s = 20 \sin(10^5 t + 60^\circ)$ V. Determine the followings:

(i) Angular frequency of the voltage. (1 mark)

(ii) Frequency of the source. (2 marks)

(iii) Period of the voltage. (2 marks)

(d) Given the complex impedances $Z_1 = 3 + j4$ and $Z_2 = -12 + j5$, calculate:

(i) $\frac{Z_1 + Z_2}{Z_1 - Z_2}$

(ii) $Z_1 Z_2$

(iii) $\frac{Z_1}{Z_2}$

(6 marks)

(e) A sinusoidal current has an rms value of 7 mA. Determine the following values:

(i) I_{peak}, I_p (2 marks)

(ii) $I_{\text{average}}, I_{\text{ave}}$ (2 marks)

(iii) $I_{\text{peak to peak}}, I_{p-p}$ (2 marks)

TERBUKA

- END OF QUESTION-

FINAL EXAMINATION

SEMESTER/SESSION : II/2017/2018
COURSE : ELECTRICAL TECHNOLOGY

PROGRAMME : DAE
COURSE CODE : DAE 11003

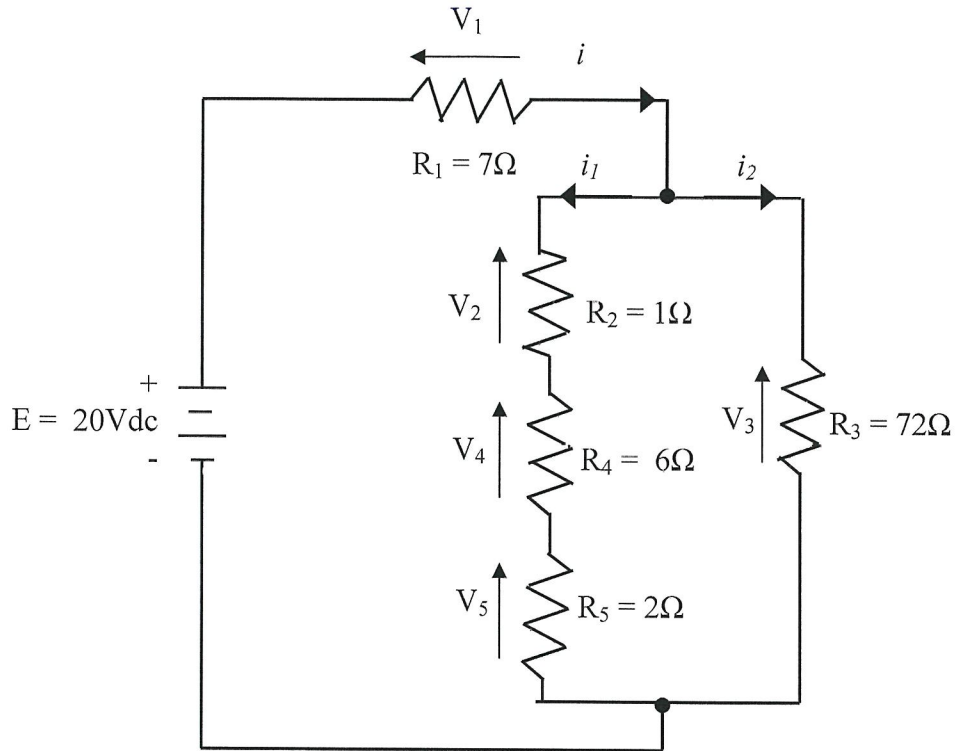


Figure Q1(f)

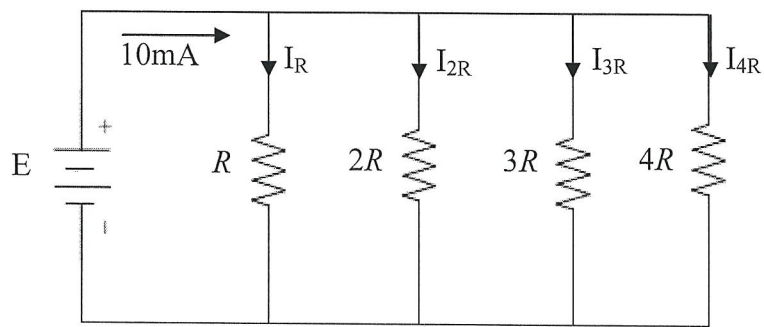


Figure Q2(c)

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION : II/2017/2018
COURSE : ELECTRICAL TECHNOLOGY

PROGRAMME : DAE
COURSE CODE : DAE 11003

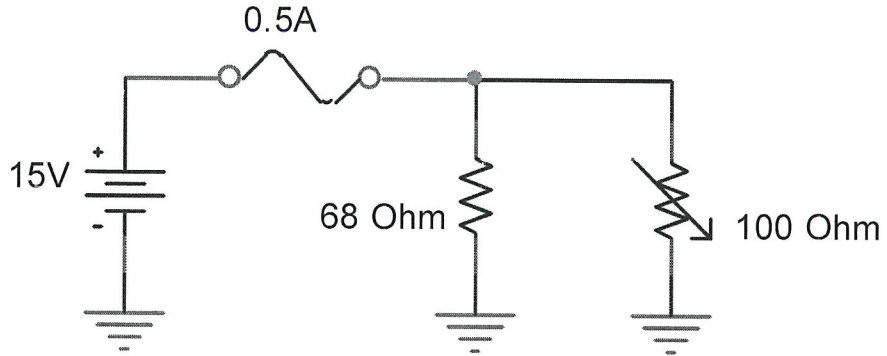


Figure Q2(d)

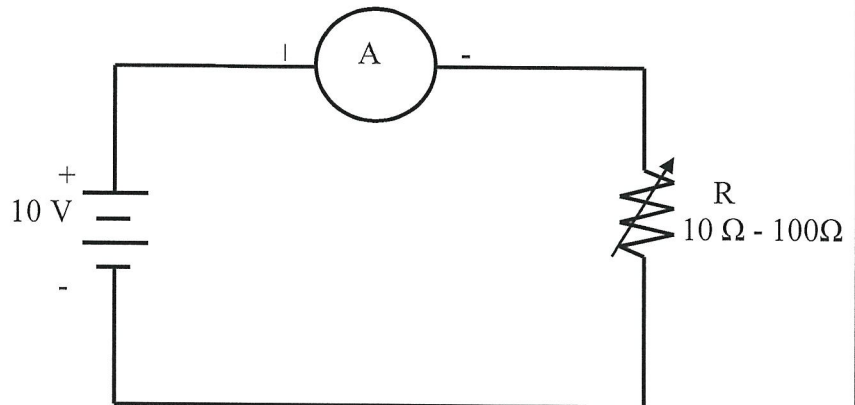


Figure Q3(b)

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION : II/2017/2018
COURSE : ELECTRICAL TECHNOLOGY

PROGRAMME : DAE
COURSE CODE : DAE 11003

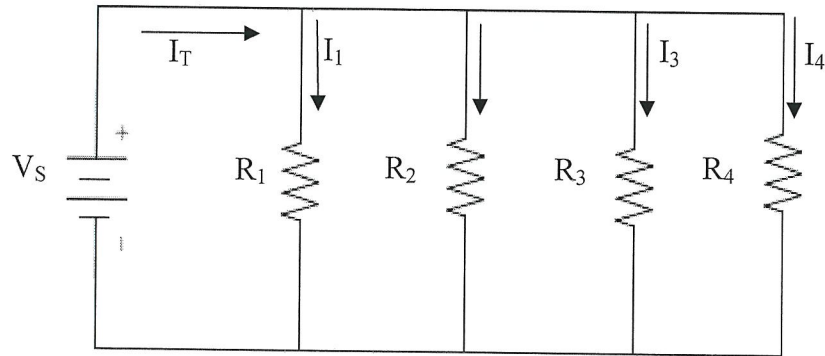


Figure Q3(c)

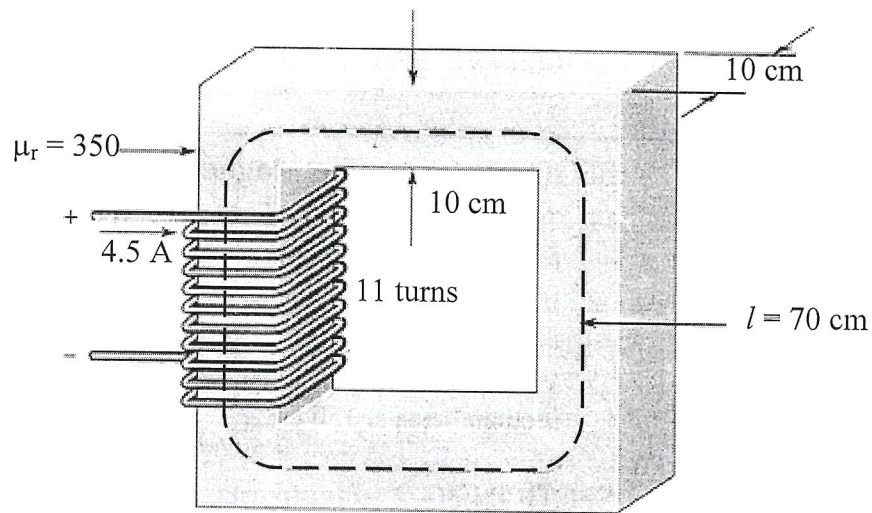


Figure Q4(c)

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION : II/2017/2018
COURSE : ELECTRICAL TECHNOLOGY

PROGRAMME : DAE
COURSE CODE : DAE 11003

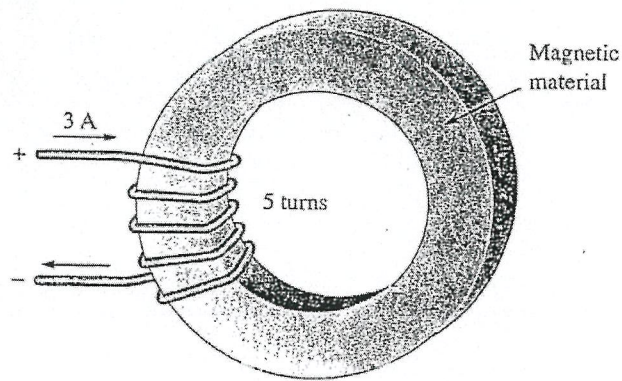


Figure Q4(d)

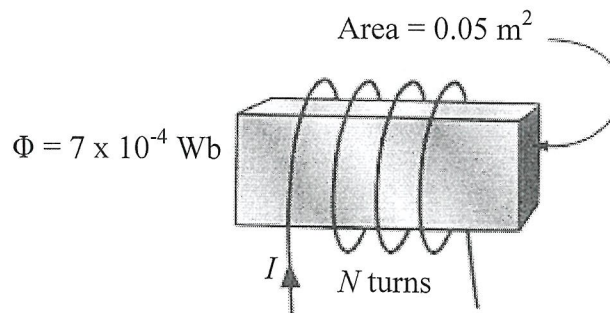


Figure Q4(e)

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION : II/2017/2018
COURSE : ELECTRICAL TECHNOLOGY

PROGRAMME : DAE
COURSE CODE : DAE 11003

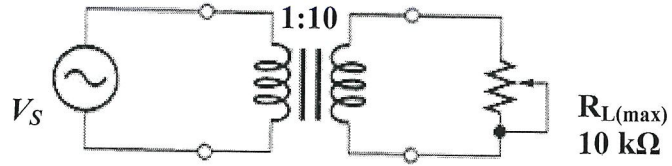


Figure Q5(d)

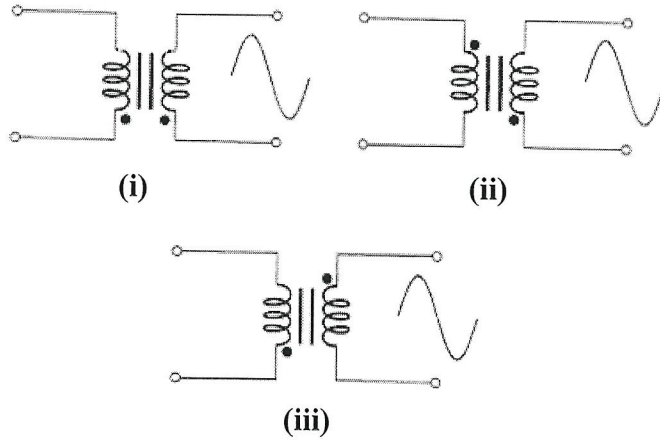


Figure Q5(e) (i), (ii) and (iii)

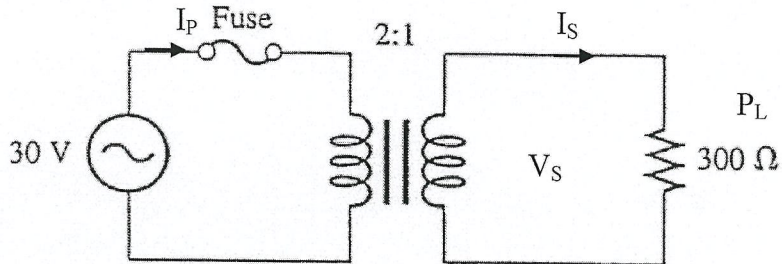


Figure Q5(g)

TERBUKA