

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2018/2019**

COURSE NAME : CIRCUIT THEORY
COURSE CODE : DAE 11103
PROGRAMME CODE : DAE
EXAMINATION DATE : JUNE / JULY 2019
DURATION : 2 HOURS 30 MINUTES
INSTRUCTION : ANSWER **ALL** QUESTIONS IN
SECTION A AND **TWO (2)**
QUESTIONS IN SECTION B.

THIS QUESTION PAPER CONSISTS OF **EIGHT (8)** PAGES

CONFIDENTIAL

SECTION A:

Q1 (a) The voltage, v across a device and the current, i through it are;

$$v(t) = 5 \cos 2t \text{ V}, \quad i(t) = 10 (1 - e^{-0.5t}) \text{ A}$$

(i) Calculate the total charge in the device at $t = 2\text{s}$ (3 marks)

(ii) Determine the power consumed by the device at $t = 2\text{s}$ (3 marks)

(b) State the definition of Kirchhoff's Current Law. (2 marks)

(c) Consider the circuit shown in **Figure Q1 (c)**.

(i) Determine the equivalent resistance, R_{ab} of the circuit. (7 marks)

(ii) If a voltage source of 5V is connected to the terminal a-b, use voltage divider rule to find the voltage drop across 20Ω and 30Ω resistors. (5 marks)

Q2 (a) In the circuit of **Figure Q2(a)**, determine v and i using nodal analysis. (10 marks)

(b) In the circuit of **Figure Q2(b)**, apply mesh analysis to find the voltage V_x . (10 marks)

Q3 (a) Define the maximum power transfer theorem. (2 marks)

(b) For the circuit in **Figure Q3(b)**,

(i) Obtain the Norton and Thevenin equivalent circuits at terminals a-b. (10 marks)

(ii) Calculate the current, i_o through $R_L = 8 \Omega$. (3 marks)

(iii) Find R_L for maximum power deliverable to R_L . (2 marks)

(iv) Determine the maximum power delivered to R_L . (3 marks)

SECTION B:

- Q4** (a) The voltage across a $5\mu\text{F}$ capacitor is given as:

$$v(t) = 50 \sin 500t \text{ V}$$

Calculate current, $i(t)$ through it.

(3 marks)

- (b) If the current through a 2 mH inductor is $i(t) = 20e^{-20t} \text{ A}$, find the voltage across the inductor and the energy stored in it.

(5 marks)

- (c) Three capacitors, $C_1 = 4\mu\text{F}$, $C_2 = 12\mu\text{F}$ and $C_3 = 28\mu\text{F}$, are connected in parallel across a 120 V DC source. Determine:

- (i) the total capacitance.

(3 marks)

- (ii) the charge on each capacitor.

(3 marks)

- (iii) the total energy stored in the parallel combination of the capacitors.

(3 marks)

- (iv) the total capacitance if the capacitors C_1 , C_2 and C_3 are connected in series across the source.

(3 marks)

- Q5** (a) For the circuit in **Figure Q5 (a)**, given that:

$$\begin{aligned} v &= 150e^{-50t} \text{ V} \\ i &= 30e^{-50t} \text{ A} \end{aligned}$$

- (i) Find the value of L and R .

(6 marks)

- (ii) Determine the time constant, τ .

(2 marks)

- (iii) Calculate the initial energy in the inductor.

(4 marks)

- (b) Assume that the switch in the circuit shown in **Figure Q5 (b)** has been in position x for a long time, and at $t = 0$ it moves to position y . Find $i(t)$ for both $t < 0$ and $t > 0$.

(8 marks)

- Q6** (a) If $R = 10 \Omega$, $L = 5 \text{ H}$, and $C = 2 \text{ mF}$ in **Figure Q6 (a)**, find
- (i) Damping factor, α (2 marks)
 - (ii) Resonant frequency, ω_0 (2 marks)
 - (iii) Natural frequencies, s_1 and s_2 (2 marks)
 - (iv) State the type of natural response that the circuit have. (1 marks)
- (b) For the circuit in **Figure Q6 (b)**, calculate the value of R needed to have a critically damped response. (5 marks)
- (c) The natural response of a series RLC circuit is

$$i(t) = 10e^{-500t} + 12e^{-800t} \text{ mA}, \quad t \geq 0.$$

- If $R = 200 \Omega$, find the value of L and C . (8 marks)

- END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2018/2019
 COURSE NAME : CIRCUIT THEORY

PROGRAMME: DAE
 COURSE CODE: DAE 11103

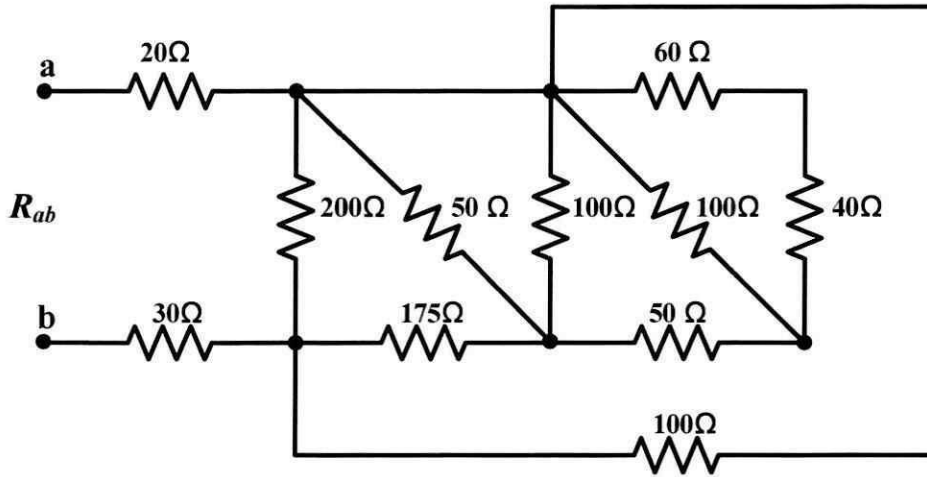


Figure Q1(c)

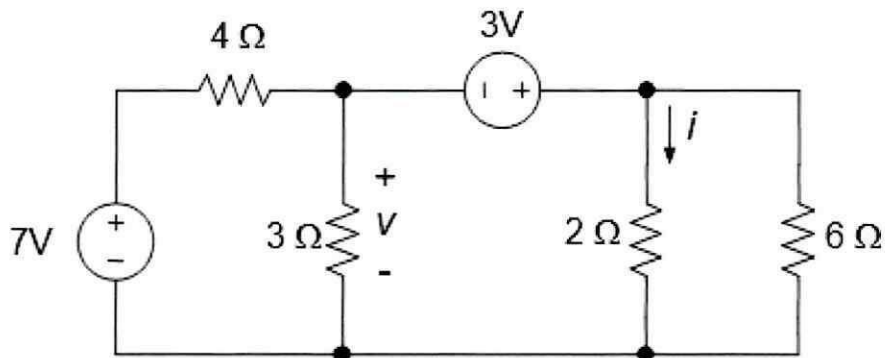


Figure Q2(a)

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2018/2019
 COURSE NAME : CIRCUIT THEORY

PROGRAMME: DAE
 COURSE CODE: DAE 11103

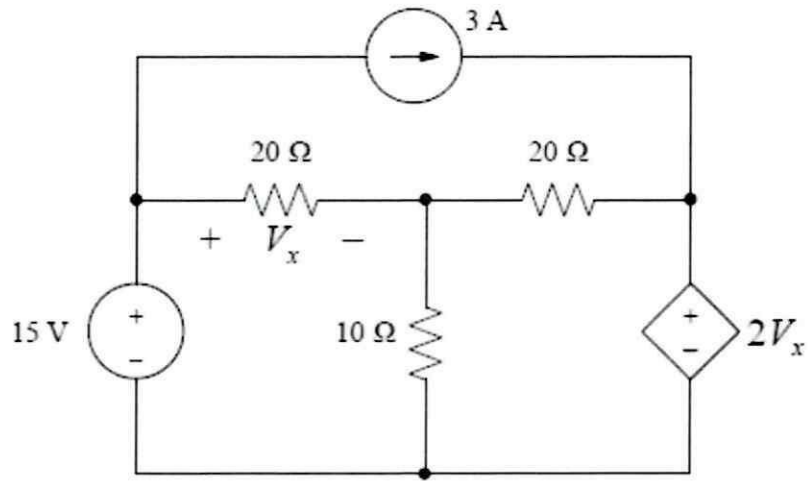


Figure Q2(b)

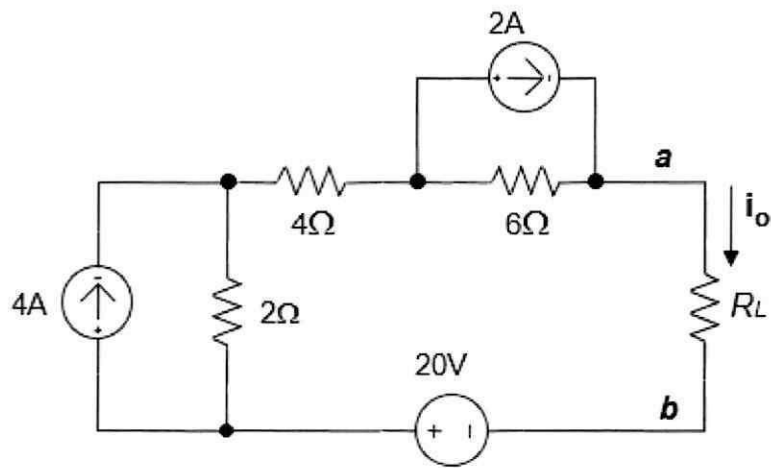


Figure Q3(b)

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2018/2019
COURSE NAME : CIRCUIT THEORY

PROGRAMME: DAE
COURSE CODE: DAE 11103

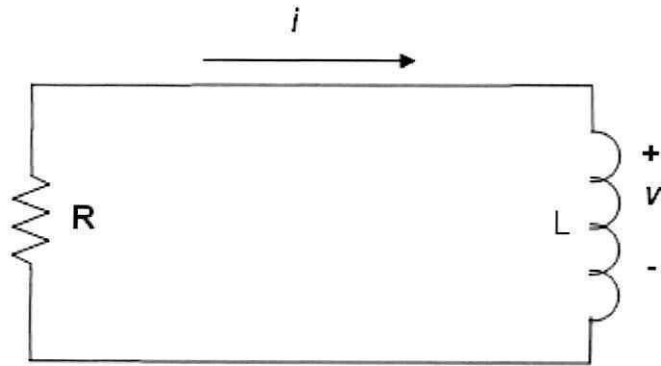


Figure Q5(a)

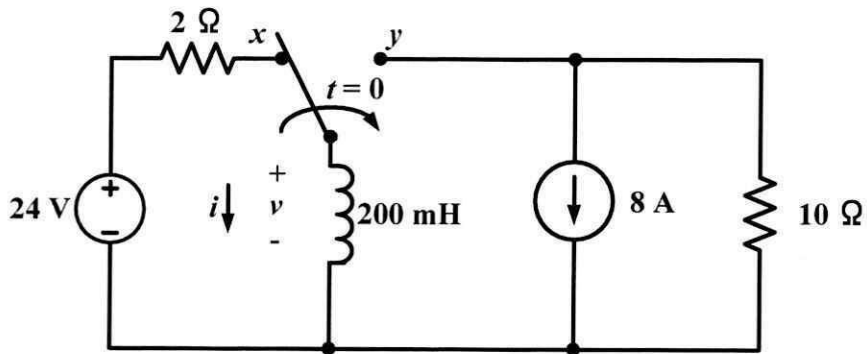


Figure Q5(b)

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2018/2019
COURSE NAME : CIRCUIT THEORY

PROGRAMME: DAE
COURSE CODE: DAE 11103

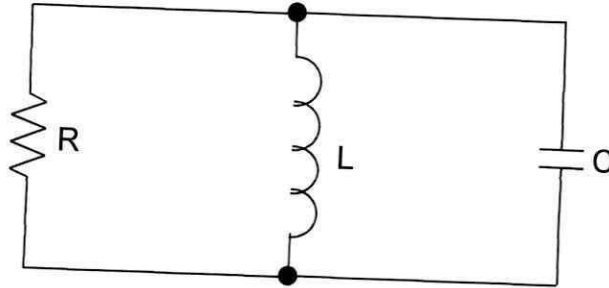


Figure Q6(a)

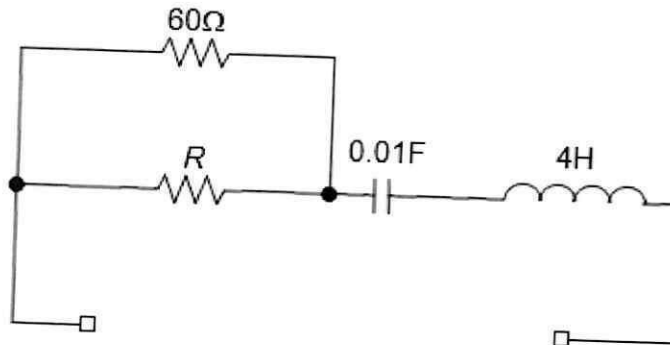


Figure Q6(b)