

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2019/2020**

COURSE NAME : PHYSICS III
COURSE CODE : DAS 24603
PROGRAMME CODE : DAU
EXAMINATION DATE : DECEMBER 2019 / JANUARY 2020
DURATION : 3 HOURS
INSTRUCTIONS : ANSWER FIVE (5) QUESTIONS ONLY

TERBUKA

THIS QUESTION PAPER CONSISTS OF EIGHT (8) PAGES

CONFIDENTIAL

- Q1** (a) A dielectric materials is placed between the two parallel plates, called capacitor. State **two (2)** advantages of using dielectrics in capacitor. (2 marks)
- (b) **Figure Q1 (b)** shows capacitors connected to a voltage source of 36 V. Calculate:
- (i) the capacitance of the equivalent capacitor. (10 marks)
- (ii) the charge stored on capacitor C_4 . (8 marks)
- Q2** (a) Two type of resistor, R_1 : coded with Yellow, Violet, Brown, Gold and R_2 : coded with Yellow, Violet, Brown, Silver are considered to be used as part of an electrical components in a circuit.
- (i) State the resistance and tolerance of each resistor. (3 marks)
- (ii) Out of the two resistors, suggest the most preferable resistor to be use in the circuit. State the reason. (2 marks)
- (b) **Figure Q2 (b)** shows seven resistors connected to a 12 V battery in a closed circuit. The resistance of the resistor is 7Ω each. Calculate:
- (i) the resistance of the equivalent resistance. (8 marks)
- (ii) the current drawn from the battery. (2 marks)
- (c) A copper wire has a length of 150 m and a diameter of 1.0 mm. If the wire is connected to a 3.5 V battery, calculate the current flows through the wire. Given the resistivity of copper, $\rho_{cu} = 1.72 \times 10^{-8} \Omega \cdot m$ (5 marks)
- Q3** (a) By referring to **Figure Q3 (a)**, calculate the amount of current I_1 , I_2 , and I_3 by using Kirchoff's Law (re-draw and label your circuit accordingly). (13 marks)
- (b) An emf source of 20 V with internal resistance $r = 0.5 \Omega$ is connected in the circuit shown in **Figure Q3 (b)**. Calculate:
- (i) the equivalent resistance for external loaded. (5 marks)
- (ii) the current drawn from the battery. (2 marks)

TERBUKA

- Q4** A series connection of resistor, inductor, and capacitor are connected to an alternating emf device that operates at $\varepsilon = (130 \text{ V}) \sin (30\pi t)$. Given the value of resistor, inductor, and capacitor are 150Ω , 530 mH , and $76 \mu\text{F}$ respectively. Calculate:
- (a) the impedance of the circuit. (7 marks)
 - (b) the power factor and the phase difference. (4 marks)
 - (c) the average power at which energy is dissipated in the resistance. (6 marks)
 - (d) the new capacitance needed to maximize the average power if the other parameters of the circuit remain the same. (3 marks)
- Q5**
- (a) State the difference between intrinsic and extrinsic semiconductor. Give an example for each type of semiconductor. (4 marks)
 - (b) Sketch and discuss the energy level diagram for insulator and semiconductor material. (8 marks)
 - (c)
 - (i) Describe how forward-bias of pn junction diode occurs. (6 marks)
 - (ii) Sketch the V-I characteristics curve of forward-bias pn junction diode. (2 marks)
- Q6**
- (a) Without using a calculator, convert the following number system into decimal number.
 - (i) $1EE7_{16}$ (2 marks)
 - (ii) 10001111_2 (2 marks)
 - (iii) 217_8 (2 marks)
 - (b) Boolean expression of an output variable is given below:

$$(\overline{A}B(C + BD) + \overline{A}B)C$$
 - (i) Draw the logic circuit diagram from the Boolean expression given. (7 marks)
 - (ii) Simplified the given Boolean expression. (6 marks)
 - (iii) According to your answer in Q6 (b)(ii), draw the simplified logic circuit. (1 mark)

- Q7** (a) Show the difference between half-wave rectifier and full-wave rectifier by sketching an output voltage waveform without capacitor filter for each type of rectifier. (4 marks)
- (b) Define the following:
- (i) Peak Inverse Voltage (PIV). (1 mark)
 - (ii) Root-mean-square Voltage (V_{rms}) (1 mark)
- (c) A 70Ω load resistance is connected across a half wave rectifier. A 2.5 mF filter capacitor is added across the load resistor. The input supply voltage (rms) is 250 V at 100 Hz. Calculate:
- (i) the average voltage. (3 marks)
 - (ii) the load current across the resistor. (2 marks)
 - (iii) the peak-to-peak voltage ($V_{\text{p-p}}$). (2 marks)
 - (iv) the ripple percentage. (3 marks)
 - (v) Sketch the output voltage waveform of the half-wave rectifier with capacitor filter. (4 marks)

- END OF QUESTION-

TERBUKA

SEMESTER / SESSION : SEM I / 2019/2020

PROGRAMME CODE : DAU

COURSE NAME : PHYSICS III

COURSE CODE : DAS 24603

LIST OF FIGURE

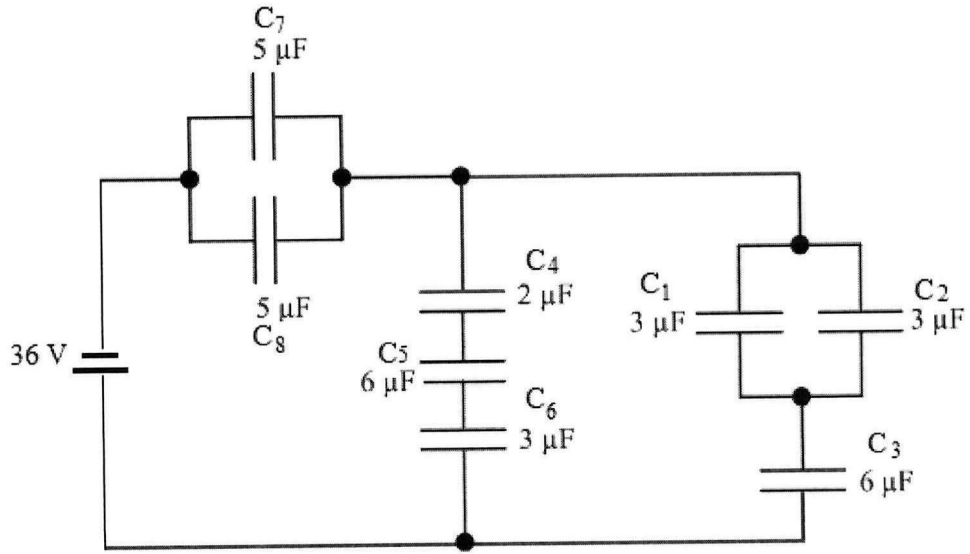


Figure Q1 (b)

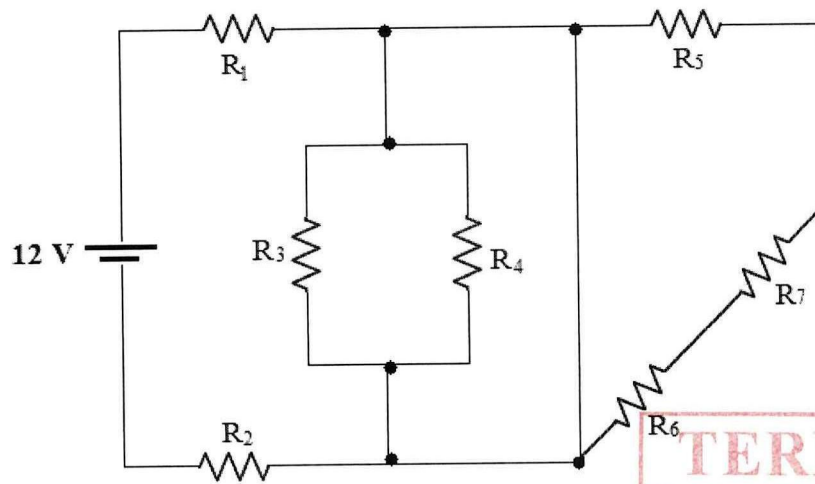


Figure Q2 (b)

TERBUKA

SEMESTER / SESSION : SEM I / 2019/2020

PROGRAMME CODE : DAU

COURSE NAME : PHYSICS III

COURSE CODE : DAS 24603

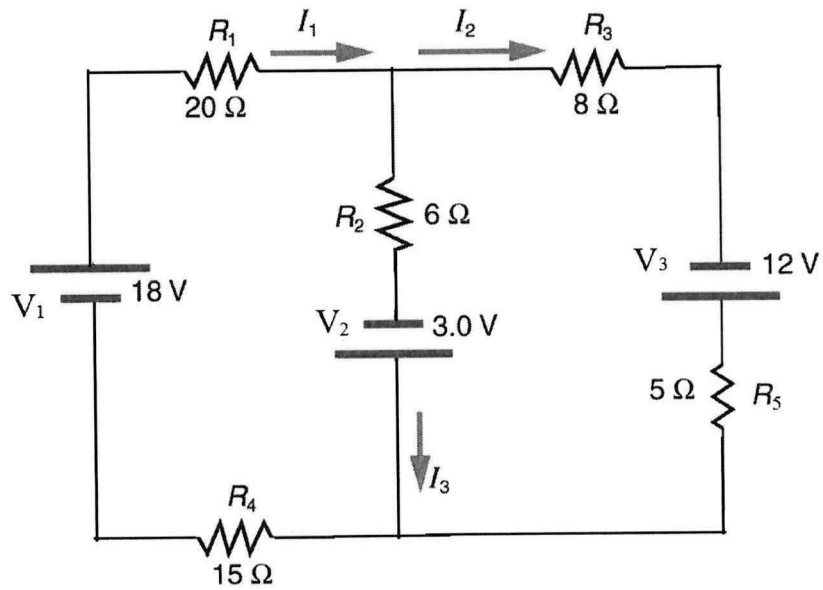


Figure Q3 (a)

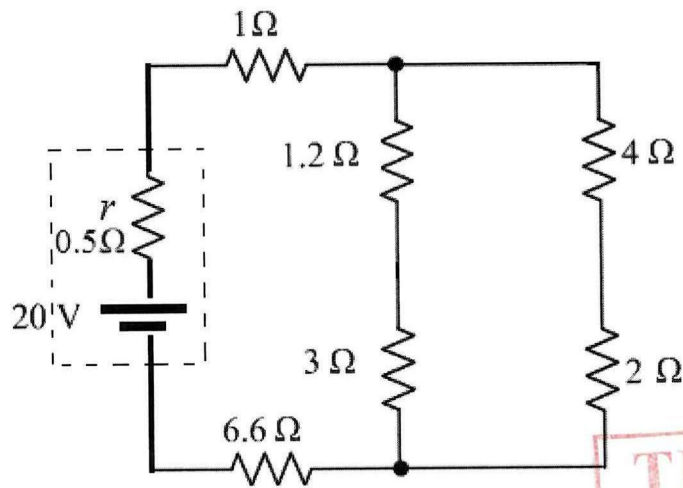


Figure Q3 (b)

TERBUKA

SEMESTER / SESSION : SEM I / 2019/2020

PROGRAMME CODE : DAU

COURSE NAME : PHYSICS III

COURSE CODE : DAS 24603

LIST OF FORMULA

$q = \pm ne$	P: $C_{eq} = C_1 + C_2$	S: $R_{eq} = R_1 + R_2$
$C = \frac{\kappa\epsilon_0 A}{d}$	S: $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$	P: $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$
$C = \frac{Q}{V}$	$V = IR$	$J = \frac{I}{A} = nve$
$R = \frac{\rho L}{A}$	$V_{ab} = \varepsilon - Ir$	$V_n = \frac{R_n}{R_T} V_T$
$\sigma = \frac{1}{\rho}$	$P = I^2 R = IV$	$I_n = \frac{I_T}{R_n} R_T$
$U = CV^2 = \frac{1}{2} QV$	$E = Pt$	$A_{p-p} = 2A_m$
$X_C = \frac{1}{2\pi fC}$	$\omega = 2\pi f$	$A_{rms} = \frac{A_m}{\sqrt{2}}$
$X_L = 2\pi fL$	$Z = \sqrt{(X_L - X_C)^2 + R^2}$	$V_{rms} = \frac{V}{\sqrt{2}}$
$\tan \phi = -\frac{X_C}{R}$	$\tan \phi = \frac{X_L - X_C}{R}$	$\cos \phi = \frac{R}{Z}$
$\tan \phi = \frac{X_L}{R}$	$V_C = I_C X_C$	$P_{avg} = I_{rms}^2 R$
$Z = \sqrt{R^2 + X_L^2}$	$V_L = I_L X_L$	$P_{avg} = I_{rms} V_{rms} \cos \phi$
$Z = \sqrt{R^2 + X_C^2}$	$I_{rms} = \frac{V_{rms}}{Z}$	$I_L = \frac{V_{avg}}{R_L}$
$N_e = 2n^2$	$V_{p-p} = \frac{I_L}{2fC}$	$V_{avg} = \frac{2V_m}{\pi}$
$V_s = V_m \sin \omega t$	$V_{p-p} = \frac{I_L}{fC}$	$V_{avg} = \frac{V_m}{\pi}$

TERBUKA

SEMESTER / SESSION : SEM I / 2019/2020

PROGRAMME CODE : DAU

COURSE NAME : PHYSICS III

COURSE CODE : DAS 24603

TABLE OF REFERENCE

Table 1: Resistor Colour Coded.

Colour	Digit	Multiplier	Tolerance (%)
Black	0	1	
Brown	1	10^1	1
Red	2	10^2	2
Orange	3	10^3	
Yellow	4	10^4	
Green	5	10^5	0.5
Blue	6	10^6	0.25
Violet	7	10^7	0.1
Grey	8	10^8	
White	9	10^9	
Gold		10^{-1}	5
Silver		10^{-2}	10
(none)			20

Table 2: Boolean Algebra Laws

Commutative		$A + B = B + A$ $A \cdot B = B \cdot A$
Associative		$A + (B + C) = (A + B) + C$ $A \cdot (B \cdot C) = (A \cdot B) \cdot C$
Distributive		$A \cdot (B + C) = A \cdot B + A \cdot C$ $A(B + C) = AB + AC$
AND	1 2 3 4	$A \cdot 0 = 0$ $A \cdot 1 = A$ $A \cdot A = A$ $A \cdot \bar{A} = 0$
OR	5 6 7 8	$A + 0 = A$ $A + 1 = 1$ $A + A = A$ $A + \bar{A} = 1$
Miscellaneous	9 10 11	$A + AB = A$ $A + \bar{A}B = A + B$ $(A + B)(A + C) = A + BC$

TERBUKA