

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2019/2020**

COURSE NAME : CIRCUIT THEORY
COURSE CODE : DAE 11103
PROGRAMME CODE : DAE
EXAMINATION DATE : DECEMBER 2019/JANUARY 2020
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS IN
SECTION A AND TWO (2)
QUESTIONS IN SECTION B.

TERBUKA

THIS QUESTION PAPER CONSISTS OF **EIGHT (8)** PAGES

CONFIDENTIAL

SECTION A:

- Q1** (a) The voltage, v across a device and the current, i through it are;
- $$v(t) = 7 \cos 5t \text{ V}, \quad i(t) = 10 (1 - e^{-0.5t}) \text{ A}$$
- (i) Calculate the total charge in the device at $t = 3\text{s}$ (3 marks)
- (ii) Determine the power consumed by the device at $t = 3\text{s}$ (3 marks)
- (b) State the definition of Kirchhoff's Voltage Law. (2 marks)
- (c) Consider the circuit shown in **Figure Q1 (c)**.
- (i) Determine the equivalent resistance, R_{ab} of the circuit. (7 marks)
- (ii) If a voltage source of 5V is connected to the terminal a-b, use voltage divider rule to find the voltage drop across 20Ω and 30Ω resistors. (5 marks)
- Q2** (a) In the circuit of **Figure Q2(a)**, determine v and i using mesh analysis. (10 marks)
- (b) In the circuit of **Figure Q2(b)**, apply nodal analysis to find the voltage across each resistor. (10 marks)
- Q3** (a) Define the maximum power transfer theorem. (2 marks)
- (b) For the circuit in **Figure Q3(b)**,
- (i) Obtain the Norton and Thevenin equivalent circuits at terminals a-b. (10 marks)
- (ii) Calculate the current, i_o through $R_L = 10 \Omega$. (3 marks)
- (iii) Find R_L for maximum power deliverable to R_L . (2 marks)
- (iv) Determine the maximum power delivered to R_L . (3 marks)

SECTION B:

- Q4** (a) The voltage across a $6\mu\text{F}$ capacitor is given as:

$$v(t) = 60 \sin 600t \text{ V}$$

Calculate current, $i(t)$ through it.

(3 marks)

- (b) If the current through a 2 mH inductor is $i(t) = 20e^{-20t} \text{ A}$, find the voltage across the inductor and the energy stored in it.

(5 marks)

- (c) Three capacitors, $C_1 = 5\mu\text{F}$, $C_2 = 15\mu\text{F}$ and $C_3 = 25\mu\text{F}$, are connected in parallel across a 150 V DC source. Determine:

- (i) The total capacitance.

(3 marks)

- (ii) The charge on each capacitor.

(3 marks)

- (iii) The total energy stored in the parallel combination of the capacitors.

(3 marks)

- (iv) The total capacitance if the capacitors C_1 , C_2 and C_3 are connected in series across the source.

(3 marks)

- Q5** (a) For the circuit in **Figure Q5 (a)**, given that:

$$\begin{aligned} v &= 150e^{-50t} \text{ V} \\ i &= 30e^{-50t} \text{ A} \end{aligned}$$

- (i) Find the value of L and R .

(6 marks)

- (ii) Determine the time constant, τ .

(2 marks)

- (iii) Calculate the initial energy in the inductor.

(4 marks)

- (b) Assume that the switch in the circuit shown in **Figure Q5 (b)** has been in position x for a long time, and at $t = 0$ it moves to position y . Find $i(t)$ for both $t < 0$ and $t > 0$.

(8 marks)

TERBUKA

- Q6** (a) If $R = 10 \Omega$, $L = 5 \text{ H}$, and $C = 2 \text{ mF}$ in **Figure Q6 (a)**, find
- (i) Damping factor, α (3 marks)
 - (ii) Resonant frequency, ω_b (3 marks)
 - (iii) Natural frequencies, s_1 and s_2 (3 marks)
 - (iv) State the type of natural response that the circuit have. (2 marks)
- (b) For the circuit in **Figure Q6 (b)**, calculate the value of R needed to have a critically damped response. (9 marks)

- END OF QUESTIONS -

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2019/2020
COURSE NAME : CIRCUIT THEORY

PROGRAMME: DAE
COURSE CODE: DAE 11103

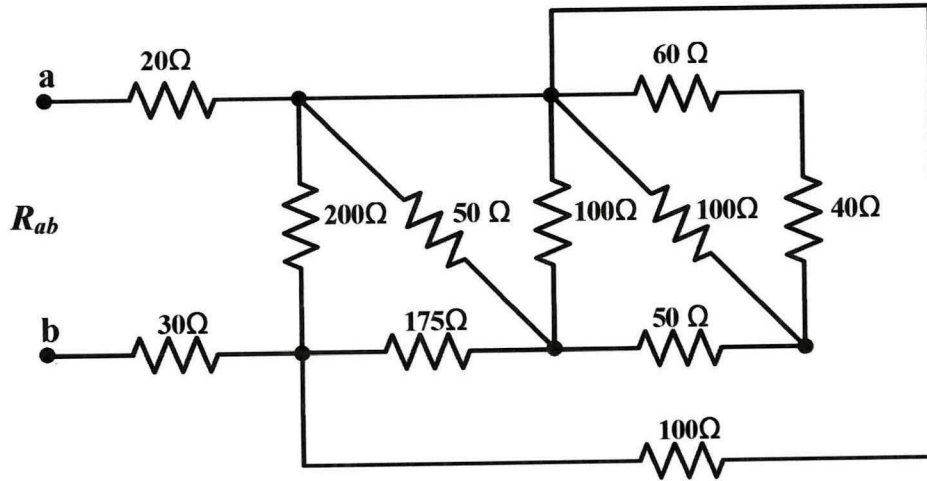


Figure Q1(c)

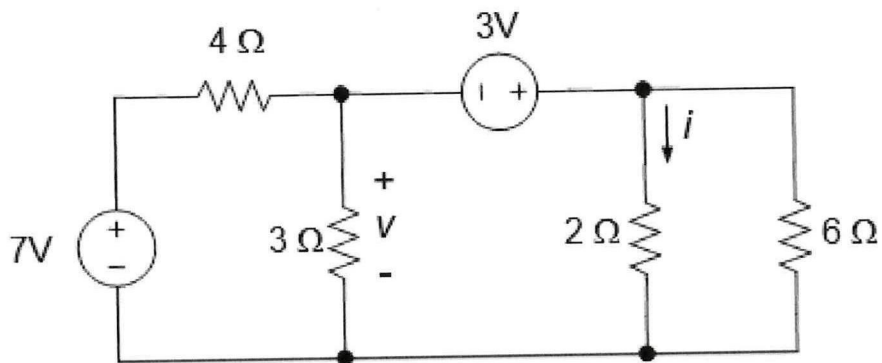


Figure Q2(a)

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2019/2020
COURSE NAME : CIRCUIT THEORY

PROGRAMME: DAE
COURSE CODE: DAE 11103

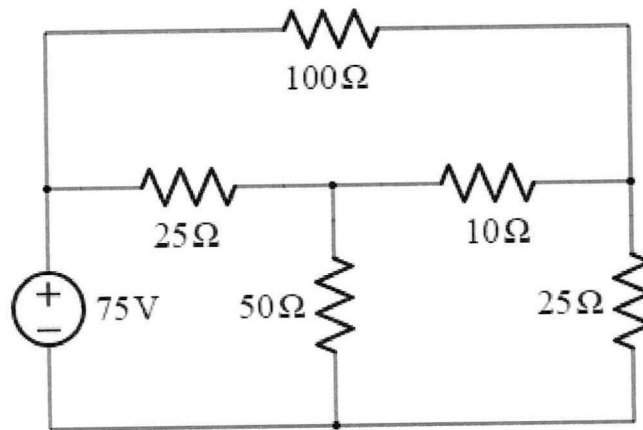


Figure Q2(b)

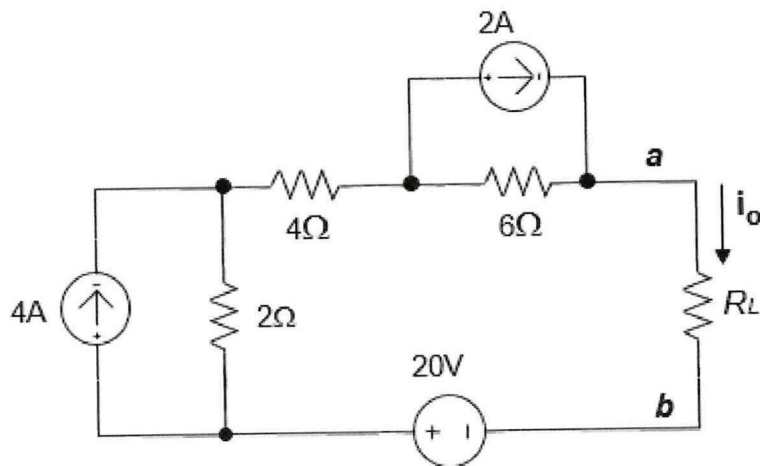


Figure Q3(b)

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2019/2020
COURSE NAME : CIRCUIT THEORY

PROGRAMME: DAE
COURSE CODE: DAE 11103

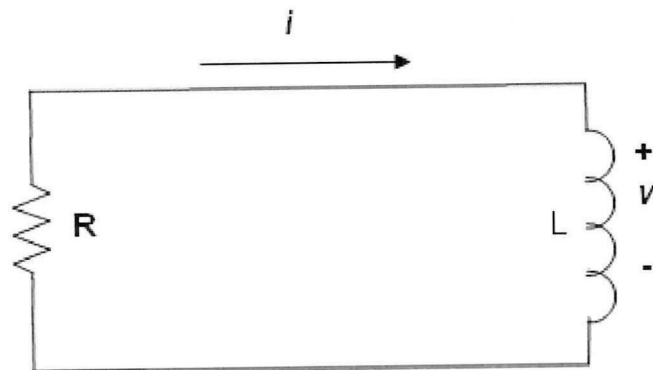


Figure Q5(a)

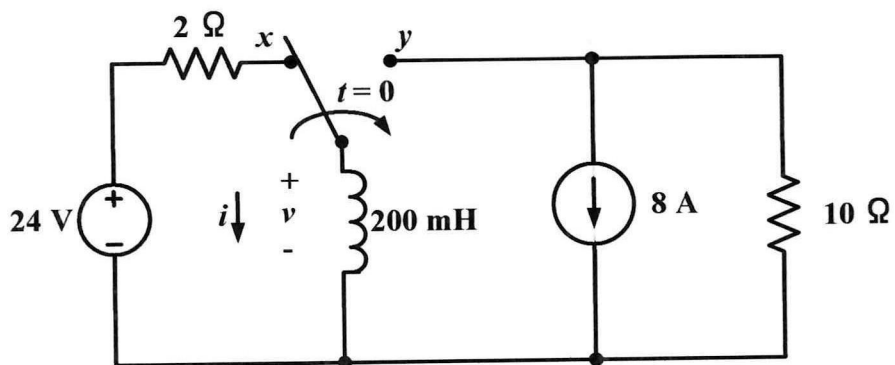


Figure Q5(b)

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2019/2020
COURSE NAME : CIRCUIT THEORY

PROGRAMME: DAE
COURSE CODE: DAE 11103

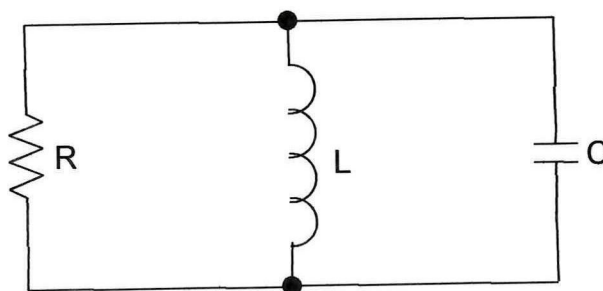


Figure Q6(a)

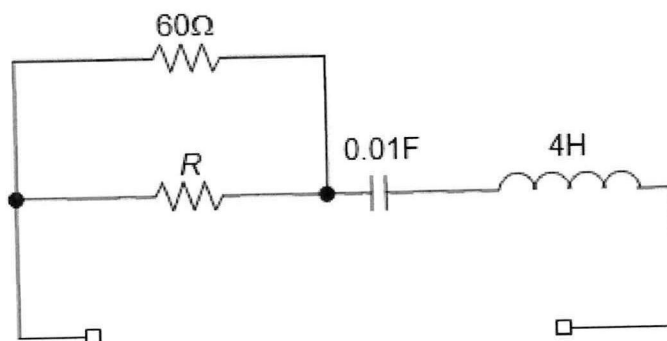


Figure Q6(b)

TERBUKA