



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESSION 2016/2017**

COURSE NAME : ELECTRONICS I  
COURSE CODE : BWC 10703  
PROGRAMME CODE : BWC  
EXAMINATION DATE : JUNE 2017  
DURATION : 3 HOURS  
INSTRUCTION : ANSWERS ALL QUESTIONS

**TERBUKA**

THIS QUESTION PAPER CONSISTS OF **FIVE (5)** PAGES

- Q1** (a) Describe Kirchoff's Voltage Law (2 marks)
- (b) As to **Figure Q1(b)** is considered,  
 (i) determine  $V_2$  using KVL  
 (ii) calculate  $I$   
 (iii) find  $R_1$  and  $R_3$  (8 marks)
- (c) For the network of **Figure Q1(c)**, by using voltage divider rule  
 (i) calculate  $V_{ab}$   
 (ii) determine  $V_b$   
 (iii) calculate  $V_c$  (10 marks)
- Q2** (a) State the Thevenin's Theorem (2 marks)
- (b) Find the Thevenin equivalent circuit for in the shaded area of the network in **Figure Q2(b)** (10 marks)
- (c) (i) What is a semiconductor? How it can be compared with a conductor and an insulator?  
 (ii) Describe forward and reverse biased of a diode  
 [Diagrams might help in these questions] (8 marks)
- Q3** **Figure Q3** shows the full wave rectifier circuit.  $T_1$  is a step down transformer, which provides the secondary voltage. This transformer secondary is called as center tapped. In this figure, each half of the secondary has a voltage of  $15 V_{ac}$ , which is one half the total secondary voltages,  $V_S$ , of  $30 V_{ac}$ . The voltage for the top half of the secondary is designated  $V_1$ , whereas the voltage for the bottom half of the secondary is designated  $V_2$ . Analyze;
- (a) top half of secondary voltage  $V_1$ , (6 marks)
- (b) bottom half of secondary voltage,  $V_2$ , (2 marks)
- (c) output voltage produced when  $D_1$  is conducted. (4 marks)
- (d) output voltage produced when  $D_2$  is conducted. (2 marks)

**TERBUKA**

- (e) the combination output voltage produced by  $D_1$  and  $D_2$  and value of  $I_L$ . (6 marks)

**Q4** (a) Explain the function of emitter and collector regions in a transistor. (2 marks)

- (b) For the circuit shown in **Figure Q4(b)**, calculate the value for  $V_B$ ,  $V_E$ ,  $I_C$ ,  $V_{CE}$ ,  $I_{C(sat)}$  and  $V_{CE(off)}$ . Then, construct a dc load line showing the value of  $I_{C(sat)}$ ,  $V_{CE(off)}$ ,  $I_{CQ}$  and  $V_{CEQ}$ . (18 marks)

**Q5** (a) Draw the schematic symbol of JFETs  
 (i) n-channel symbol  
 (ii) offset-gate symbol  
 (iii) p-channel symbol (6 marks)

- (b) Assume that the JFET circuit in **Figure Q5(b)** is to be mass produced. The JFET has the following parameters:

<u>Parameter</u>	<u>Minimum</u>	<u>Maximum</u>
$I_{DSS}$	2 mA	20 mA
$V_{GS(off)}$	-2 V	-8 V

Calculate the minimum and maximum value for  $I_D$  and  $V_{DS}$  if  $V_{GS} = -1.5$  V for the range of JFET parameters shown and conclude the finding. (14 marks)

**TERBUKA**

– END OF QUESTIONS –

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2016/2017  
COURSE NAME : ELECTRONICS I

PROGRAMME CODE : BWC  
COURSE CODE : BWC 10703

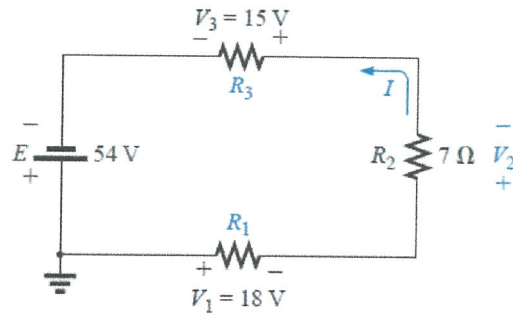


Figure Q1(b)

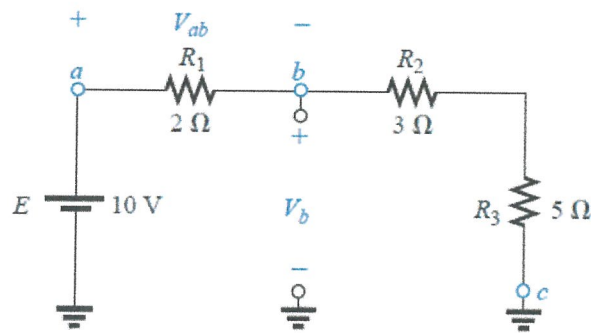


Figure Q1(c)

 


Figure Q2(b)

**TERBUKA**

Copyright © 2016 by BWC. All rights reserved. No part of this publication may be reproduced, stored in a retrieval system, or transmitted, in any form or by any means, without the prior written permission of BWC.

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2016/2017  
 COURSE NAME : ELECTRONICS I

PROGRAMME CODE : BWC  
 COURSE CODE : BWC 10703

 


Figure Q3

 


Figure Q4(b)

 


Figure Q5(b)

**TERBUKA**

This document is the property of the University of Technology, Malaysia. It is not to be distributed outside the institution.