



# UNIVERSITI TUN HUSSEIN ONN MALAYSIA

## FINAL EXAMINATION SEMESTER II SESION 2008/2009

COURSE NAME : DIGITAL SYSTEM DESIGN  
COURSE CODE : BEE 3133  
PROGRAM : 3 BEE  
DATE OF EXAMINATION : APRIL/MEI 2009  
DURATION : 2 HOURS 30 MINUTE  
INSTRUCTION : ANSWER FOUR (4) QUESTIONS ONLY  
OF SIX (6) QUESTIONS.

THIS QUESTION PAPER CONTAINS EIGHT (8) PAGES

- Q1** (a) Predictions of Gordon Moore in 1965 have proved to be remarkably accurate based on transistor growing trends. State the Moore's Laws. (4 marks)
- (b) Transistor becomes smaller, less resistive, faster, conducting more electricity and using less power.
- (i) Give a definition of scaling. (4 marks)
- (ii) State THREE (3) goals of technology scaling. (3 marks)
- (iii) Explain briefly THREE (3) types of technology scaling model. (6 marks)
- (iv) Explain briefly FOUR (4) main problems occur in technology scaling and the solution for these problems. (8 marks)
- Q2** (a) VHDL was founded in 1980s by US Department of Defense. It is simply a type of high level computer language used to describe all of the important characteristics of a logic network and also a text based language used to describe hardware.
- (i) State THREE (3) types of VHDL modeling. (3 marks)
- (ii) Figure 2(a) illustrates full adder that created using two half adder blocks and an OR gate. Given half\_add entity in Figure 2(b), compose VHDL code for the full adder. (10 marks)
- (b) Given logic function  $f(x_1, x_2, x_3, x_4) = \sum m(0, 1, 3, 4, 7, 11, 13, 15) + D(9, 12, 14)$ .
- (i) Synthesize a minimum-cost SOP function. (6 marks)
- (ii) Realize the SOP function using Boolean gates. Assume that the input variables are available in both true and complement. (4 marks)
- (iii) Calculate implementation cost of the SOP function. (2 marks)

**Q3** A sequence detector consists of a single-input and single-output. This sequence detector will produce an output of '1' if the input sequence detects 101 patterns.

- (a) Draw a Moore-type state diagram for the sequence detector. (5 marks)
- (b) Derive state table for the detector. (5 marks)
- (c) Derive state-assigned table for the detector. (2 marks)
- (d) Build the detector circuit using D flip-flop. (5 marks)
- (e) Compose VHDL code of the state diagram in Q3(a) using sequential statement. (8 marks)

**Q4** (a) Figure Q4(a) presents a logic circuit constructed using logic gates.

- (i) Compute logic expression of the logic circuit. (3 marks)
- (ii) Construct CMOS transistor circuit for the logic circuit. (10 marks)

(b) Figure Q4(b) shows a stick diagram for a CMOS circuit.

- (i) Construct Euler path for the circuit. (9 marks)
- (ii) Write logic equation for the stick diagram. (3 marks)

**Q5** (a) Relate current flow and capacitance charge to small  $B'$  and large  $B'$  of a MOSFET. (6 marks)

(b) For nFET transistor, assume that  $k_n' = 100 \times 10^{-6} \text{ A/V}^2$ ,  $W/L = 0.25 \mu\text{m}/0.2 \mu\text{m}$ ,  $V_{DD} = 5\text{V}$ , and  $V_{GS} = 1\text{V}$ .

- (i) Calculate the maximum current flow in the nFET. (5 marks)
- (ii) Determine the aspect ratio needed to obtain a maximum current of 8mA and  $W = 5 \mu\text{m}$ . (5 marks)

(c)  $t_{LH}$  defines as a time needed for the output arise from the 10%  $V_{DD}$  to 90%  $V_{DD}$  in

digital waveform. Given  $t_r = \tau_p \ln \left( \frac{1}{1 - \frac{V_{out}}{V_{DD}}} \right)$ , prove that  $t_{LH} = 2.2 R_p C_{out}$ .

(9 marks)

- Q6** (a) Given a simple circuit in Figure Q6(a).
- (i) Derive a fault table for the circuit to show the coverage of the various stuck-at-0 and stuck-at-1 faults by the eight possible tests. (15 marks)
  - (ii) Find the minimal test set for this circuit. (4 marks)
- (b) Analyze the logic circuit in Figure Q6(b) to identify the tests that can detect each of the faults:
- (i)  $w_2/0$
  - (ii)  $b/1$
  - (iii)  $d/1$
- (6 marks)

## PEPERIKSAAN AKHIR

SEMESTER/SESI : II 2008/09  
 NAMA MATAPELAJARAN: REKABENTUK SISTEM DIGIT

KURSUS : 3 BEE  
 KOD : BEE 3133

 


Figure Q2(a)

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY half_add IS
    PORT (x, y : IN STD_LOGIC;
          s, c : OUT STD_LOGIC);
END half_add;

ARCHITECTURE LogicFunc OF half_add IS
BEGIN
    s <= x XOR y;
    c <= x AND y;
END LogicFunc ;
  
```

Figure Q2(b)

**PEPERIKSAAN AKHIR**

SEMESTER/SESI : II/2008/09  
NAMA MATAPELAJARAN: REKABENTUK SISTEM DIGIT

KURSUS : 3 BEE  
KOD : BEE 3133

```
PROCESS (w)
BEGIN
CASE w IS
WHEN "1000" =>
    y <- "11";
WHEN "0100" =>
    y <- "10";
WHEN "0010" =>
    y <- "01";
WHEN OTHERS =>
    y <- "00";
END CASE;
END PROCESS;
```

**Figure Q3(a)**


**PEPERIKSAAN AKHIR**

SEMESTER/SESI : II/2008/09  
 NAMA MATAPELAJARAN: REKABENTUK SISTEM DIGIT

KURSUS : 3 BEE  
 KOD : BEE 3133



**Figure Q4(a)**

 

**Figure Q4(b)**

## PEPERIKSAAN AKHIR

SEMESTER/SESI : II/2008/09  
NAMA MATAPELAJARAN: REKABENTUK SISTEM DIGIT

KURSUS : 3 BEI  
KOD : BEI 3133

 


Figure Q6(a)

 


Figure Q6(b)