



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

FINAL EXAMINATION SEMESTER II SESSION 2008/2009

SUBJECT NAME : ELECTRICAL TECHNOLOGY
SUBJECT CODE : BEE 1223
COURSE : I BEE
EXAMINATION DATE : APRIL/MAY 2009
DURATION : 2 1/2 HOURS
INSTRUCTIONS : ANSWER ANY FOUR (4)
QUESTIONS FROM THE SEVEN
(7) QUESTIONS GIVEN

THIS QUESTION PAPER CONSISTS OF SIX (6) PAGES

- Q1** (a) A current source in a linear circuit has $i_s = 5 \cos(2000t - 25^\circ)$ A .
- Find the amplitude of the current
 - Find the period of the current
 - Find the frequency of the current
 - Calculate i_s at $t = 3.0$ ms
- (10 marks)
- (b) Convert $v_L = 100 \sin(2000t + 180^\circ)$ to cosine form.
- (3 marks)
- (c) Given the complex numbers $z_1 = -3 + j4$ and $z_2 = 12 + j5$, find :
- $z_1 z_2$
 - $\frac{z_1}{z_2^*}$
 - $\frac{z_1 + z_2}{z_1 - z_2}$
 - $3z_1^* z_2$
- (12 marks)
- Q2** (a) Explain briefly the time-domain and frequency-domain paradigms with aid of appropriate diagrams and equations. Is it possible to combine the time-domain and the frequency-domain paradigms in one axis for analysis purposes?. Give support of your answer.
- (9 marks)
- (b) The current in a series circuit of $R = 5 \Omega$ and $L = 30$ mH lags the applied voltage by 80° . By drawing the impedance diagram, determine the source frequency and the impedance of this series circuit.
- (8 marks)

- (c) A series RC circuit with $R = 27.5 \Omega$ and $C = 66.7 \mu\text{F}$, has sinusoidal voltage and current, with angular frequency 1500 rad/s . Find the phase angle between the current and voltage.

(8 marks)

- Q3** (a) Compute the equivalent impedance Z_{eq} and admittance Y_{eq} for the four-branch circuit as shown in Figure Q3(a).

(9 marks)

- (b) The total current (I_1) entering the circuit as shown in Figure Q3(a) is $33.0 \angle -13.0^\circ \text{ A}$. Obtain the branch current I_2 and the voltage V_3 .

(8 marks)

- (c) Determine the current I_1 and I_2 in the parallel circuit of Figure Q3(c).

(8 marks)

- Q4** (a) Briefly describe the node voltage method for a frequency domain network.

(9 marks)

- (b) Using the node voltage method as in part (a) above, obtain the current I in the network of Figure Q4 (b).

(16 marks)

- Q5** (a) Show that the line-to-line voltage V_{Line} in a three phase system is $\sqrt{3}$ times the line-to-neutral voltage V_{Phase} .

(7 marks)

- (b) A three-phase, nps system, with a rms line voltage 70.7 V , has a balanced delta connected load with impedances $20 \angle 45^\circ \Omega$. Obtain the line currents and draw the voltage-current phasor diagram.

(9 marks)

- (c) A three-phase, three wire nps system, with a rms line voltage of 106.1 V , has a balanced Y-connected load with impedances $5 \angle -30^\circ \Omega$. Obtain the currents and draw the voltage-current phasor diagram.

(9 marks)

- Q6** (a) Explain briefly the following terms :
Use an appropriate diagram or equations to support your explanations.
- (i) Mutual inductance
 - (ii) Ideal transformer
 - (iii) Real transformer
- (13 marks)
- (b) A 150 kVA , 2400/240 V transformer has the following parameters:
- | | | |
|----------------------|-----------------------|----------------------|
| $R_p = 0.2 \Omega$ | $X_p = 0.45 \Omega$ | $R_c = 10000 \Omega$ |
| $R_s = 0.002 \Omega$ | $X_s = 0.0045 \Omega$ | $X_m = 1550 \Omega$ |
- By using equivalent circuit referred to the primary :
- (i) Calculate the primary voltage of the transformer at rated load with 0.8 lagging power factor
 - (ii) Determine the efficiency and voltage regulation of the transformer
- (12 marks)
- Q7** (a) Describe the characteristics of the following motors using an appropriate diagram and equations to support your explanations :
- (i) DC shunt motor
 - (ii) DC series motor
- (13 marks)
- (b) A 250 V shunt generator has an armature resistance of 0.25Ω and a field resistance of 125Ω . At no load, the generator takes a line current of 5.0 A, while running at 1200 rpm. If the line current at full load is 52 A, calculate the full load speed.
- (12 marks)

FINAL EXAMINATION

SEMESTER/SESSION : II/2008/2009
 SUBJECT : ELECTRICAL TECHNOLOGY

COURSE : I BEE
 SUBJECT CODE : BEE 1223

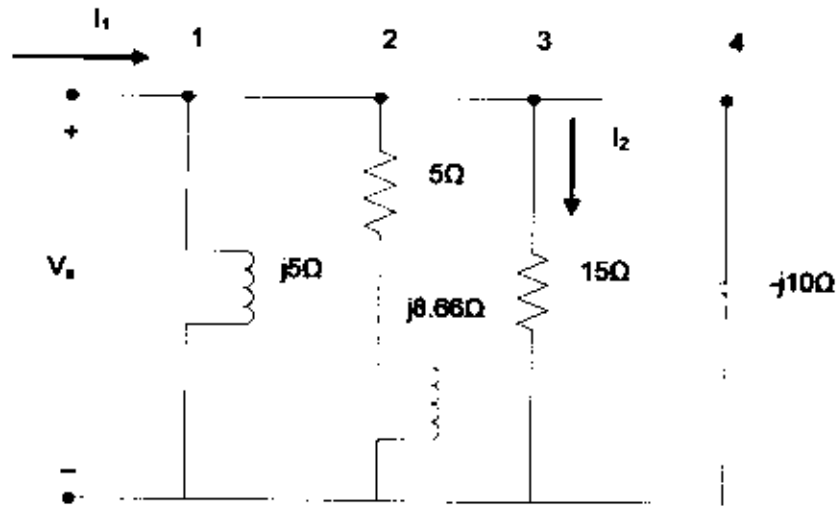


Figure Q3(a)

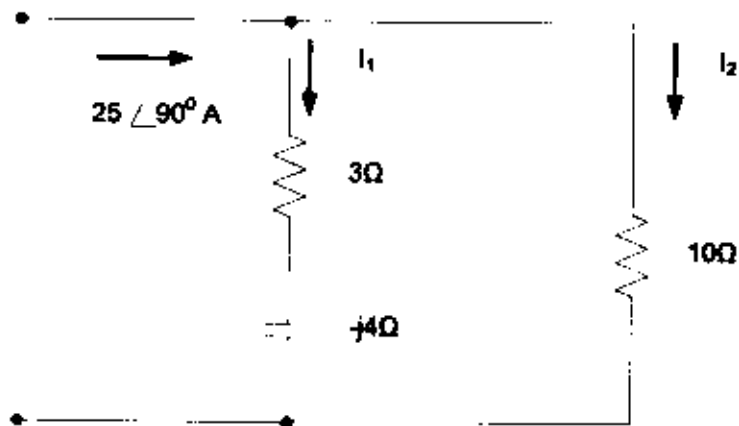


Figure Q3(c)

FINAL EXAMINATION

SEMESTER/SESSION : II/2008/2009
 SUBJECT : ELECTRICAL
 TECHNOLOGY

COURSE : I BEE
 SUBJECT CODE : BEE 1223

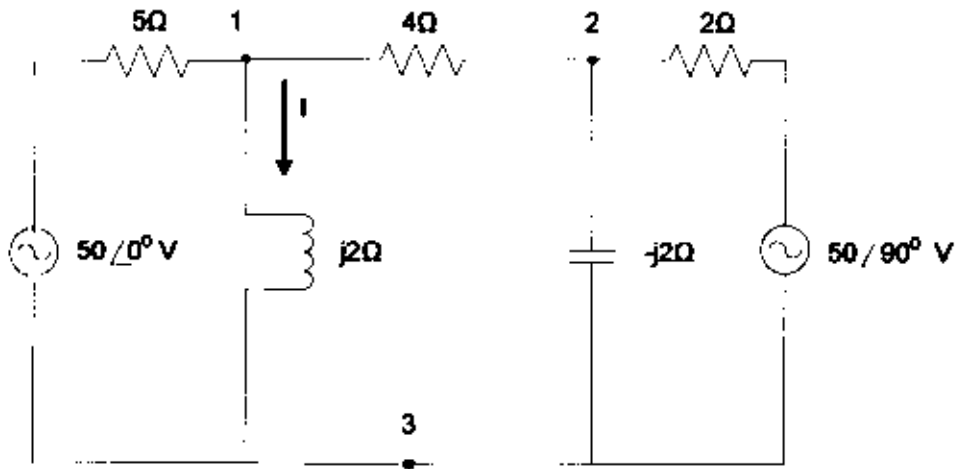


Figure Q4(b)

