



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

FINAL EXAMINATION
SEMESTER I
SESSION 2009/2010

SUBJECT NAME : POWER ELECTRONICS
SUBJECT CODE : BEE 4113
COURSE : 4 BEE
EXAMINATION DATE : NOVEMBER 2009
DURATION : 2 ½ HOURS
INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS FROM
FIVE (5) QUESTIONS

THIS EXAMINATION PAPER CONSISTS OF (9) PAGES

- Q1**
- (a) Define the purpose of Power Electronics Converters. (3 marks)
 - (b) List three causes of rapid growth in power electronics. (3 marks)
 - (c) State three effects of reverse recovery of power diode and sketch the forward current characteristic for soft-recovery and fast-recovery operation. (5 marks)
 - (d) Differentiate between a snubber circuit and a gate driver circuit. (6 marks)
 - (e) Figure Q1(e) shows the control signal, voltage and current of a MOSFET which operates at 100 kHz. V_d is the voltage across the switch during off-state and I_o is the current flowing through the switch during on-state. The current rise time, t_{ri} is 12 ns and the turn-off interval time, t_{off} is 60% of its switching period. The total average power dissipated is 8 W while the current flowing through the switch during on-state is 4 A. Determine
 - (i) the turn-on interval time, t_{on} , of the switch
 - (ii) the average power dissipated during on-state, P_{on}
 - (iii) the average switching power loss, P_s
 - (iv) the voltage fall time, t_{fv} , if the turn-off crossover interval $t_{c(off)} = 50$ ns.(8 marks)
- Q2**
- (a) Describe briefly the function of a rectifier. List two advantages of full-wave rectifiers as compared to half-wave rectifiers. (3 marks)
 - (b) Given the full bridge uncontrolled rectifier as shown in Figure Q2(b) with resistance and inductance as load. Assuming that inductance L is large enough to provide constant current.
 - (i) Sketch output voltage, V_o across the load of rectifier
 - (ii) Sketch waveform of the current flowing through diode 1, I_{D1} .
 - (iii) Sketch waveform of the current flowing through the inductance, I_o .(6 marks)

- (c) Switching devices for the full-bridge rectifier in Figure Q2(b) had been changed from diodes to thyristors. It receives a supply voltage of 240Vrms at 50 Hz frequency. The output current of the load in the discontinuous current mode is given by the expression

$$i_o(\omega t) = 9.58 \left[\sin(\omega t - 32.14^\circ) - 0.388 e^{-\frac{-(\omega t - 0.96)}{0.628}} \right] A$$

From information given, determine

- (i) The resistance R and inductance L of the load;
- (ii) The delay angle, (α);
- (iii) The average output voltage, $V_{o,avg}$, if extinction angle $\beta=212^\circ$;
- (iv) The average output current, $I_{o,avg}$;
- (v) The power absorbed by the load if the rms output current is 6.03A; and
- (vi) The efficiency of the rectifier.

(16 marks)

- Q3 (a) Define what is switching-mode regulator and list down four basic types of switching-mode regulators.
(5 marks)
- (b) State the two ways to vary the output voltage of DC-DC converter with the aid of the signal waveforms.
(4 marks)
- (c) Define the duty cycle D, for switching frequency f_s , of a DC converter.
(2 marks)
- (d) Explain briefly the operation of the converter in Continuous Current Mode (CCM) and Discontinuous Current Mode (DCM).
(4 marks)
- (e) A buck-boost converter circuit as shown in Figure Q3(e) has $V_s = 9V$, $D = 0.6$. $R = 15\Omega$, $L = 60 \mu H$, $C = 400 \mu F$ and switching frequency $f_s = 40$ kHz.
- (i) Derive the output voltage formula using volt-second balance technique.
 - (ii) Calculate the output voltage.
 - (iii) Determine the average, maximum, and minimum inductor current.
 - (iv) Find the output voltage ripple.
- (10 marks)

- Q4 (a) Draw the equivalent circuit of the single phase full bridge inverter as given in Figure Q4(a) when
- Power Semiconductor devices $T_1 - T_2$ are closed and $T_3 - T_4$ are open.
 - Power Semiconductor devices $T_1 - T_2$ are open and $T_3 - T_4$ are closed.
 - Draw the output voltage of the inverter during for Q4 a(i).
 - Draw the output voltage of the inverter during for Q4 a(ii).
- (8 marks)
- (b) A quasi square-wave full-bridge inverter has a fundamental current of 10A rms at $\alpha = 0^\circ$, an output frequency of 50Hz and RLC series load with $R=20\Omega$, $L=25.465\text{mH}$ and $C=455\mu\text{F}$.
- Calculate the suitable source voltage.
 - Calculate the THD of the load current up to 9th order harmonic when the value of $\alpha = 0^\circ$.
 - Calculate the THD of the load current up to 9th order harmonic when the value of $\alpha = 30^\circ$.
- (17 marks)
- Q5. (a) Although the half-wave AC phase controller can vary the output voltage by varying the delay angle α , it is not generally used in practical applications. State two disadvantages of single phase half-wave AC phase controllers.
- (4 marks)
- (b) Figure Q5(b) shows a single phase full wave ac voltage controller is being employed for controlling the power flow from 220 Vrms, 50 Hz source into a load circuit consisting of a 4Ω load resistor and a 6Ω load inductance.
- Calculate the control range of the firing angle α .
 - Sketch the gate current i_{g1} , i_{g2} , output current, i_o , and the output voltage v_o , at the minimum value of the firing angle $\alpha = 0$.
 - Determine the maximum value of RMS load current.
 - Determine the maximum value of output power and power factor.
 - Determine the maximum value of average and RMS thyristor current.
- (21 marks)

FINAL EXAMINATION

SEMESTER/SESSION : I/2009/2010
 SUBJECT NAME : POWER ELECTRONICS

COURSE : 4 BEE
 SUBJECT CODE : BEE 4113

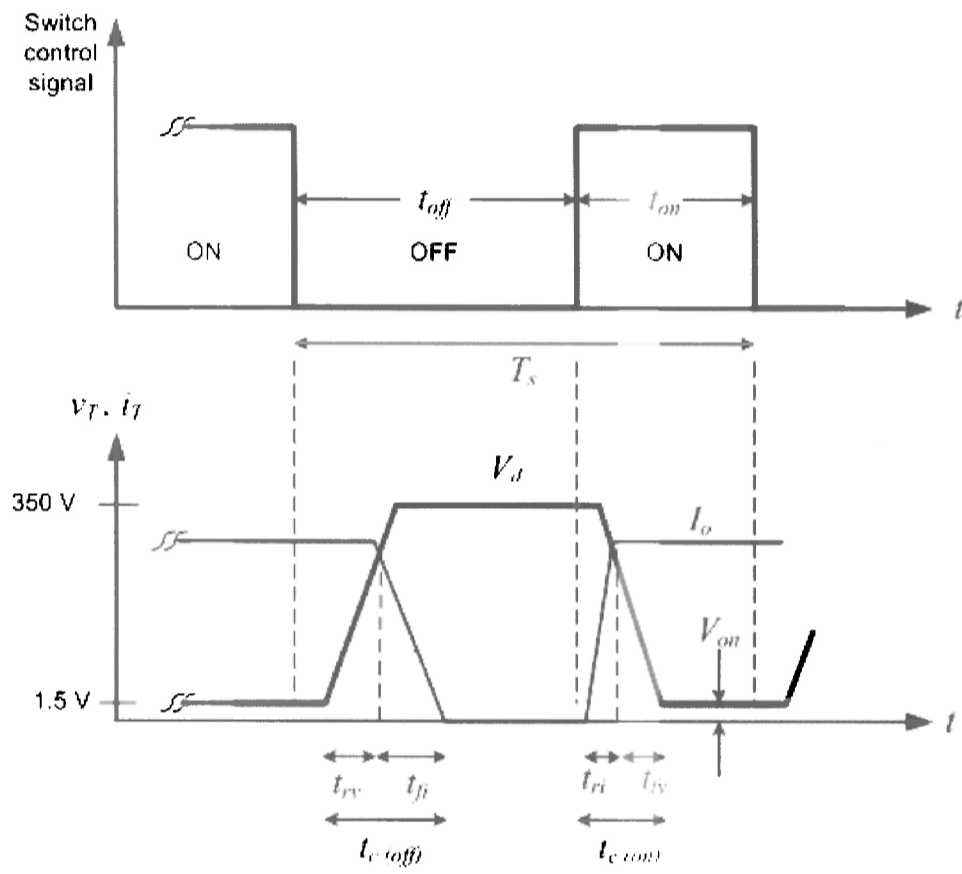


FIGURE O1(e)

FINAL EXAMINATION

SEMESTER/SESSION : 1/2009/2010
 SUBJECT NAME : POWER ELECTRONICS

COURSE : 4 BEE
 SUBJECT CODE : BEE 4113

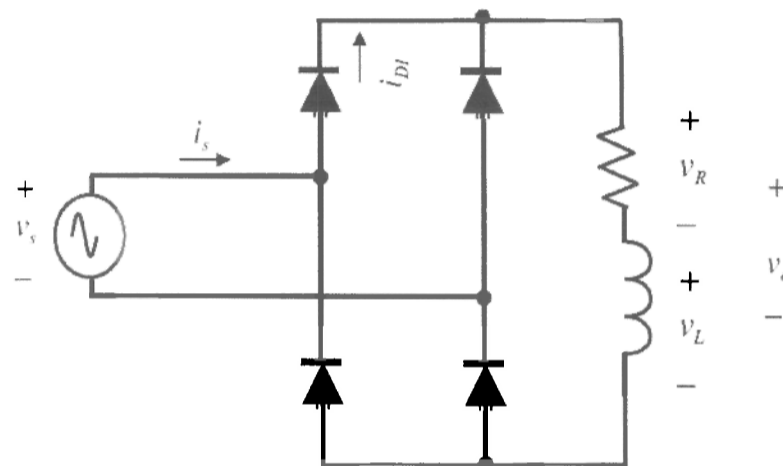


FIGURE O2(b)

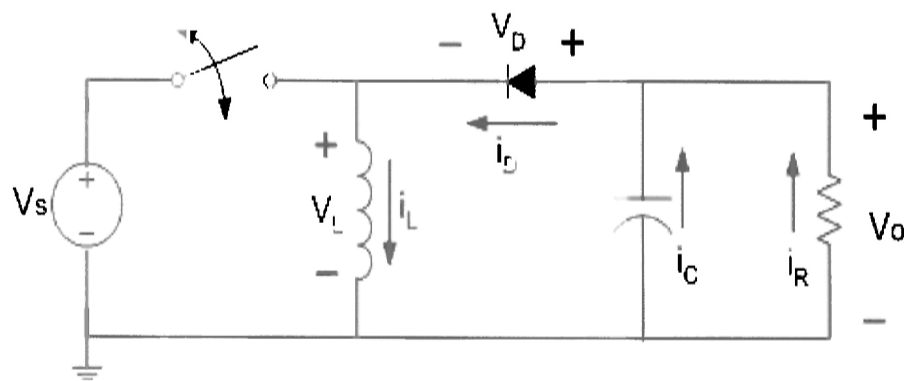


FIGURE O3(e)

FINAL EXAMINATION

SEMESTER/SESSION : 1/2009/2010

COURSE : 4 BEE

SUBJECT NAME : POWER ELECTRONICS

SUBJECT CODE : BEE 4113

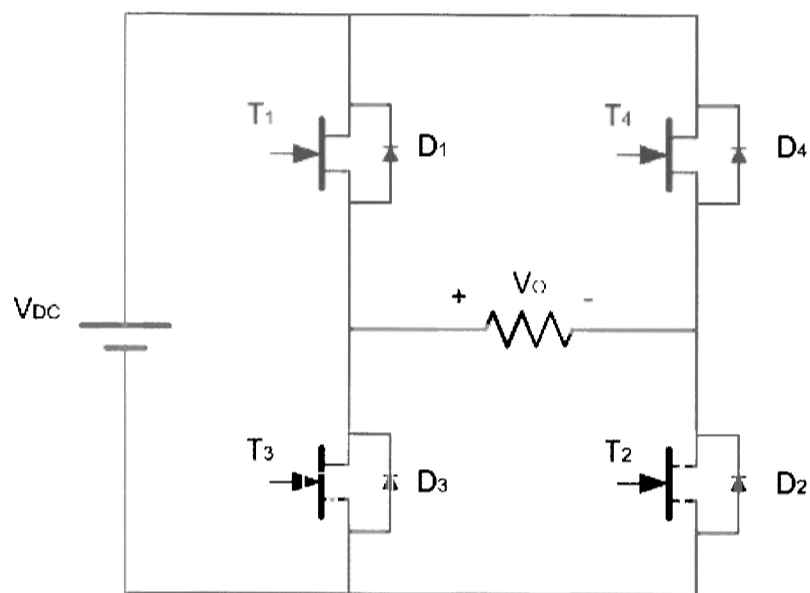


FIGURE O4(a)

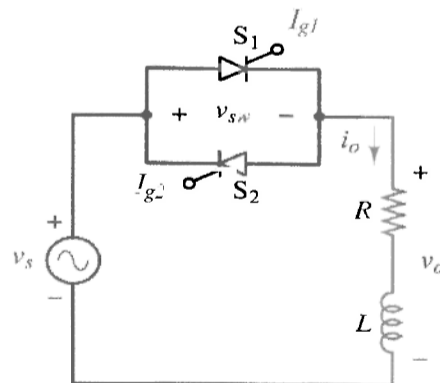


FIGURE O5(b)

FINAL EXAMINATION

SEMESTER/SESSION : 1/2009/2010
 SUBJECT NAME : POWER ELECTRONICS

COURSE : 4 BEE
 SUBJECT CODE : BEE 4113

Formulas

Trigonometry Identity

$$2 \sin^2 A = 1 - \cos 2A$$

Exponential Integration

$$\int e^{ax} dx = \frac{e^{ax}}{a}$$

Switching Power Loss

$$t_{c(on)} = t_{ri} + t_{fv}$$

$$t_{c(off)} = t_{rv} + t_{fi}$$

$$P_s = \frac{1}{2} V_d I_o f_s (t_{c(on)} + t_{c(off)})$$

$$P_{on} = V_{on} I_o \frac{t_{on}}{T_s}$$

$$P_T = P_{on} + P_s$$

Full Bridge Rectifier with R-L load

$$i_o(\omega t) = \frac{V_m}{Z} [\sin(\omega t - \theta) - \sin(\alpha - \theta) e^{-\frac{(\omega t - \alpha)}{\omega \tau}}]$$

$$V_{avg} = \frac{1}{\pi} \int_{\alpha}^{\beta} V_m \sin \omega t d\omega t$$

$$Z = \sqrt{R^2 + (X_L)^2}$$

$$\theta = \tan^{-1} \left(\frac{X_L}{R} \right)$$

$$\tau = \frac{L}{R}$$

DC-DC Converter

$$I_{\max} = I_L + \frac{\Delta i_L}{2} = \frac{V_s D}{R(1-D)^2} + \frac{V_s DT}{2L}$$

$$I_{\min} = I_L - \frac{\Delta i_L}{2} = \frac{V_s D}{R(1-D)^2} - \frac{V_s DT}{2L}$$

$$\frac{\Delta V_o}{V_o} = \frac{D}{RCf}$$

FINAL EXAMINATION

SEMESTER/SESSION : 1/2009/2010
 SUBJECT NAME : POWER ELECTRONICS

COURSE : 4 BEE
 SUBJECT CODE : BEE 4113

Single-phase Full-wave AC Voltage Controller

$$i_{S1} = \frac{V_m}{Z} \left[\sin(\omega t - \theta) - \sin(\alpha - \theta) e^{\frac{R}{\omega L}(\omega t - \alpha)} \right]$$

$$V_o(rms) = \frac{V_m}{\pi} \left[\beta - \alpha + \frac{\sin 2\alpha}{2} - \frac{\sin 2\beta}{2} \right]^{1/2}$$

$$I_T(avg) = \frac{1}{2\pi} \int_{\alpha}^{\beta} i_{S1} d(\omega t)$$

$$I_T(rms) = \left[\frac{1}{2\pi} \int_{\alpha}^{\beta} (i_{S1})^2 d(\omega t) \right]^{1/2}$$

$$\beta - \alpha = \delta = \pi$$