



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

FINAL EXAMINATION SEMESTER I SESSION 2010/2011

COURSE : DIGITAL SYSTEM DESIGN

COURSE CODE : BEE 3133

PROGRAMME : 3BEE

EXAMINATION DATE : NOVEMBER / DECEMBER 2010

DURATION : 3 HOURS

INSTRUCTION : ANSWER ALL QUESTIONS IN PART A
AND THREE (3) QUESTIONS ONLY IN
PART B.

THIS PAPER CONSISTS OF NINE (9) PAGES.

PART A

Q1 Very-Large-Scale Integration (VLSI) is the process of creating integrated circuits by combining thousands of transistor-based circuits into a single chip.

- (a) State three (3) critical VLSI design considerations. (3 marks)
- (b) Give three (3) reasons why the CMOS technology leading in IC market. (3 marks)
- (c) Give two (2) differences between top down and bottom up approach. (4 marks)
- (d) Propose two (2) solutions for these common design problems:
 - (i) The growing number of transistor in IC design.
 - (ii) Cross talk in circuit design.
 - (iii) High interconnect delay. (6 marks)
- (e) The following are VLSI design styles; Full Custom, Application -Specific Integrated Circuit (ASIC), Programmable Logic (PLD, FPGA) and System-on-a chip (SoC). Briefly explain any two (2) of them. (4 marks)

Q2 Suppose that the test set $w_1 w_2 w_3 w_4 = 0100, 1010, 0011, 1111$ and 0110 are chosen randomly to test the circuit in Figure Q2. Find the percentage of single faults can be detected using these tests. (20 marks)

PART B

- Q3** (a) Determine all the subcircuits defined in the VHDL code in Figure Q3(a).
(2 marks)
- (b) Explain the purpose of signal in VHDL code.
(2 marks)
- (c) Draw the schematic diagram for the circuit represented by the VHDL description in Figure Q3(a).
(16 marks)

- Q4** (a) Given a function, $G = A\bar{C}E + A\bar{C}F + A\bar{D}E + A\bar{D}F + BCDE\bar{F}$. Assume that the input variables are available in both uncomplemented and complemented forms.
- (i) Determine the Boolean expression by using factoring technique.
(3 marks)
- (ii) Determine the Boolean expression by using functional decomposition technique.
(3 marks)
- (iii) Sketch the circuit for the Boolean expression in Q4(a)(ii) and calculate the cost.
(5 marks)
- (b) Map the following function in a Karnaugh map.

$$F(a,b,c,d,e) = \Sigma m(0, 3, 4, 5, 6, 7, 8, 12, 13, 14, 16, 21, 23, 24, 29, 31)$$

Based on the K-map,

- (i) Find the minimum Sum-of-Product.
(5 marks)
- (ii) Find the Product-of-Sum equation based on question Q4(b)(i).
(4 marks)

- Q5** (a) The architecture log VHDL contains the code that is synthesized into hardware. It describes the behavior of the model.
- (i) Architecture contains the synthesizable code, and must be written correctly. There are three (3) major classifications for architecture declaration. List them. (3 marks)
 - (ii) List two (2) assignment statements for Behavioral Modeling. (2 marks)
 - (iii) Concurrent statement is used to assign a value to a signal in an architecture body. VHDL provides four (4) different types of concurrent statements. List these statements. (2 marks)
- (b) A multiplexer is a logic component that has several inputs but only a single output. The purpose of the multiplexer circuit is to multiplex the n data inputs onto the single data output under control of the select inputs. The functionality of 4-to-1 multiplexer (referred as 4:1 mux) can be described in the truth table in Figure Q5(b)(a). The bit represented by S_1 and S_0 selects one of the data inputs as the output of the multiplexer. Construct the VHDL code in architecture statement for the truth table using:
- (i) Selected assignment. (4 marks)
 - (ii) Conditional assignment. (4 marks)
 - (iii) IF statement. (5 marks)

- Q6** (a) CMOS stand for Complementary Metal Oxide Semiconductor.
- (i) What is the advantage of CMOS structure? (2 marks)
 - (ii) Justify your reason in proposing the construction with visual aid. (5 marks)
- (b) Figure Q6(b) shows half of a CMOS circuit.
- (i) Construct truth table for the circuit. (6 marks)
 - (ii) Derive the simplest sum-of-products expression for the truth table in part Q6(b)(i). (3 marks)
 - (iii) Derive the other half that contains the PMOS transistors. (4 marks)
- Q7** Refer to the waveform in Figure Q7.
- (a) Derive the simplest Boolean expression by using K-map. (3 marks)
 - (b) Construct minimum transistor level circuit using CMOS technology. (6 marks)
 - (c) Determine either the circuit in Q7(b) is AOI or OAI. (2 marks)
 - (d) Draw the Euler path for the circuit. (4 marks)
 - (e) Sketch the stick diagram for the circuit. (5 marks)

FINAL EXAMINATION

SEMESTER/SESSION : I/2010/11
COURSE : DIGITAL SYSTEM DESIGN

PROGRAMME : 3BEE
COURSE CODE : BEE 3133

 


Figure Q2

FINAL EXAMINATION

SEMESTER/SESSION : I/2010/11
 COURSE : DIGITAL SYSTEM DESIGN

PROGRAMME : 3BEE
 COURSE CODE : BEE 3133

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY litar IS
PORT(w : IN STD_LOGIC_VECTOR(0 TO 15);
      s : IN STD_LOGIC_VECTOR(3 DOWNT0 0);
      a,b,c,d,e : IN STD_LOGIC;
      f : OUT STD_LOGIC);
END litar;

ARCHITECTURE structure OF litar IS
SIGNAL m : STD_LOGIC_VECTOR(0 TO 3);
SIGNAL y : STD_LOGIC_VECTOR(0 TO 3);

COMPONENT mux4to1
PORT(w0,w1,w2,w3 : IN STD_LOGIC;
      s : IN STD_LOGIC_VECTOR(1 DOWNT0 0);
      f : OUT STD_LOGIC);
END COMPONENT;

COMPONENT my_chip
PORT(x,y : IN STD_LOGIC;
      z : OUT STD_LOGIC);
END COMPONENT;

BEGIN
Chip1: my_chip PORT MAP (y(0),y(1),m(0));
Chip2: my_chip PORT MAP (a,b,m(1));
Chip3: my_chip PORT MAP (y(2),y(3),m(2));
m(3)<= (not c and not d) or e;
Mux1: mux4to1 PORT MAP (w(0),w(1),w(2),w(3),s(1 DOWNT0 0),y(0));
Mux2: mux4to1 PORT MAP (w(4),w(5),w(6),w(7),s(1 DOWNT0 0),y(1));
Mux3: mux4to1 PORT MAP (w(8),w(9),w(10),w(11),s(1 DOWNT0 0),y(2));
Mux4: mux4to1 PORT MAP (w(12),w(13),w(14),w(15),s(1 DOWNT0
0),y(3));
Mux5: mux4to1 PORT MAP (m(0),m(1),m(2),m(3),s(3 DOWNT0 2),f);
END structure;

```

Figure Q3(a)


FINAL EXAMINATION

SEMESTER/SESSION : I/2010/11
 COURSE : DIGITAL SYSTEM DESIGN

PROGRAMME : 3BEE
 COURSE CODE : BEE 3133

S_1	S_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

(a)

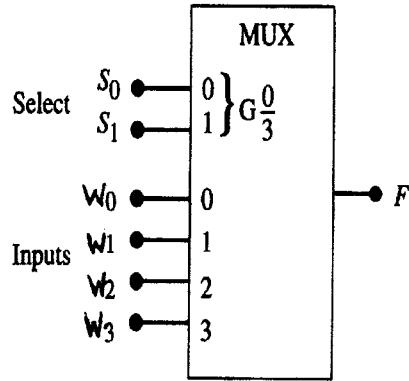

(b)

Figure Q5(b)

 


Figure Q6(b)

FINAL EXAMINATION

SEMESTER/SESSION : I/2010/11
 COURSE : DIGITAL SYSTEM DESIGN

PROGRAMME : 3BEE
 COURSE CODE : BEE 3133

 


Figure Q7