



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2010/2011**

COURSE : **ELECTRIC CIRCUIT ANALYSIS II**
COURSE CODE : **BEF 12503**
PROGRAMME : **1 BEF**
EXAMINATION DATE : **APRIL/MAY 2011**
DURATION : **3 HOURS**
INSTRUCTION : **ANSWER FIVE (5) QUESTIONS ONLY**

THIS PAPER CONSIST OF ELEVEN (11) PAGES

- Q1** (a) State the difference between capacitor and resistor in term of its energy characteristic. (2 marks)
- (b) In your own words, explain why the circuit given in **Figure Q1 (b) (i)** can be redrawn as **Figure Q1 (b) (ii)** when it is operating under dc condition. Also, describe how to calculate the energy stored in the inductor and capacitor in **Figure Q1 (b) (i)**. (4 marks)
- (c) Voltage waveform in **Figure Q1 (c) (i)** is applied across the terminal a–b in **Figure Q1 (c) (ii)**. Illustrate:
 (i) the current waveform that flows into terminal a-b
 (ii) the energy waveform of 100 μ F capacitor (9 marks)
- (d) If the voltage across a 4 H inductor is given by:

$$v(t) = \begin{cases} 40t^2 \text{ V} & t > 0\text{s} \\ 0 \text{ V} & t < 0\text{s} \end{cases}$$

- (i) Calculate the current through the inductor when $t = 2\text{ms}$.
 (ii) Calculate the energy stored by the inductor within $0 < t < 7 \text{ s}$.
 (iii) Formulate the equation for instantaneous power of the inductor. (5 marks)

- Q2** (a) List down two (2) ways of supplying energy to the first order circuit. (2marks)
- (b) Explain briefly on the time constant, τ of the first order circuit. (4 marks)
- (c) The switch in the circuit shown in **Figure Q2 (c)** has been closed for a long time and it is opened at $t = 0 \text{ s}$. Solve for:
 (i) the initial voltage, $v(0)$.
 (ii) the initial energy stored in the capacitor.
 (iii) the time constant for the circuit.
 (iv) the expression of $v(t)$ for $t > 0\text{s}$. (9 marks)
- (d) The switch in the circuit shown in **Figure Q2 (d)** remained connected to the 40V source for a long time. At $t = 0\text{s}$ the switch was moved to the 100V supply.
 (i) Calculate the initial value $i(0)$ and final value $i(\infty)$ of the inductor current $i(t)$.
 (ii) Propose the general expression of $i(t)$ in terms of time constant, τ for $t > 0\text{s}$. (5 marks)

- Q3**
- (a) Define the meaning of second order circuit. (2 marks)
- (b) Explain on the effect of resonant frequency and damping factor to the response of series RLC circuit. (4 marks)
- (c) For the circuit shown in **Figure Q3 (c)**, solve for $v(t)$ when $t > 0$ s. (9 marks)
- (d) For the parallel RLC Circuit shown in **Figure Q3 (d)**:
- (i) Deduce its characteristic equation.
- (ii) Design a parallel RLC circuit that will produce critically damped response when $R = 2.5 \text{ k}\Omega$. (5 marks)
- Q4**
- (a) Define the meaning of phasors. (2 marks)
- (b) Describe the relationship between the types of load and complex power triangle. (4 marks)
- (c) For the circuit shown in **Figure Q4 (c)**, use mesh analysis to find the mesh currents $i_1(t)$ and $i_2(t)$. Let $v_1(t) = 10 \cos 4t \text{ V}$ and $v_2(t) = 20 \cos (4t - 30^\circ) \text{ V}$. (9 marks)
- (d) For the circuit shown in **Figure Q4 (d)**:
- (i) Determine $i(t)$ by using superposition theorem.
- (ii) Deduce the new $i(t)$ if dc voltage is doubled. (5 marks)
- Q5**
- (a) State the importance of locus diagram. (2marks)
- (b) Give one example of a locus diagram for the circuit given in **Figure Q5 (b)**. (4 marks)
- (c) A 12Ω resistor is in parallel connection with series combination of a 12Ω inductive reactance and a resistor which varies from 0Ω to $\infty \Omega$. A $120 \angle 0^\circ \text{ V}$ supply is connected at the terminal of those parallel impedances. Illustrate the locus diagram for the total current and use it to solve for:
- (i) Current at unity power factor.
- (ii) Maximum current and its corresponding power factor.
- (iii) Minimum power factor and its corresponding current. (9 marks)

- (d) The total current locus diagram of a parallel circuit that is connected to $120\angle 0^\circ$ V supply is shown in **Figure Q5 (d)**.
- Analyze the circuit and calculate all of the circuit components if $\omega = 1$ rad/s.
 - Propose the maximum real power that can be supplied to the circuit
- (5 marks)

- Q6** (a) Define the meaning of mutual inductance. (2 marks)
- (b) Explain on how to determine mutual voltage polarity by using dot convention. (4 marks)
- (c) For the circuit given in **Figure Q6 (c)**, solve for the power absorbed by the $4\ \Omega$ and $5\ \Omega$ resistor. (9 marks)
- (d) For the coupled coils in **Figure Q6 (d)**:
- Calculate the total inductance
 - By using any two coils in **Figure Q6 (d)**, construct a coupled coils with series opposing condition.
- (5 marks)

- Q7** (a) State a difference between step up transformer and step down transformer. (2 marks)
- (b) Explain on any two (2) types of transformer losses. (4 marks)
- (c) The secondary winding of a step down transformer has a terminal voltage of $v_s(t) = 282.8 \sin 377t$ V. The turns ratio of the transformer is 100:200. If the secondary current of the transformer is $i_s(t) = 7.07 \sin (377t - 36.87^\circ)$ A, illustrate the phasor diagram of the transformer. The impedances of this transformer referred to the primary side are
- | | |
|-------------------------|---------------------|
| $R_{eq} = 0.20\ \Omega$ | $R_C = 300\ \Omega$ |
| $X_{eq} = 0.75\ \Omega$ | $X_M = 80\ \Omega$ |
- (9 marks)
- (d) For the circuit in **Figure Q7 (d)**:
- Calculate the input impedance
 - Propose a suitable base voltage and base power at the input terminal such that the per unit input impedance is $0.256 + j0.112$ pu
- (5 marks)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/ 2010/2011

PROGRAMME : 1 BEF

COURSE : ELECTRIC CIRCUIT ANALYSIS II

COURSE CODE : BEF 12503

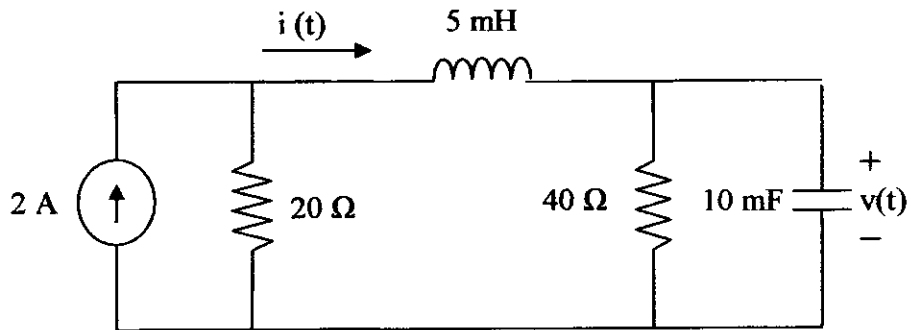


FIGURE Q1 (b) (i)

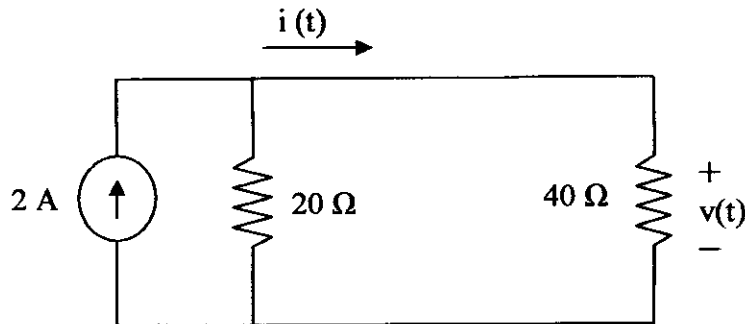


FIGURE Q1 (b) (ii)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/ 2010/2011

PROGRAMME : 1 BEF

COURSE : ELECTRIC CIRCUIT ANALYSIS II

COURSE CODE : BEF 12503

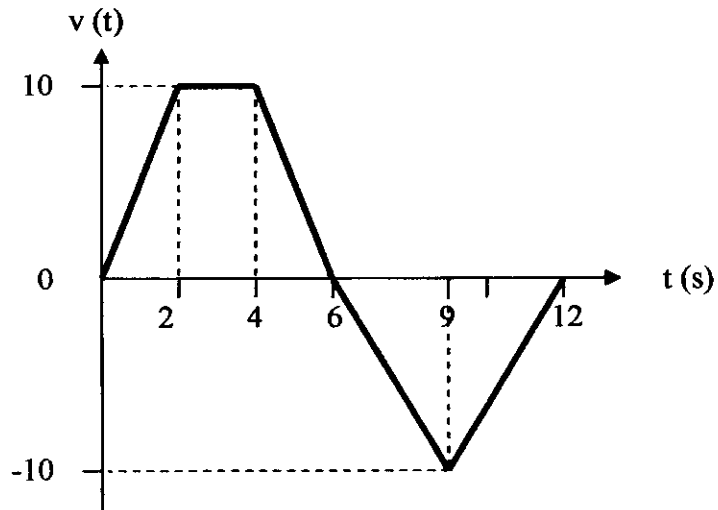


FIGURE Q1 (c) (i)

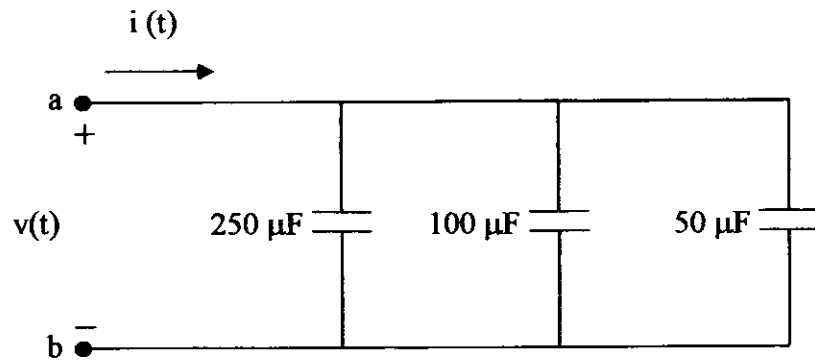


FIGURE Q1 (c) (ii)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/ 2010/2011
 COURSE : ELECTRIC CIRCUIT ANALYSIS II

PROGRAMME : 1 BEF
 COURSE CODE : BEF 12503

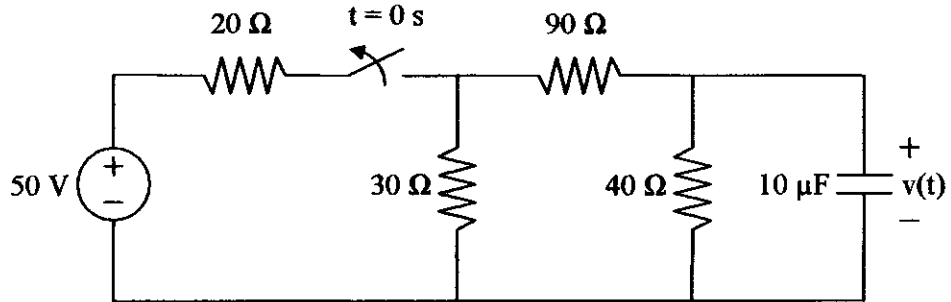


FIGURE Q2 (c)

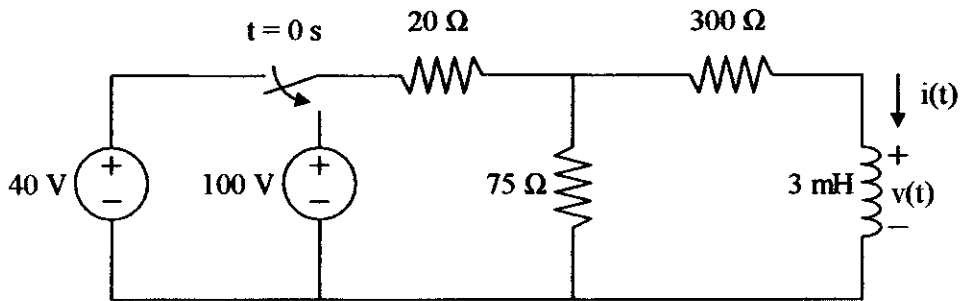


FIGURE Q2 (d)



FINAL EXAMINATION

SEMESTER/SESSION : SEM II/ 2010/2011

PROGRAMME : 1 BEF

COURSE : ELECTRIC CIRCUIT ANALYSIS II

COURSE CODE : BEF 12503

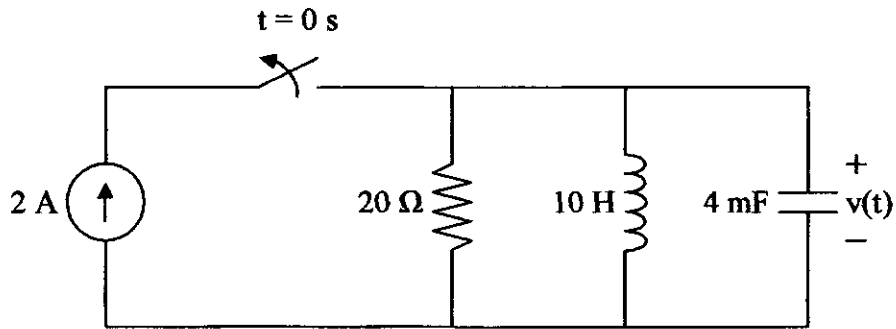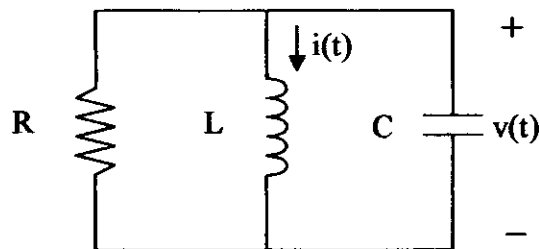**FIGURE Q3 (c)****FIGURE Q3 (d)**

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/ 2010/2011
 COURSE : ELECTRIC CIRCUIT ANALYSIS II

PROGRAMME : 1 BEF
 COURSE CODE : BEF 12503

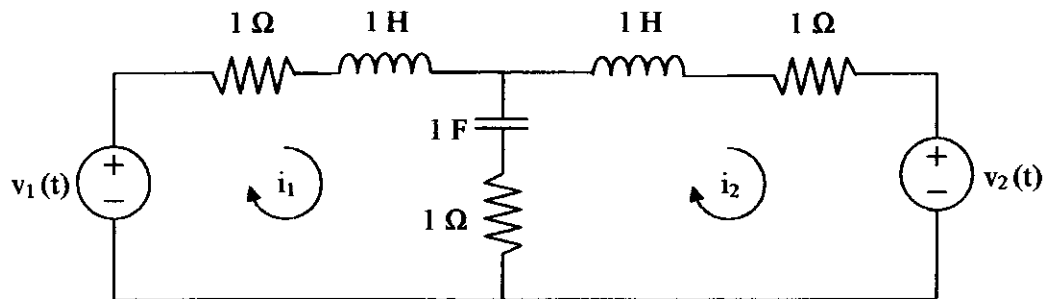


FIGURE Q4 (c)

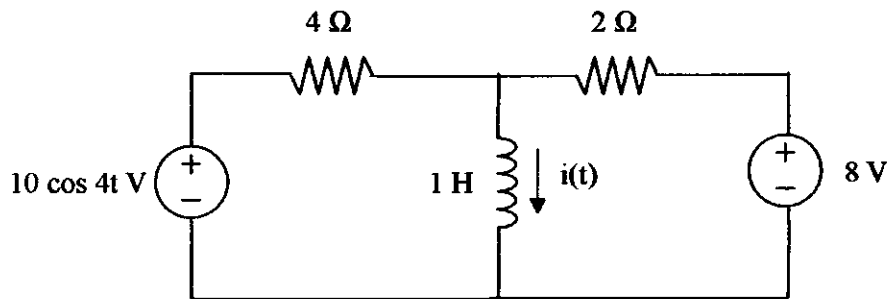


FIGURE Q4 (d)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/ 2010/2011
 COURSE : ELECTRIC CIRCUIT ANALYSIS II

PROGRAMME : 1 BEF
 COURSE CODE : BEF 12503

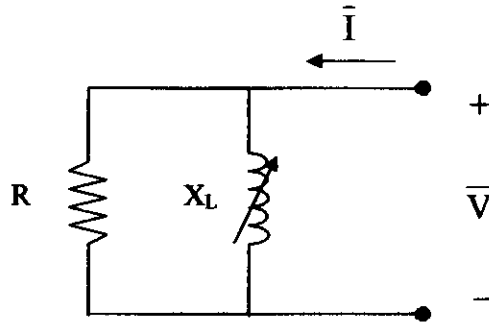


FIGURE Q5 (b)

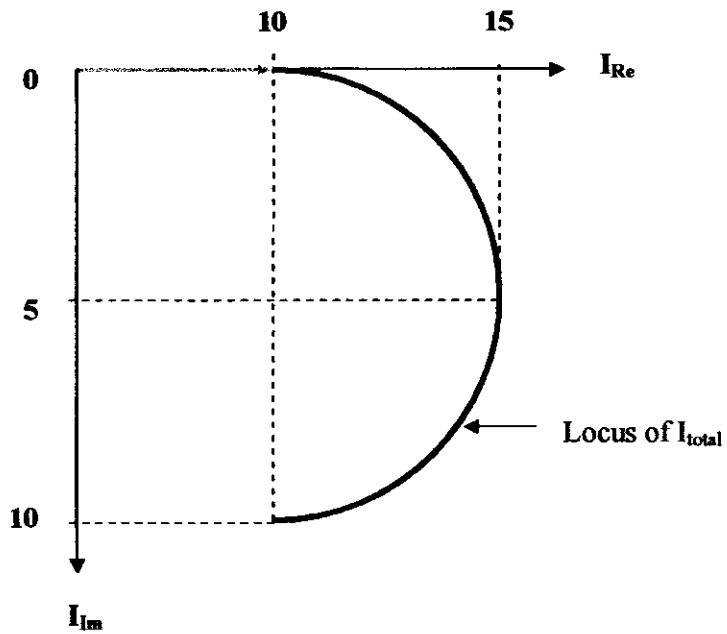


FIGURE Q5 (d)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/ 2010/2011
 COURSE : ELECTRIC CIRCUIT ANALYSIS II

PROGRAMME : 1 BEF
 COURSE CODE : BEF 12503

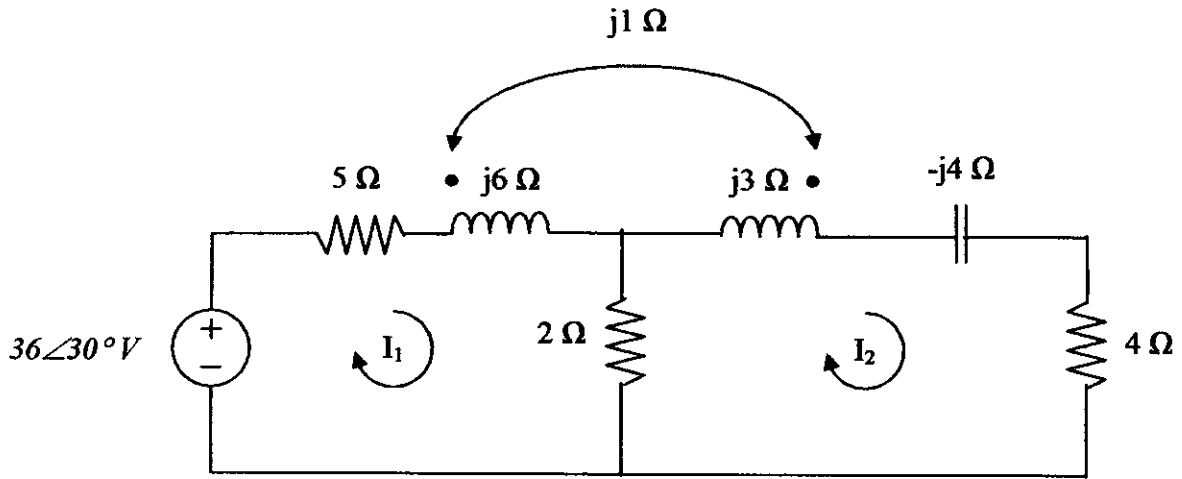


FIGURE Q6 (c)

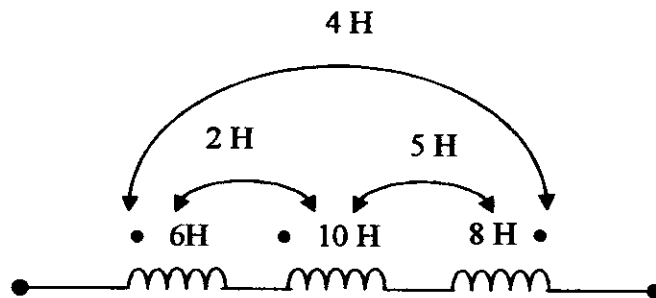


FIGURE Q6 (d)

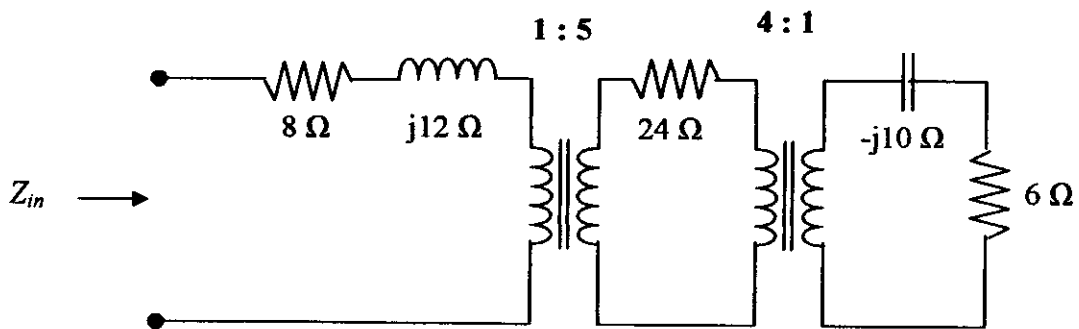


FIGURE Q7 (d)