



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2010/2011**

COURSE NAME : ELECTRIC NETWORK ANALYSIS AND SYNTHESIS

COURSE CODE : BEX 31303 / BEE 3113

PROGRAMME : BACHELOR OF ELECTRICAL ENGINEERING WITH HONOURS

EXAMINATION DATE : APRIL / MEI 2011

DURATION : 2 HOURS 30 MINUTES

INSTRUCTION : THIS EXAMINATION PAPER CONSISTS OF PART A AND PART B. ANSWER ONLY **FOUR (4) QUESTIONS FROM PART A & ONE (1) QUESTION FROM PART B.**

THIS PAPER CONSISTS OF NINE (9) PAGES

PART A: ANSWER **FOUR (4)** QUESTIONS ONLY

- Q1** (a) Given a function, $f(t) = 2t^2 + 10e^{-2t} \cosh at u(t)$. By using the Laplace Transform definition, determine the Laplace Transform of the time integration $f(t)$. Given that $\cosh x = \frac{1}{2}(e^x + e^{-x})$. (6 marks)
- (b) Obtain the Laplace Transform of the function in **Figure Q1(b)**. (6 marks)
- (c) Determine the time domain function, $v(t)$ for $V(s) = \frac{14s^2 + 10}{s(s+8)(s+6)^2}$. (6marks)
- (d) Find the final value for the function, $F(s) = \frac{14s^2 + 6}{s(s+1)(s+5)}$. (2 marks)
- Q2** (a) Convolution is important tools as it relates the input, output and transfer function of a system. **Figure Q2(a)** shows the system's impulse function, $h(t)$ and input, $x(t)$. Find the output, $y(t)$ of the system using convolution integral. (8marks)
- (b) A system has a circuit shown in **Figure Q2(b)**. With all the component values given and assuming there is no initial energy stored,
- (i) find the system's transfer function, $\frac{Vo(s)}{Vi(s)}$. (7 marks)
- (ii) plot the pole-zero diagram for the system. (2 marks)
- (iii) is the system producing a stable response? Please justify your answer. (3 marks)
- Q3** (a) Consider the circuit shown in **Figure Q3(a)**. The input to this circuit is $V_{in}(t)$, and the output is $V_{out}(t)$. Assuming that there is no initial condition in the circuit,
- (i) derive the circuit transfer function, $H(s) = \frac{V_o(s)}{V_i(s)}$. (6 marks)
- (ii) let $R = 4\Omega$, $L = 2H$ and $C = 5mF$, sketch the magnitude and phase bode plot for the transfer function, $H(s)$ derived in part Q3(a)(i). (9 marks)

- (b) The Quality Factor (Q) and the value of resistor (R) in the circuit shown in **Figure Q3(b)** are given by $Q = 5$ and $R = 10\text{K}\Omega$. Based on the given Q and R values,
- (i) find the inductance value of the inductor (L) shown in **Figure Q3(b)**. (3 marks)
 - (ii) determine the Bandwidth (B) for the response. (2 marks)
- Q4** (a) Describe the magnitude response for each type of the following filter:
- (i) Bandpass filter. (2 marks)
 - (ii) First order low pass Chebychev Type 1 filter. (2 marks)
 - (iii) Second order high pass Butterworth filter. (2 marks)
- (b) An engineer has proposed a filter network given in **Figure Q4(b)**. Assume zero initial condition. Let $R_m = 10\text{k}\Omega$.
- (i) Solve for the transfer function $H(s) = V_o(s)/V_s(s)$ in symbolic form. Simplify your expression as much as possible. (6 marks)
 - (ii) Identify the type of filter (2marks)
 - (iii) Find the values of capacitor, C, resistors, R_1 and R_2 if the gain is 5 and the cutoff frequency is 3 kHz. (4 marks)
 - (iv) In your opinion, suggest how to increase the overall gain of the filter. (2 marks)
- Q5** (a) Define a two port network (2 marks)
- (b) Determine the y-parameter of the two-port network if **Figure Q5(a)**. (11 marks)
- (c) Determine the h- parameter based on the y-parameter obtained from part Q5(b). (7 marks)

PART B: ANSWER ONE (1) QUESTION ONLY.

Q6 (a) For the periodic functions in **Figure Q6(a)**,

(i) identify the type of symmetry. (2 marks)

(ii) determine the frequency, ω_0 in radians per second. (1 mark)

(b) Sketch the amplitude and phase spectra for a function if the trigonometric Fourier series of the function is given by:

$$f(t) = 6 + 4 \cos(t + 50^\circ) + 2 \cos(2t + 35^\circ) + \cos(3t + 25^\circ) + 0.5 \cos(4t + 20^\circ)$$

(3 marks)

(c) The periodic triangular wave in **Figure Q6(c)(i)** is applied to the RC circuit shown in **Figure Q6(c)(ii)**. Let the values of $T_0 = 2\pi$ ms, $R = 10$ k Ω and $C = 50$ nF. If the Fourier coefficients of the input are:

$$a_0 = 0 \quad a_n = 0 \quad b_n = \frac{160}{(n\pi)^2} \sin\left(n \frac{\pi}{2}\right)$$

(i) express $v_0(t)$ in terms of $v_i(t)$. (3 marks)

(ii) find the first three nonzero terms in the Fourier series of $v_0(t)$. (9 marks)

(iii) based on your result in part (c)(ii), what can you conclude about the magnitude of the nth harmonic as $n \rightarrow \infty$. (2 marks)

Q7 (a) Determine the Fourier transform of the following signal,

$$f(t) = \begin{cases} \frac{At}{B}; & 0 \leq t \leq B \\ 0; & \text{otherwise} \end{cases}$$

(7 marks)

(b) Let the signal calculated in part Q7(a) be the input voltage, V_i , to an ideal op-amp filter circuit shown in **Figure Q7(b)**. Based on the circuit,

(i) determine the circuit transfer function, $H(\omega)$. (9 marks)

(ii) find the Fourier transform of the output voltage, V_o , of the corresponding circuit. (4 marks)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2010/2011
 COURSE NAME : ELECTRIC NETWORK ANALYSIS
 AND SYNTHESIS

PROGRAMME : 2 BEE / 3 BEE
 COURSE CODE : BEX 31303 /
 BEE 3113

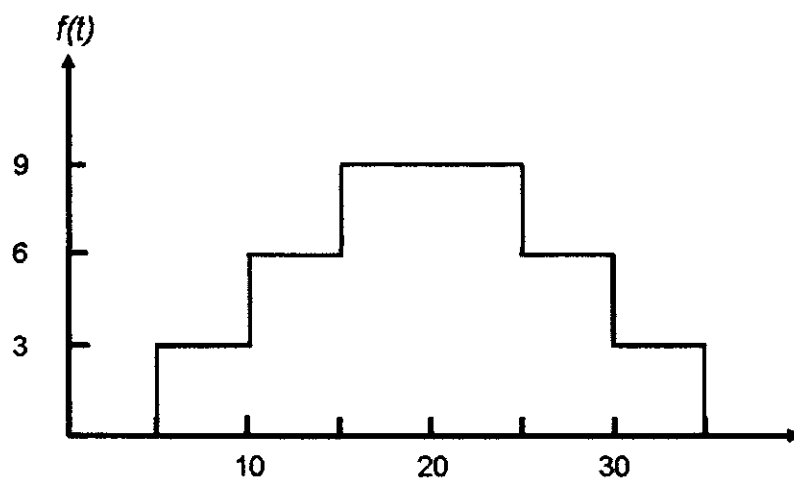


Figure Q1(b)

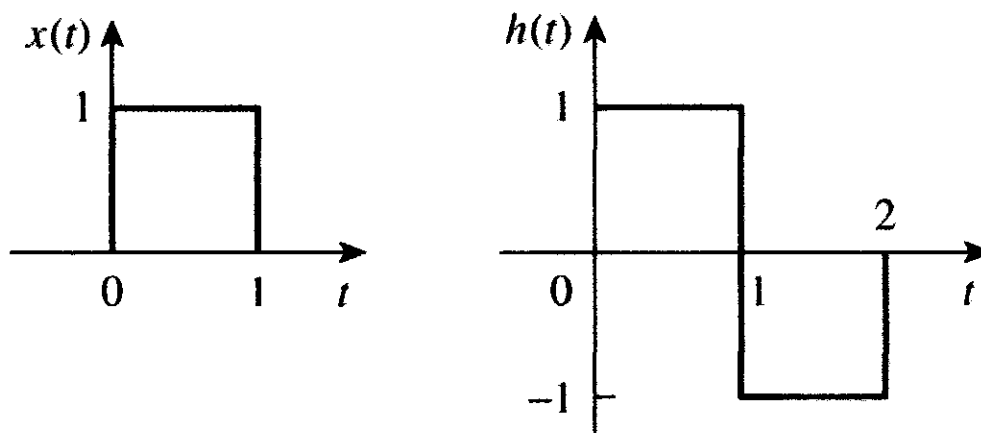


Figure Q2(a)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2010/2011
 COURSE NAME : ELECTRIC NETWORK ANALYSIS
 AND SYNTHESIS

PROGRAMME : 2 BEE / 3 BEE
 COURSE CODE : BEX 31303 /
 BEE 3113

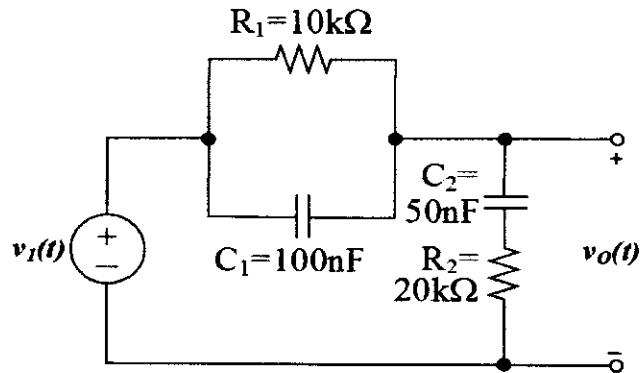


Figure Q2(b)

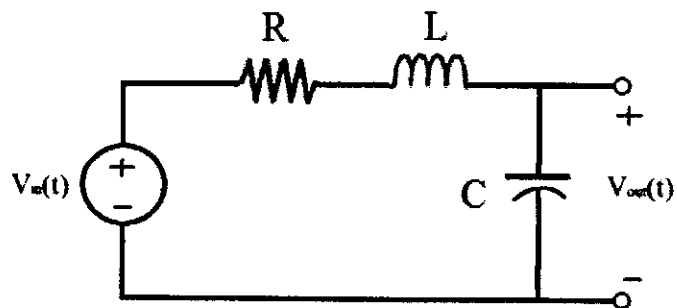


Figure Q3(a)

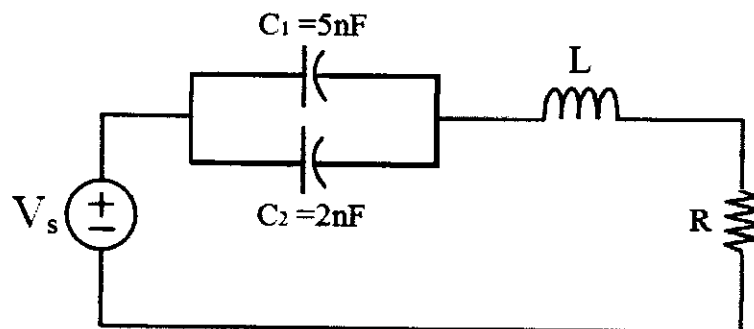


Figure Q3(b)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2010/2011
 COURSE NAME : ELECTRIC NETWORK ANALYSIS
 AND SYNTHESIS

PROGRAMME : 2 BEE / 3 BEE
 COURSE CODE : BEX 31303 /
 BEE 3113

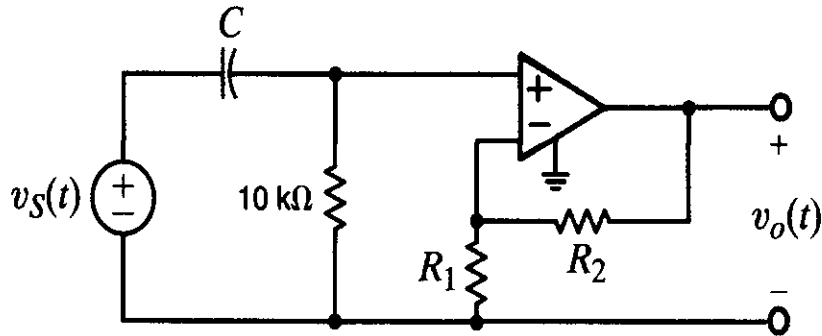


Figure Q4(b)

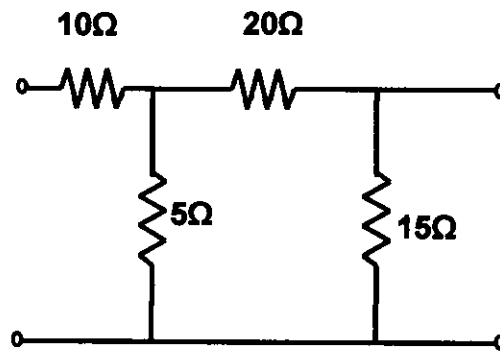


Figure Q5(a)

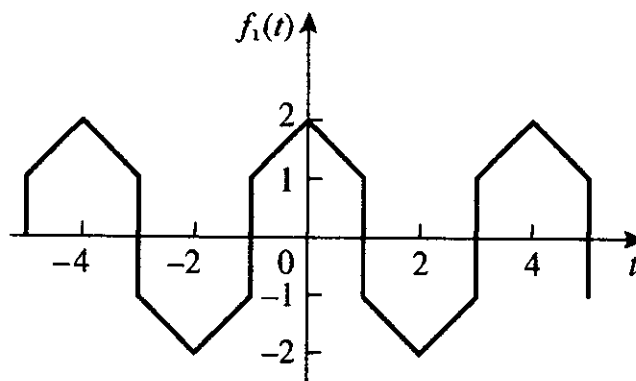


Figure Q6(a)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2010/2011
 COURSE NAME : ELECTRIC NETWORK ANALYSIS
 AND SYNTHESIS

PROGRAMME : 2 BEE / 3 BEE
 COURSE CODE : BEX 31303 /
 BEE 3113

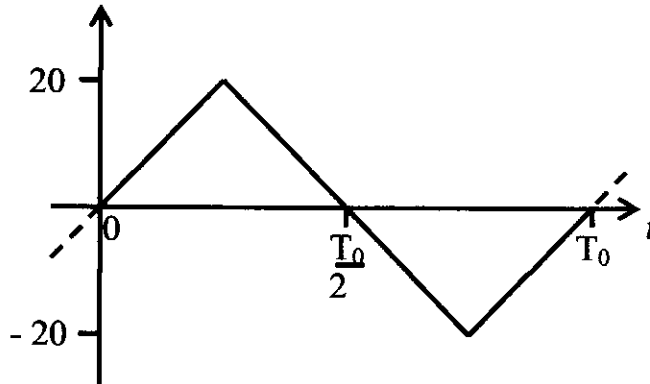


Figure Q6(c)(i)

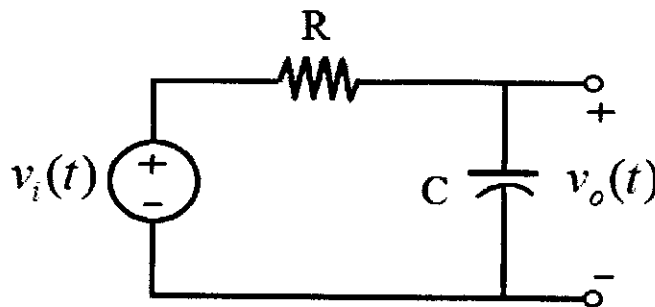


Figure Q6(c)(ii)

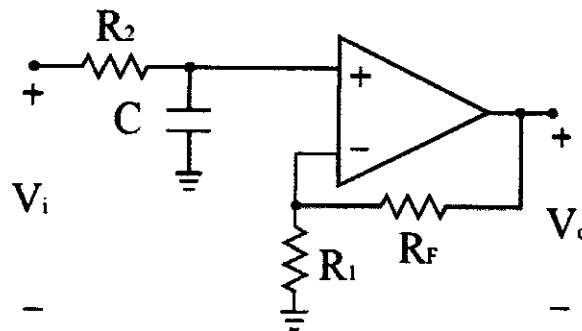


Figure Q7(b)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2010/2011
 COURSE NAME : ELECTRIC NETWORK ANALYSIS
 AND SYNTHESIS

PROGRAMME : 2 BEE / 3 BEE
 COURSE CODE : BEX 31303 /
 BEE 3113

Table 1: Properties of Laplace Transform		
No.	f(t)	F(s)
1.	$\delta(t)$	1
2.	$u(t)$	$1/s$
3.	$tu(t)$	$1/s^2$
4.	$t^n u(t)$	$(n!)/s^{n+1}$
5.	$e^{-at} u(t)$	$1/(s+a)$
6.	$\sin \omega t u(t)$	$\omega/(s^2+\omega^2)$
7.	$\cos \omega t u(t)$	$s/(s^2+\omega^2)$
8.	$f(at)$	$\frac{1}{a} F\left(\frac{s}{a}\right)$
9.	$e^{-at} f(t)$	$F(s+a)$
10.	$f(t-a) u(t-a)$	$e^{-as} F(s)$
11.	$\frac{df}{dt}$ $\frac{d^n f}{dt^n}$	$sF(s) - f(0^-)$ $s^n F(s) - s^{n-1} f(s)$ $- s^{n-2} f'(0^-) \dots - f^{(n-1)}(0^-)$
12.	$\int_0^t f(t) dt$	$\frac{1}{s} F(s)$
13.	$tf(t)$	$-\frac{d}{ds} F(s)$
14.	$\frac{f(t)}{t}$	$\int_0^\infty F(s) ds$
15.	$f(t+nT)$	$\frac{F_1(s)}{1 - e^{-sT}}$
16.	$f(0)$	$\lim_{s \rightarrow \infty} sF(s)$
17.	$f(\infty)$	$\lim_{s \rightarrow 0} sF(s)$
18.	$f_1(t) * f_2(t)$	$F_1(s) \cdot F_2(s)$